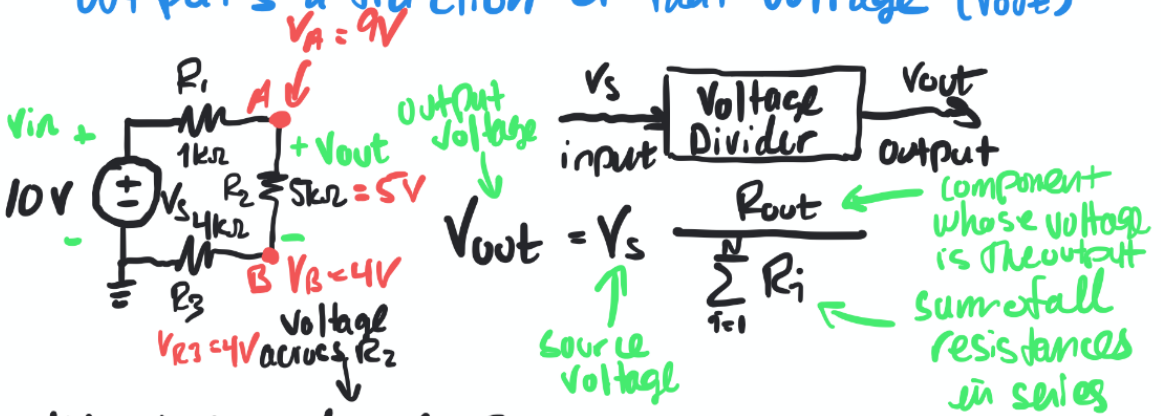


Made as a Component

1) Voltage Divider: component in a circuit

- For an input voltage V_s , a voltage divider outputs a fraction of that voltage (V_{out})




Example: what is $V_{R2} = V_{out}$?

$$V_{out} = \frac{R_2}{R_1 + R_2 + R_3} V_{in} = \frac{5k\Omega}{1k\Omega + 5k\Omega + 4k\Omega} \cdot 10V = \frac{5}{10} \cdot 10 = \underline{5V}$$

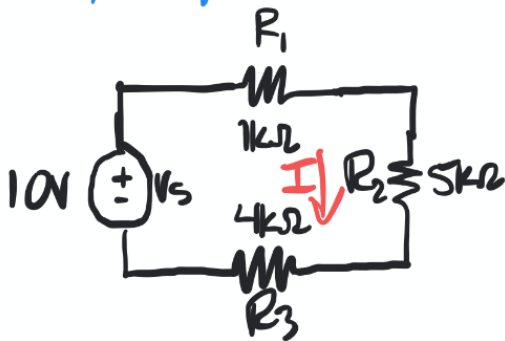2) Circuit Analysis Method #1: Circuit Reduction

- combine R in series & parallel to get a simpler circuit we can solve with a voltage divider or Ohm's Law, then back calculate quantity of interest



Ex: Find I :


a) combine $R_1, R_2, R_3 \rightarrow R_{eq}$

$$R_{eq} = R_1 + R_2 + R_3 \text{ (series)} = 1k\Omega + 5k\Omega + 4k\Omega = 10k\Omega$$




b) $V_s = I R_{eq} \rightarrow I = \frac{V_s}{R_{eq}} = \frac{10V}{10k\Omega} = \underline{1mA}$

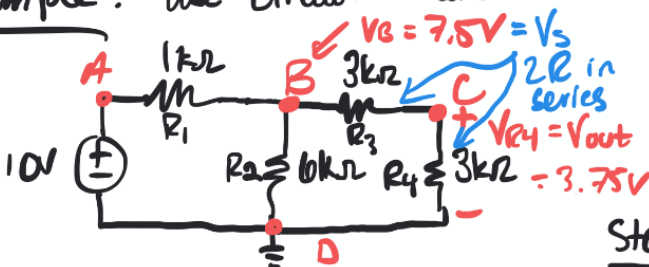Example: Use circuit reduction to find V_{R4}



We want a circuit of the form

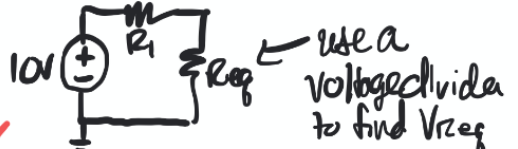



Step #1: Combine R_3 and R_4 (series)

$$R_{eq1} = R_3 + R_4 = 6k\Omega$$

Step #2: Combine R_2 and R_{eq1} (parallel)
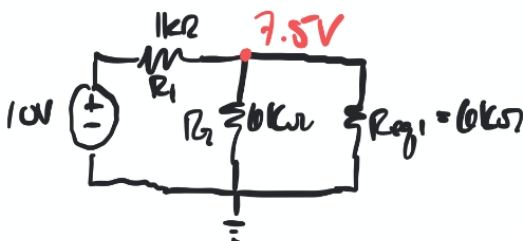
$$R_{eq2} = R_{eq1} \parallel R_2 = \frac{1}{\frac{1}{R_{eq1}} + \frac{1}{R_2}}$$



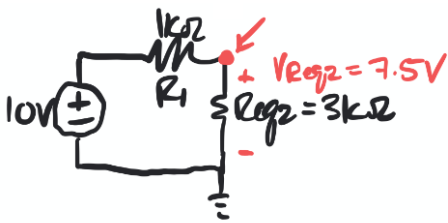

$$= \frac{1}{\frac{1}{6k\Omega} + \frac{1}{6k\Omega}} = \frac{1}{\frac{2}{6k\Omega}} = \frac{6k\Omega}{2} = 3k\Omega$$

Step #3: $V_{Req2} = 10V \cdot \frac{3k\Omega}{1k\Omega + 3k\Omega} = 7.5V$

$\begin{matrix} \downarrow V_i & \downarrow V_{Req2} \\ \uparrow R_1 & \uparrow R_{eq2} \end{matrix}$


Step #4: (see 1st circuit)

$V_B = 7.5V$, we want to find V_{R4}

$$V_{R4} = V_B \cdot \frac{R_4}{R_3 + R_4} = 7.5 \cdot \frac{3k\Omega}{3k\Omega + 3k\Omega} = \underline{3.75V}$$

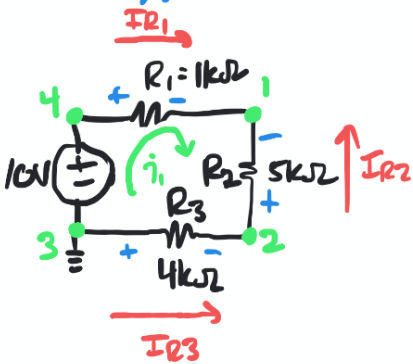3) Circuit Analysis Method #2: KVL/KCL/Ohm's Law

Use KVL and KCL to derive equations for the voltage across R or current through R , then put them into a matrix form to solve them



Procedure: 1) Place reference marks across all resistors in the circuit: "+" and "-" signs. Current flows from "+" to "-". Defines direction of current flow through each resistor.


2) Count the number of unknowns in the circuit. Equal to the number of resistors: V_R or I_R are the unknowns. In this case: V_{R1}, V_{R2}, V_{R3}
3 unknowns

3) Find all nodes and loops in the circuit: 4 nodes, 1 loop

4a) Choose best nodes and loops and write KCL and KVL equations

Hint 1: don't choose nodes connected to ground or a voltage source

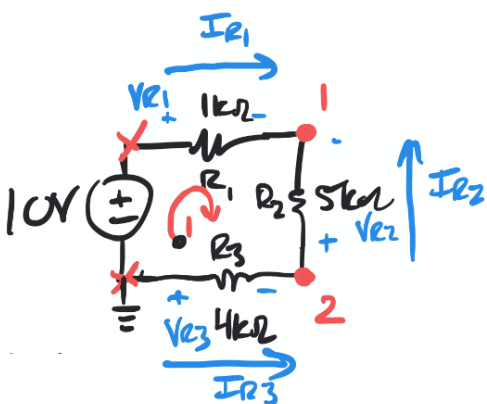Hint 2: don't include loops that include other loops




KCL:

node 1: $I_{R1} + I_{R2} = 0$

node 2: $-I_{R2} + I_{R3} = 0$


3 eq. 3 unknowns

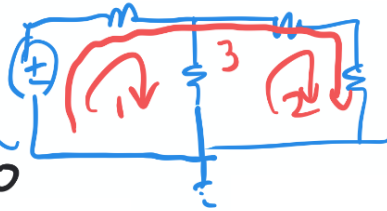

choose 1 and 2, don't choose 3

KVL:

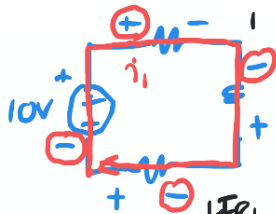loop 1: $10V + V_{R1} - V_{R2} - V_{R3} = 0$



4b) Convert equations to all voltages or all currents

use Ohm's law to convert

$I_R = \frac{V_R}{R}$ or $V_R = I_R R$

node 1: $\frac{V_{R1}}{R_1} + \frac{V_{R2}}{R_2} = 0$

node 2: $-\frac{V_{R2}}{R_2} + \frac{V_{R3}}{R_3} = 0$

5) Put equations into matrix form and solve

$$\begin{matrix} \text{loop 1} \rightarrow \\ \text{node 1} \\ \text{node 2} \end{matrix} \begin{bmatrix} 1 & -1 & -1 \\ R_1 & R_2 & 0 \\ 0 & -R_2 & R_3 \end{bmatrix} \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

Matrix Multiplication matrix equation


$Ax = b$

coefficients unknowns

constants

Solution is $A^{-1}b = x$

$A \cdot x = b$

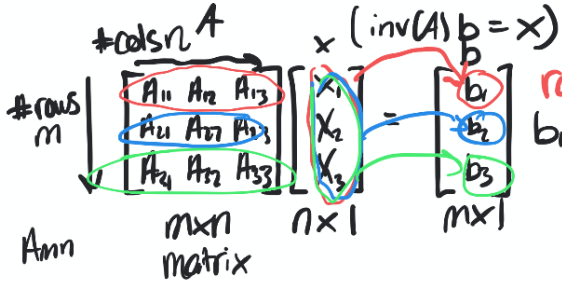

row 1 of A x col 1 of x = row 1 of b


$b_1 = A_{11}x_1 + A_{12}x_2 + A_{13}x_3$
 $10 = 1k \cdot V_{R1} + 1k \cdot V_{R2} + 0 \cdot V_{R3}$

Solve:

$$\begin{bmatrix} 1 & -1 & -1 \\ 1000 & 1000 & 0 \\ 0 & -1000 & 1000 \end{bmatrix} \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$A \cdot x = b$

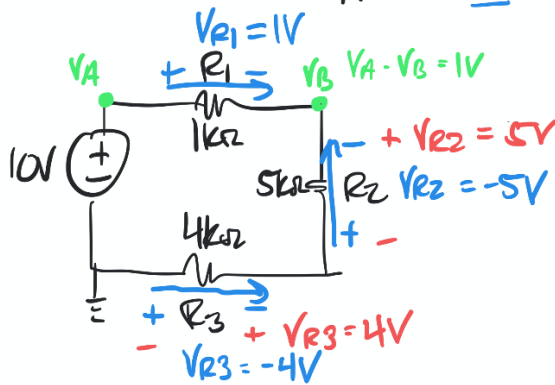
$A^{-1}b = x = \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} = \begin{bmatrix} 1 \\ -5 \\ -4 \end{bmatrix}$



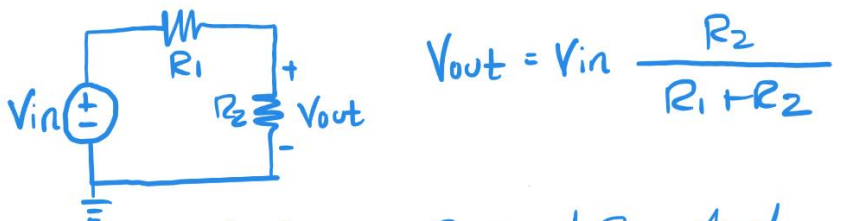Problem #1: Create a voltage divider that outputs 0.6 of the input voltage: $V_{out} = 0.6 V_{in}$
 The voltage divider equation is

$$V_{out} = V_{in} \frac{R_{out}}{\sum_{i=1}^n R_i}$$

The simplest voltage divider is a 2-resistor circuit



$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

So, we must choose R_1 and R_2 such that $\frac{R_2}{R_1 + R_2} = 0.6 \rightarrow \{V_{out} = 0.6 V_{in}\}$


There are an infinite number of solutions, so I'll just choose $R_1 = 1k\Omega$

$$0.6 = \frac{R_2}{1k\Omega + R_2} \rightarrow 0.6k\Omega + 0.6R_2 = R_2$$


$$0.6k\Omega = 0.4R_2$$

$$R_2 = \frac{0.6k\Omega}{0.4} = 1.5k\Omega$$

So the solution is:

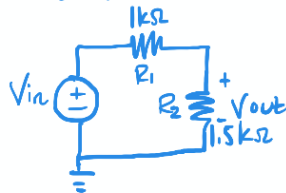


Problem #2:

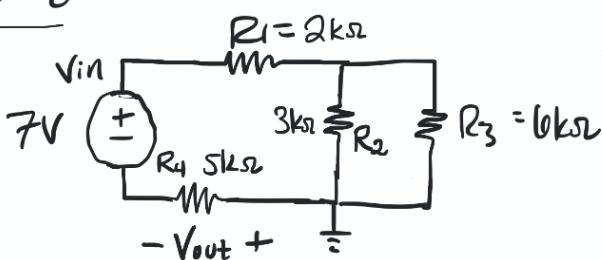

- Solve for $V_{R4} = V_{out}$ using
- circuit reduction method AND
 - KVL/KCL/Ohm's Law method

a) Circuit reduction

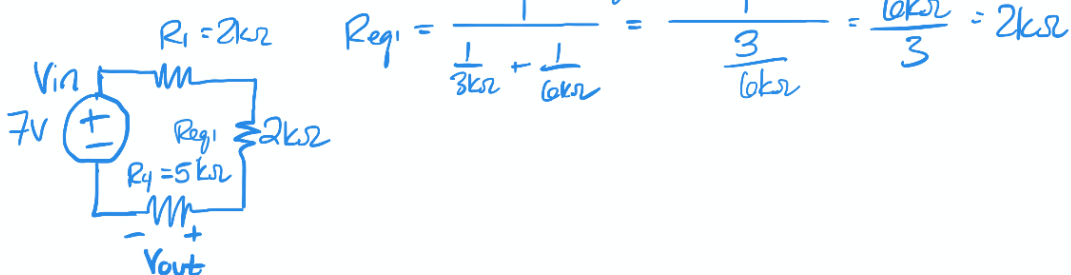1) Combine R_2 and R_3 : $R_2 \parallel R_3 = R_{eq1}$




2) Use a voltage divider to find $V_{out} = V_{R4}$

$$V_{R4} = V_{out} = \frac{R_4}{R_1 + R_{eq1} + R_4} \cdot V_{in}$$

$$= \frac{5k\Omega}{2k\Omega + 3k\Omega + 5k\Omega} \cdot 7V = \frac{5}{9} \cdot 7V = \frac{35V}{9} = \underline{3.889V}$$

b) KVL/KCL/Ohm's Law

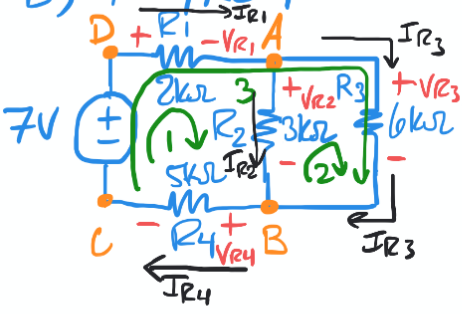

- 1) Place reference marks
- 2) Count number of unknowns = number of resistors = 4
- 3) Count number of nodes and loops
 nodes: 4
 loops: 3
- 4) Choose best nodes and loops, then write KCL and KVL equations in terms of V_R or I_R (use Ohm's Law where needed to convert $V_R \leftrightarrow I_R$)
 - Best nodes: nodes NOT connected to a voltage source or ground: A & B
 - Best loops: loops that do NOT contain any other loops: 1 & 2

node A: $I_{R1} - I_{R2} - I_{R3} = 0$ $\xrightarrow{\text{convert to } V_R \text{ via Ohm's Law}}$ $\frac{V_{R1}}{R_1} - \frac{V_{R2}}{R_2} - \frac{V_{R3}}{R_3} = 0$ $\leftarrow b_1$

node B: $I_{R3} + I_{R2} - I_{R4} = 0$ $\xrightarrow{\text{convert to } V_R \text{ via Ohm's Law}}$ $\frac{V_{R3}}{R_3} + \frac{V_{R2}}{R_2} - \frac{V_{R4}}{R_4} = 0$ $\leftarrow b_2$

loop 1: $-7V + V_{R1} + V_{R2} + V_{R4} = 0$

loop 2: $-V_{R2} + V_{R3} = 0$ $\leftarrow b_3$

5) Put equations into matrix form:


Equation $A \cdot X = b$ since we have 4 unknowns, our "A" matrix will now be 4x4

node A	$\begin{bmatrix} 1/R_1 & -1/R_2 & -1/R_3 & 0 \\ 0 & 1/R_2 & 1/R_3 & -1/R_4 \\ 1 & 1 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$	$\begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \\ V_{R4} \end{bmatrix}$	$=$	$\begin{bmatrix} 0 \\ 0 \\ 7 \\ 0 \end{bmatrix}$
--------	--	--	-----	--

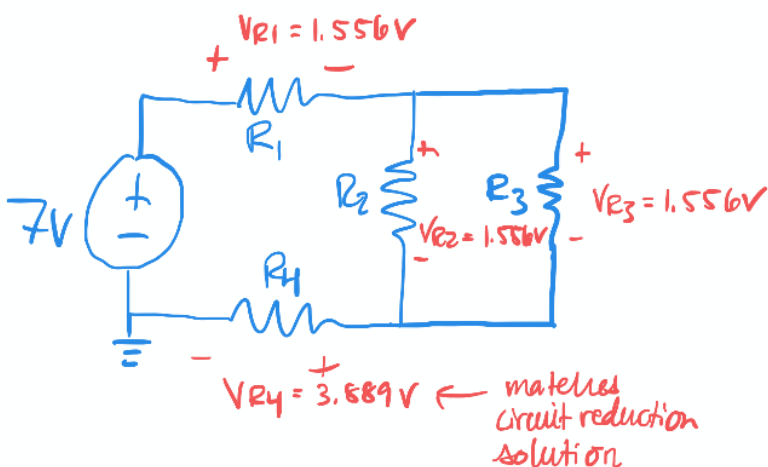e) Solve using Matlab or calculator $A^{-1}b = X$

$$\begin{bmatrix} 1/2000 & -1/3000 & -1/6000 & 0 \\ 0 & 1/3000 & 1/6000 & -1/5000 \\ 1 & 1 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}^{-1} \begin{bmatrix} 0 \\ 0 \\ 7 \\ 0 \end{bmatrix} = \begin{bmatrix} 1.556 \\ 1.556 \\ 3.589 \\ 1.556 \end{bmatrix} V$$

$\leftarrow \text{inv}(A) \text{ in matlab}$



Quiz: Combining R in series and parallel (circuit reduction)

- voltage dividers
- KCL/KVL/Ohm's Law Circuit Analysis Method
- Coming to class and trying proof of skills
- Write matrix equations

-
- open book & open notes from course materials
 - notes must be hand-written or printed out
 - no electronic devices except a non-communicating calculator
 - no discussion allowed during the quiz