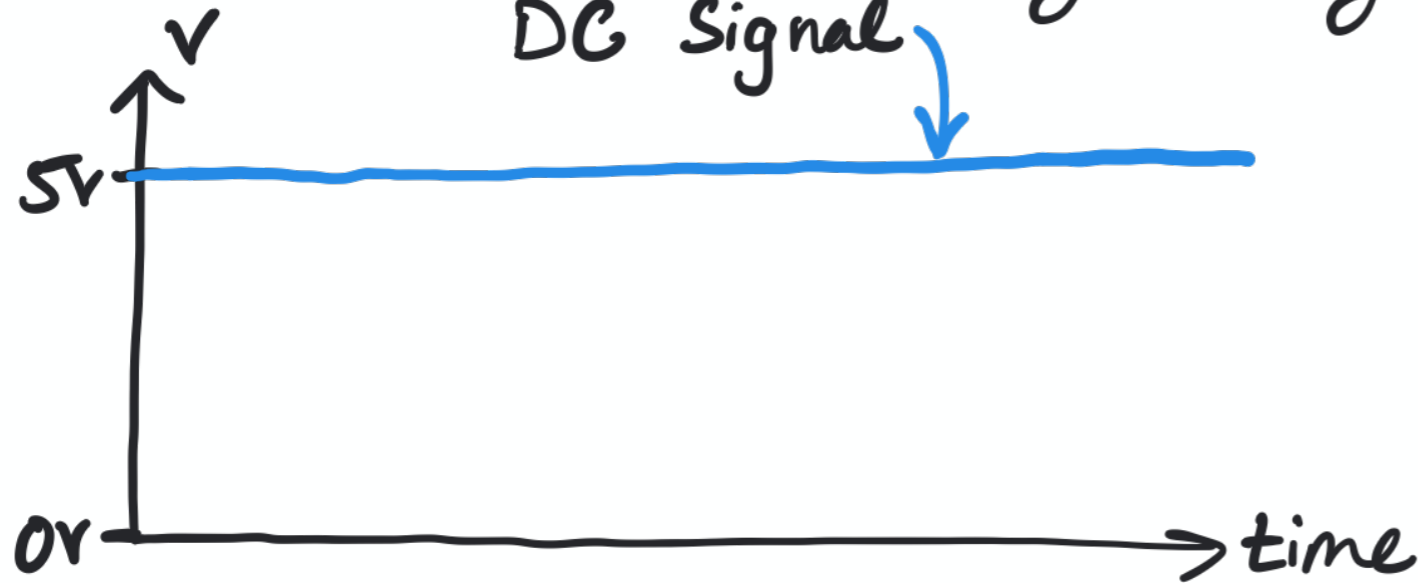


# Intro to ECSE Lecture Notes: Time vs. Frequency Domain 4/4/23 1

## 1) Signals in the Time Domain

+ So far, we've been using mostly DC signals




direct current  
DC signals ( $f = 0\text{Hz}$ )

- Useful for power supplies, but not interesting for signal processing

+ The "other" type of signal is AC (or alternating current)  
→ signal amplitude changes in time:  $f > 0\text{Hz}$

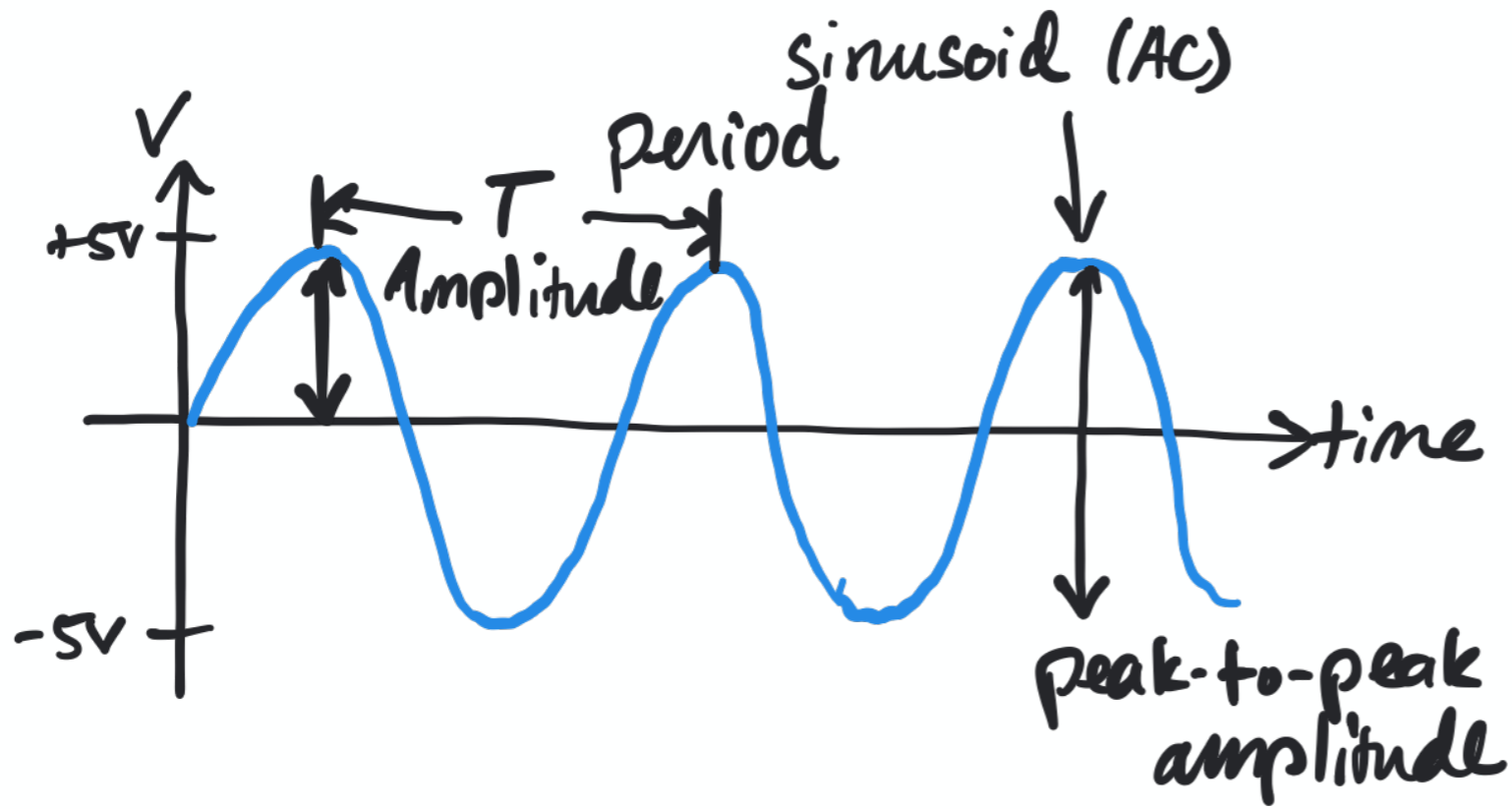
typically AC = sinusoidal (periodic signal)



$$\text{frequency} = 1/T \quad 2$$

To summarize:  $\left\{ \begin{array}{l} \text{DC} : f=0 \rightarrow \text{does not change over time} \\ \text{AC} : f>0 \rightarrow \text{changes over time} \end{array} \right.$

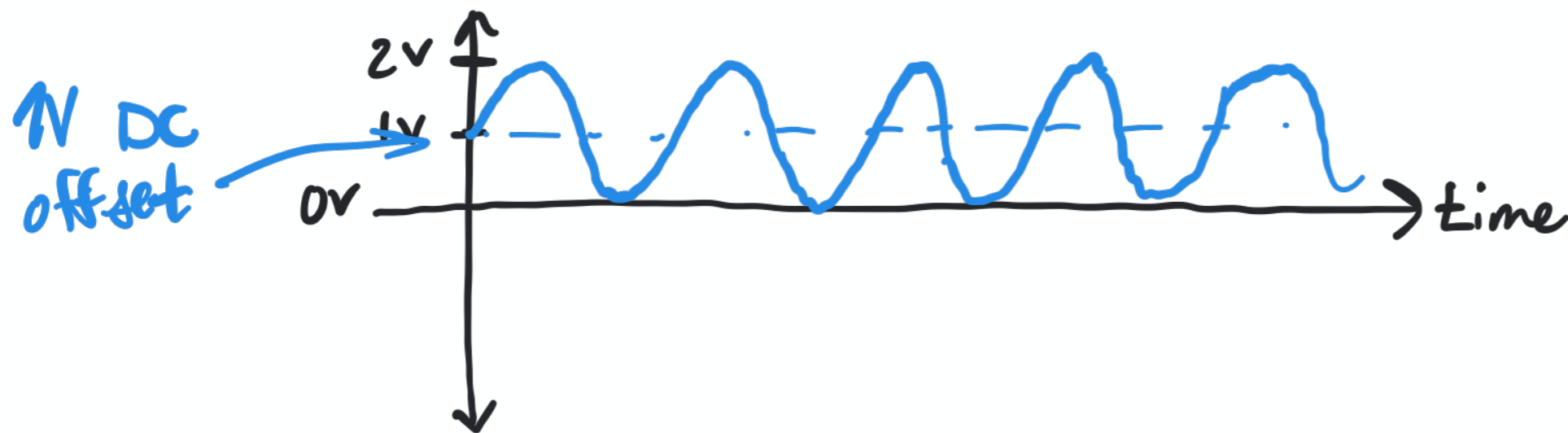+ In general, signals can have both a DC and an AC component



DC offset  
sinusoidal

$$V(t) = V_{DC} + V_{AC}(t)$$

## 2) Capacitors and Inductors

resistance

3

- Resistors: behave according to Ohm's Law:  $V = IR$ 
  - resistors don't care about the signal's frequency

- The two remaining fundamental circuit elements:

Capacitors and inductors DO care about the signal frequency


C and L are still linear circuit elements

- Capacitors and Inductors in the time domain

↓ (in the frequency domain) not like Ohm's Law

### Capacitor (C)


### Inductor (L)

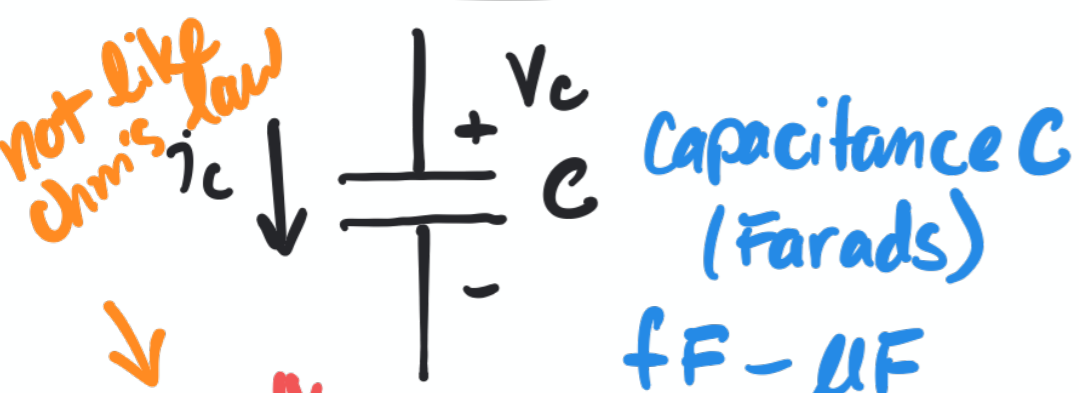

$i_c = C \frac{dV_c}{dt}$  ← time domain (typical range)

open circuit ↓ at DC

no voltage change = no current flow

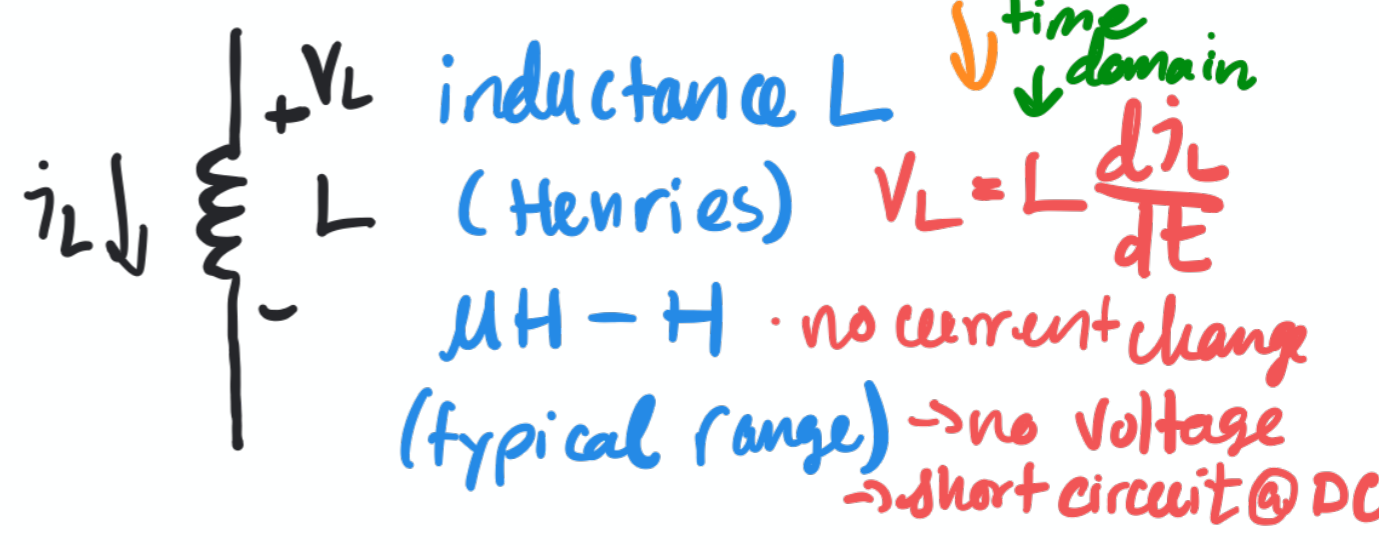

$V_L = L \frac{di_L}{dt}$


no current change → no voltage

→ short circuit @ DC

### 3) Time Domain Math

4

#### a) 1st Order Circuits

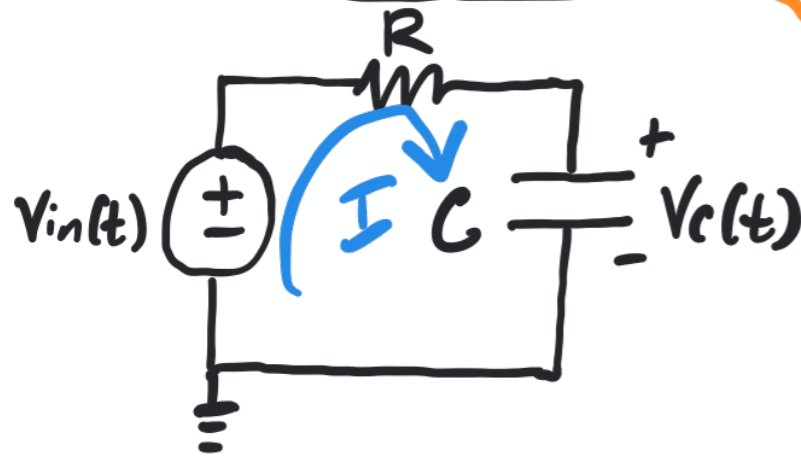

• Find  $V_c(t)$ :  $-\text{Vin}(t) = V_R(t) + V_C(t)$

$\leftarrow I = i_C$


$$V_{in}(t) = IR + V_C(t)$$
$$V_{in}(t) = RC \frac{dV_C(t)}{dt} + V_C(t)$$

KVL

$$i_C = C \frac{dV_C(t)}{dt}$$

1st order ODE

#### b) 2nd Order Circuits

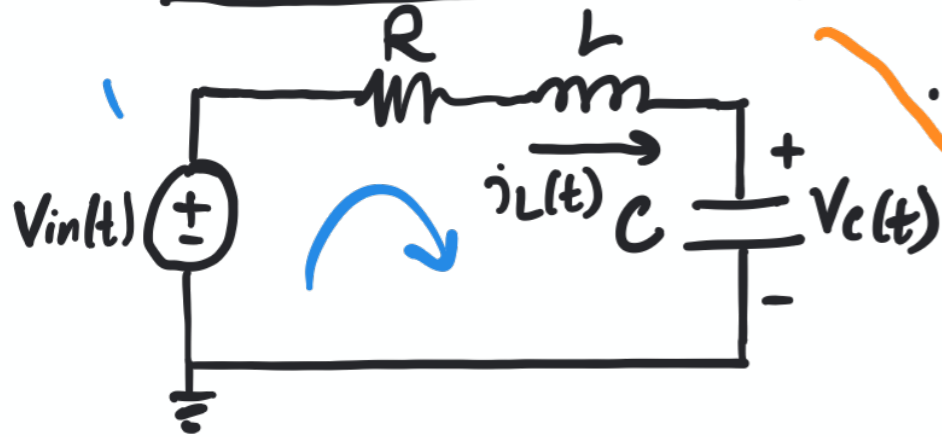

• Find  $V_c(t)$ :

$$\frac{d^2 V_C(t)}{dt^2} + \frac{R}{L} \frac{dV_C(t)}{dt} + \frac{1}{LC} V_C(t) = \frac{1}{LC} V_{in}(t)$$

2nd order ODE

$$i_C = C \frac{dV_C}{dt}$$
$$V_L = L \frac{di_C}{dt}$$

• often, there's an easier way  $\rightarrow$  frequency domain




## 4) Impedances

5

- In the frequency domain, there is an Ohm's-Law-like relationship between  $V$  and  $I$  for  $R, L$ , and  $C$ :


$$V = I \boxed{Z} \leftarrow \text{Impedance } (Z)$$

Resistor

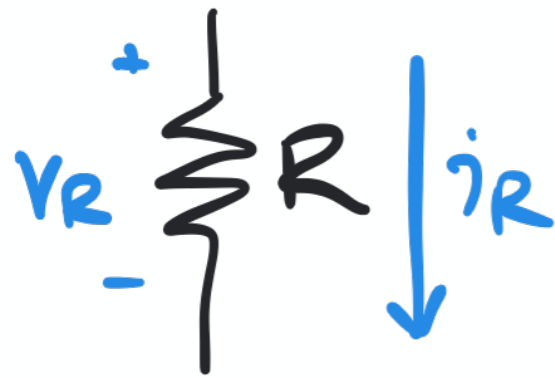

Impedance:  $Z_R = R$

Capacitor

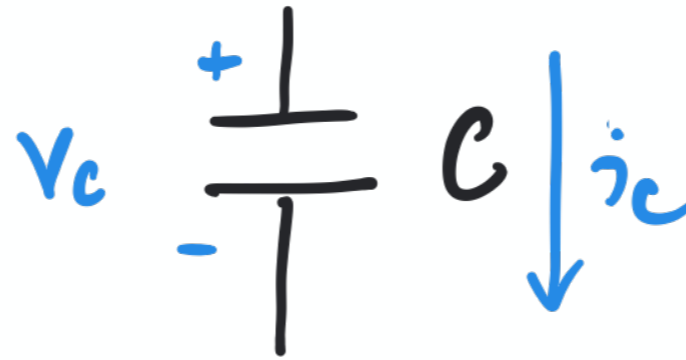


$$Z_C = \frac{1}{sC}$$

*imaginary*  $\# = \sqrt{-1}$  *freq. in Hz = 1/s*

$$= \frac{1}{j\omega C}$$

here  $s = j\omega$   $\omega = 2\pi f$  = radial frequency [rad/s]

Inductor

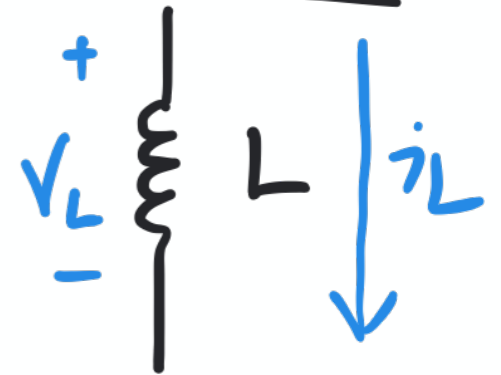

$$Z_L = sL$$
$$= \underline{j\omega L}$$

• what is s? Via the Laplace Transform:

6

$$s = \sigma + j\omega$$

↑  
real number

↑  
real number


$$x(t) = e^{st} = \underline{e^{\sigma t}} \underline{e^{j\omega t}}$$

→ decay or growth → oscillation → AC signals →  $s = j\omega$

• What does this mean? If  $x(t) = e^{st} = \underline{e^{\sigma t}} \underline{e^{j\omega t}}$  is the input

$e^{+\sigma t} \rightarrow$  growth  
 $e^{-\sigma t} \rightarrow$  decay

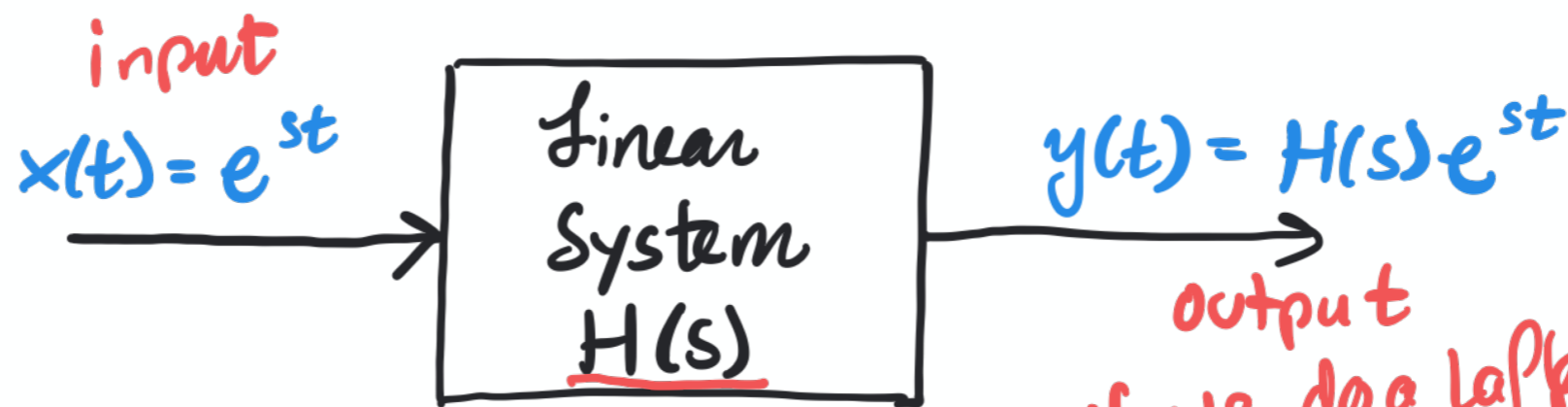
$e^{j\omega t} = \cos(\omega t) + j\sin(\omega t)$   
↑  
Oscillation



• We will only be dealing with  $s = j\omega$  → purely oscillatory signal  
if we do a Laplace transform and then set  $s = j\omega$  → Fourier Transform


Example:

7

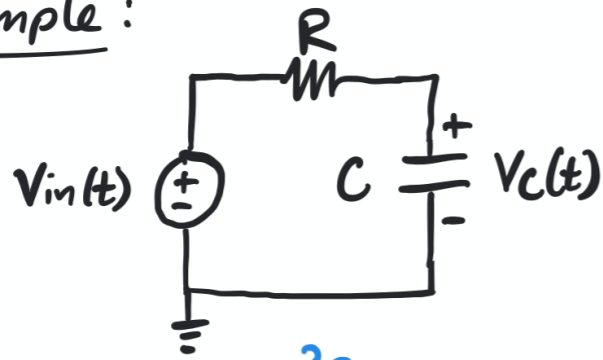

If  $V_{in}(t) = A \cos(\omega t)$ , find  $V_R(t)$  and  $V_C(t)$ .
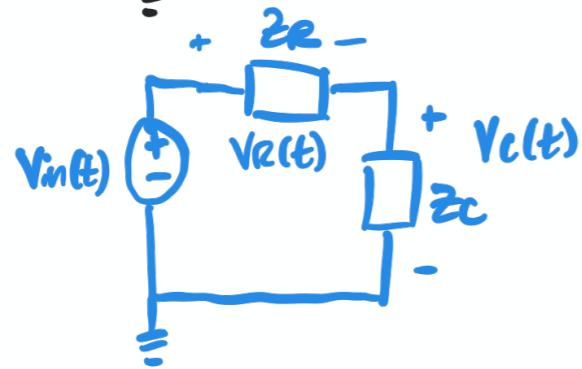
$$V = IZ \rightarrow \begin{cases} Z_R = R \\ Z_C = 1/j\omega C \end{cases}$$



$$V_C = V_{in} \frac{Z_C}{Z_R + Z_C}$$

$$= V_{in} \frac{1/j\omega C}{R + 1/j\omega C} \cdot \frac{j\omega C}{j\omega C} = \frac{1}{j\omega RC + 1} V_{in}$$

$$V_R = V_{in} \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + 1/j\omega C} V_{in} = \frac{j\omega RC}{j\omega RC + 1} V_{in}$$

$V_{in} = A \sin(\omega t)$

$i_c \propto \frac{dV_C}{dt} \rightarrow \frac{d}{dt}(A \sin(\omega t)) = A \omega \cos(\omega t) = A \omega \sin(\omega t + \pi/2)$



$|V_C|$  = what we measure (only real voltages)

$\angle V_C$  = phase shift (imaginary number)

