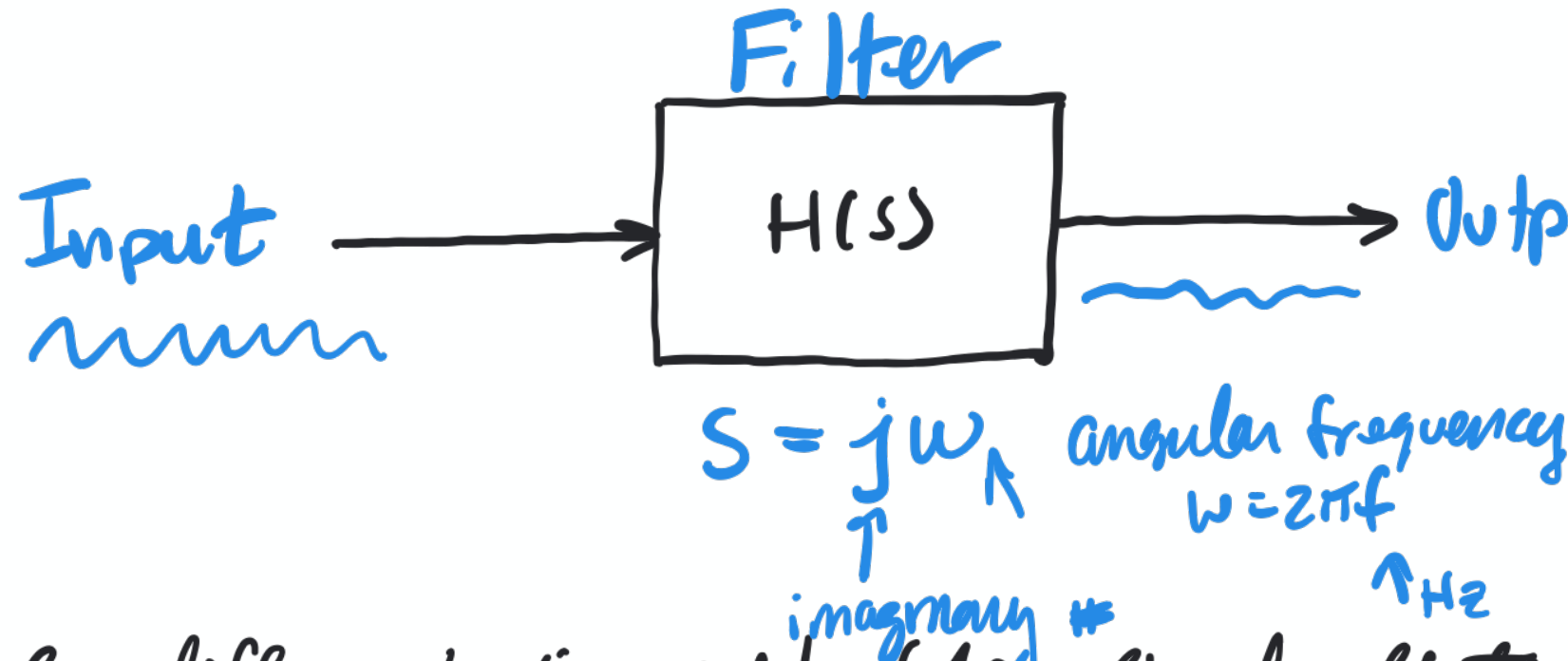


# Intro to ECSE Lecture Notes

1

## Frequency Response (Filters) Pt. 2

### 1) Filters as Transfer Functions



• Filters are defined by their transfer functions  $H(s)$

### 2) $s$ for different sinusoids (AC Steady State Signals)

sinusoid #1:   $f_1 = 60 \text{ Hz}$

Which one has the higher frequency?

sinusoid #2:   $f_2 = 120 \text{ Hz}$

1 or (2)

• What is  $s$  for #1?  $s_1 = j\omega_1 = j2\pi f_1 = j376.99 \text{ [rad/s]}$

#2?  $s_2 = j\omega_2 = j2\pi f_2 = j753.98 \text{ [rad/s]}$

# Complex Numbers and the Complex Plane



$$z = a + jb$$

$\uparrow$  complex number  
 $\uparrow$  real part  
 $\uparrow$  imaginary part

Complex conjugate (\*)

$$z^* = a - jb$$

replace  $j$  with  $-j$

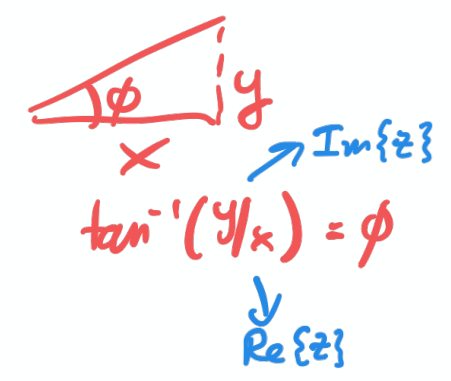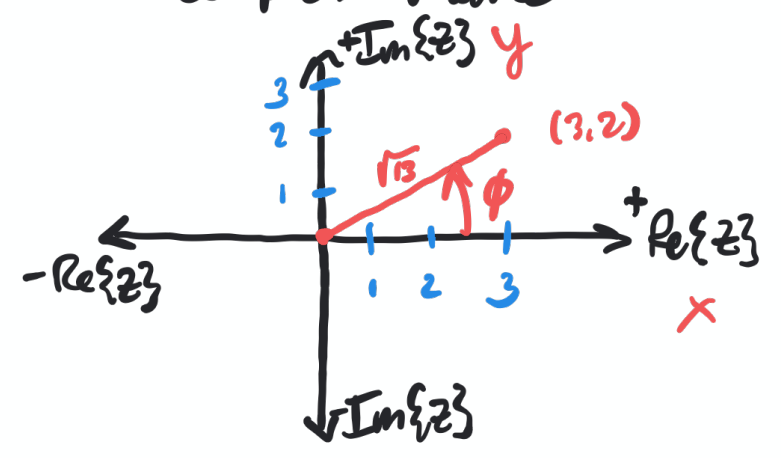

Plot the number:  $3 + j2$

$$\begin{aligned} \text{Re}\{z\} &= 3 \\ \text{Im}\{z\} &= 2 \end{aligned}$$

Find the magnitude  $|z|$

$$\begin{aligned} \text{magnitude } |z| &= \sqrt{z z^*} = \sqrt{(3+j2)(3-j2)} \\ &= \sqrt{3^2 + j^2 4 - j^2 4 + 2^2} \\ &= \sqrt{13} \end{aligned}$$

$$\begin{aligned} j \cdot j &= -1 \\ +j \cdot (-j) &= 1 \end{aligned}$$


$$V_{out} = H(j\omega) \cdot V_{in}$$

$|V_{out}|$  is what we measure (real)

Find the phase  $\angle z$


$$\angle z = \tan^{-1}(\text{Im}(z)/\text{Re}(z)) = \tan^{-1}(2/3) \approx \underline{33.7^\circ}$$

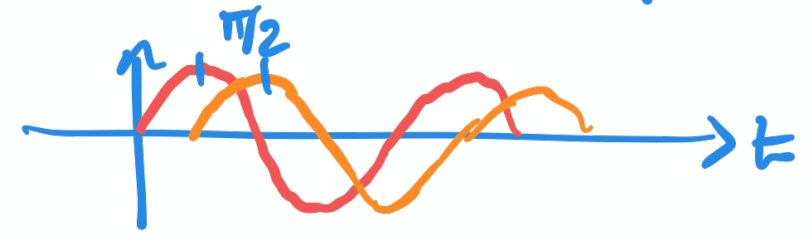Phase is how much the output is shifted relative to the input



### 3) Anatomy of a Filter Transfer Function

3

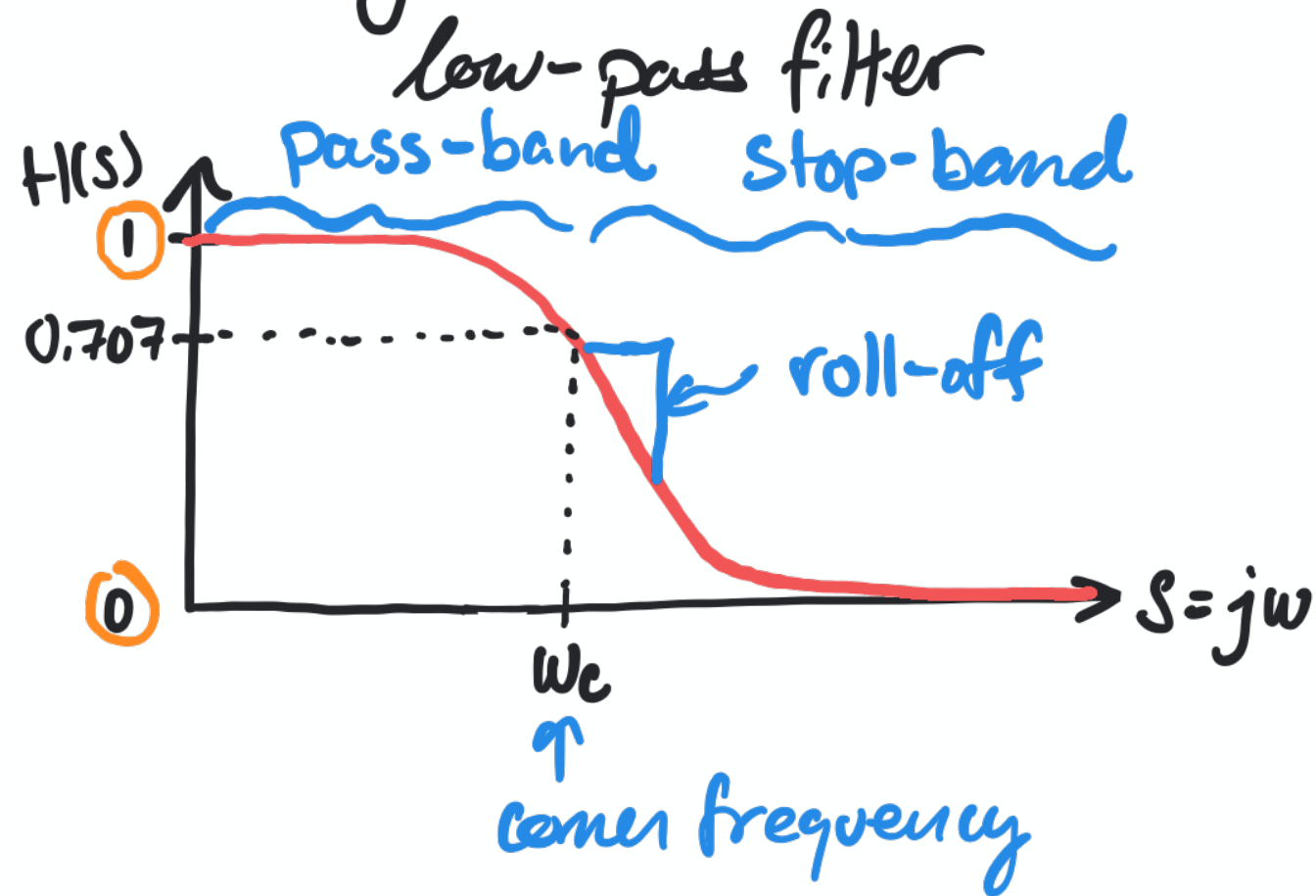

when  $H = 1 \rightarrow V_{out} = V_{in}$

$H = 0 \rightarrow V_{out} = 0$

attenuation: opposite of amplification


- corner frequency is where  $|H(jw)| = 1/\sqrt{2}$   
→ tells us where the filter begins to change the output signal

- Pass-band: filter allows frequency components to go through

- Stop-band: filter blocks these frequencies

- roll-off: steepness of the transfer function of the filter → determines how quickly signal is attenuated vs. frequency
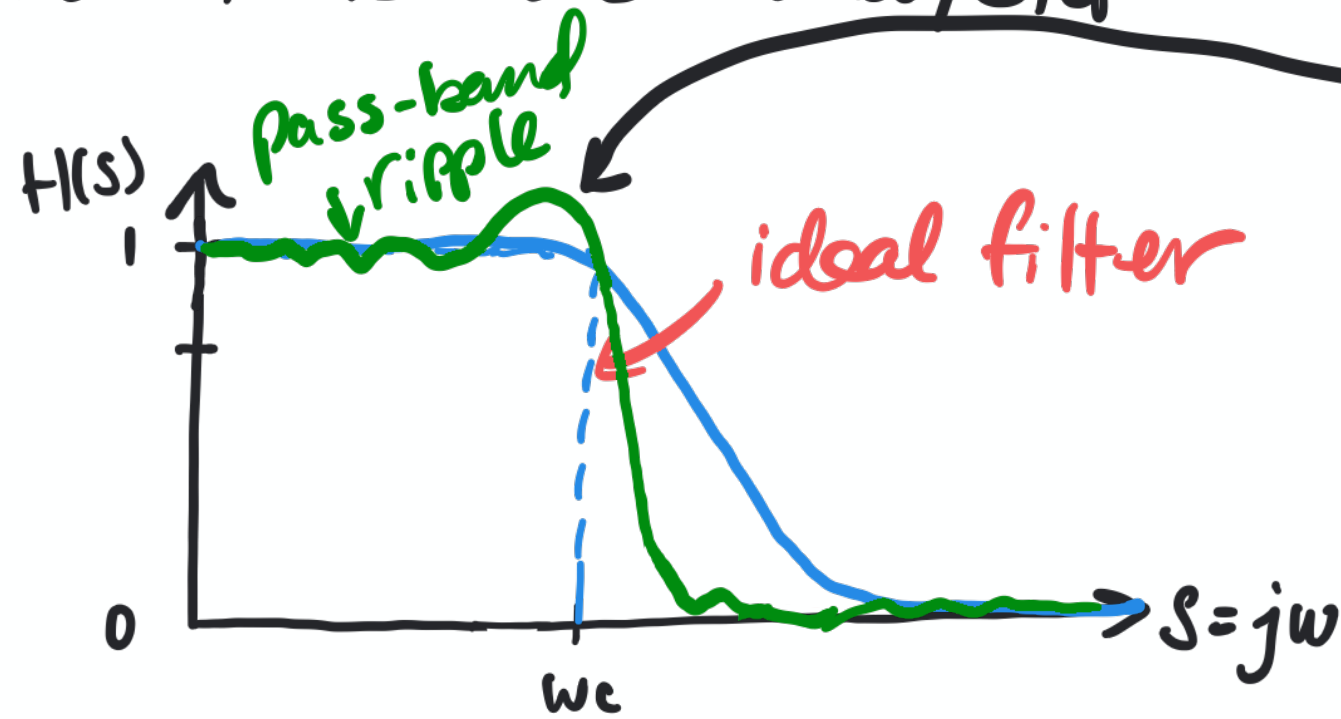
#### 4) Roll-off vs. Pass-band/Stop-band Flatness (vs. complexity) 4



- Stop-band/pass-band ripple can distort the signal because one component gets amplified more than others.

# 5) Review of RLC and Impedance



$j\omega$ :  $Z_R = R$        $Z_C = 1/j\omega C$        $Z_L = j\omega L$

Resistor      Capacitor      Inductor


$s$ :  $Z_R = R$        $Z_C = 1/sC$        $Z_L = sL$

Circuit equivalent	$s \rightarrow 0$	$R$ 	$Z_C \rightarrow \infty$ open circuit	$Z_L \rightarrow 0$ short circuit
	$s \rightarrow \infty$	 $R$	short circuit	open circuit



b) 1st Order RC Circuit (Example using s)

b

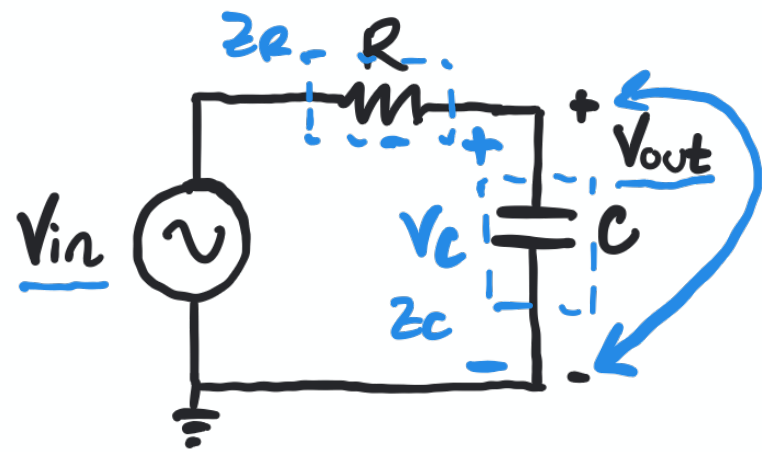

a) What is  $V_{out}$ ?  $V_{out} = V_c$

$$V_{out} = V_{in} \frac{Z_c}{Z_R + Z_c} = V_{in} \frac{1/j\omega C}{R + 1/j\omega C} \cdot \frac{j\omega C}{j\omega C}$$

$$= V_{in} \frac{1}{j\omega RC + 1} \rightarrow H(j\omega) = \frac{1}{j\omega RC + 1}$$

b) What is  $H(\omega \rightarrow 0)$ ?

$$H(\omega \rightarrow 0) = \frac{1}{0 + 1} = \underline{1}$$

c) What is  $H(\omega \rightarrow \infty)$ ?

$$H(\omega \rightarrow \infty) = \frac{1}{\infty + 1} = \frac{1}{\infty} \rightarrow \underline{0}$$

d) What kind of filter is this?

low-pass filter

