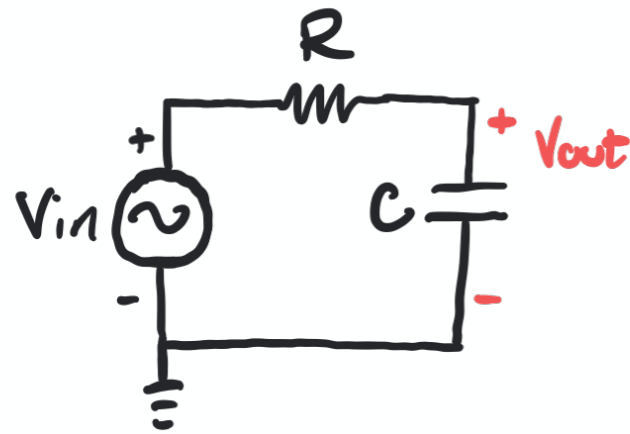


Intro to ECSE Lecture Notes 4/14


Filters... Part 3: Review: first order RC filter

1



• Transfer function: $H(j\omega) = \frac{1}{j\omega RC + 1}$

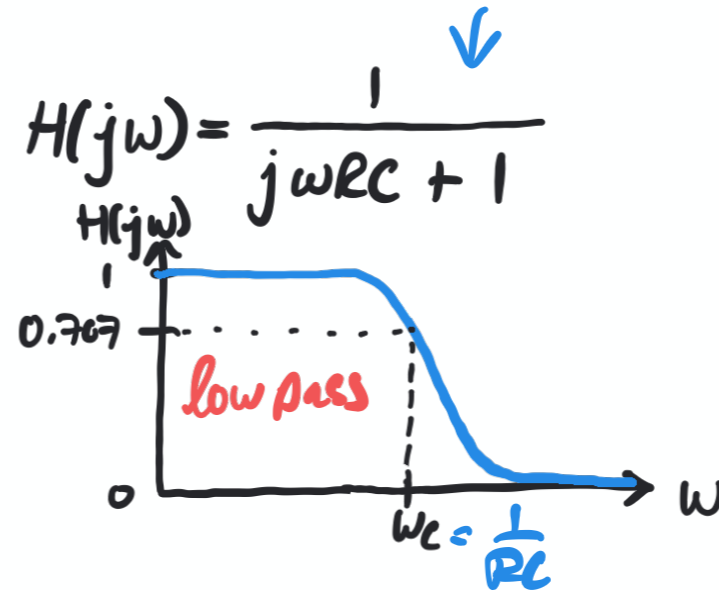- $H(\omega \rightarrow 0) \rightarrow 1$
- $H(\omega \rightarrow \infty) \rightarrow 0$



• What about the corner frequency? $|H(\omega_c)| = 1/\sqrt{2}$

• Why $1/\sqrt{2}$? $P = I^2 R = \frac{V^2}{R} \cdot V = \frac{V^2}{R}$ $\leftarrow H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{V}{V}$

Power transfer function: $|H(j\omega)|^2 \propto V^2 \rightarrow$ when power $\rightarrow 1/2$

• $\omega_c = ?$ $|H(j\omega)|^2 = \frac{1}{2} \rightarrow |H(j\omega)|^2 = H(j\omega)H(-j\omega) = \left(\frac{1}{j\omega RC + 1}\right) \cdot \left(\frac{1}{-j\omega RC + 1}\right)$

$$(\omega RC)^2 + 1 = 2$$

$$\omega_c = \frac{1}{RC} \text{ corner frequency}$$

$$f_c = \frac{1}{2\pi RC} \text{ [Hz]}$$


$$= \frac{1}{(\omega RC)^2 + 1} = \frac{1}{2}$$

$$\uparrow (j\omega RC) \cdot (-j\omega RC) = (\omega RC)^2 \cdot \overbrace{(j)(-j)}^1$$

$$j \cdot j = -1$$

$$j = \sqrt{-1}$$

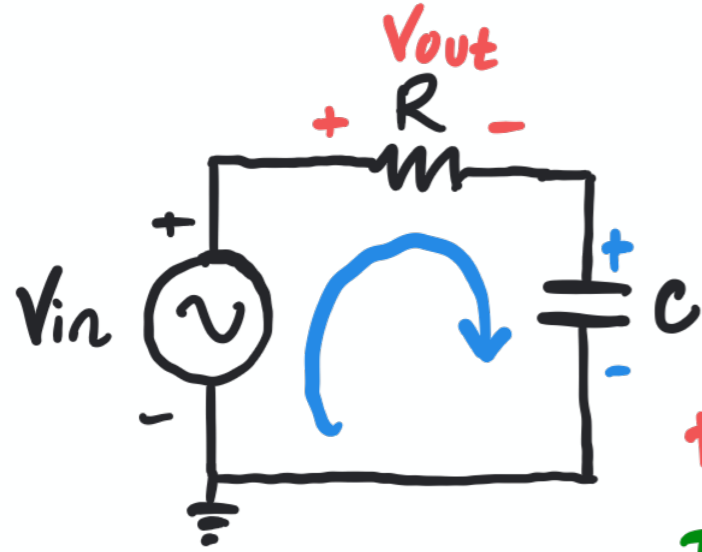• What would we get if we measured across R instead? ²




• KVL: $-V_{in} + V_R + V_C = 0$

$V_{in} = V_R + V_C$
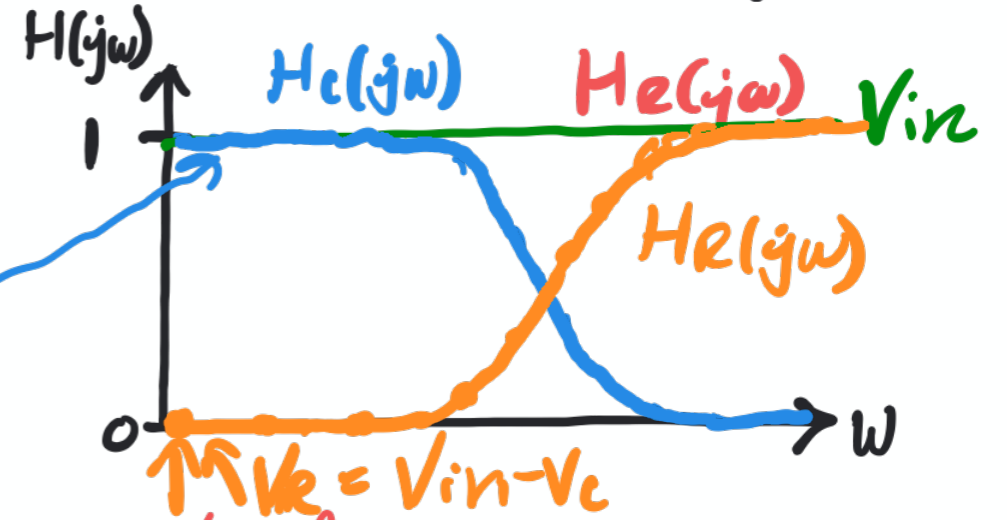
#1, C: $V_{in} = V_R + V_{out}$

IF $V_{in}(w)$ is 1: what do we get when we measure across R?




• we get a high pass filter

$V_R = V_{in} - V_C$ \leftarrow curve defined by $H(jw)$
 constant

• Transfer function $H(jw) = \frac{Z_R}{Z_R + Z_C} = \frac{R}{R + 1/jwC} \cdot \frac{jwC}{jwC} = \frac{jwRC}{jwRC + 1}$

$H(w \rightarrow 0) = \frac{0}{0+1} = 0$
 $H(w \rightarrow \infty) = \frac{\infty}{\infty+1} \approx \frac{\infty}{\infty} = 1$ } high-pass filter

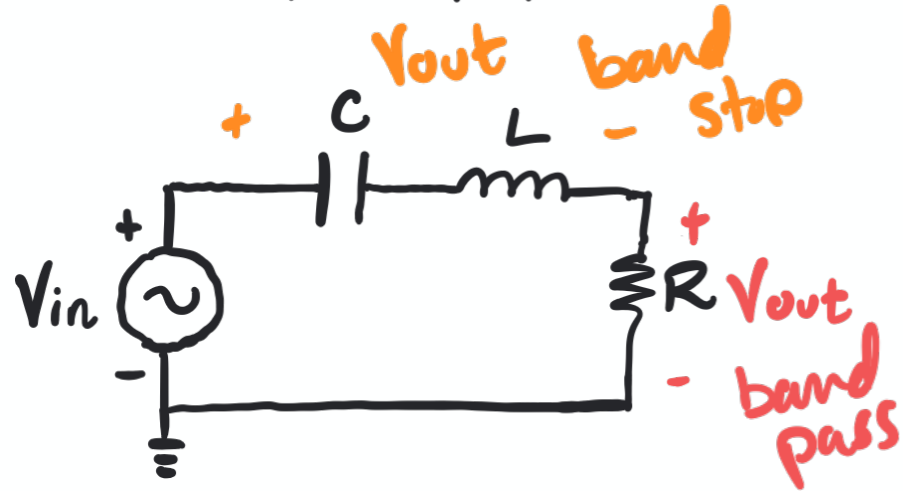• Band-Pass Filter (2nd order) [Example using s]



a) what is V_{out} ?

$$V_{out} = V_{in} \frac{Z_R}{Z_R + Z_C + Z_L} = \frac{R}{R + \frac{1}{sC} + sL} V_{in}$$

$$= \frac{(sL)}{(sL)} \frac{R}{R + \frac{1}{sC} + sL} V_{in} = \frac{sR}{s^2 + s\frac{R}{L} + \frac{1}{LC}} V_{in}$$

want $\frac{SC}{s^2 + as + b}$
 constant
 \uparrow const. \uparrow

b) What is the transfer function?

$$H(s) = \frac{sR/L}{s^2 + sR/L + 1/LC}$$


c) what is $H(s \rightarrow 0)$? $H \rightarrow \frac{0}{0 + 0 + 1/LC} = 0$

d) what is $H(s \rightarrow \infty)$?

$$H \rightarrow \frac{sR/L}{s(s + R/L) + 1/LC} \xrightarrow{\text{for very large } s} \frac{sR/L}{s(s + R/L) + 1/LC} = \frac{sR/L}{s^2 + 1/LC}$$

$s \gg R/L$ $s^2 \gg 1/LC$
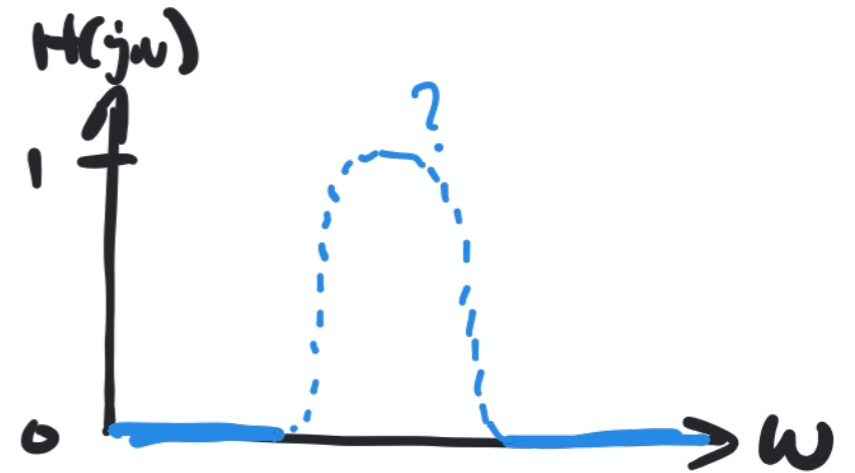
$$= \frac{sR/L}{s^2} = \frac{R/L}{s} \rightarrow \text{if } s \rightarrow \infty, H \rightarrow \frac{R/L}{\infty} \rightarrow 0$$



e) Where does $|H(j\omega)| = 1$?

$$H(s) = \frac{sR/L}{s^2 + sR/L + 1/LC} \cdot \frac{(L/s)}{(L/s)} = \frac{1}{s\frac{L}{R} + 1 + \frac{1}{sRC}} = 1$$

$$s\frac{L}{R} + 1 + \frac{1}{sRC} = 1 \rightarrow s^2 = -\frac{1}{LC} = (j\omega)^2 = -\omega^2 \rightarrow \omega = \frac{1}{\sqrt{LC}}$$

center frequency $\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow H=1$

f) What about the corner frequencies?

$$\left. \begin{aligned} \omega_{c1} &= \frac{R}{L} \\ \omega_{c2} &= \frac{1}{RC} \end{aligned} \right\}$$

$\omega_{c2} - \omega_{c1} = \text{bandwidth of filter}$

