
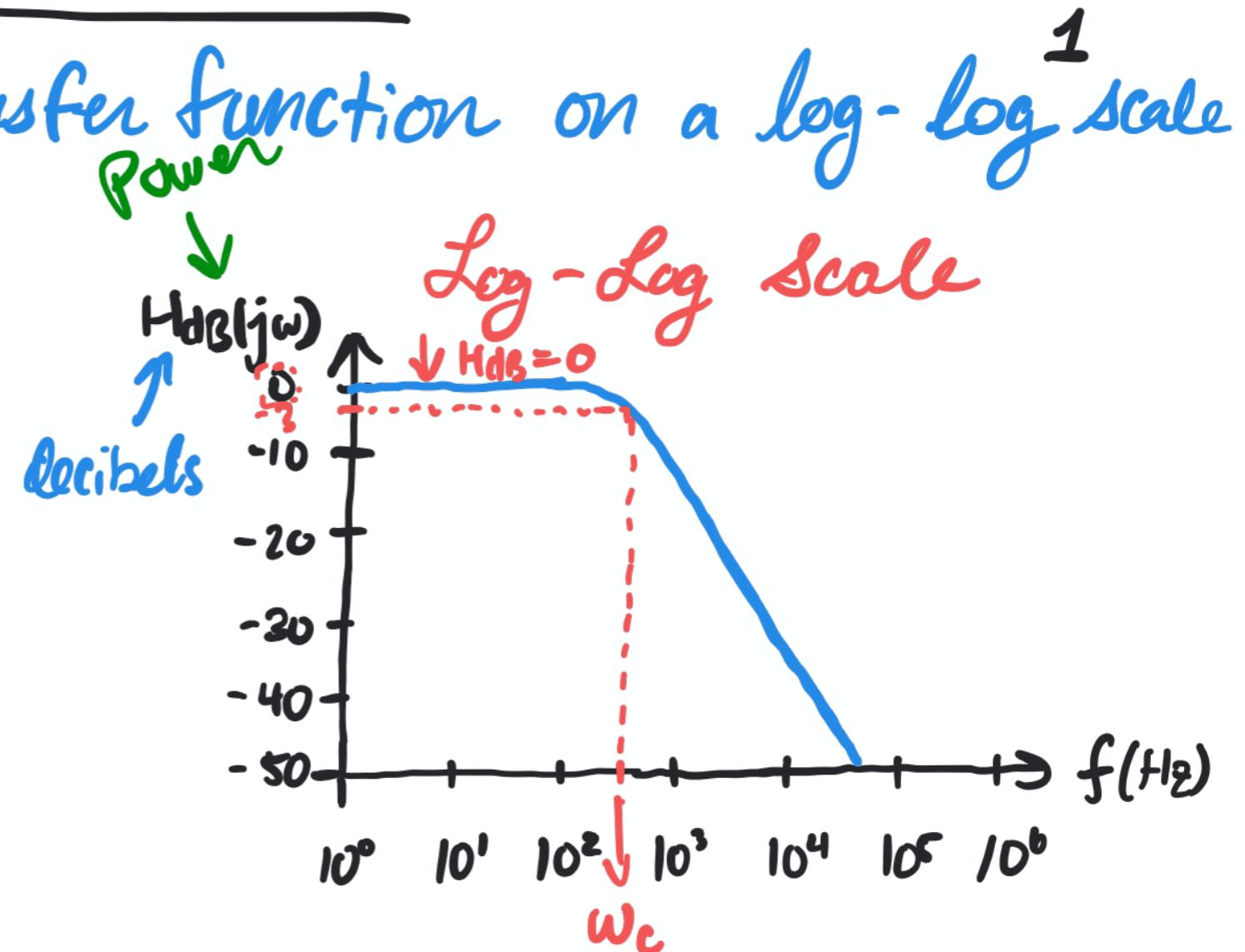


Intro to ECSE Lecture Notes 4/18/23

1) Bode Plots : plot of transfer function on a log-log scale

Voltage

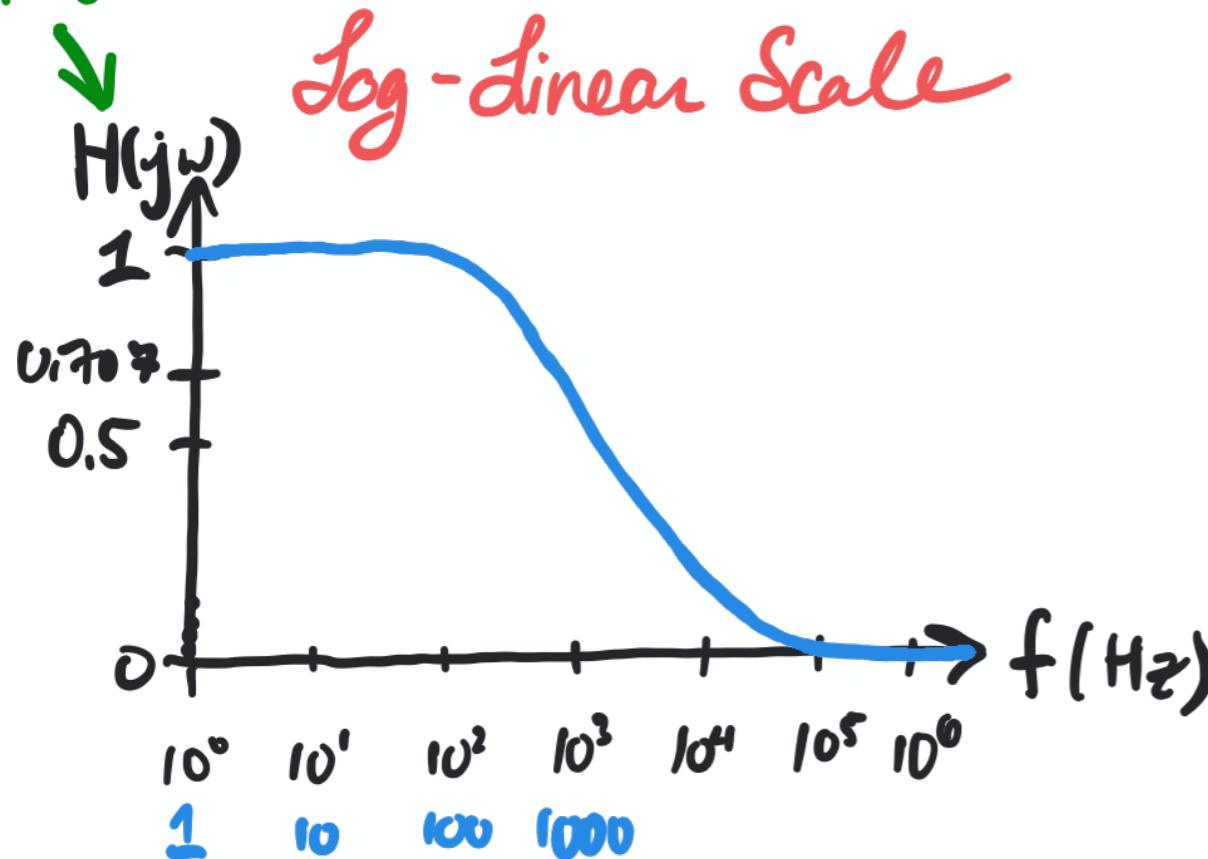

- The y-axis of a Bode plot is given in decibels
- A decibel is a logarithmic power ratio

$$\text{Power ratio} = \frac{P_{\text{out}}}{P_{\text{in}}} \xrightarrow{\text{output power}} \xleftarrow{\text{input power}}$$

2) Decibels: \log_{10} based representation of a power ratio 2

$$\text{Power Ratio} = \frac{P_{\text{out}}}{P_{\text{in}}}$$

- In many cases, these power ratios are very small (10^{-6}) or very large (10^6), so it is more convenient to express them in terms of a logarithm:

$$\log_{10}(\text{Power Ratio}) = \log_{10}\left(\frac{P_{\text{out}}}{P_{\text{in}}}\right) = 1 \text{ bel}$$

Alexander
Graham
Bell

1bel = 10 decibels (metric prefix deci = 0.1)

$$(?) 0.1 \text{ dB} = \log_{10}\left(\frac{P_{\text{out}}}{P_{\text{in}}}\right) \rightarrow 1 \text{ dB} = \underline{10 \log_{10}\left(\frac{P_{\text{out}}}{P_{\text{in}}}\right)} = \text{Power}$$

- What is the power ratio $\frac{1}{2}$ in dB?

$$(\frac{1}{2})_{\text{dB}} = 10 \log_{10}\left(\frac{1}{2}\right) = -3.01 \text{ dB}$$

on a Bode Plot, this is the location of ω_c
($\frac{1}{2}$ on a linear scale)

- If we want H in Volts/Volt expressed logarithmically

$$H_{\text{V, dB}} = 20 \log_{10}(H)$$

↑ Volts

- What is H_{dB} when $\frac{V_{\text{out}}}{V_{\text{in}}} = 1$?

$$H_{\text{dB}} = 10 \log_{10}(1) = 0$$

$$1 = 10^a \rightarrow \log_{10}(10^a) = a$$

Filter Circuit Steps :

1) Convert circuit elements to impedances

2) Find output voltage using a voltage divider using Z

3) Replace the Z variables with their expressions in terms of their component values ($Z_C = 1/j\omega C$)

4) Find $H = \frac{V_{out}}{V_{in}}$



5) Use algebra to get $H(s) = \frac{N(s)}{s + a}$

\nwarrow numerator
 (may have s) \nwarrow 1st order
 \nwarrow constant $= \omega_c$ circuits

b) Sketch a Bode Plot by evaluating



$H(s \rightarrow 0)$ and $H(s \rightarrow \infty)$.

 4*) Find $|H| = \sqrt{HH^*}$
 and evaluate at different frequencies

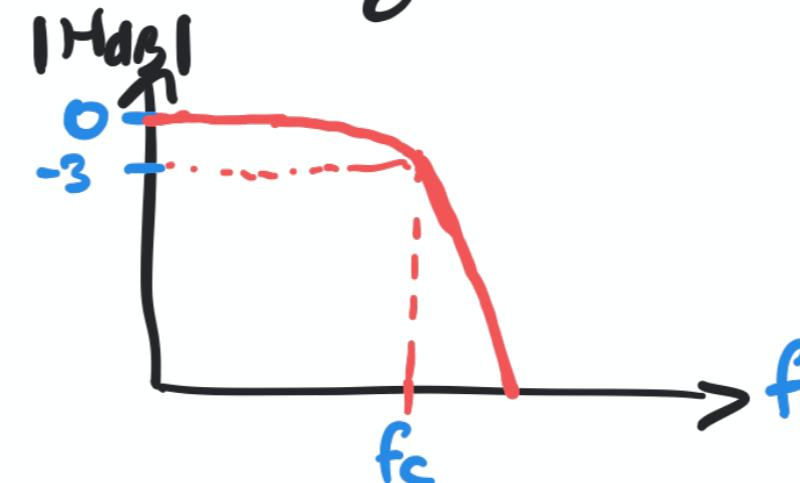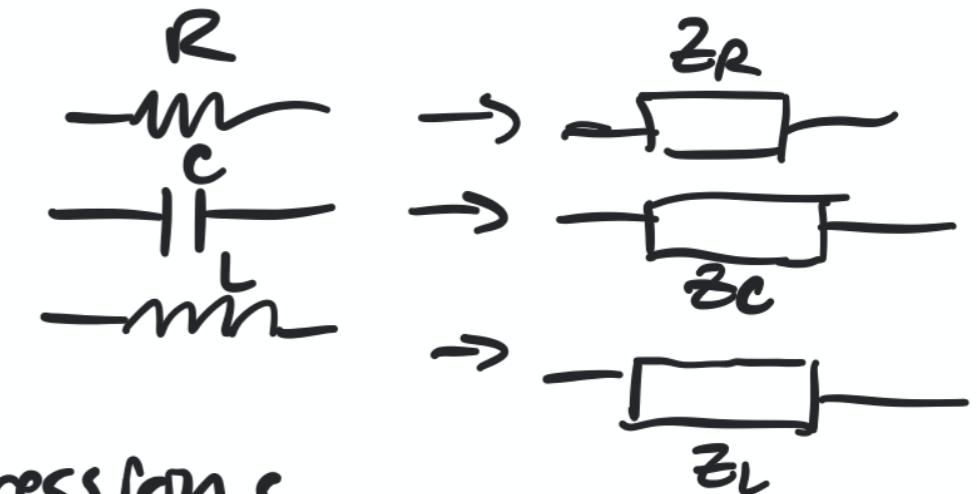

Example Problem #1:

4

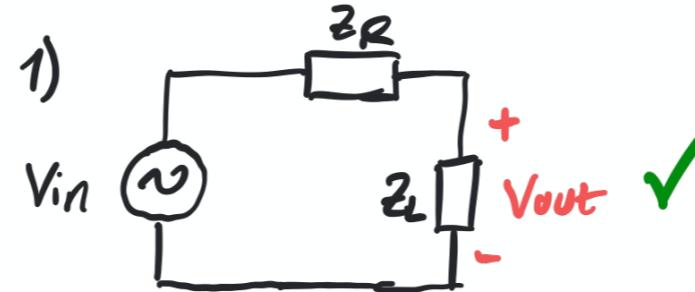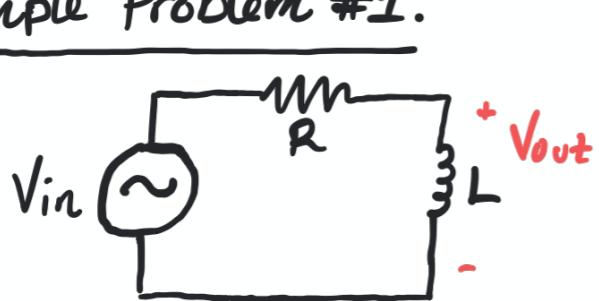

$$2) V_{out} = V_{in} \frac{Z_L}{Z_L + Z_R} \quad \checkmark$$

$$Z_L = sL$$

$$Z_R = R$$

$$4*) |H(j\omega)| = \sqrt{H(j\omega) \cdot H(-j\omega)} \quad b) V_{out} = V_{in} \frac{sL}{sL + R} \quad \checkmark$$

$$H(j\omega) = \frac{j\omega}{j\omega + R/L} \quad j \cdot j = -1 \quad j(-j) = 1$$

$$4) H(s) = \frac{sL}{sL + R} \quad \checkmark$$

$$|H(j\omega)| = \sqrt{\left(\frac{j\omega}{j\omega + R/L}\right) \cdot \left(\frac{-j\omega}{-j\omega + R/L}\right)}$$

$$= \sqrt{\frac{\omega^2}{\omega^2 + j\omega R/L - j\omega R/L + (R/L)^2}}$$

$$= \frac{\omega}{\sqrt{\omega^2 + (R/L)^2}} = |H(j\omega)|$$

$$5) H(s) = \frac{s}{s + R/L} \quad \checkmark$$



0dB
decade = factor
of 10
inf (for example
 $10 \rightarrow 100$)

$$H(s \rightarrow 0) = \frac{0}{0 + R/L} = 0$$

$$H(s \rightarrow \infty) = \frac{\infty}{\infty + R/L} \sim \frac{\infty}{\infty} \sim 1$$


$$f_c = \frac{R}{2\pi L}$$

LT Spice: $R = 100\Omega$

$$L = 5mH$$

$$f_c = 3183 \text{ Hz}$$

$V_{out} = |H(j\omega)| V_{in}$
Voltage amplitude
that would be measured

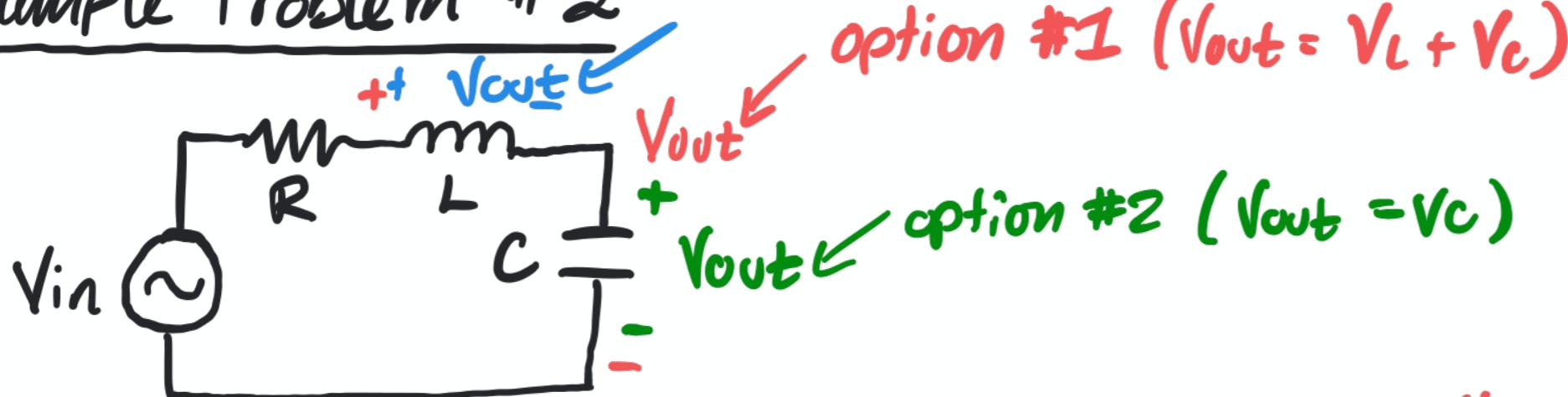Example Problem #2option #3 ($V_{out} = V_L$)option #1 ($V_{out} = V_L + V_C$)option #2 ($V_{out} = V_C$)

$$\#1) H(s) = \frac{sL + 1/sC}{R + sL + 1/sC} = \frac{s^2 + 1/LC}{s^2 + sR/L + 1/LC} \rightarrow H(s \rightarrow 0) = 1 \quad \rightarrow H(s \rightarrow \infty) = 1$$

$$\#2) H(s) = \frac{1/sC}{R + sL + 1/sC} = \frac{1/LC}{s^2 + sR/L + 1/LC} \rightarrow H(s \rightarrow 0) : 1 \quad \rightarrow H(s \rightarrow \infty) : 0$$

$$\#3) H(s) = \frac{sL}{R + sL + 1/sC} = \frac{s^2}{s^2 + sR/L + 1/LC} \rightarrow H(s \rightarrow 0) : 0 \quad \rightarrow H(s \rightarrow \infty) : 1$$

