

Intro to ECSE Lecture Notes 4/21


1

Quiz 3 Topics:


- Difference between DC and AC signals
- Signals in the time domain vs. frequency domain
- Representations of sine waves in the time and frequency domains
- Impedance of resistors, capacitors, and inductors
- Transfer functions for 1st and 2nd order filter circuits
 - magnitude (be able to calculate), phase (be able to describe)
 - corner frequency (1st order low-pass and high-pass filters)
 - center frequency (2nd order band-pass + band-stop filters)
 - Bode plots
 - decibels
- Application of filters

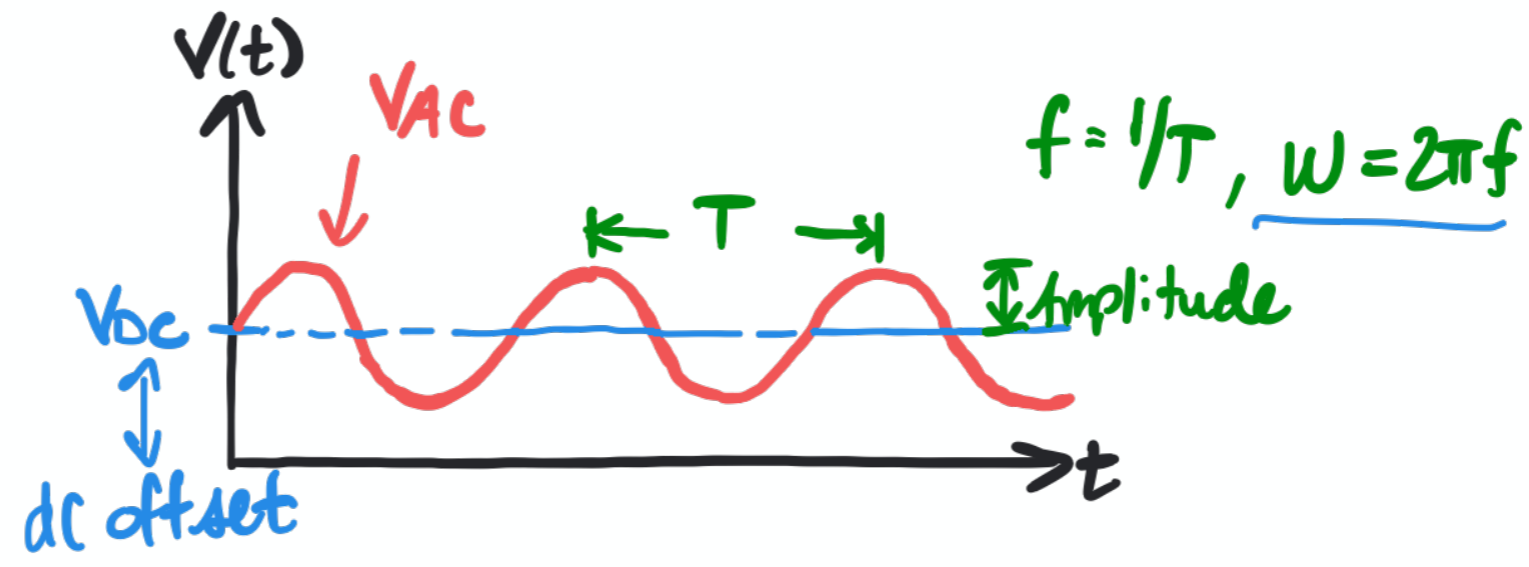1) DC vs. AC signals :

$$V(t) = \underline{V_{DC}} + \underline{V_{AC}}(t)$$




2) Time vs. Frequency Domain

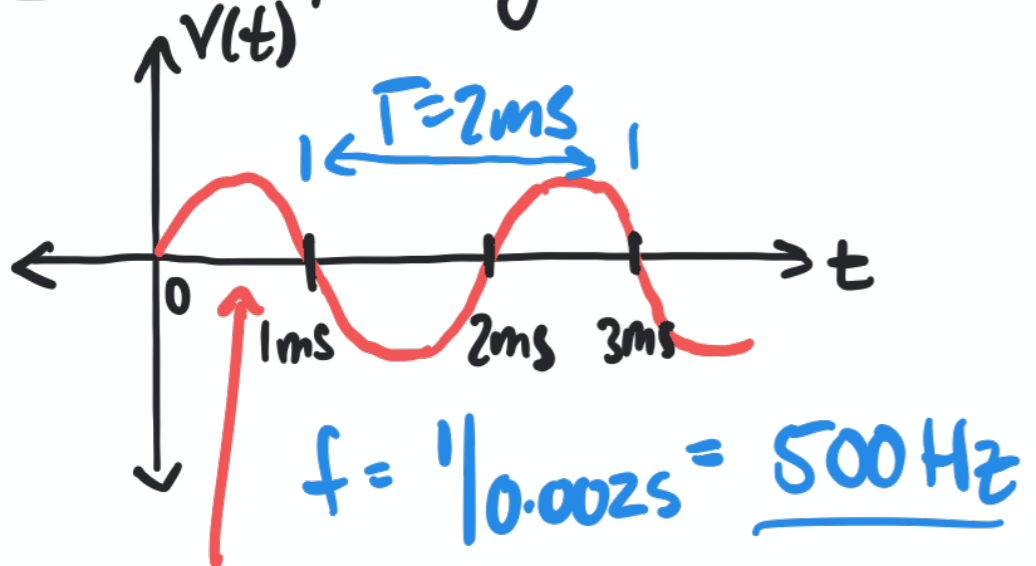

$$A \sin(2\pi \cdot 500 \cdot t)$$

↑
Hz

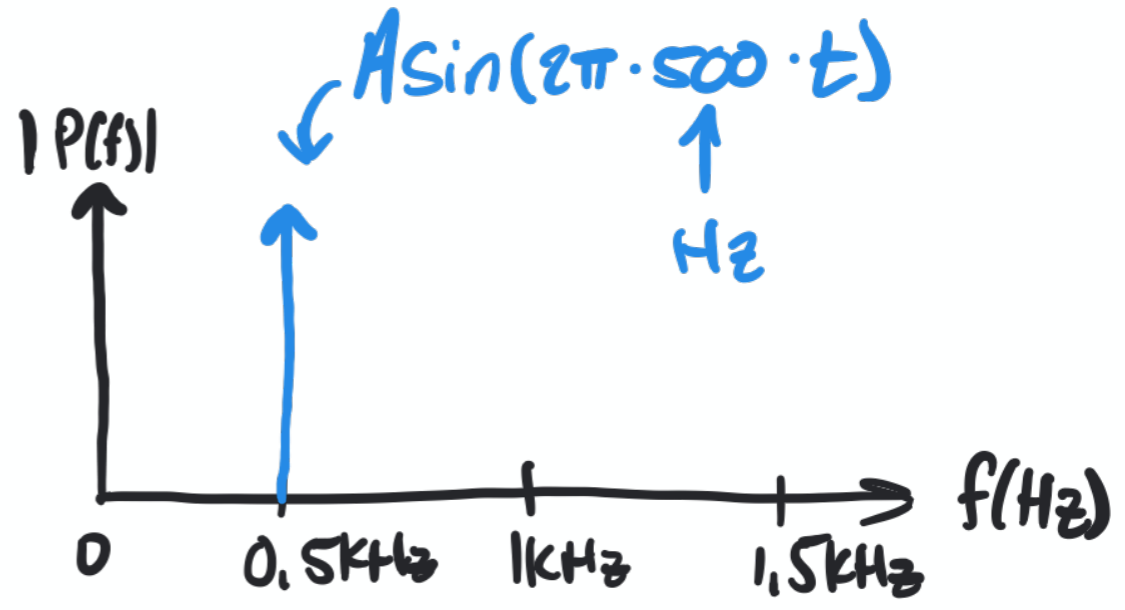

• In the frequency domain $\sin(2\pi f t)$ is a peak at $f = f_0$

3) Impedance of Resistors, Capacitors and Inductors

$Z_R = R$; $Z_C = \frac{1}{j\omega C}$; $Z_L = j\omega L$ where $\omega = 2\pi f$

• at low frequency ($\omega \rightarrow 0$): $\begin{cases} Z_R = R \\ Z_C \rightarrow \infty \text{ open circuit} \\ Z_L \rightarrow 0 \text{ short circuit} \end{cases}$

• at high frequency ($\omega \rightarrow \infty$): $\begin{cases} Z_R = R \\ Z_C \rightarrow 0 \text{ short circuit} \\ Z_L \rightarrow \infty \text{ open circuit} \end{cases}$

4) Transfer Functions for Filter Circuits


Given a filter circuit: 1) find V_{out} & $H(s)$ (find $|H(s)|$)

2) Evaluate for $s \rightarrow 0$; $s \rightarrow \infty$

3) Sketch Bode plot

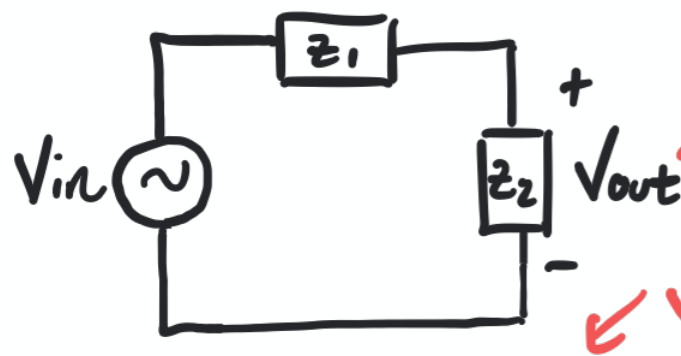4) find corner or center frequency

$H_{v,dB} = 20 \log_{10} \left(\frac{P_{out}}{P_{in}} \right)$




← voltage

$H_{v,dB} = 20 \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$ also be able to convert H to Decibels

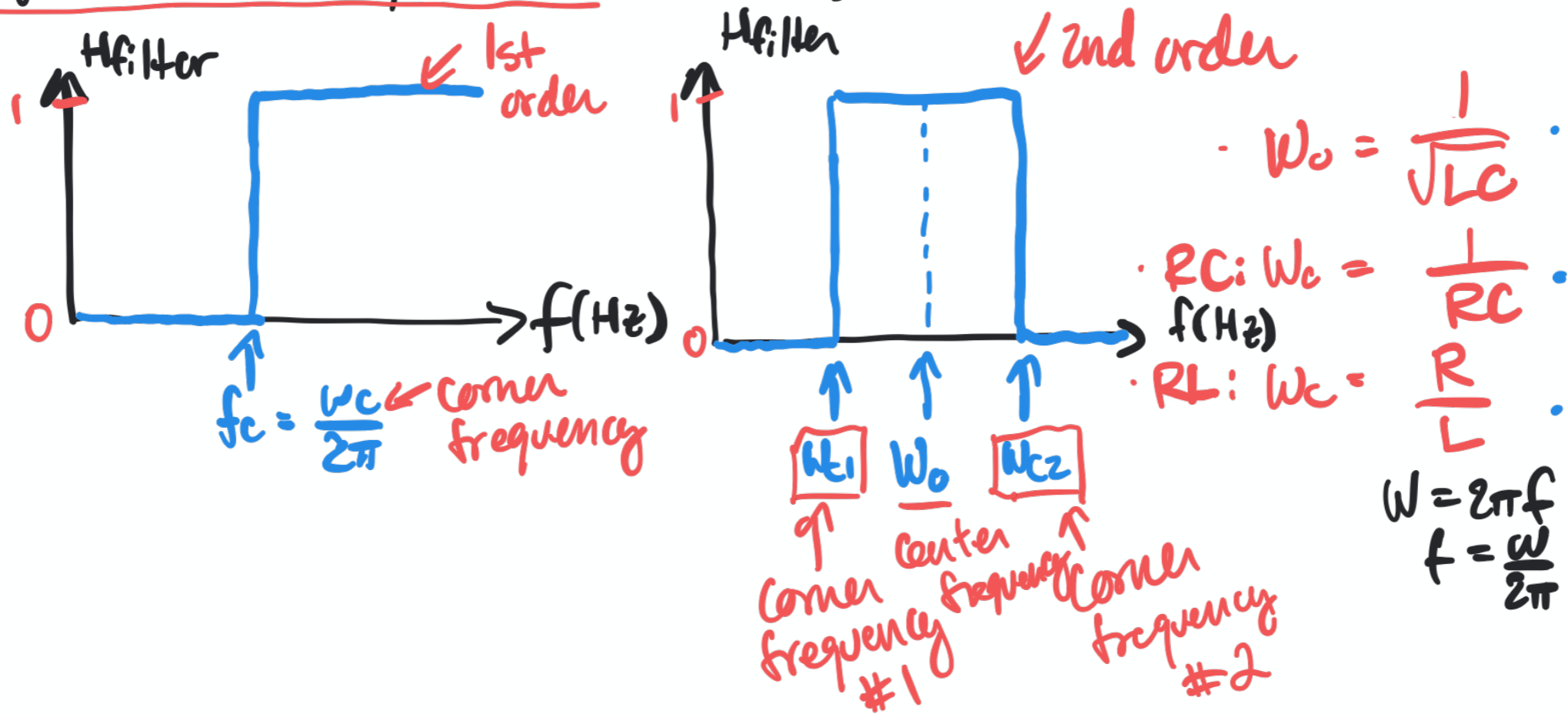5) Applications of Filters

↓ information


- Given a desired range of frequencies and a frequency response plot, be able to identify where the desired information is and where the noise is. BPF, BSF, LPF, HPF
- Know what kind of ideal filter we can use to isolate the information/noise
- Be able to specify an appropriate corner frequency (1st order) or center frequency & corner frequencies (2nd order) for an ideal filter.



Notes on the Final Exam: Wednesday 5/3, 3pm - 6pm Academy Auditorium ⁵

- Cumulative: will test material covered by lab01 - lab03
- May mix concepts from multiple parts of the course, for example:

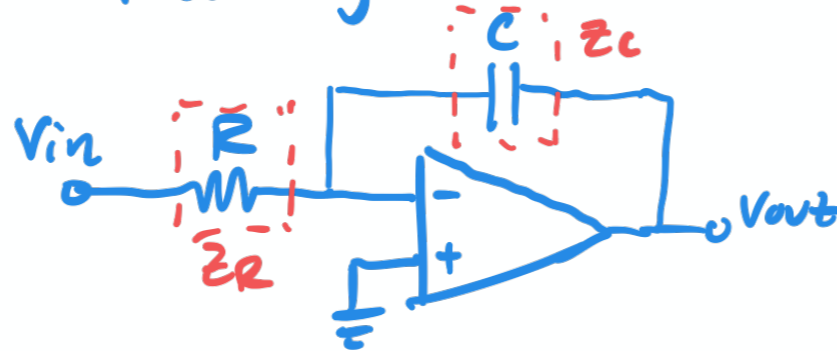Find the transfer function of the following circuit: inv. amp: $H = -\frac{R_f}{R_i}$



$$H(s) = -\frac{Z_c}{Z_R} = -\frac{1}{j\omega RC}$$

$$V_{out} = -\frac{1}{RC} \int V_{in}(t) dt$$

- Open notes: cannot be electronic or include quiz solutions
- Non-communicating calculator allowed
- Requirements for opting out of final:

- 2/3 omega labs completed
- 80%+ on those two omega labs
- ~88/88 on proof of skills

→ I will let you know after Quiz 3 if you are able to opt out (if you completed 2/3 omega labs)

→ If you may opt out, but still want to take the final, *it cannot lower your grade, only help!*