


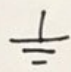
1) Voltage - unit: Volts (V)



EE language: { "voltage across" an element (i.e. resistor)
 "voltage at" a location (i.e. node)
 Voltage = $\frac{\Delta \text{potential energy}}{\Delta \text{charge}} = \frac{dW}{dq}$

2) Current - unit: Amperes (A)

EE language: { "current through" an element (i.e. resistor)
 "current to" a location (a node)
 "current from" a location (a node)
 current = $\frac{\Delta \text{charge}}{\Delta \text{time}} = \frac{dq}{dt} = i$

3) Ground: our reference point for voltage in circuits

Symbols:  

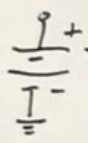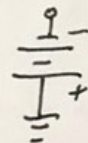
 7.8V  6.7V ← voltage difference can be negative! $V < 0$



4) Power: $P = \frac{\Delta \text{energy}}{\Delta \text{time}} = \frac{dW}{dt}$


EE language: "power applied" to an element/component
 "power dissipated" in/by an element/(i.e. resistor) component


• always referenced to a component


5) I-V Characteristics

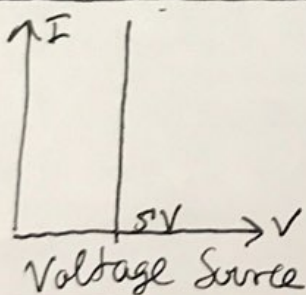

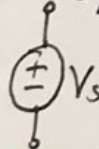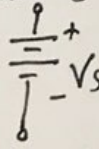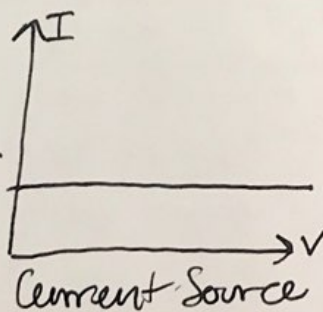Symbols:  V_s  $-V_s$
 • supplies constant voltage across all currents 1A



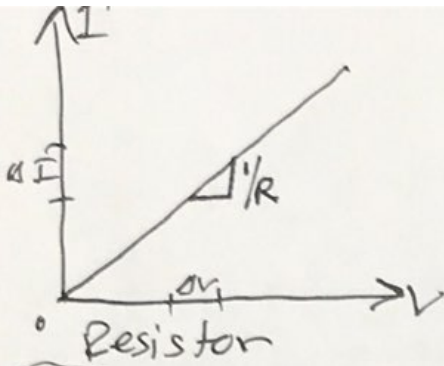
Symbol: 
 • supplies constant current across all voltages




~~$\Delta V = \Delta I R$~~ $\Delta V = \Delta I R \rightarrow \frac{1}{R} = \frac{\Delta I}{\Delta V}$

slope: $\frac{dy}{dx} = \frac{\Delta I}{\Delta V}$

(2)

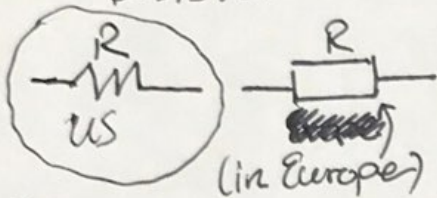



Passive Sign Convention

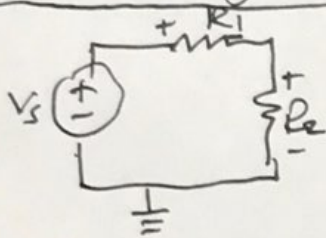


EE convention
 $\begin{matrix} + & \longrightarrow & - \\ \uparrow & & \uparrow \end{matrix}$
 reference marks

- For KVL & KCL, choose/place reference marks first
- For nodal analysis, choose current direction first

Example Problem

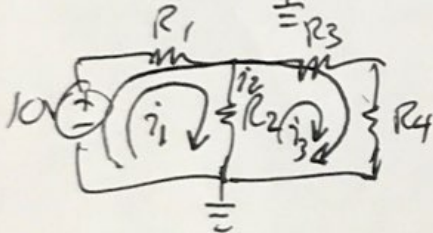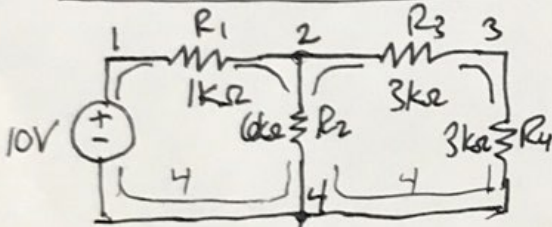

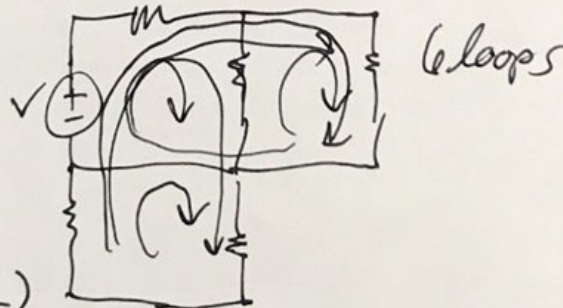
- 1) What is anode? Any connections between any number of components
- 2) What is a loop? Any enclosed circle in the circuit




Kirchoff's Current Law (KCL)

+ conservation of charge \rightarrow all current entering a node must sum to zero

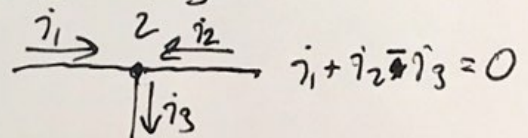• current pointing away from the node gets a "-" sign, towards gets a "+" sign



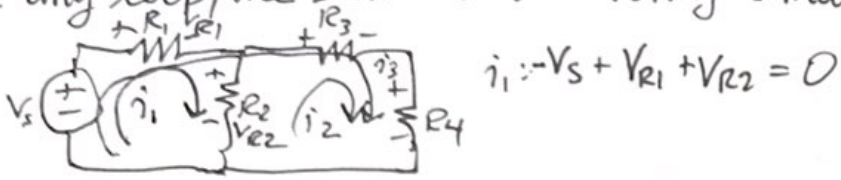
8) Kirchoff's Voltage Law (KVL) - conservation of energy
 • in any loop, the sum of the voltages must equal zero (3)



9) Circuit Reduction: combining elements to simplify a circuit

Resistors in parallel:


Symbol: $R_1 || R_2$
 $R_{eq}^{par} = R_1 || R_2$
 $= \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

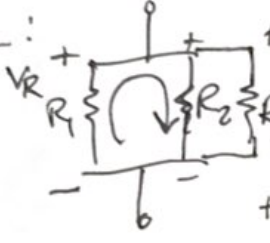

+ Resistors in parallel create a loop containing no other elements


+ Voltage across resistors in parallel is the same
 $R_{eq}^{parallel} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

Resistors in Series:

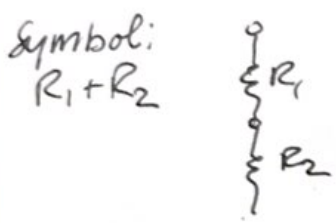

+ have one common node to which no other elements are connected
 $R_{eq}^{series} = R_1 + R_2$

10) "Quiz"

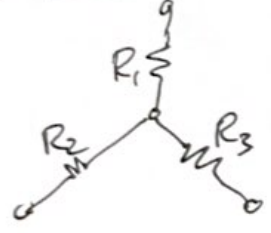


Series? Parallel? Neither?



- Not series because a 3rd element is connected in between the other 2
- Not parallel because none of the resistors form a loop (they're not connected at both ends)

11) Task: Find $V_{out} = V_{R4}$

(4)

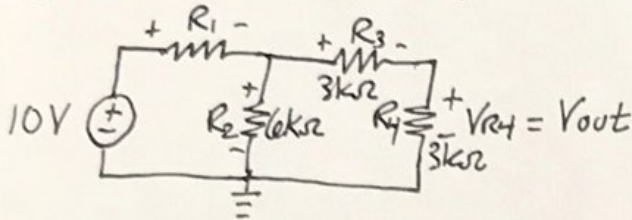


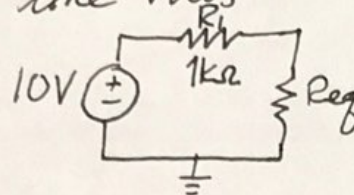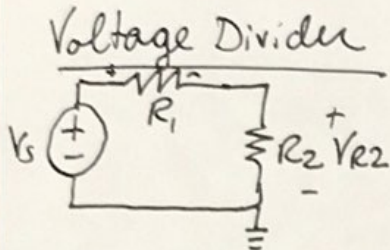Goal is to solve this via the method of circuit reduction:
We want a circuit that looks like this:




In a series circuit with a voltage source, the source voltage is divided up between each of the resistors, proportional to their resistance values via the following formula:

Step 1) Combine R_3 and R_4 (series)

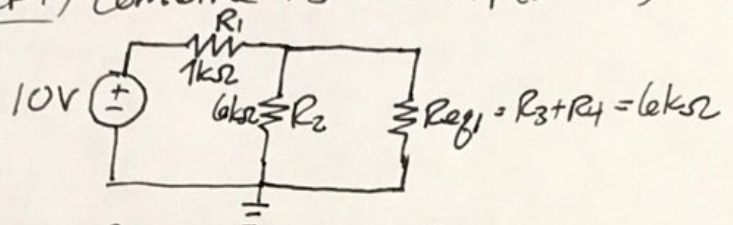


Step 2) Combine R_2 and Req_1

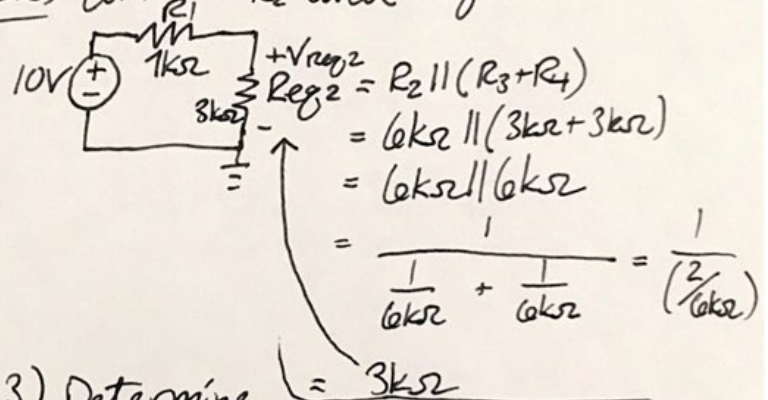

$$V_{out} = V_{in} \frac{R_{out}}{\sum_i R_i} \text{ where}$$

- R_{out} is the resistance over which the voltage of interest is dropped
- $\sum_i R_i$ is the sum of all resistances R_i in the series circuit.

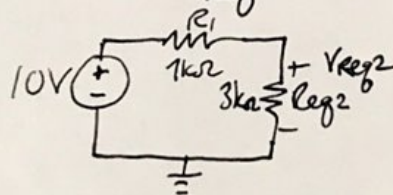
Step 3) Determine V_{Req2} via a voltage divider



$$\begin{aligned} V_{Req2} &= \frac{V_{in} R_{eq2}}{R_1 + R_{eq2}} \\ &= 10V \frac{3k\Omega}{1k\Omega + 3k\Omega} \\ &= 10V \times \frac{3}{4} = 7.5V \end{aligned}$$

Example: $V_{R2} = \frac{R_2}{R_1 + R_2}$ in the circuit above

Step 4) Determine $V_{R4} = V_{out}$

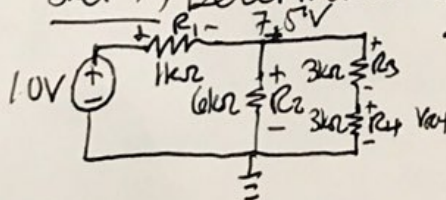


V_{R4} is given by the voltage divider:

$$\begin{aligned} V_{R4} &= 7.5V \frac{3k\Omega}{3k\Omega + 3k\Omega} \\ &= 7.5V \times \frac{1}{2} \\ &= \underline{3.75V} \end{aligned}$$

2) Voltage Divider Derivation

(5)

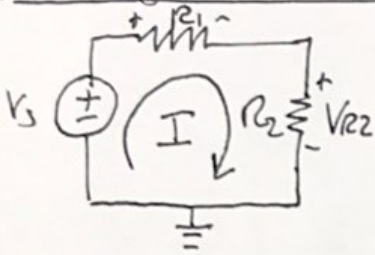

1) Find V_{R2} in terms of R_2 and I

$$\cdot V_{R2} = I R_2$$

2) Find I in terms of V_s , R_1 , and R_2


$$\cdot I = \frac{V_s}{R_1 + R_2}$$

3) Substitute the expression for I from (2) into the expression from (1) for V_{R2} :

$$V_{R2} = \left(\frac{V_s}{R_1 + R_2} \right) R_2 = V_s \underbrace{\frac{R_2}{R_1 + R_2}}_{\text{Voltage divider formula}}$$

Generalization:

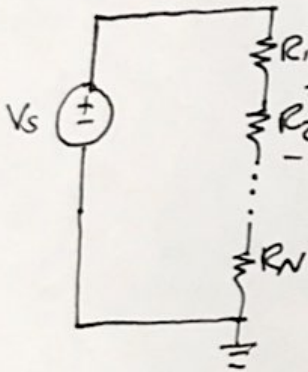• If we instead have N resistors in series in a circuit:



and we want to find the voltage drop across a particular resistor, say R_2 , we use the following formula:

$$V_{R2} = V_s \frac{R_2}{R_1 + R_2 + \dots + R_N} = V_s \frac{R_2}{\sum_{i=1}^N R_i}$$