

# ECSE 2010 Alpha Lab 01 Proof of Concepts Sec 2

TOTAL POINTS

**10 / 10**

QUESTION 1

1 I can use a bridge circuit to measure small variations of resistance 1 / 1

✓ - 0 pts Correct

- 1 pts One or more Screenshots missing
- 2 pts Several Screenshots missing
- 3 pts Missing

QUESTION 2

2 I can make a reference voltage with a comparator to help make decisions 1 / 1

✓ - 0 pts Correct

- 1 pts One wrong or incomplete answer
- 2 pts Two or more wrong or incomplete answers
- 2 pts Missing

QUESTION 3

3 I can multiply or divide a signal with a gain that I specify by changing component values in an op amp circuit. 1 / 1

✓ - 0 pts Correct

- 1 pts screenshot missing
- 2 pts 2 or more screenshots are not clear
- 2 pts Missing
- 1 pts Incorrect format of document
- 1 pts Nodes are not labelled or inconsistent with results
- 1 pts Screenshot missing captions or labels

QUESTION 4

4 I can integrate or differentiate a signal by changing component values and positions in an op amp circuits. 1 / 1

✓ - 0 pts Correct

- 1 pts Not Adequate Expanation for one or more comparisons

- 2 pts Missing several comparisons of analytical, simulation and experiment results

- 3 pts Missing

QUESTION 5

5 I can design a potential solution to a sensor problem by integrating two or circuits learned in this lab. 1 / 1

✓ - 0 pts Correct

- 0.5 pts build the circuit
- 0.5 pts simulation

QUESTION 6

6 I can identify non-idealities or unexpected results and attempt to explain why they may exist. 1 / 1

✓ - 0 pts Correct

QUESTION 7

7 I can answer for myself "Is this right?" by comparing mathematical calculations to simulation and experimental results. 1 / 1

✓ - 0 pts Correct

- 1 pts missing mathematical calculations

QUESTION 8

8 I can show plots and diagrams that are easy to read, scaled correctly and clearly labeled. 1 / 1

✓ - 0 pts Correct

- 1 pts several plots/diagrams not clear
- 1 pts missing simulation results/plots

QUESTION 9

9 I can use consistent variable labels and component values in mathematical calculation, simulation and experimental results for easy comparison. 1 / 1

✓ - 0 pts Correct

QUESTION 10


10 I can accurately answer conceptual questions found throughout the lab. 1 / 1

✓ - 0 pts Correct

# Proof of Concepts

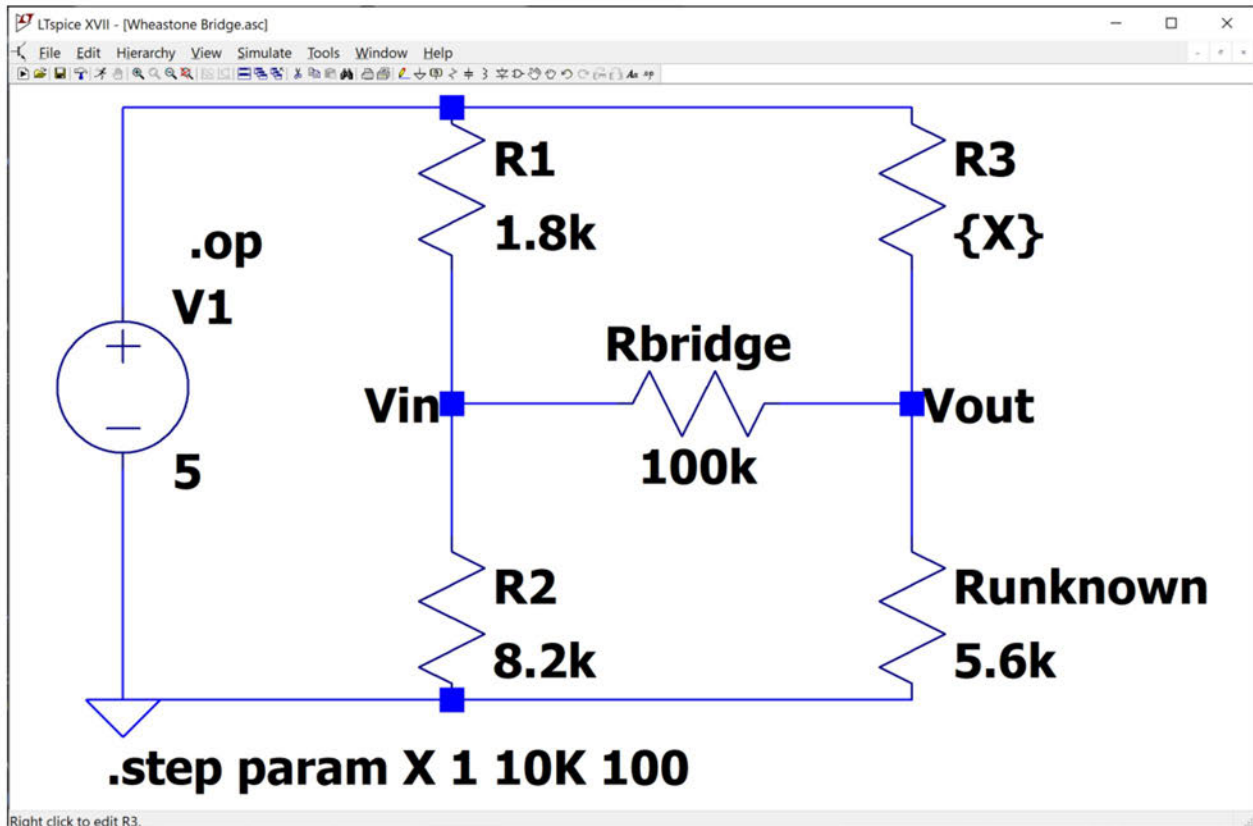1. **Proof of concept (A1):** Prove the concept of a balanced bridge
2. **Building Block:** Short description and schematic

Clearly label all nodes you will reference for example



The above schematics shows a typical representation of Wheatstone bridge. V1, R1, R2 and Rbridge has known value. Runknown has a value of 1k so that when parametric simulation is done on R3, the response of voltage across Rbridge can be observed.

### 3. Analysis:


Equation and short description.

In order for the bridge to be balanced, in another sense no current flowing through Rbridge, R1 and R2, and R3 and R4 are in parallel with each other, the voltage across each pair of the resistor is the same. To achieve a balanced bridge, the voltage across Vin and Vout as labeled on the schematic must be same. This derived the equation:

$$\frac{R2}{R1 + R2} = \frac{Ru}{Ru + R3}$$


### 4. Simulation:

Screenshot of simulation

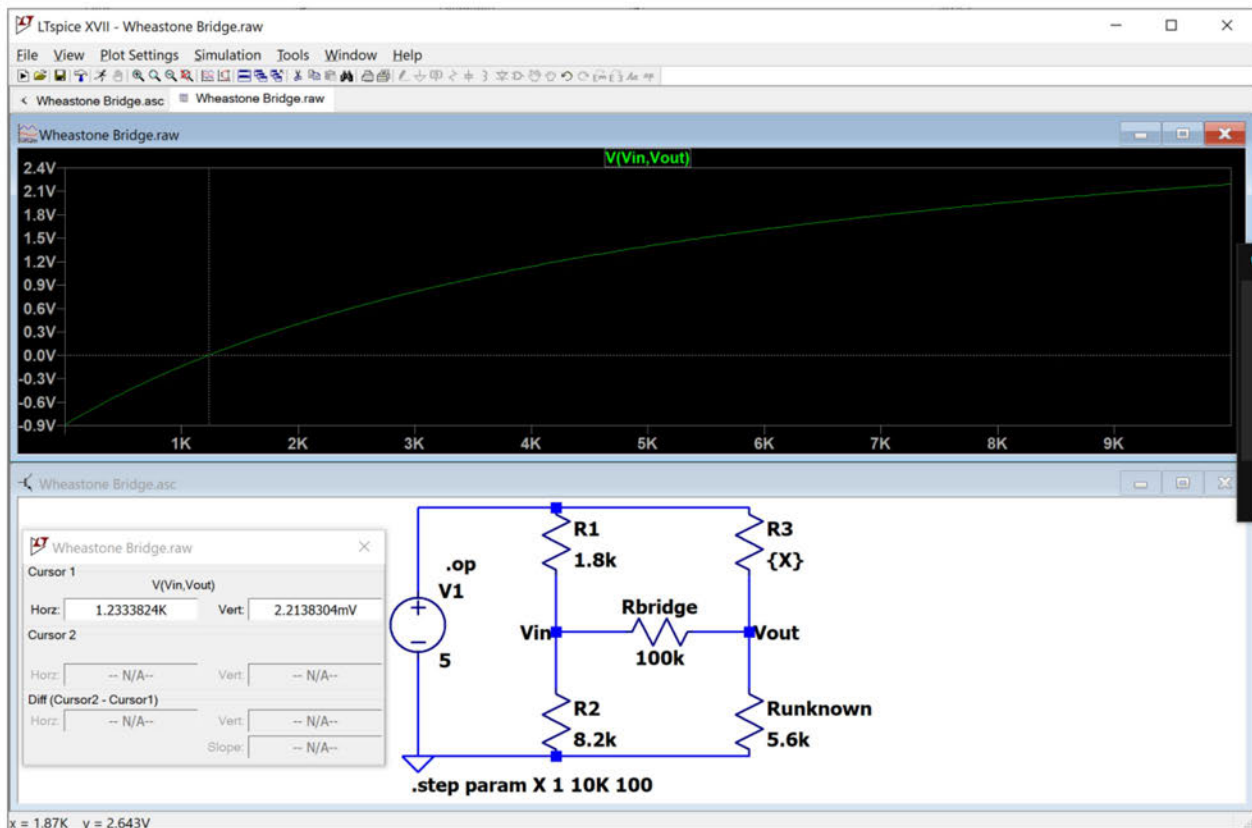


## 5. Measurement:

Balanced bridge

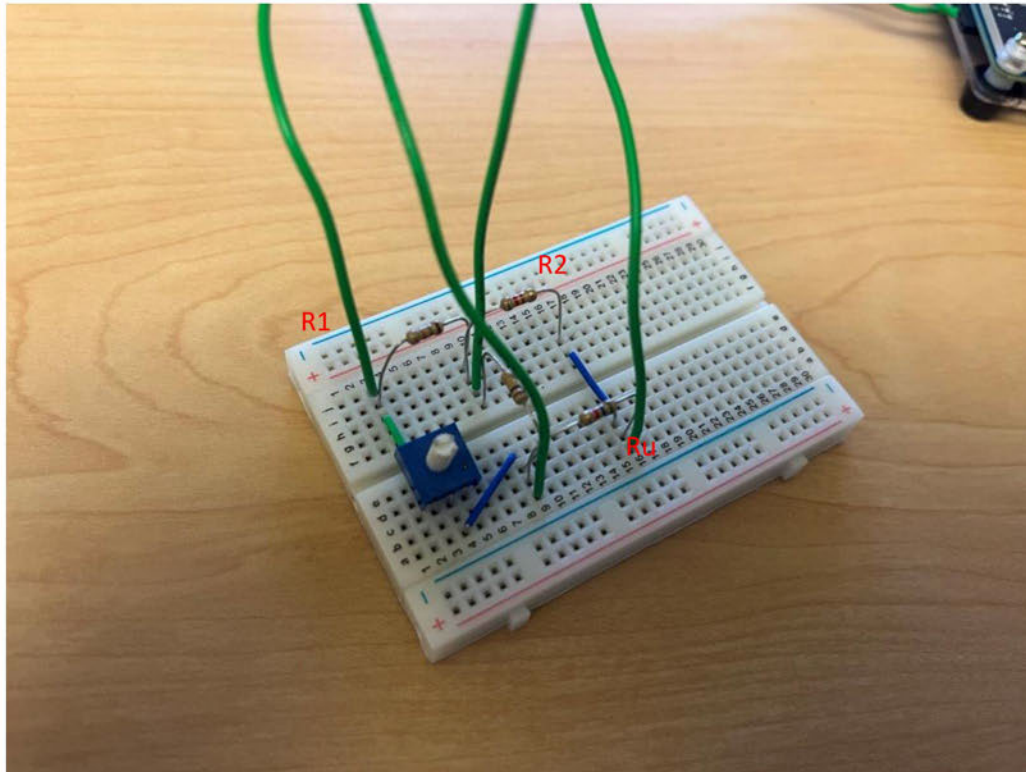

ALM...	
<b>CA Volts</b>	<b>4.0792</b>
CA Max Volts	4.0876
CA Min Volts	4.0745
<b>CB Volts</b>	<b>4.0725</b>
CB Max Volts	4.6343
CB Min Volts	3.7203
<b>CA-CB V</b>	<b>0.0067</b>
<input checked="" type="radio"/> Stop	<input checked="" type="radio"/> Run
Reset Min/Max	
<input checked="" type="checkbox"/> Enab	Analog Meter
Channel Gain / Offset Adjustment	
CA-V	1.0 0.0 Save
CB-V	1.0 0.0 Load

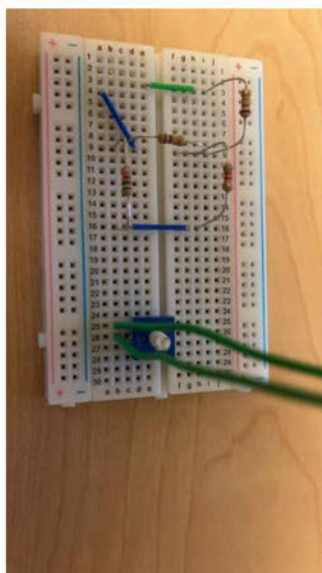Measuring the Resistance of the potentiometer



ALM1000 Meter-Source 1.3 8 March 2022)			
<input checked="" type="radio"/> Stop <input checked="" type="radio"/> Run Exit Save Config Load Config Digital Controls AD5626 Output			
<b>CA Meter</b>	<b>CB Meter</b>	<b>CA Source</b>	<b>CB Source</b>
CA V 4.9864	CB V 0.3454	CA mW 21.16	CB mW ----
A-B V 4.6410	B-A V -4.6410	<input type="radio"/> CHA off <input checked="" type="radio"/> CHA on	<input checked="" type="radio"/> CHB off <input type="radio"/> CHB on
CA mA 4.24	CB mA ----	<input checked="" type="radio"/> CHA V <input type="radio"/> CHA I	<input checked="" type="radio"/> CHB V <input type="radio"/> CHB I
CH A Gain/Offset calibration		<input type="checkbox"/> Split I/O	<input type="checkbox"/> Split I/O
VA 1.0 0.0	VB 1.0 0.0	CA-V 5.0 Volts	CB-V 0.0 Volts
IA 1.0 0.0	IB 1.0 0.0	CA-I 0.0 mAmps	CB-I 0.0 mAmps
Board # 0			

## 6. Discussion (and answer related questions in Alpha Lab):

The LT spice simulation shows that to achieve a balanced bridge, R3 must have a value around 1.23KΩ. Using an potentiometer, under the same circuit composition, the resistance of te potentiometer equals to  $\frac{4.9864V}{4.24mA} = 1.18k\Omega$ . Based on mathematical calculation, a balanced bridge need to satisfy relationship:

$$\frac{R2}{R1 + R2} = \frac{Ru}{Ru + R3}$$

Substituting the resistor value from the circuit schematics,  $\frac{8.2K}{1.8K+8.2K} = \frac{5.6K}{R3+5.6K} \rightarrow R3 = 1.23K$

Simulation result matches with the mathematical expression of an balanced circuit. The measurement result would be reflective of the simulation result because the resistor used in the experiment has a tolerance of 5%. The variation between resistances in the simulation and experiment is within such tolerance. The error can also be coming from potentiometer and LT spice readout. As shown in the above pictures, it is difficult to balance the bridge and achieve 0 voltage across difference. And the voltage across the bridge resistor can't be adjust to matched exactly due to the precision of potentiometer and LT spice cursor.