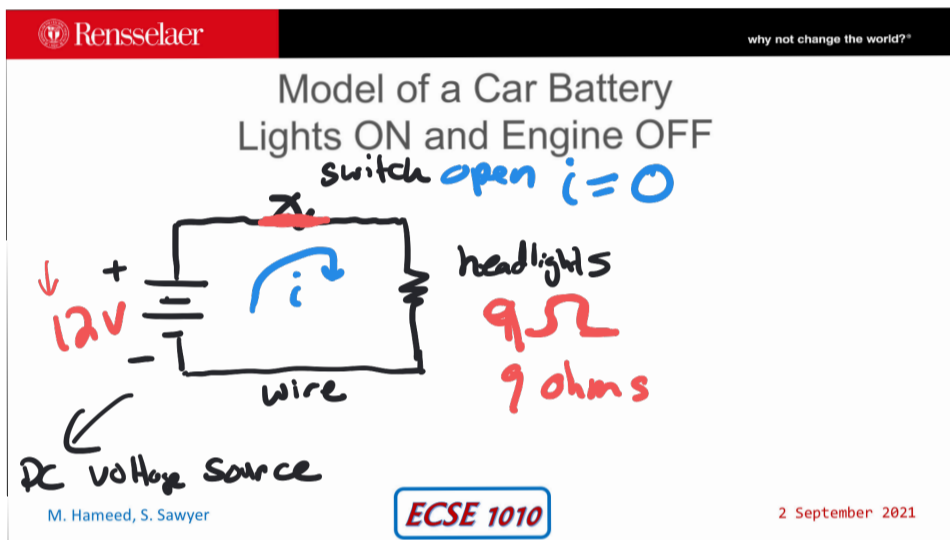



Intro to ECSE - CLASS 2

KCL, KVL, Series, Parallel \rightarrow

ECSE
+ \rightarrow -



DC voltage source

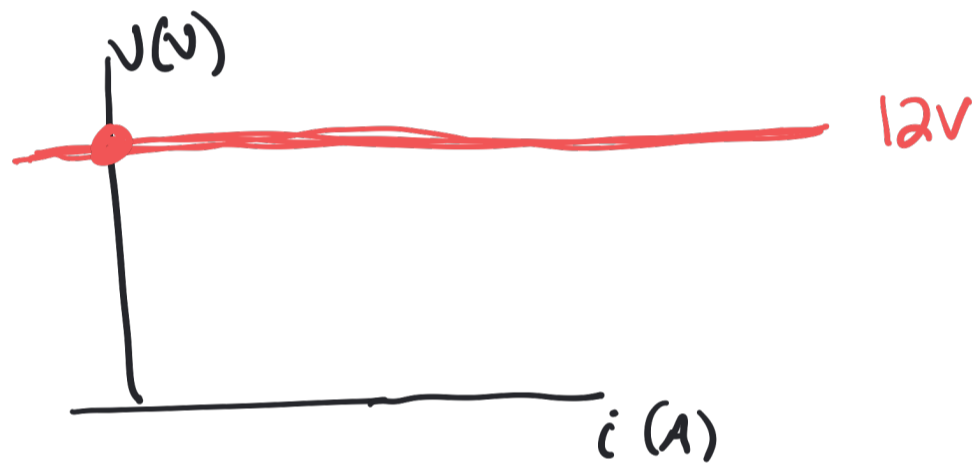

I-V characteristic
current \leftarrow voltage \downarrow

+
- =

(+
-)

$$i_{\text{headlights}} = \frac{V_{\text{headlights}}}{R_{\text{headlights}}}$$

$$i_{HL} = \frac{12V}{9\Omega}$$

ohm's law

$$V = IR$$

Ohm's Law $V = iR$



Voltage across on element is directly proportional to the current through it

$V \propto i$ proportionality constant is R

M. Hameed, S. Sawyer

ECSE 1010

2 September 2021

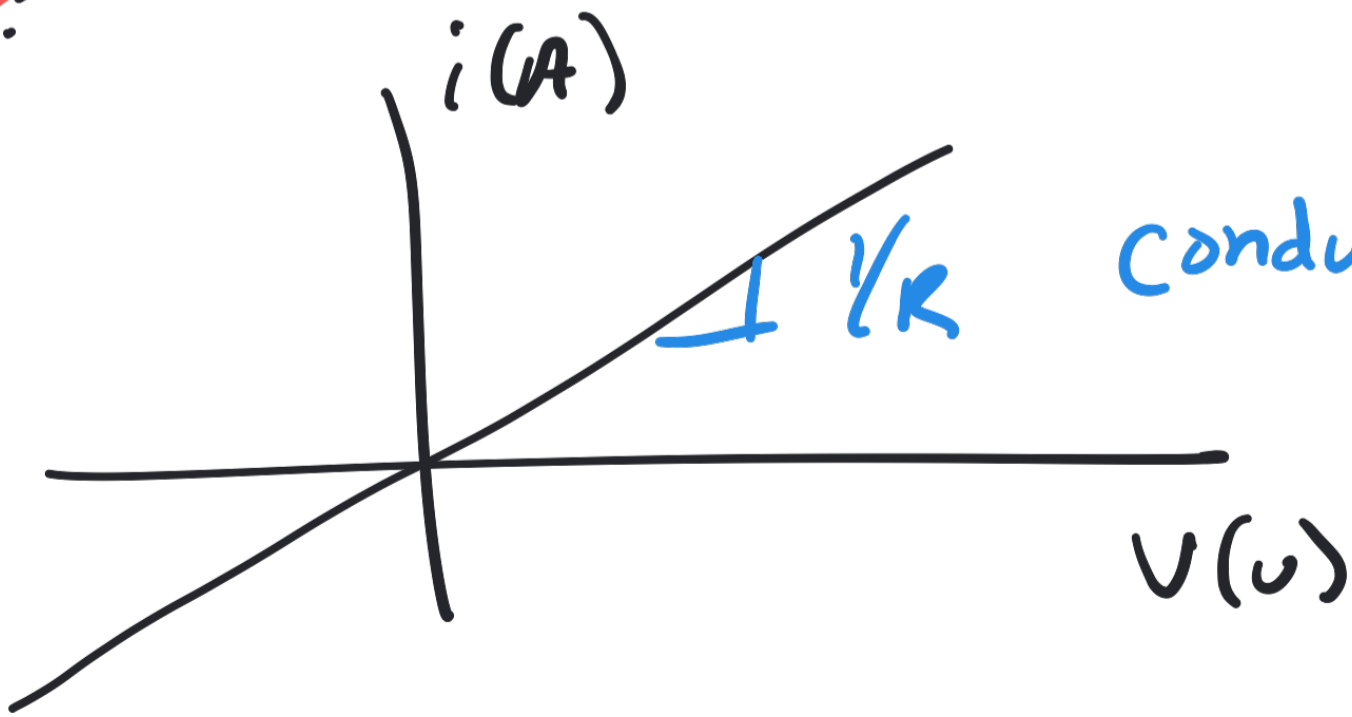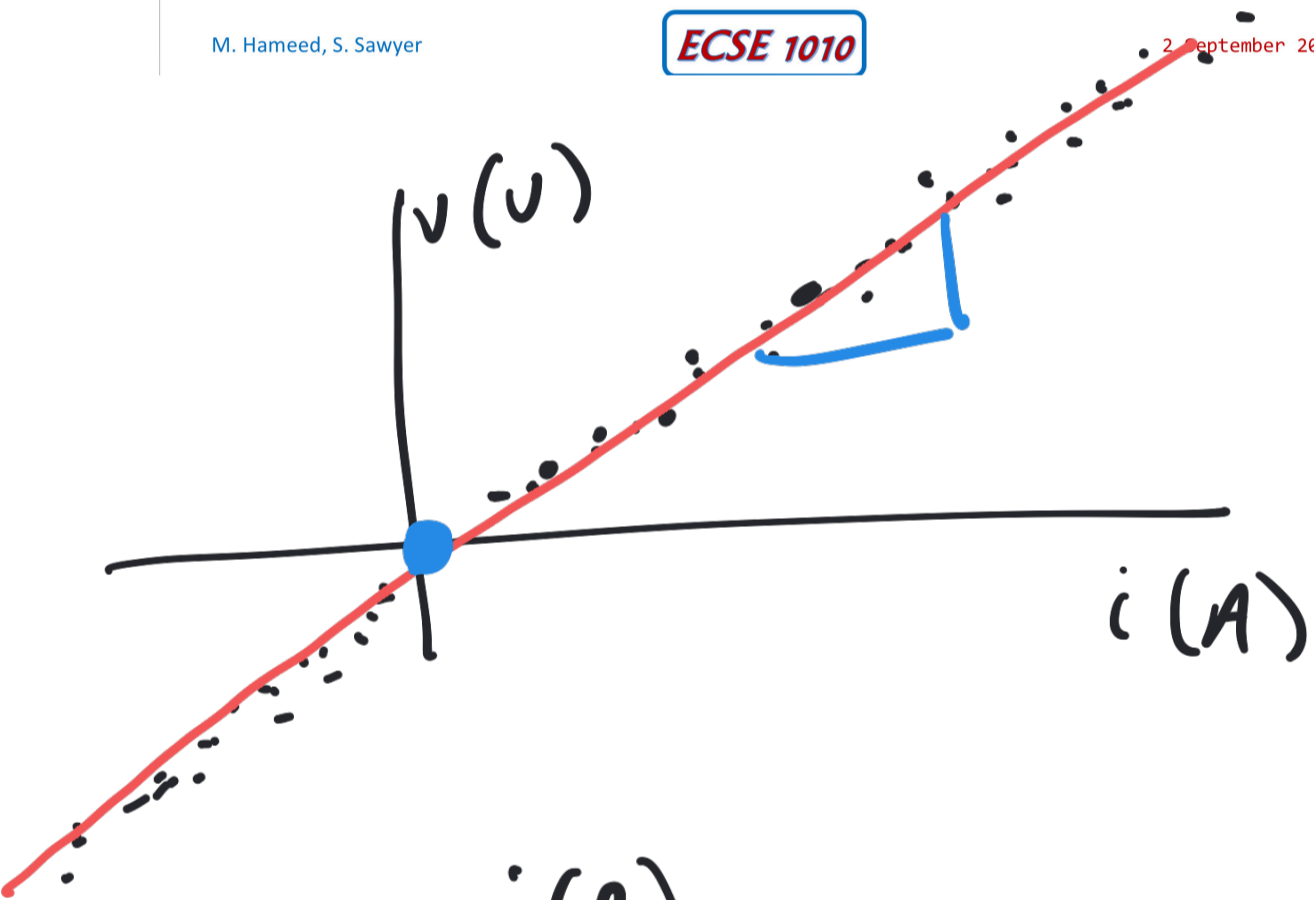

conductance

ohms


Ω

siemens

$$y = mx + c$$

$$V = mi + 0$$

$$m = R$$

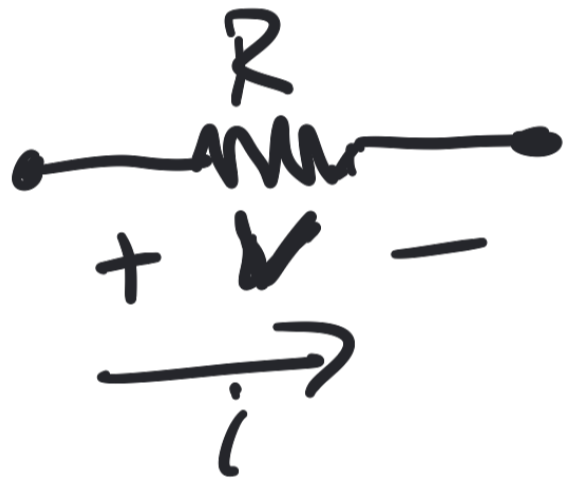

What is so cool about resistors?

Resistors are dope

Light Dependent Resistors (LDRs)

thermistor (temperature dependent resistors)

piezoelectric

strain gauge

What about power absorbed by resistors

- Resistors are passive linear elements
- They can only absorb power
- Power relationships:

Watts (w)

$$\begin{aligned}
 v &= iR \\
 i &= \frac{v}{R} \\
 P &= vi \\
 &= (iR) \left(\frac{v}{R} \right) \\
 P &= \frac{v^2}{R} \\
 P &= i^2 R
 \end{aligned}$$

Rensselaer why not change the world?

Kirchoff's Current Law (KCL)
Conservation of charge


Current coming into
a node (point in the circuit)
and out of
a node = 0

ECSE 1010 2 September 2021

M. Hameed, S. Sawyer

$$-i_1 - i_2 + i_3 - i_4 + i_5 = 0$$


$$i_1 + i_2 + i_4 = i_3 + i_5$$

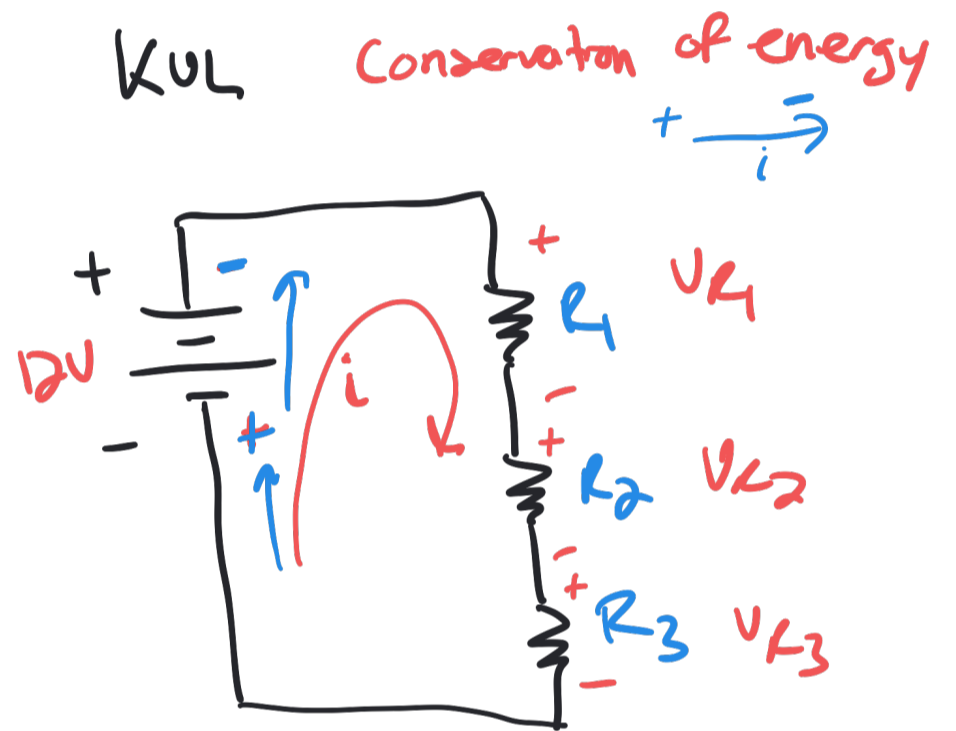

$$-12 + V_{R1} + V_{R2} + V_{R3} = 0$$

$$V_{R1} + V_{R2} + V_{R3} = 12$$


Resistors in Series

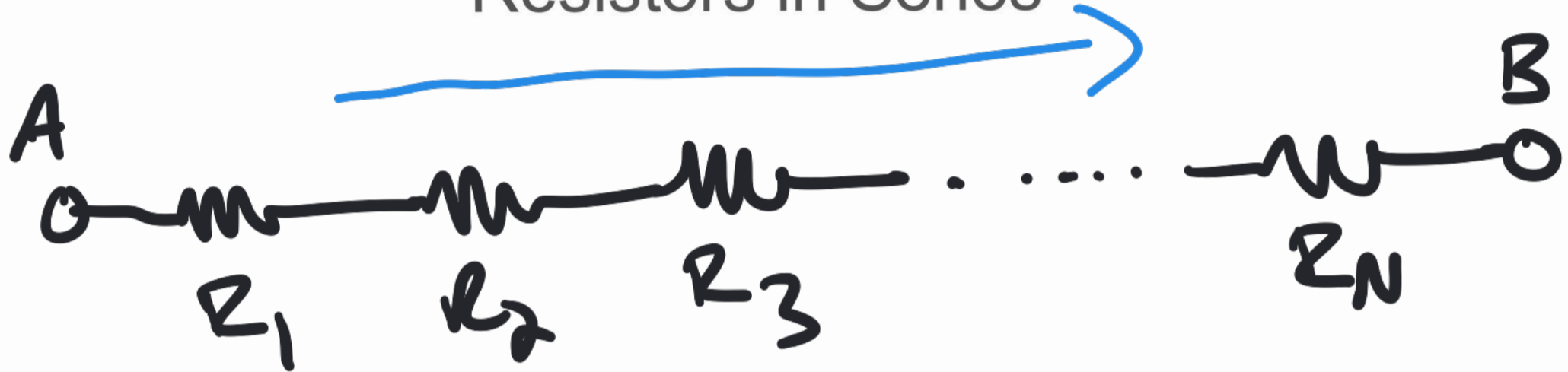

Resistor in series have the same current

$$R_{AB} = R_1 + R_2 + R_3 + \dots + R_N$$
$$= \sum_{i=1}^N R_i$$

Resistors in Parallel

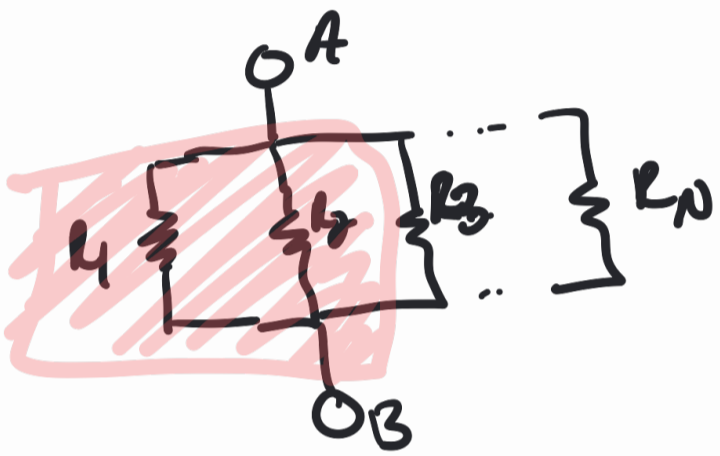

$$R_{AB} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_N} \right)^{-1}$$

more than 2 resistors

$$R_{12} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$





$$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3}$$

$$R_{SAM} =$$

R 357621

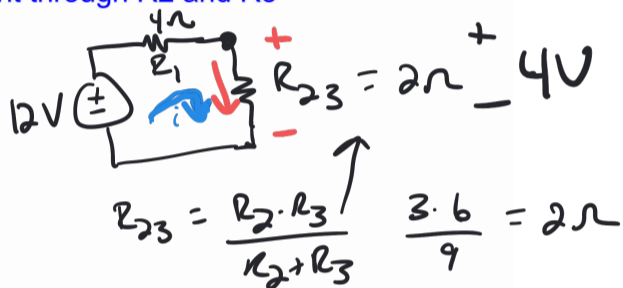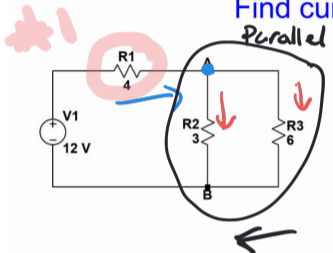Example 1: Circuit Analysis
Find current through R2 and R3



M. Hameed, S. Sawyer

ECSE 1010

2 September 2021

Way #2

#1 $i_{R_{23}} = V_{R_{23}} = 2A(2\Omega) = 4V$


#2 recognize || resistors have same voltage

$V_{R_2} = V_{R_3} = 4V$

$i = \frac{12}{4 + R_{23}} = \frac{12}{4 + 2} = 2A$

Way 1



$V_{R_1} = i R_1 = 4A(2\Omega) = 8V$

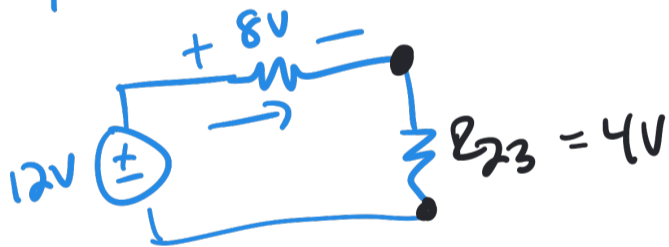

Things in parallel have same voltage
 $V_{R_2} = 4V$ $V_{R_3} = 4V$

Example 2: Circuit Analysis

Find current through R1

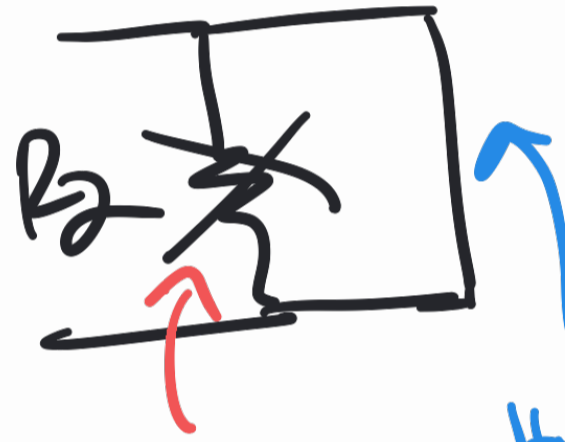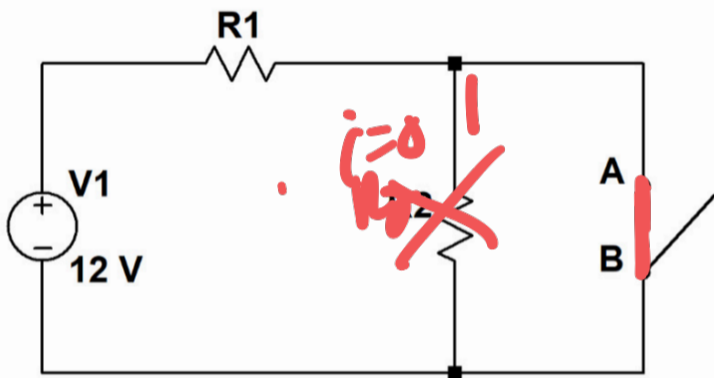

Shunting a resistor

HOOSICK ON FRIDAY

Hyperloop with no traffic

M. Hameed, S. Sawyer

ECSE 1010

2 September 2021



Activity 2: KCL, KVL, Series and Parallel Resistors

- Go to the class website
- Look under class 2
- Find activity 2
- Do the activity
 - One submission per group
 - Encouraged to discuss with others in the class
- Answer the activity using template (attached class 2)
- When complete – upload to Gradescope
 - Due Thursday, September 9th at 11:59 pm
 - Use guides to learn how to upload documents
 - Add your partner to submission after upload is complete.