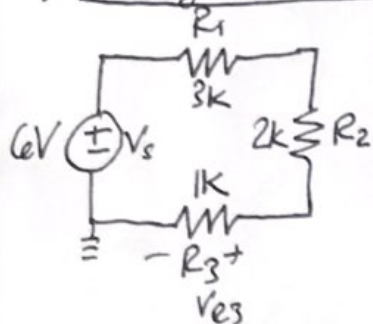



1) Voltage divider



• What is the voltage across R_3 (i.e. V_{R3})?
Use a voltage divider

$$\begin{aligned} \rightarrow V_{R3} &= V_s \frac{R_3}{R_1 + R_2 + R_3} \\ &= 6V \frac{1k}{3k + 2k + 1k} = \frac{6V}{6} \frac{1k}{1k} = \boxed{1V} \end{aligned}$$


2) Circuit Reduction

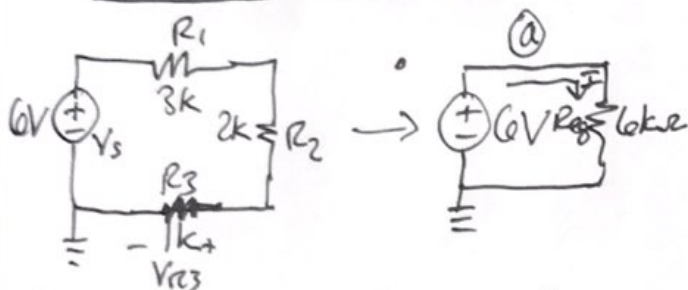

• What is I ? $I = \frac{6V}{6k} = 1mA$

• What is V_{R3} ? $V_{R3} = I R_3 = 1mA \cdot 1k = \boxed{1V}$

3) KCL, KVL, and Ohm's Law

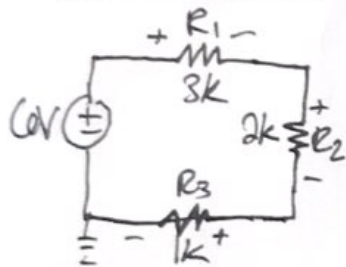


• Solving for voltage across each resistor or current through each resistor.

Step 1) Label components with reference marks "+" and "-" \rightarrow determines direction of current flow through components

Step 2) Count # of unknowns = # of resistors = # linearly independent eqn's needed to solve the circuit

Step 3) Find nodes and loops

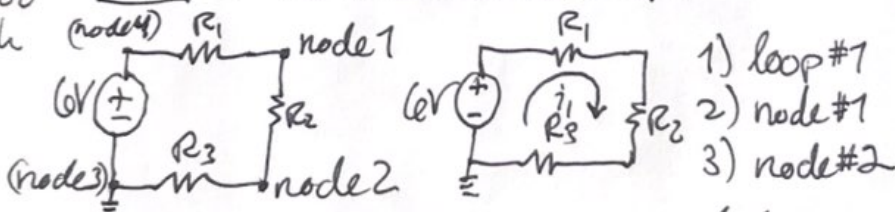


Step 4) Pick the "best" nodes and loops \rightarrow knowing which to pick will come with practice

Step 5) Use KVL and KCL (Ohm's Law) to write equations in terms of $V_{resistor}$ or $I_{resistor}$ variables.

(Doesn't matter which you choose - just be consistent!)
 d) My conventions: KCL convention


②

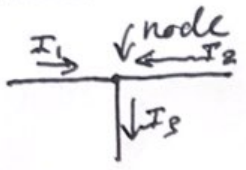

$$0 = I_1 + I_2 - I_3$$

- Current flowing INTO a node (I_1, I_2) is positive ("+")
- Current flowing OUT of a node (I_3) is negative ("-")


KVL convention

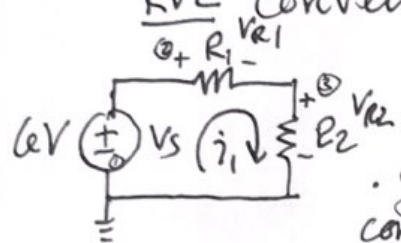

$$0 = -V_s + V_{R1} + V_{R2}$$

• going in the direction of the loop, each component's voltage is assigned the sign (from reference marks) that is encountered first. (i.e. we encounter the "-" on V_s first, so it gets "-")

d) back to the problem

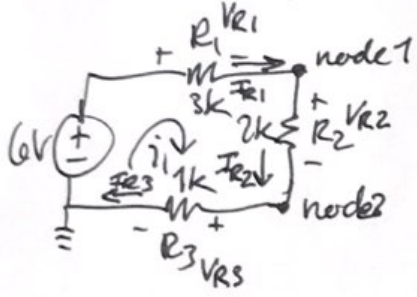

• loop #1 (KVL): $0 = V_{R1} + V_{R2} + V_{R3} - 6$ (1)

"Standard constant form" → constants on one side of "=", variables on the other

• node #1 (KCL): $0 = I_{R1} - I_{R2}$
 • node #2 (KCL): $0 = I_{R2} - I_{R3}$


* Want to solve for voltages, so must convert I to V/R via Ohm's Law

• node #1 (KCL) in voltages: $0 = \frac{V_{R1}}{R_1} - \frac{V_{R2}}{R_2}$
 • node #2 (KCL) in voltages: $0 = \frac{V_{R2}}{R_2} - \frac{V_{R3}}{R_3}$

Put into matrix form: $b = Ax \rightarrow$

Matrix multiplication: row 1 x col 1
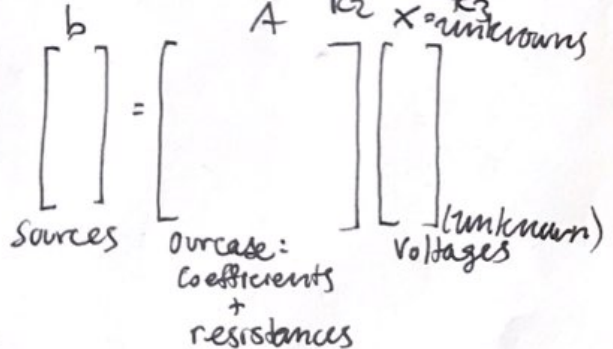
$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix} \begin{bmatrix} x \\ y \\ z \end{bmatrix} = \begin{bmatrix} ax+by+cz \\ dx+ey+fz \\ gx+hy+iz \end{bmatrix}$$



$$(1) \begin{bmatrix} 1 & 1 & 1 \\ \frac{1}{R_1} & -\frac{1}{R_2} & 0 \\ 0 & \frac{1}{R_2} & -\frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix}$$

matrix multiplication reproduces KCL & KVL equations

Plugging in numerical values:

(3)

$$\begin{matrix} & A & & x & & b \\ \begin{bmatrix} 1 & 1 & 1 \\ \frac{1}{3000} & -\frac{1}{2000} & 0 \\ 0 & \frac{1}{2000} & -\frac{1}{1000} \end{bmatrix} & \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} & = & \begin{bmatrix} 6 \\ 0 \\ 0 \end{bmatrix} \end{matrix}$$

Solve with MATLAB or
Calculator: $x = A^{-1}b$

$$X = \begin{bmatrix} V_{R1} \\ V_{R2} \\ V_{R3} \end{bmatrix} = \begin{bmatrix} 3 \\ 2 \\ 1 \end{bmatrix} V$$