


Cascading Op-Amps

$$V_{\text{supply}+} = +9V$$

$$V_{\text{supply}-} = -9V$$

What is V_{out} in terms of V_{in} ?


Inverting Amplifier

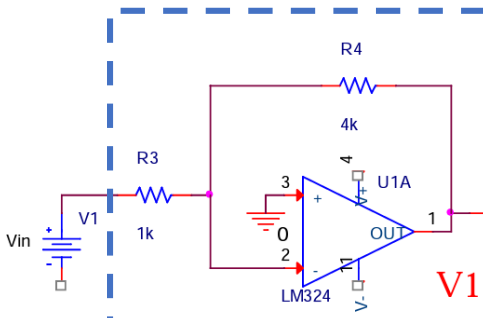

H_1

$$H_1 = -\frac{R_4}{R_3} = -\frac{4k}{1k} = -4$$


Voltage Divider

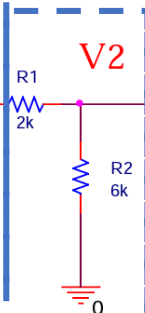

H_2

$$H_2 = \frac{R_2}{R_1 + R_2} = \frac{6k}{8k} = \frac{3}{4}$$


Voltage Follower

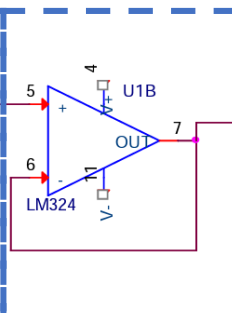

H_3

$$H_3 = 1$$

Non-Inverting Amplifier

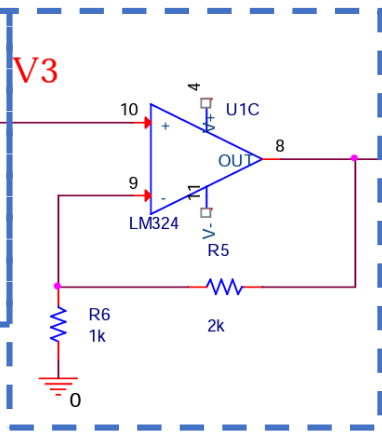

H_4

$$H_4 = 1 + \frac{R_5}{R_6} = 1 + \frac{2k}{1k} = 3$$


$$H_{\text{total}} = H_1 H_2 H_3 H_4 = (-4) \left(\frac{3}{4}\right) (1)(3) = -9 \longrightarrow V_{\text{out}} = -9V_{\text{in}}$$

Example: If $V_{\text{in}} = 3V$, what is V_1 ?


- Mathematically, $V_1 = (3V)(-4) = -12$, however the supply voltages are $\pm 9V$, meaning that the signal will saturate at either $+9V$ or $-9V$, so $V_1 = -9V$

Why use a voltage follower?

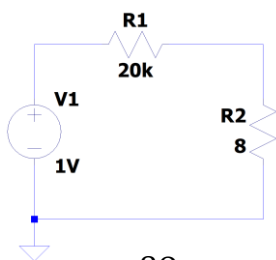- It stops any current from flowing from the right side of the voltage follower to the left side of the voltage follower (no current enters the terminals of ideal op-amps); it isolates one circuit from another
- It can transform impedance, enabling more efficient voltage transfer


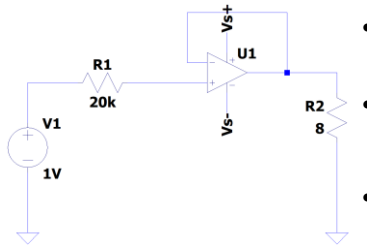
$$V_{R2} = 1V \frac{8\Omega}{20k\Omega + 8\Omega} = 0.4mV$$



$$V_+ = 1V \frac{2M\Omega}{2M\Omega + 20k\Omega} = 990mV$$

- Op-amp has input impedance of about $2M\Omega$ (in series with R_1)
- Op-amp has output impedance of about 5Ω (in series with R_2)
- Voltage follower greatly improves voltage transfer from V_1 to V_{R2}

$$V_{R2} = 990mV \frac{8\Omega}{5\Omega + 8\Omega} = 609mV$$