

Finding the Magnitude of a Transfer Function

- If we want to use the transfer function to calculate the output voltage of a system given an input voltage and H contains complex numbers, we need to find the magnitude of H: $|H(j\omega)|$

$$V_{out} = |H(j\omega)| V_{in}$$

- How do we find $|H(j\omega)|$?

$$|H(j\omega)| = \sqrt{H(-j\omega)H(j\omega)}$$

$|H(j\omega)|$ will always be real: it should never contain "j" and always be ≥ 0

- Example: Transfer function for an RC low-pass filter: $H(j\omega) = \frac{1/j\omega C}{R + 1/j\omega C}$

What is $|H(j\omega)|$?

$$1) |H(j\omega)| = \sqrt{H(-j\omega)H(j\omega)}$$

properties of "j"

$$\cdot j \cdot j = -1$$

$$\cdot -j \cdot j = 1$$

$$\cdot (-j) \cdot (-j) = -1$$

$$= \sqrt{\frac{-1/j\omega C}{R - 1/j\omega C} \times \frac{1/j\omega C}{R + 1/j\omega C}}$$

$$= \sqrt{\frac{-\frac{1}{j^2} \frac{1}{\omega^2 C^2}}{(R - 1/j\omega C)(R + 1/j\omega C)}} = \sqrt{\frac{1/\omega^2 C^2}{R^2 - \cancel{R/j\omega C} + \cancel{R/j\omega C} - \frac{1}{j^2} \frac{1}{\omega^2 C^2}}}$$

$$= \sqrt{\frac{1/\omega^2 C^2}{R^2 + 1/\omega^2 C^2}} = \boxed{\frac{1}{\sqrt{\omega^2 C^2 R^2 + 1}}} = |H(j\omega)|$$

In terms of V_{in} and $|H|$:

$$\boxed{V_{out} = \frac{V_{in}}{\sqrt{(\omega RC)^2 + 1}}}$$