

# Transmission Lines

## Steady State (Continuous Wave)

### Phasor Notation

$$v(z,t) = \Re\{\tilde{V}(z)e^{j\omega t}\}$$

$$i(z,t) = \Re\{\tilde{I}(z)e^{j\omega t}\}$$

### Voltage Wave

$$\tilde{V}(z) = V_o^+ e^{-\gamma z} + V_o^- e^{\gamma z} = V_o^+ (e^{-\gamma z} + \Gamma e^{\gamma z}) = V_o^+ e^{-\gamma z} (1 + \Gamma(z)) \quad (\text{general form})$$

$$\tilde{V}(z) = V_o^+ e^{-j\beta z} + V_o^- e^{j\beta z} = V_o^+ (e^{-j\beta z} + \Gamma e^{j\beta z}) = V_o^+ e^{-j\beta z} (1 + \Gamma(z)) \quad (\text{for lossless lines})$$

### Current Wave

$$\tilde{I}(z) = I_o^+ e^{-\gamma z} + I_o^- e^{\gamma z} = \frac{V_o^+}{Z_o} (e^{-\gamma z} - \Gamma e^{\gamma z}) = \frac{V_o^+}{Z_o} e^{-\gamma z} (1 - \Gamma(z)) \quad (\text{general form})$$

$$\tilde{I}(z) = I_o^+ e^{-j\beta z} + I_o^- e^{j\beta z} = \frac{V_o^+}{Z_o} (e^{-j\beta z} - \Gamma e^{j\beta z}) = \frac{V_o^+}{Z_o} e^{-j\beta z} (1 - \Gamma(z)) \quad (\text{for lossless line})$$

### Wavelength

$$\lambda = \frac{u_p}{f}, \text{ where } u_p \text{ is the propagation velocity; } \beta = \frac{2\pi}{\lambda} \text{ and } u_p = \frac{\omega}{\beta}$$

### Propagation Constant

$$\gamma = \alpha + j\beta = \sqrt{(R' + j\omega L')(G' + j\omega C')} \quad (\text{general form})$$

$$\gamma = j\beta = j\omega\sqrt{L'C'}, \quad \alpha = 0 \quad (\text{for lossless lines})$$

### Characteristic Impedance

$$Z_o = \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad Z_o = \sqrt{\frac{L'}{C'}} = Z_o^o \quad (\text{for lossless line})$$

### Phase Velocity

$$u_p = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\mu\epsilon}} \quad (\text{For lossless or low-loss lines})$$

**Total Wave Impedance at location  $z$ :** 
$$\tilde{Z}(z) = \frac{\tilde{V}(z)}{\tilde{I}(z)} = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

### Reflection Coefficient

$$\Gamma(z) = \frac{V_o^-}{V_o^+} e^{2\gamma z} = \Gamma e^{2\gamma z} \quad (\text{General form})$$

$$\Gamma(z) = \Gamma e^{j2\beta z} \quad (\text{For lossless lines})$$

Normalized impedance

**Reflection from load:** 
$$\Gamma = \Gamma_L = \frac{V_o^-}{V_o^+} = -\frac{I_o^-}{I_o^+} = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{z_L - 1}{z_L + 1} = |\Gamma| e^{j\theta_\Gamma}$$
 
$$\left( z_L = \frac{Z_L}{Z_o} \right)$$


**Reflection from generator:** 
$$\Gamma_g = \frac{Z_g - Z_o}{Z_g + Z_o}$$

**Input Impedance ( $z = -l$ )** 
$$Z_{in} = Z_o \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}}, \quad \Gamma_{in} = \Gamma e^{-2\gamma l} = |\Gamma| e^{j\theta_\Gamma - 2\gamma l}$$

For lossless lines: 
$$\Gamma_{in} = \Gamma e^{-j2\beta l} = |\Gamma| e^{-j(2\beta l - \theta_\Gamma)}$$

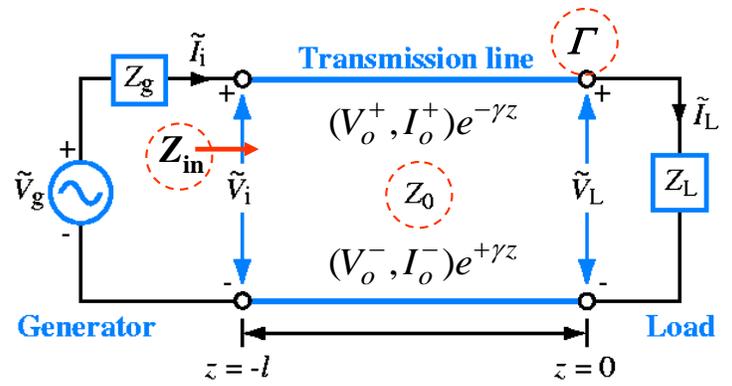**Input impedance of a lossless transmission line of length  $d$  with load  $Z_L$ ,**

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan \beta d}{Z_o + jZ_L \tan \beta d} = Z_o \frac{z_L + j \tan \beta d}{1 + jz_L \tan \beta d}$$



**Forward wave amplitude:**

$$V_0^+ = \tilde{V}_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{1}{e^{\gamma l} + \Gamma e^{-\gamma l}} = \tilde{V}_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{e^{-\gamma l}}{1 + \Gamma_l} \quad (\text{General form})$$

$$V_0^+ = \tilde{V}_g \frac{Z_{in}}{Z_g + Z_{in}} \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \quad (\text{For lossless lines})$$


**Magnitude of voltage:**  $|\tilde{V}(d)| = |V_0^+| [1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_\gamma)]^{1/2}$   
 (Lossless T-line)

**Standing Wave Ratio:**

$$S = SWR = \frac{|V|_{\max}}{|V|_{\min}} = \frac{|I|_{\max}}{|I|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \geq 1$$

$$|V|_{\max} = |V_0^+| (1 + |\Gamma|)$$

$$|V|_{\min} = |V_0^+| (1 - |\Gamma|)$$

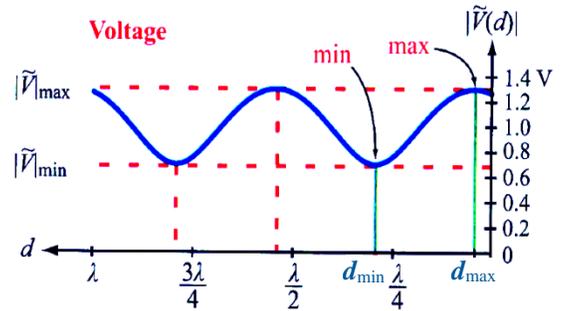

**Average Power:**

$$P_{av}(z) = \frac{1}{2} \Re \{ \tilde{V}(z) \tilde{I}^*(z) \} = \frac{|\tilde{V}(z)|^2}{2} \Re \left\{ \frac{1}{Z^*(z)} \right\};$$

**For lossless line:**  $P_{av} = \frac{|V_0^+|^2}{2Z_0} (1 - |\Gamma|^2)$

**Low-Loss lines** ( $G' \approx 0$  and  $R' \ll \omega L'$ ):

$$Z_o \approx \sqrt{\frac{L'}{C'}} \left( 1 - j \frac{R'}{2\omega L'} \right) = Z_o^o \left( 1 - j \frac{R'}{2\omega L'} \right); \quad Z_o^o = \sqrt{\frac{L'}{C'}}$$


$$\gamma = \alpha + j\beta \quad \alpha \approx \frac{R'}{2Z_o^o} \quad \text{and} \quad \beta \approx \omega \sqrt{L'C'}$$

**For distortionless line:**  $G'/C' = R'/L'$

$$Z_o = \sqrt{\frac{L'}{C'}} = Z_o^o$$

$$\gamma = \alpha + j\beta \quad \alpha = \frac{R'}{Z_o^o} \quad \text{and} \quad \beta = \omega \sqrt{L'C'}$$

**Transient Response:**

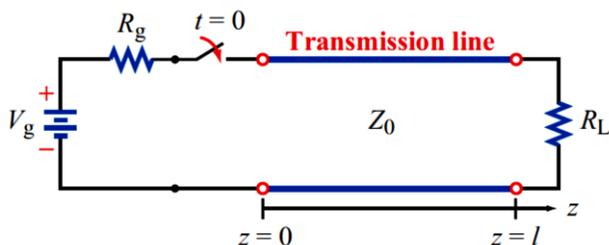

$$T = \frac{l}{u_p}$$

$$V_1^+ = \frac{V_g Z_o}{Z_g + Z_o}$$

**Impedance Matching** (Smith Chart):

$$z_l = \frac{1 + \Gamma_l}{1 - \Gamma_l} \quad y_l = \frac{1}{z_l} = \frac{1 - \Gamma_l}{1 + \Gamma_l} \quad \Gamma_l = \Gamma e^{-2\beta l}$$

**Goal:**  $\Gamma_{in} = 0, z_{in} = 1$  ( $y_{in} = 1$ )

Short-circuited:  $Z_{in} = jZ_o \tan \beta l$ , or  $z_{in} = j \tan \beta l$

Open-circuited:  $Z_{in} = -jZ_o \cot \beta l$ , or  $z_{in} = -j \cot \beta l$

