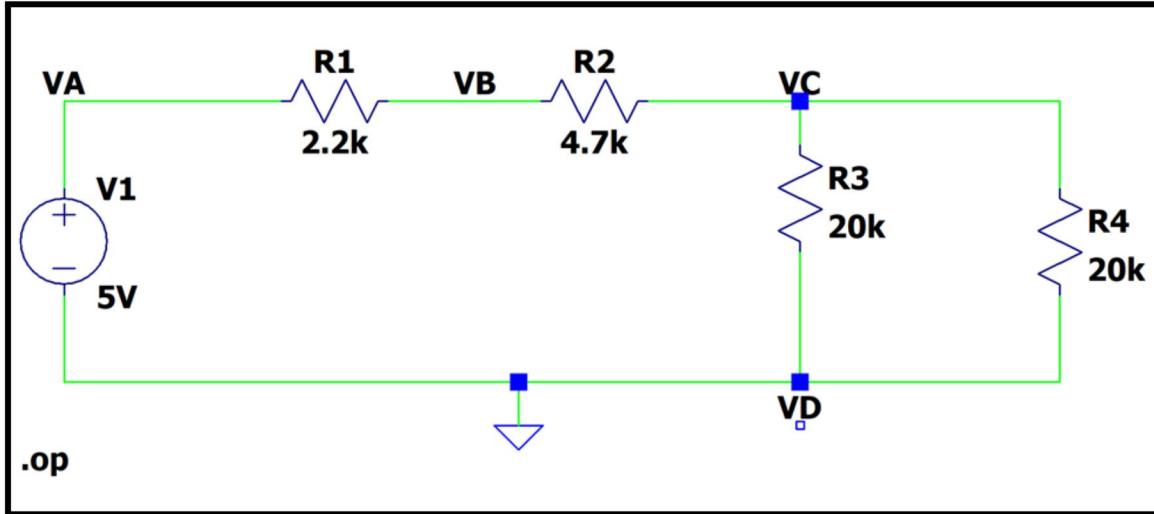


# Building Block



Here we have a simple circuit with resistors **R1** (2.2 kΩ) and **R2** (4.7 kΩ) in series with a loop containing resistors **R3** and **R4** (20 kΩ each) in parallel. The circuit is powered by a 5 V DC voltage source **V1**, and nodes **VA–VD** are labeled to show where our voltage readings are taken.

## Analysis:

Combining Kirchhoff's Voltage Law ( $\sum V = 0$  in a loop) and Ohm's Law ( $V = IR$ ) produced all the unknown node voltages and currents through each component.

KVL + Ohm's Law, in  $k\Omega$  & mA:

$$5 + 2.2I + 4.7I + I/(1/20 + 1/20) = 0$$
$$5 + 16.9I = 0$$
$$I = -5/16.9$$

Through  $V_1$ ,  $R_1$ , and  $R_2$ ,

$$I = -.295858 \text{ mA}$$

$V_B = V_A + V_{R_1}$

$V_B = 5 + V_{R_1} = 5 + IR_1$

$V_B = 5 + 2.2(-0.295858)$

$(V_B = 4.34911 \text{ V})$

$V_C = V_B + V_{R_2} = 4.34911 + IR_2$

$V_C = 4.34911 + 4.7(-0.295858)$

$(V_C = 2.95858 \text{ V})$


$V_C = I_{R_3} R_3 = I_{R_4} R_4$

$2.95858 = 20I_{R_3} = 20I_{R_4}$

$I_{R_3} = I_{R_4} = 2.95858/20$

$(I_{R_3} = I_{R_4} = .147929 \text{ mA})$



# Simulation:

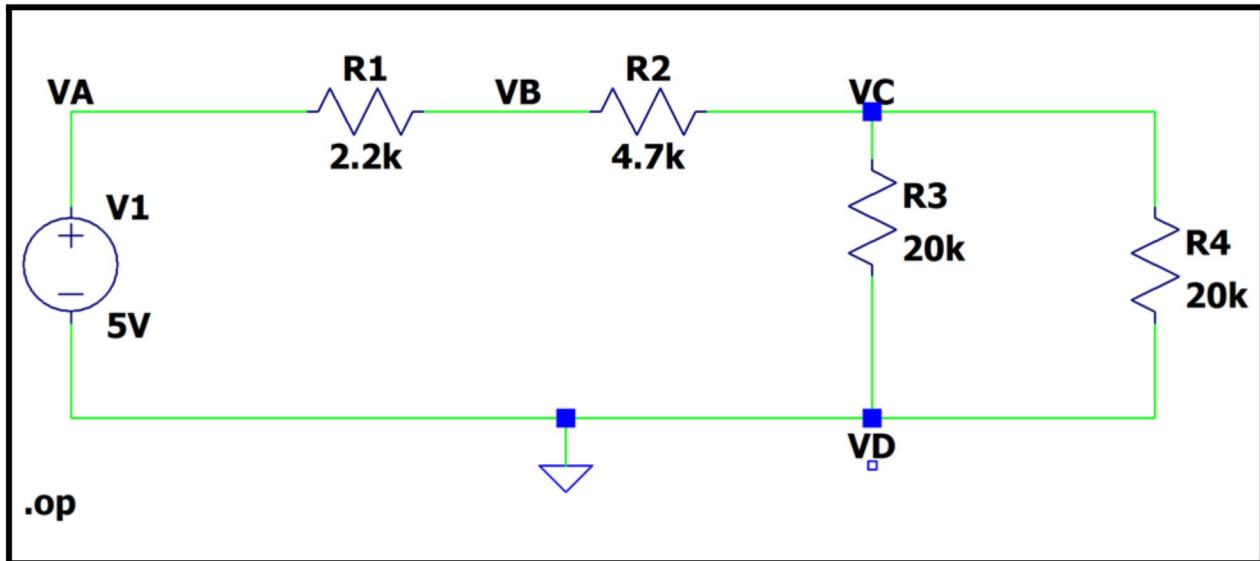



```
--- Operating Point ---
V(va) :      5          voltage
V(vb) :  4.34911      voltage
V(vc) :  2.95858      voltage
I(R4) : 0.000147929 device_current
I(R3) : 0.000147929 device_current
I(R2) : -0.000295858 device_current
I(R1) : -0.000295858 device_current
I(V1) : -0.000295858 device_current
```

# Measurement:



## Node A:

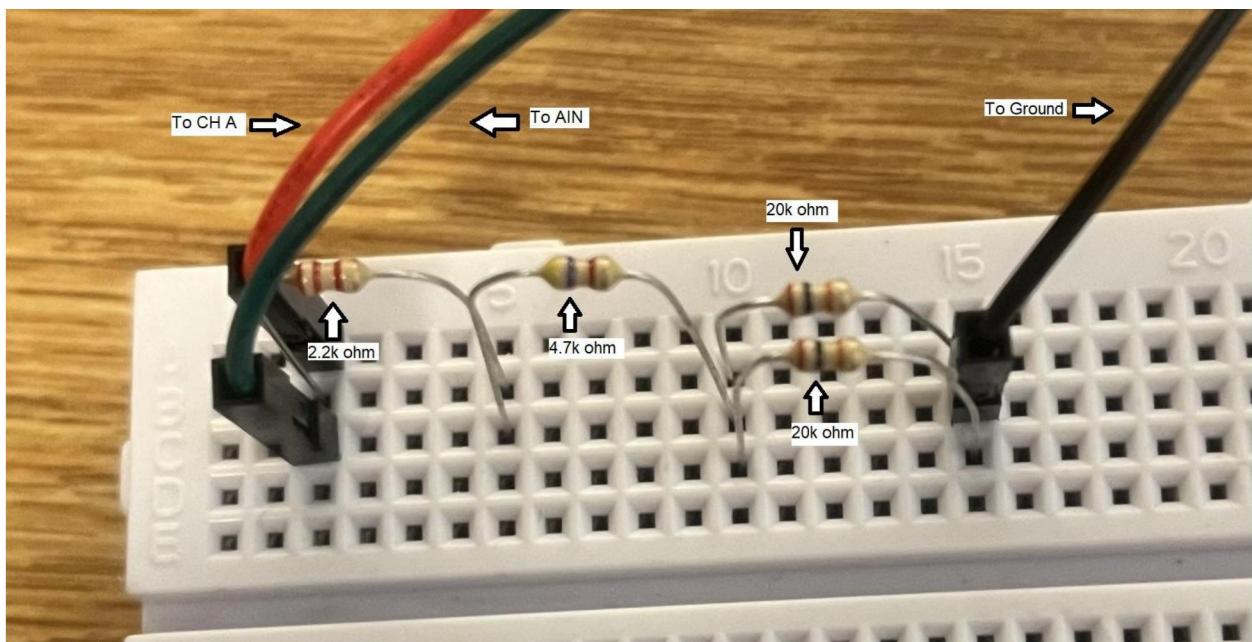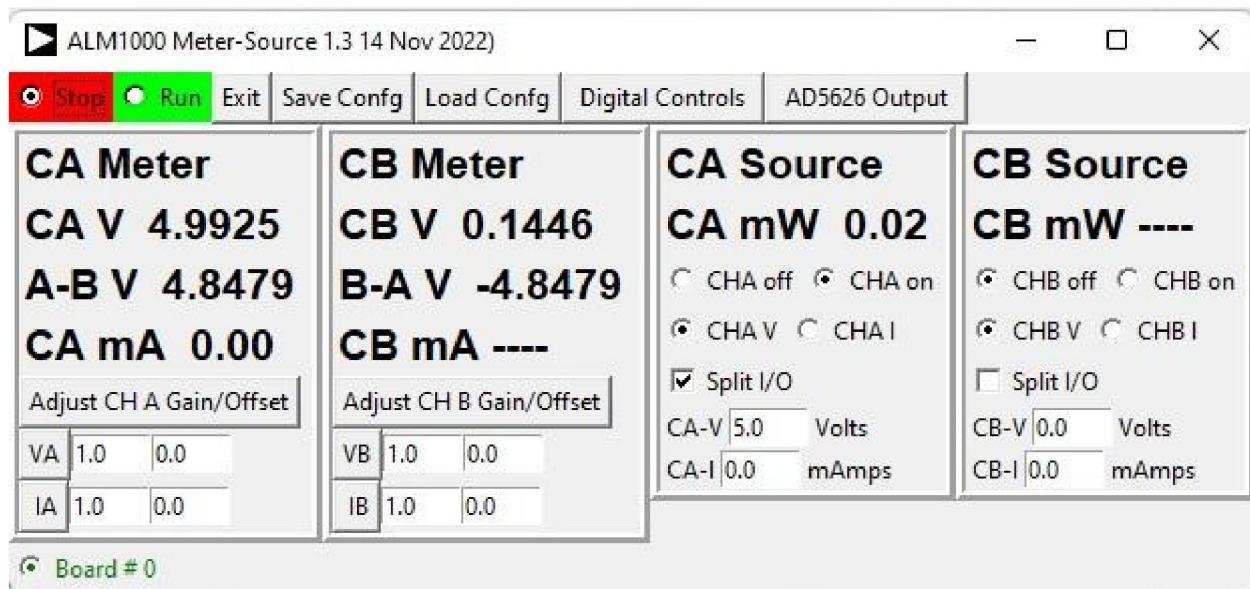



## Node B:

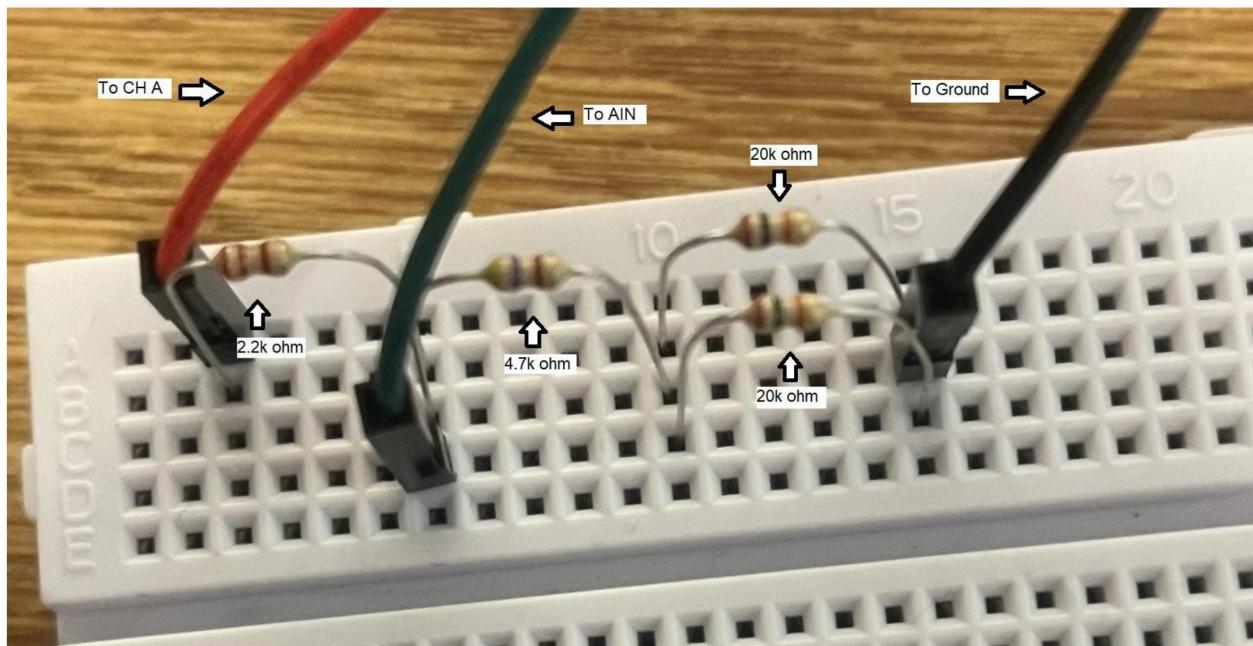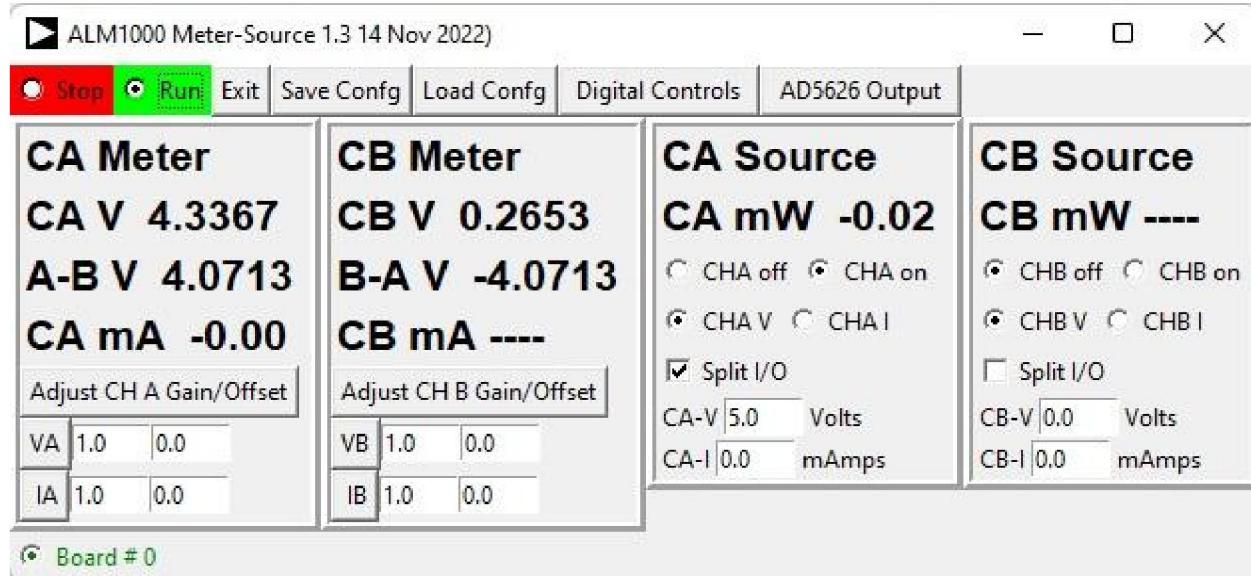

## Node C:

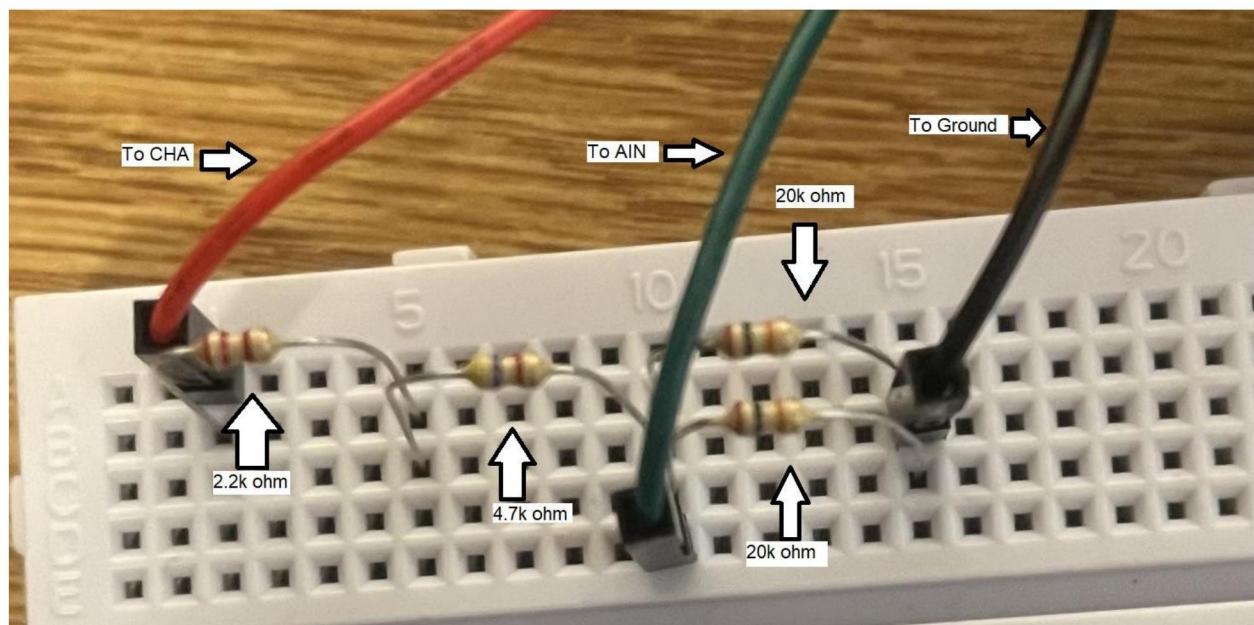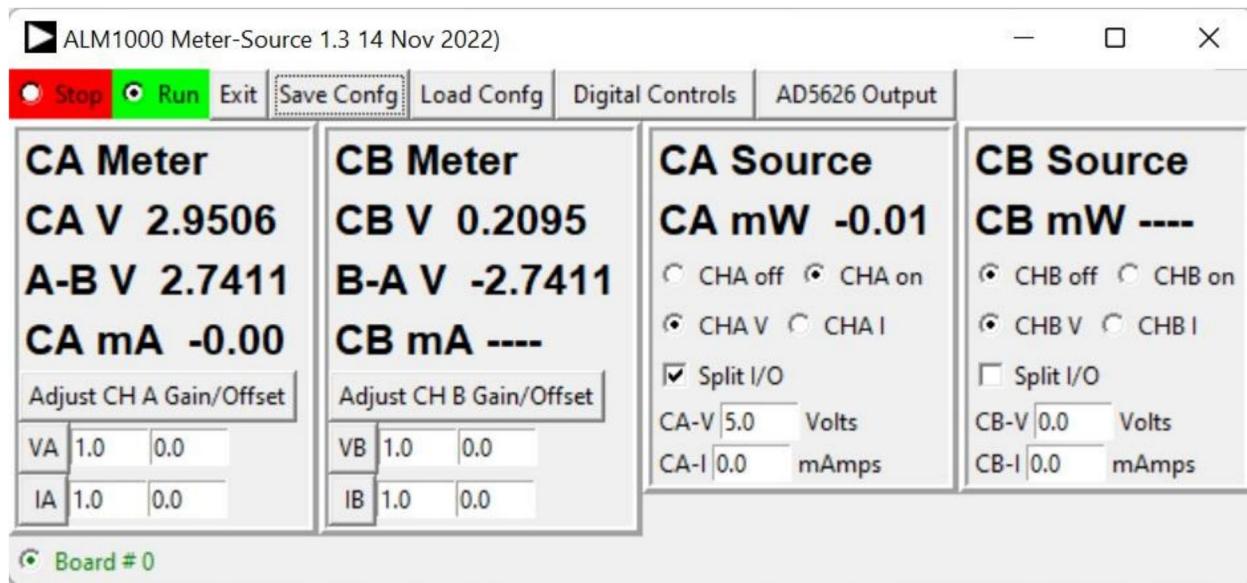

## Node D:

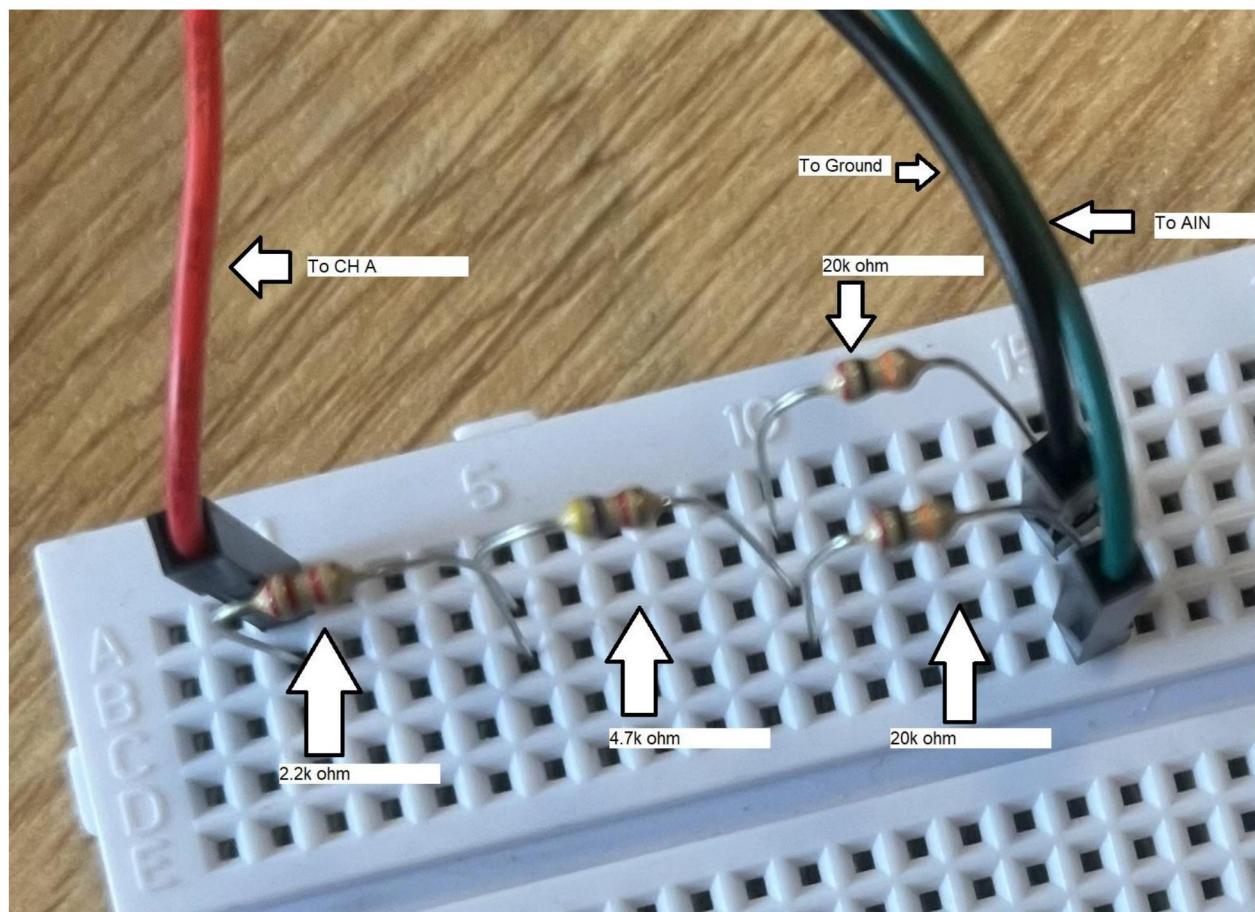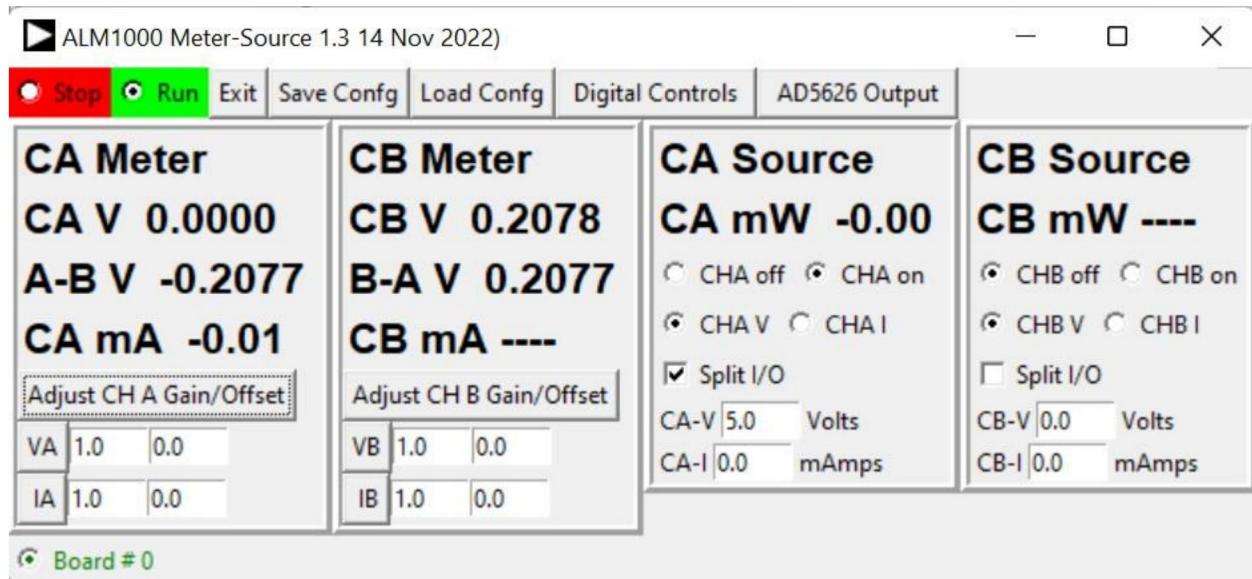

## **Discussion:**

### **1. Prove Ohm's Law, KCL, and KVL in a circuit.**

The calculated, simulated, and measured values are within an acceptable range of each other. The simulated and calculated values for the voltages across R1 and R2, as well as at node C, are the exact same. The only variation we see is between these values and those measured on the M1k board. These slight variations can be attributed to unaccounted resistances of the wires. Another discrepancy is that the M1k doesn't output a constant voltage; rather, it fluctuates over time. Overall, our results back up Ohm's law, KCL and KVL.