

ENGR-2300

Electronic Instrumentation

Quiz 1

Spring 2017

Name \_\_\_\_\_

Section \_\_\_\_\_

Question I (20 points) \_\_\_\_\_

Question II (20 points) \_\_\_\_\_


Question III (20 points) \_\_\_\_\_

Question IV (20 points) \_\_\_\_\_

LMS Question (20 points) (graded on LMS)

Total (80 points) \_\_\_\_\_

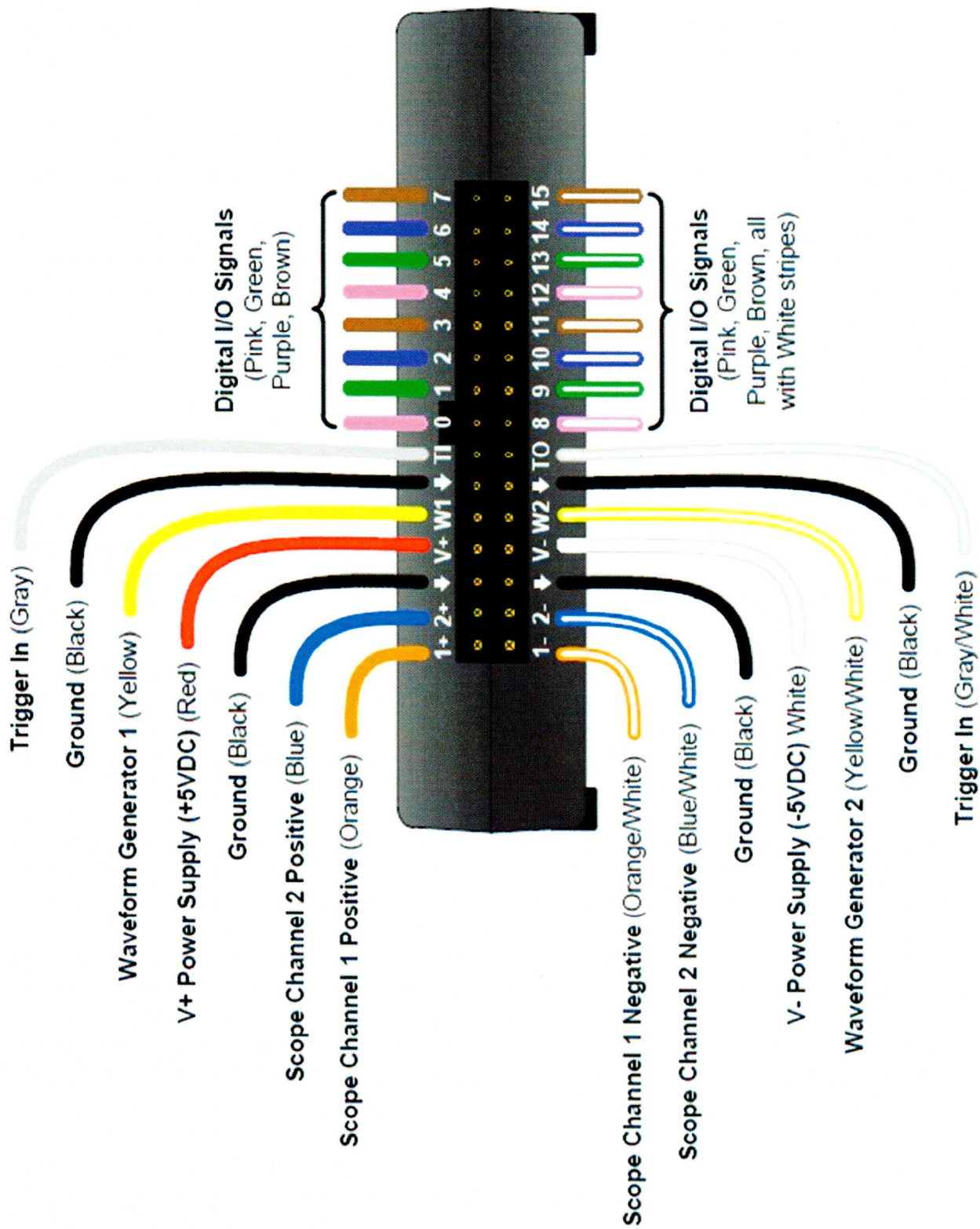On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.



Type	$R_{int}$ ( $\Omega$ )	$V_{oc}$ (V)	Capacity <sup>a</sup> continuous, to 1V/cell				Size (in)	Weight (gm)	Connect <sup>b</sup>	Comments
			(mAh) @ (mA)	(mAh) @ (mA)	(mAh) @ (mA)	(mAh) @ (mA)				
<b>9V "1604"</b>										
Le Clanche	35	9	300	1	160	10	0.65x1x1.9	35	S	
Heavy Duty	35	9	400	1	180	10	"	40	S	
Alkaline	2	9	500	1	470	10	"	55	S	280mAh@100mA
Lithium	18	9	1000	25	950	80	"	38	S	Kodak Li-MnO <sub>2</sub>

### Analog Discovery Specs:

#### 10.1 Analog Inputs (Scope)

- Two fully differential channels; 14-bit converters; 100 MSPS real-time sample rate
- 500uV to 5V/division; 1M $\Omega$ , 24pF inputs with 5MHz analog bandwidth
- Input voltages up to  $\pm 25V$  on each input ( $\pm 50V$  differential); protected to  $\pm 50V$
- Up to 16k samples/channel buffer length
- Advanced triggering modes (edge, pulse, transition types, hysteresis, etc.)

...

#### 10.2 Analog Outputs (Arbitrary Waveform Generator)


- Two channels; 14-bit converters; 100 MSPS real-time sample rate
- Single-ended waveforms with offset control and up to  $\pm 5V$  amplitude
- 5MHz analog bandwidth and up to 16k samples/channel.
- Easily defined standard waveforms (sine, triangle, sawtooth, etc.)
- Easily defined sweeps, envelopes, AM and FM modulation
- User-defined arbitrary waveforms can be defined within WaveForms software user interface or using standard tools (e.g. Excel)
- Cross-triggering between Analog input channels, Logic Analyzer, Pattern Generator or external trigger

#### 10.6 Power Supplies

- Two fixed power supplies derive power from USB port
- +5V up to 50mA and -5V up to 50mA (100mA total)

**Notes from Experiment 3:** If the core cylinder has a radius equal to  $r_c$  and we wind a coil  $N$  times around the cylinder to cover a length  $d$ , the inductor will, ideally, have an inductance equal to:

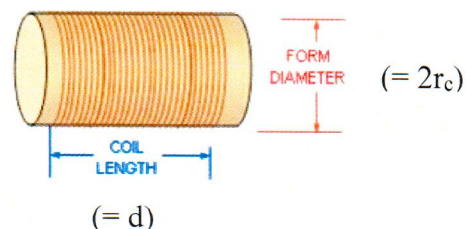
$$L = \frac{(\mu_0 N^2 \pi r_c^2)}{d} \text{Henries}$$



Solan

**I. Voltage Dividers (20 points)** As stated on the cover page: **Round answers to 3 significant digits. Show formulas first and show your work. No credit will be given for numbers that appear without justification.** Note: Pages 2 and 3 of this quiz have background information.

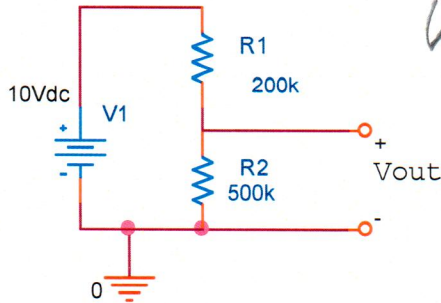a) Find the voltage  $V_{out}$  in the circuit below. (4 pts)



$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_1 = \frac{500}{500 + 200} \cdot 10$$

$$= 7.14V$$

b) Find the current  $I$  in resistor  $R_1$ . (4 pts)

OR  $I_{R_1} = I_{R_2} = \frac{7.14}{500k} = 14.3 \mu A$

$$V_{R_1} = 10 - 7.14 = 2.86V$$

$$I_R = \frac{V_{R_1}}{200k} = 14.3 \mu A$$

c) Find the power dissipated by  $R_2$ . (4pts)

$$P = I^2 R = \frac{V^2}{R} = VI = (7.14)(14.3 \times 10^{-6}) = 102 \mu W = 0.102 mW$$


d) The Analog Discovery board is now connect to measure  $V_{out}$  using the analog channel 1+ and 1- (also called the scope channel.) (8pts)

a. What is the input resistance of an Analog Discovery analog channel? (2pts)

see Background info  $\rightarrow 1M\Omega$  ~~2k\Omega~~

$0 = 1M\Omega$

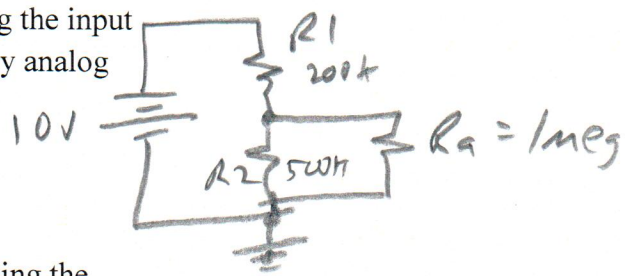b. In the space on the right, hand draw the schematic for this circuit including the input resistance of the Analog Discovery analog channel. (3pts)




c. What voltage will be measured using the Analog Discovery? Give your answer in Volts. (3pts)

$$500k // 1000k = 333k\Omega$$


$$V_{out} = \frac{333k}{333k + 200k} \cdot 10 = 6.25V$$

**II. Resistor Combinations, filters, concepts and miscellaneous (20 points)** Please note that pages 2 and 3 of this quiz have background info.

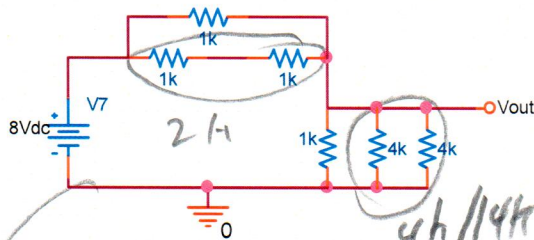- a) Find  $V_{out}$  for the circuit below. Note: unless otherwise stated, all voltages are relative to the 0V ground node. . (4pts)




$2k // 1k \Rightarrow 0.667k$

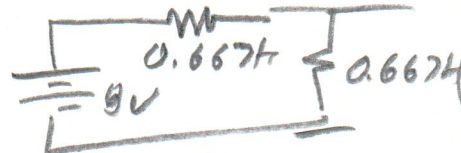

$V_{out} = \frac{1}{2} \cdot V$   
 $= 4V$

$4k // 4k = 2k, 2k // 1k = 0.667k$

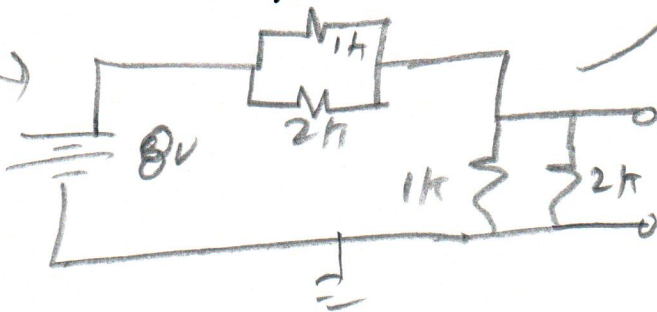You must show your intermediate steps to receive credit for this part. Typically this means drawing equivalent circuit diagrams but there are other ways find the values.



- b) The Analog Discovery board has a -5V power supply. (2pts)

- 1) What is the color of the wire that has this voltage?

White

- 2) What is the maximum current that this supply can provide to a circuit?

50mA


- c) What are the color bands for a  $1k\Omega$  resistor and a  $220\Omega$  resistor? (2pts)

1000  
 $1k$   
102  
 Brown, Black, Red

22000  
 $220\Omega$   
 220 Ohms, 221  
 Red, Red, Brown

*Solu*

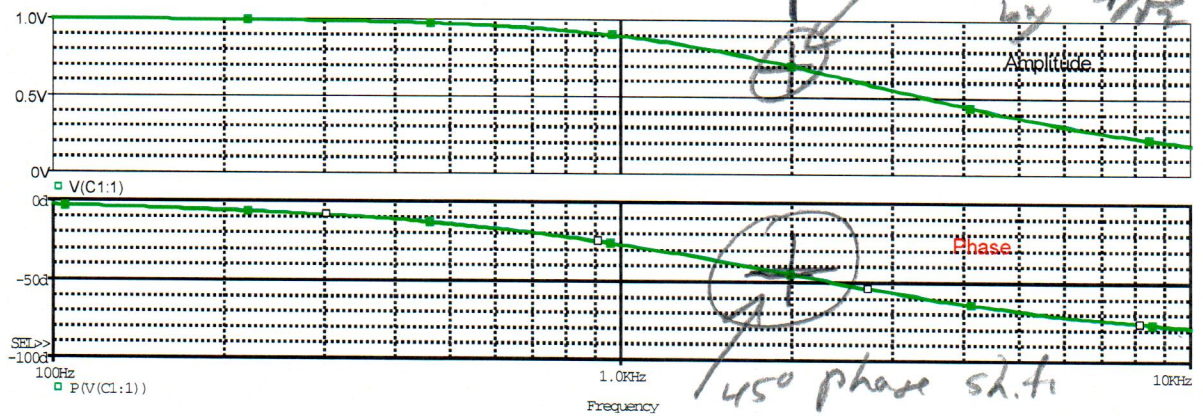d) The traces below are the amplitude and phase angle for the transfer function of a simple RC, RL, CR, or LR circuit. (3pts)



1) Is this a low pass or high pass filter? Circle one: Low Pass High Pass

2) What is the corner frequency for this filter? List the value and also mark both plots.

$f_c =$  2 kHz


*$f_c \Rightarrow$  magnitude =  $\frac{1}{\sqrt{2}}$  point*

*phase shift =  $45^\circ$*

e) On the figure below, draw lines to represent the wires you need to connect to determine the transfer function of the circuit shown using only the Analog Discovery (no additional instrumentation) (3pts)

*Must connect WF Generator*

*" measure both input & output.*

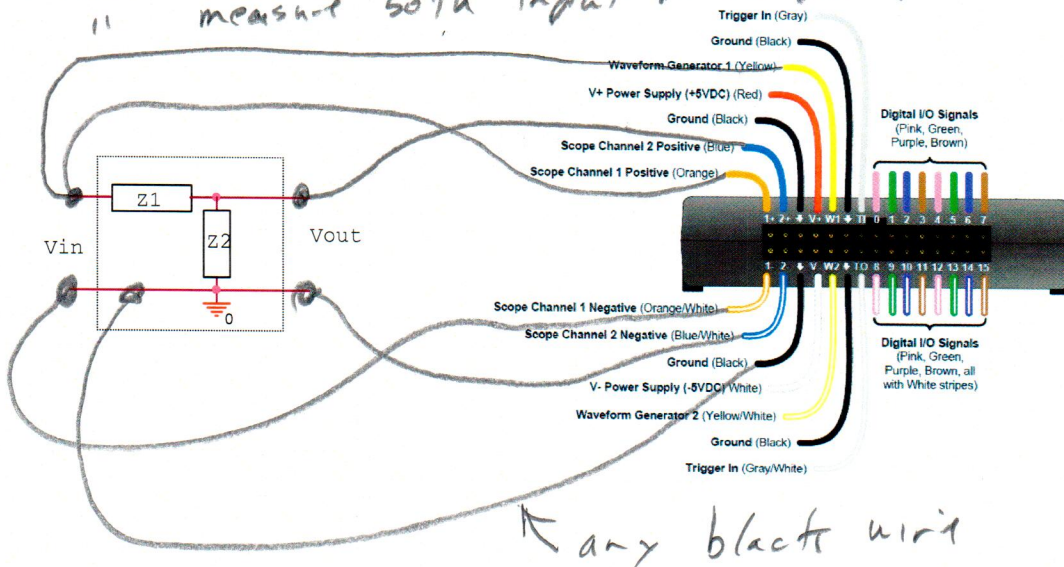

Solu

- f) You built a coil on a plastic tube as you did for experiment 3. The measured inductance was  $30\mu\text{H}$  with a resistance of  $0.3\Omega$ . Your partner built one using the same gauge and length of wire at the one you built, but put in on a plastic tube that has  $\frac{1}{2}$  the diameter of yours. Your partner wound her/his coil so that the length of the coil was the same as yours and still used all of the wire. What would the expected values of the inductance and resistance be for your partner's coil based on what you measured for your coil? (4pts)

$$L = \underline{30\mu\text{H}}$$

see page 3

$$R = \underline{0.3\Omega}$$

$$L = \frac{\mu_0 N^2 \pi r_c^2}{d}$$

wire length doesn't change,  $R$  doesn't change

for  $L$   $\mu_0, \pi, d$  are the same

$r_c$  drops by  $\frac{1}{2}$

But since wire length =  $2\pi r_c \cdot N$





length is const.,  $N$  goes up by 2

$$N^2 r_c^2 \approx \text{const.}$$

$$L \approx \text{const.}$$

Soln.

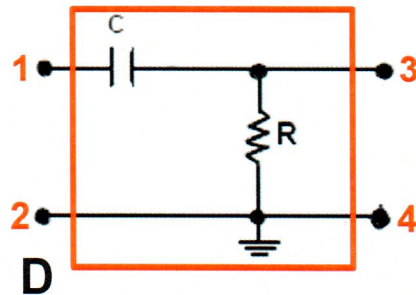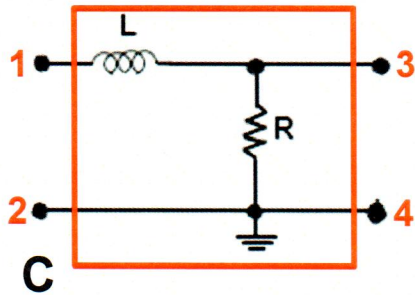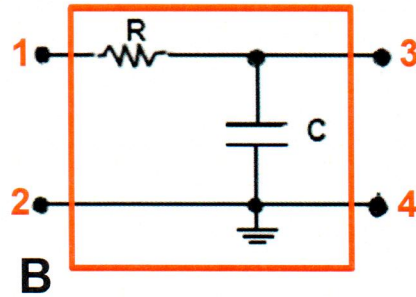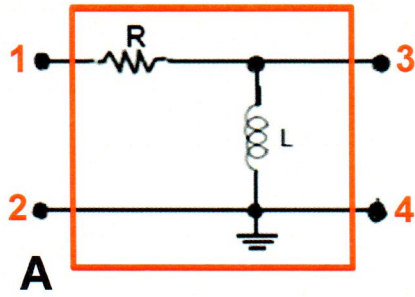III. Filters & Transfer Functions (20 points)



a) Shown above are the four basic, two-element, passive filter configurations made with RL and RC combinations. Determine the general complex transfer function for each circuit in terms of R, L, C and frequency  $\omega$ , by modeling each as a voltage divider. (4 pts)

A) RL:  $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} = \frac{j\omega L}{R + j\omega L}$

B) RC:  $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} = \frac{1/j\omega C}{R + 1/j\omega C}$   
 $= \frac{1}{j\omega RC + 1}$


C) LR:  $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} = \frac{R}{R + j\omega L}$

D) CR:  $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} = \frac{R}{R + 1/j\omega C}$   
 $= \frac{j\omega RC}{j\omega RC + 1}$

b) Assume all four circuits are made with ideal components. Identify which are high pass filters and which are low pass filters by circling the high pass and underlining the low pass in the following list (4 pts): RC (CR) (RL) (LR)



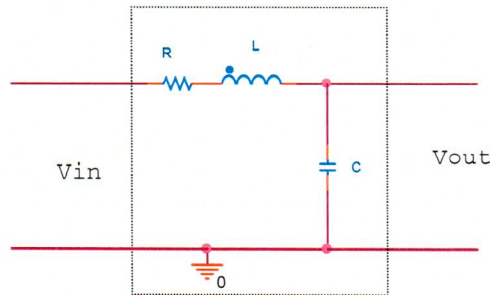c) For this question use the circuit below. C is the value of the capacitor in Farads, L is the value of the inductor in Henries, and R is the value of the resistor in Ohms. Assume  $V_{in}$  is a sinewave. This is an AC steady state problem.



For all parts, the solution is in terms of R, L, C, and  $j\omega$

1) Write the transfer function for  $V_{out}/V_{in}$  as a ratio of polynomials, (in terms of R, L, C, and  $j\omega$ .) (2pts)

$$H(j\omega) = \frac{1/j\omega C}{1/j\omega C + j\omega L + R} = \frac{1}{1 + j\omega^2 LC + j\omega RC}$$

$$= \frac{1}{1 - \omega^2 LC + j\omega RC}$$

2) What is the magnitude and phase angle of the transfer function at very low (but not zero) frequencies? (1pt)

$$|H(j\omega)| = 1 \text{ at small } \omega$$

$$\angle H(j\omega) = 0^\circ \text{ at small } \omega$$

↑  
pure real

3) What is the magnitude and phase at very high (but not infinite) frequencies? (1pt)

$$H(j\omega) \approx \frac{1}{- \omega^2 LC} \text{ at } \omega \text{ large}$$

Magnitude =  $\frac{1}{\omega^2 LC}$

angle =  $-180^\circ$  or  $+180^\circ$   
or  $-\pi$  or  $+\pi$

4) What is the magnitude and phase of the transfer function at the resonant frequency? (2pt)

(2pt)  $\omega = \frac{1}{\sqrt{LC}}$  at  $\omega_0$


$$H(j\omega) = \frac{1}{1 - \frac{LC}{LC} + (jRC)(\frac{1}{\sqrt{LC}})} = \frac{1}{j(\frac{RC}{\sqrt{LC}})} = -j \frac{\sqrt{LC}}{RC}$$

Magnitude =  $\frac{\sqrt{LC}}{RC}$  or  $\frac{1}{R} \sqrt{\frac{L}{C}}$

OR =  $-j \frac{1}{R} \sqrt{\frac{L}{C}}$

angle =  $-90^\circ$  or  $-\pi/2$

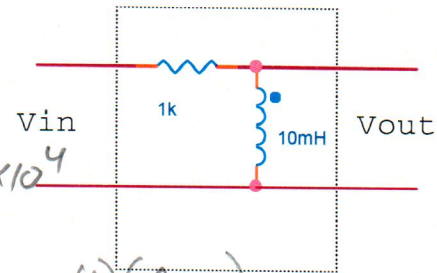- d) Find the magnitude and phase angle of the transfer function for the circuit shown on the right given that  $V_{in}$  is a sinewave with a frequency of 8kHz. To receive credit, you must show your work for this and all problems. (4pts)  
Give the phase in degrees.



$$H(j\omega) = \frac{j\omega L}{R + j\omega L} = \frac{(j)(5.03 \times 10^4)(0.01)}{1000 + j(5.03 \times 10^4)(0.01)}$$

$$= \frac{j 503000}{1000 + j 503000} = \frac{503 \angle 90^\circ}{1120 \angle 26.7^\circ} = 0.449 \angle 63.3^\circ$$

$$\text{Mag} = \sqrt{1000^2 + 503^2} = 1.12 \times 10^3$$

$$\text{ang} = \tan^{-1} \frac{503}{1000} = 26.7^\circ$$

$$\text{OR } H(j\omega) = \frac{(j 503)(1000 - j 503)}{(1000 + j 503)(1000 - j 503)} \Rightarrow$$

- e) Using the results of part d) what is the time domain equation for  $V_{out}$  if  $V_{in} = 10V \sin(2\pi 8000t + 0^\circ)$   $V_{out}$  must have the form of  $V_{out} = A \sin(\omega t + \theta)$  (2pts)

$$\text{Mag} = (10)(0.449) = 4.49$$


$$\theta = 0^\circ + 63.3^\circ$$

$$V_{out} = 4.49V \sin(2\pi 8000t + 63.3^\circ)$$

$$\text{OR } 4.49V \sin(2\pi 8000t + 1.1 \text{ radians})$$

IV – Signals, Transformers and Inductors (20 points)

Solu

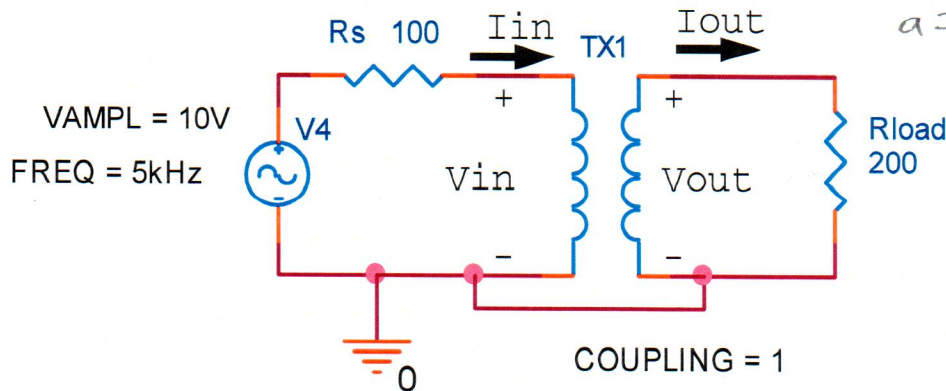

$$a = \frac{N_2}{N_1} = \frac{1000}{500} = 2$$

Given:  $N_1=500$ , the number of turns on the primary.  $N_2=1000$ , the number of turns on the secondary. Assume an ideal transformer with full coupling. In your answers to the following questions, use all available and useful information.

- a) For the given information, write out the expressions for the ratios  $V_{out}/V_{in}$ ,  $I_{out}/I_{in}$  and the transformer input impedance  $R_{in}$ . ( $R_{in}$  is  $V_{in}/I_{in}$ ) (6 pts)

$$\frac{V_2}{V_1} = \frac{V_{out}}{V_{in}} = a = 2 \quad \frac{V_{out}}{V_{in}} = 2$$

$$\frac{I_{out}}{I_{in}} = \frac{1}{a} = \frac{1}{2}$$

$$R_{in} = \frac{R_{load}}{a^2} = \frac{200}{4} = 50\Omega$$

- b) Draw the circuit diagram for the voltage divider consisting of the transformer input impedance  $R_{in}$  and the resistance  $R_s$ . Then solve for  $V_{in}$ , the voltage across the input terminals of the ideal transformer. (4 pts)



$$V_{in} = \frac{50}{50+100} \cdot 10 = 3.33V$$

c) Find  $V_{out}$  from your value for  $V_{in}$ . (2 pts)

Soln

$$\frac{V_{out}}{V_{in}} = 2 \quad V_{out} = 2V_{in} = \underline{6.67V}$$

d) Determine both the primary and secondary currents ( $I_{in}$  and  $I_{out}$ ). (2 pts)

$$I_{out} = \frac{V_{out}}{200} = 33.3 \text{ mA}$$

$$I_{in} = 2I_{out} = 66.7 \text{ mA}$$

e) Determine the power loss in both  $R_s$  and  $R_{load}$ . (2 pts)

$P = I^2 R, V^2/R, VI$

$$W_{R_s} = (66.7 \text{ mA})^2 (100) = \underline{0.444 \text{ W}}$$

$$W_{R_{load}} = V \cdot I = 6.67 \text{ V} \cdot 33.3 \text{ mA} = \underline{0.222 \text{ W}}$$

f) Assume that  $R_s$  and  $R_{load}$  are set by the system and can't change them. You can change the number of turns in the secondary of the transformer, with the goal of getting the maximum power into  $R_{load}$ . It can be shown that maximum power transfer will occur when input resistance at the transformer ( $R_{in}$ , part b) equals the source resistance,  $R_s$ .


**Determine the turns ratio,  $a$ , that will result in  $R_{in} = R_s$  ( $R_{in}$  as stated in part b).**

**What  $N_2$  will give you this ratio?** ( $N_1$  is also fixed) (2pts)

$$R_{in} = \frac{R_{load}}{a^2} = R_s \quad \frac{200}{a^2} = 100 \quad \frac{N_2}{N_1} = 1.41 = \frac{N_2}{500}$$

$$a^2 = 2 \quad \underline{a = 1.41} \quad \underline{N_2 = 705}$$

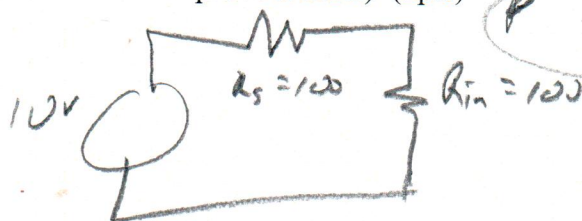g) What is the power loss in  $R_s$  and  $R_{in}$  with the new  $N_2$ ? (Note: It can also be proved that the power loss in what we call  $R_{in}$  equals to the power delivered to the  $R_{load}$ , but don't prove it here.) (2pts)



$$P_{R_s} = \frac{V_{R_s}^2}{R_s} = \frac{5^2}{100} = 0.25 \text{ W}$$

$$P_{R_{in}} = \frac{V_{R_{in}}^2}{R_{in}} = \frac{5^2}{100} = 0.25 \text{ W}$$