

ENGR-2300

Electronic Instrumentation

Quiz 1

Fall 2019

Name SOLUTIONSSection

Question I (20 points) _____

Question II (20 points) _____

Question III (20 points) _____

Question IV (20 points) _____

LMS Question (20 points) (graded on LMS)

Total (80 points) _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

Analog Discovery 2 partial set of Specifications -**Analog Inputs**

Channels: 2
 Channel type: differential
 Resolution: 14-bit
 Input impedance: $1\text{M}\Omega \parallel 24\text{pF}$
 Scope scales: 500uV to 5V/div
 Analog bandwidth with included flywires: 9 MHz @ 3dB, 2.9 MHz @ 0.5dB, 0.8 MHz @ 0.1dB
 Input range: $\pm 25\text{V}$ ($\pm 50\text{V}$ diff)
 Input protected to: $\pm 50\text{V}$
 Cursors with advanced data measurements
 Captured data files can be exported in standard formats
 Scope configurations can be saved, exported, and imported

Arbitrary Waveform Generator

Channels: 2
 Channel type: single ended
 Resolution: 14-bit
 AC amplitude (max): $\pm 5\text{V}$
 DC Offset (max): $\pm 5\text{V}$
 Analog bandwidth with included flywires: 9 MHz @ 3dB, 2.9 MHz @ 0.5dB, 0.8 MHz @ 0.1dB
 Slew rate (10V step): $400\text{V}/\mu\text{s}$
 Standard waveforms: sine, triangle, sawtooth, etc.
 Advanced waveforms: Sweeps, AM, FM.
 User-defined arbitrary waveforms: defined within WaveForms software user interface or using standard tools (e.g. Excel)

Power Supplies


Voltage range: 0.5V...5V and -0.5V...-5V
 Pmax (USB powered): 500mW total
 Imax (USB powered): 700mA for each supply
 Pmax (AUX powered): 2.1W for each supply
 Imax (AUX powered): 700mA for each supply
 Accuracy (no load): $\pm 10\text{mV}$
 Output impedance: $50\text{m}\Omega$ (typical)

Voltmeters

Channels (shared with scope): 2
 Channel type: differential
 Measurements: DC, AC, True RMS
 Resolution: 14-bit
 Accuracy (scale $\leq 0.5\text{V}/\text{div}$): $\pm 5\text{mV}$
 Accuracy (scale $\geq 1\text{V}/\text{div}$): $\pm 50\text{mV}$
 Input impedance: $1\text{M}\Omega \parallel 24\text{pF}$
 Input range: $\pm 25\text{V}$ ($\pm 50\text{V}$ div)
 Input protected to: $\pm 50\text{V}$

I. Voltage Dividers (20 points) As stated on the cover page: Round answers to 3 significant digits. Show formulas first and show your work. No credit will be given for numbers that appear without justification.

Consider the circuit diagram shown below. R_m represents the resistance of an ammeter (a current measuring device). The circuit with the dashed line is the model of an ohmmeter, which can be used to measure the value of an unknown resistance R_x .

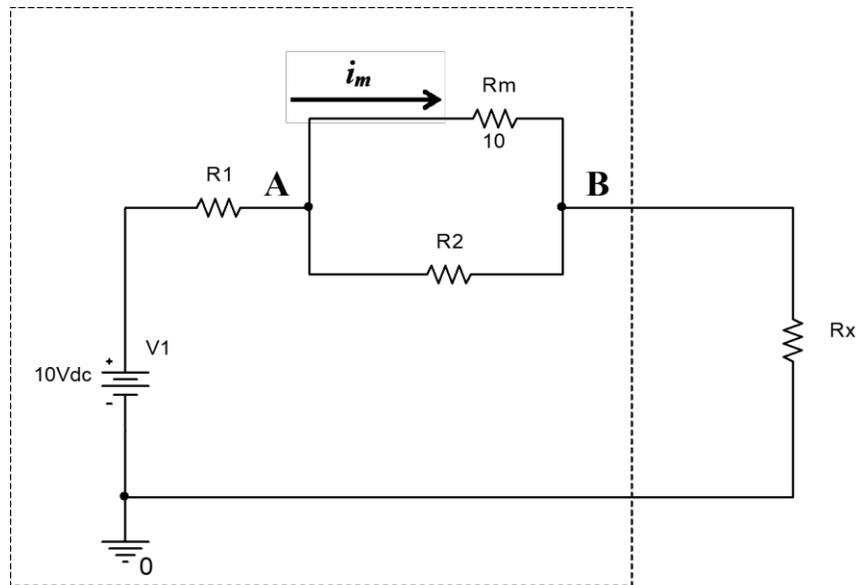

Case 1: Given that when $R_x = 0 \Omega$, the current through resistor R_m is 2 mA, i.e. $i_m = 2 \text{ mA}$.

Case 2: Given that when $R_x = 2000 \Omega$, the current through resistor R_m is 1 mA, i.e. $i_m = 1 \text{ mA}$.

a. (2 pts) Find voltage between points A and B for each of the cases described above.

$$\text{Case 1: } V_{AB} = i_m R_m = 20 \text{ mV}$$

$$\text{Case 2: } V_{AB} = i_m R_m = 10 \text{ mV}$$

b. (1 pt) What is the equivalent resistance between points A and B, R_{AB} ? (Express in terms of R_2)

$$R_{AB} = R_2 \parallel R_m = \frac{10 R_2}{10 + R_2}$$

- c. (5 pts) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 1.

$$V_{AB} = 20\text{mV} = V_1 \left(\frac{R_{AB}}{R_1 + R_{AB} + R_x} \right)$$

\swarrow 10V
 \searrow 0Ω

$$\Rightarrow (R_1 + R_{AB}) 2\text{mV} = R_{AB}$$

$$\Rightarrow R_1 + \frac{10R_2}{10+R_2} = \frac{5000 R_2}{10+R_2} \Rightarrow 10R_1 - 4990R_2 + R_1R_2 = 0$$

Equation 1

- d. (8 pts) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 2.

$$V_{AB} = 10\text{mV} = V_1 \left(\frac{R_{AB}}{R_1 + R_{AB} + R_x} \right)$$

\swarrow 10V
 \searrow 2000Ω

$$\Rightarrow \left(R_1 + \frac{10R_2}{10+R_2} + 2000 \right) 1\text{mV} = \frac{10R_2}{10+R_2}$$

$$\Rightarrow 10R_1 - 7990R_2 + R_1R_2 = -20000 \quad \text{equation 2}$$

- e. (4 pts) Solve the linear relationships derived in the previous parts, to determine the values of resistors R_1 and R_2 such that both case 1 and 2 are satisfied.

equation 1 - equation 2

$$\Rightarrow 3000R_2 = 20000 \Rightarrow R_2 = 6.667 \Omega$$


Substitute in equation 1.

$$10R_1 - 33268.33 + 6.667R_1 = 0$$

$$\Rightarrow R_1 = 1996 \Omega$$

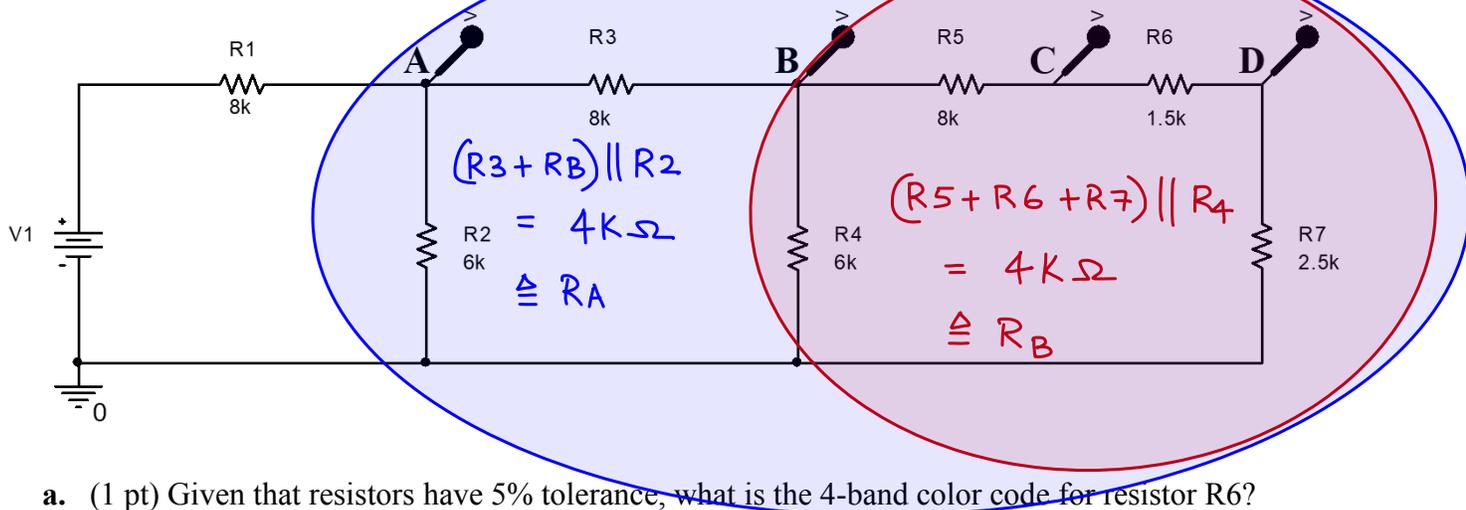II. Resistor Combinations, concepts and miscellaneous (20 points) Note: Page 2 of this quiz has background information.

The following circuit consists of 7 resistors, 1 DC voltage source and has 4 voltage markers placed at points A, B, C, and D. **Note** that the following questions are generally independent of each other.



- a. (1 pt) Given that resistors have 5% tolerance, what is the 4-band color code for resistor R6?

Brown - Green - Red Gold

$\hookrightarrow 1.5\text{k}\Omega$

- b. (6 pts) Given that voltage at point A, $V_A = 9\text{V}$, find the voltages at point B and the source voltage V_1 .

$$V_A = V_1 \left(\frac{R_A}{R_A + R_1} \right) \Rightarrow 9 = V_1 \left(\frac{4\text{k}}{4\text{k} + 8\text{k}} \right)$$

$$\Rightarrow \boxed{V_1 = 27\text{V}}$$

$$\begin{aligned} \text{Voltage @ point B} = V_B &= V_A \left(\frac{4\text{k}}{8\text{k} + 4\text{k}} \right) \\ &= 9 \left(\frac{4\text{k}}{12\text{k}} \right) = 3\text{V} \end{aligned}$$

$$\boxed{V_B = 3\text{V}}$$

- c. (2 pts) Given that voltage at point B, $V_B = 4V$, find the current through resistor R_6 ?

$$I_{R_6} = \frac{V_B}{R_5 + R_6 + R_7} = \frac{4}{12K} = 0.333 \text{ mA}$$

- d. (2 pts) Given that the current through R_6 is 0.25 mA , find the power dissipated through resistor R_7 ?

$$I_{R_6} = I_{R_7} \quad \text{Resistors in series}$$

$$P_{R_7} = I_{R_7}^2 \cdot R_7 = (0.25 \text{ mA})^2 \times 2.5K = 0.15625 \text{ mW}$$


- e. (1 pts) A ceramic capacitor has a code "1 0 3" written on it. What is its capacitance?

$$0.01 \mu\text{F}$$


$$10 \times 10^3 \text{ pF} \\ = 10^4 \text{ pF}$$

Now consider that the same resistive circuit is built on a protoboard, V_1 is set to $5V$ DC supplied by Analog discovery 2 board, and voltage at point A is being measured using scope channel 2.

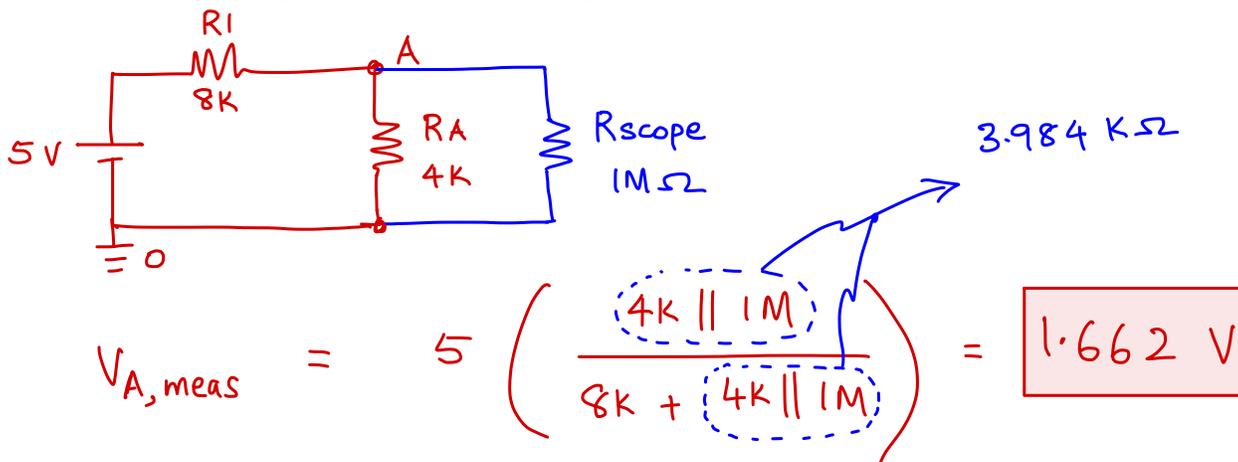- f. (2 pts) What voltage would the analog discovery scope channel 2 measure at point A? Hint: Add the input resistance of Analog Discovery channel.



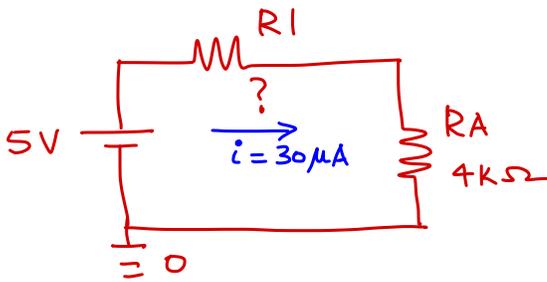- g. (4 pts) You are now asked to change R_1 from $8\text{k}\Omega$ to a new value such that the current through resistor R_1 is close to $30\ \mu\text{A}$. Voltage source V_1 is set to 5V . What is your new choice of R_1 ?



$$5\text{V} = i (R_1 + R_A)$$

$$\Rightarrow R_1 + 4\text{k} = \frac{5}{30\ \mu}$$

$$\Rightarrow R_1 = 162.67\ \text{k}\Omega$$

- h. (2pts) When defining the VSIN component (sinusoidal voltage source), indicate any two (of the four) parameters that are available when you place the part.

Amplitude
offset



Frequency
AC

III. Filters & Transfer Functions (20 points) For this problem assume AC Steady State.

a) Use the circuit shown for this part.

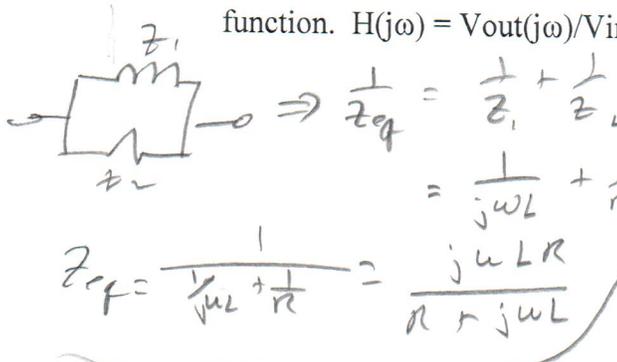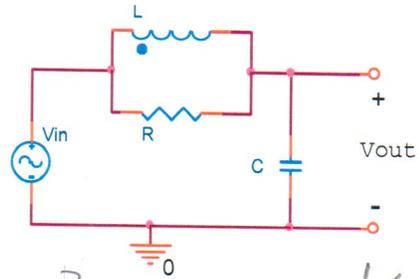1. Find the transfer function of the circuit shown.

Simplify such that there are no fractions in the numerator or denominator of the transfer function. $H(j\omega) = V_{out}(j\omega)/V_{in}(j\omega)$ (6pts)



$$\frac{1}{Z_{eq}} = \frac{1}{Z_L} + \frac{1}{R}$$

$$Z_{eq} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{R}} = \frac{j\omega LR}{R + j\omega L}$$

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_C + Z_{eq}} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + \frac{j\omega LR}{R + j\omega L}}$$

$$H(j\omega) = \frac{(R + j\omega L)(1/j\omega C)}{R + j\omega L + j^2\omega^2 LRC}$$

$$H(j\omega) = \frac{j(R + j\omega L)C}{R + j\omega L - \omega^2 LRC}$$

2. Determine the amplitude and phase of the transfer function for the circuit for very small frequency and for very high frequency. Do not take this to 0 or infinite Hz. (4pts)

ω small

$$H(j\omega) \approx \frac{R}{R} = 1 \angle 0^\circ$$

amp = 1 angle = 0°

ω large



$$H(j\omega) \approx \frac{j\omega L}{-\omega^2 LRC} = \frac{-j}{\omega RC}$$

mag = $\frac{1}{\omega RC}$ Phase = -90°

3. Redraw the circuit and simplify the circuit for operation at low and high frequency. For this part you take it to extremes, low frequency is dc operation. High is approaching infinity. (2pts)

Low Frequency
L = short C = open


High Frequency
L = open C = short

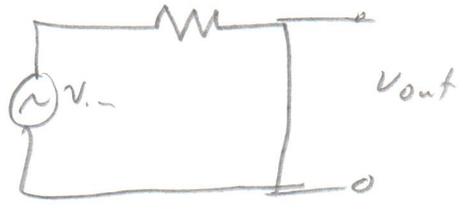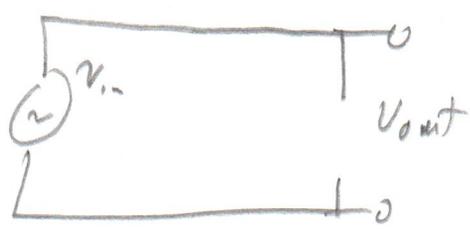



Note: mag = 1, phase = 0

can't get magnitude Note
0 phase
P. Schoch and M. Hameed

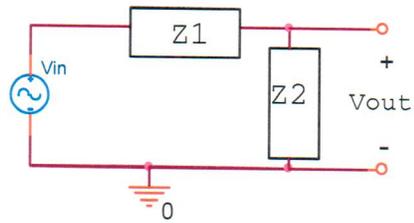- b) In the circuit shown, Z1 and Z2 represent a single component, either a resistor, capacitor or inductor. Complete the table below by entering a Y for yes is that configuration of Z1 and Z2 would be a low pass or a high pass filter. (5pts)




Z1	Z2	Low Pass (Y or N)	High Pass (Y or N)
R	C	Y	N
C	R	N	Y
R	R	N	N
R	L	N	Y
L	R	Y	N

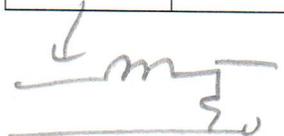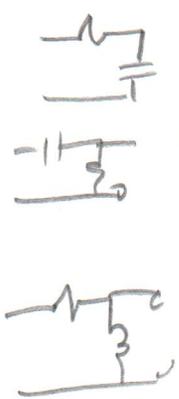

all Req. the same
↑↑↑
←

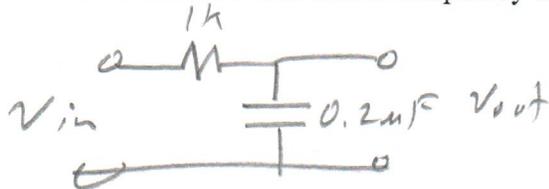- c) Draw a low pass filter using just a 1kΩ resistor and a 0.2μF capacitor. Label the input and output.



in hertz

And calculate the corner frequency for this circuit. (3pts)


corner freq $\left| \frac{1}{j\omega C} \right| = R$

$$\omega = \frac{1}{RC} = \frac{1}{(10^3)(2 \times 10^{-7})}$$

$$\omega = 5 \times 10^3$$

$$f = \frac{\omega}{2\pi} = 796 \text{ Hz}$$

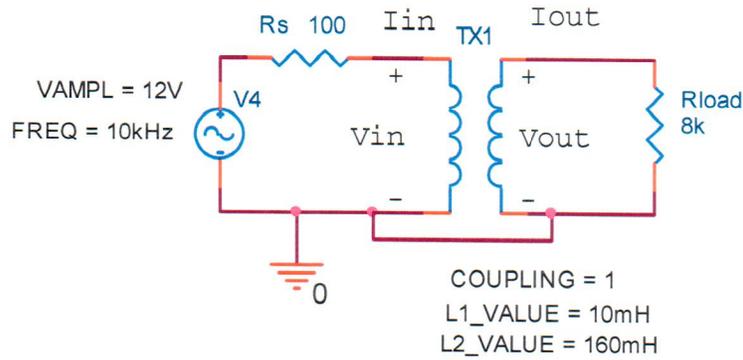IV – Phasors and Transformers (20 points)



1) Assume an ideal transformer with full coupling.

a. For the given information, determine the turns ratio, a . And determine the ratios

V_{out}/V_{in} , I_{out}/I_{in} and the transformer input impedance R_{in} . (R_{in} is V_{in}/I_{in}) (6 pts)

$$a = \sqrt{\frac{L_2}{L_1}} = \sqrt{\frac{160}{10}} = 4$$

$$Z_{in} = \frac{Z}{a^2}$$

$$R_{in} = \frac{8000}{16} = 500$$

$$V_2 = a V_1 = \frac{V_{out}}{V_{in}} = 4$$

$$I_{out} = \frac{1}{a} I_{in}, \frac{I_{out}}{I_{in}} = \frac{1}{4} = 0.25$$

$a = 4$ (2pt)
 $V_{out}/V_{in} = 4$ (1pt)
 $I_{out}/I_{in} = 0.25$ (1pt)
 $R_{in} = 500$ (2pt)

b. Solve for V_{in} (voltage across the input terminals of the ideal transformer) and V_{out} , the voltage across the output terminals and the of the ideal transformer. Assume the phase of V_4 is zero degrees and give the answer in the form of $v(t) = V_1 \cos(\omega t + \theta_1)$ (2 pts)

$$R_{in} = 500$$

$$V_{in} = \frac{500}{500+100} \cdot 12 = 10V$$

$$V_{in}(t) = 10 \cos(2\pi \cdot 10^4 t + 0^\circ)$$

$$V_{out}(t) = 4 \cdot V_{in} = 40 \cos(2\pi \cdot 10^4 t)$$

OR $10 \cos(2\pi \cdot 10^4 t)$ OR $10 \cos(6.3 \times 10^4 t)$

c. Above you were told to assume that the transformer is ideal. For that to be valid, the impedance of the primary inductor should be much larger than the source resistance. Is that valid in this case? Explain or justify. Would it be valid if the signal source was at 60Hz? (3pts)

At 10kHz $|j\omega L| = (2\pi)(10^4)(10^{-2}) = 628\Omega$


$628\Omega \gg 100\Omega$ - reasonably true so Yes Valid

At 60Hz $|j\omega L| = 3.8\Omega$ this is much less than 100Ω **NO**

EI You must include units. 4 P. Schoch and M. Hameed 10pt

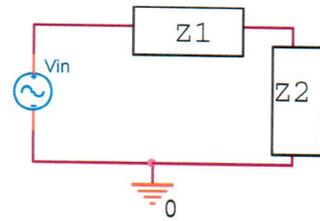- 2) Phasors: This circuit shown has 2 complex impedances, Z_1 and Z_2 , connected as shown.


Given: $V_{in} = 10V \angle 0^\circ$ and the voltage across Z_2 is measured to be $V_{Z2} = 6V \angle 30^\circ$



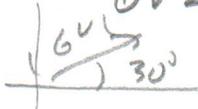- a. Write V_{in} and V_{Z2} in Cartesian form. (2pts)

$$10V \angle 0^\circ \Rightarrow 10 + j0V = 10V$$

$$6V \angle 30^\circ \Rightarrow 6 \cos \theta + j 6 \sin \theta = (5.2 + j3)V$$



- b. Determine V_{Z1} , the voltage across Z_1 in Cartesian and polar form (3pts)

$$\vec{V}_{in} = \vec{V}_{Z1} + \vec{V}_{Z2} \quad \text{use Cartesian} \quad \vec{V}_{Z1} = \vec{V}_{in} - \vec{V}_{Z2}$$

$$= 10 - (5.2 + j3) = (4.8 - j3)V$$

$$4.8 - j3 \Rightarrow (4.8^2 + 3^2)^{1/2} \angle \tan^{-1} \frac{-3}{4.8} = 5.66 \angle -32^\circ$$

- c. If Z_2 is a $1k\Omega$ resistor, and only a resistor, what is the current through Z_2 in both polar and Cartesian form? (3pts)

$$\vec{I} = \frac{\vec{V}}{R} = \frac{6 \angle 30^\circ}{1k} = 6 \angle 30^\circ \text{ (mA)} \quad \text{1pt}$$

$$\vec{I} = \frac{5.2 + j3}{1000} = (5.2 + j3) \text{ (mA)} \quad \text{2pt}$$

- 3) Give the names of 2 of the people teaching this course. This can be first names or last names and can be the professors and/or the teaching assistants. (1pt)

see bottom of page - or

Zhihua

Wesley

Liang

Fong

Ruixuan

Melissa

Yan

Shuex

James

Jenna

Cassidy

Kentoffio

spelling doesn't matter