

ENGR-2300
Electronic Instrumentation



Quiz 2

Spring 2013

Name Solutim

Section

Question I (25 points) _____

Question II (25 points) _____



Question III (25 points) _____

Question IV (25 points) _____


Total (100 points) _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

20 March – Vernal Equinox

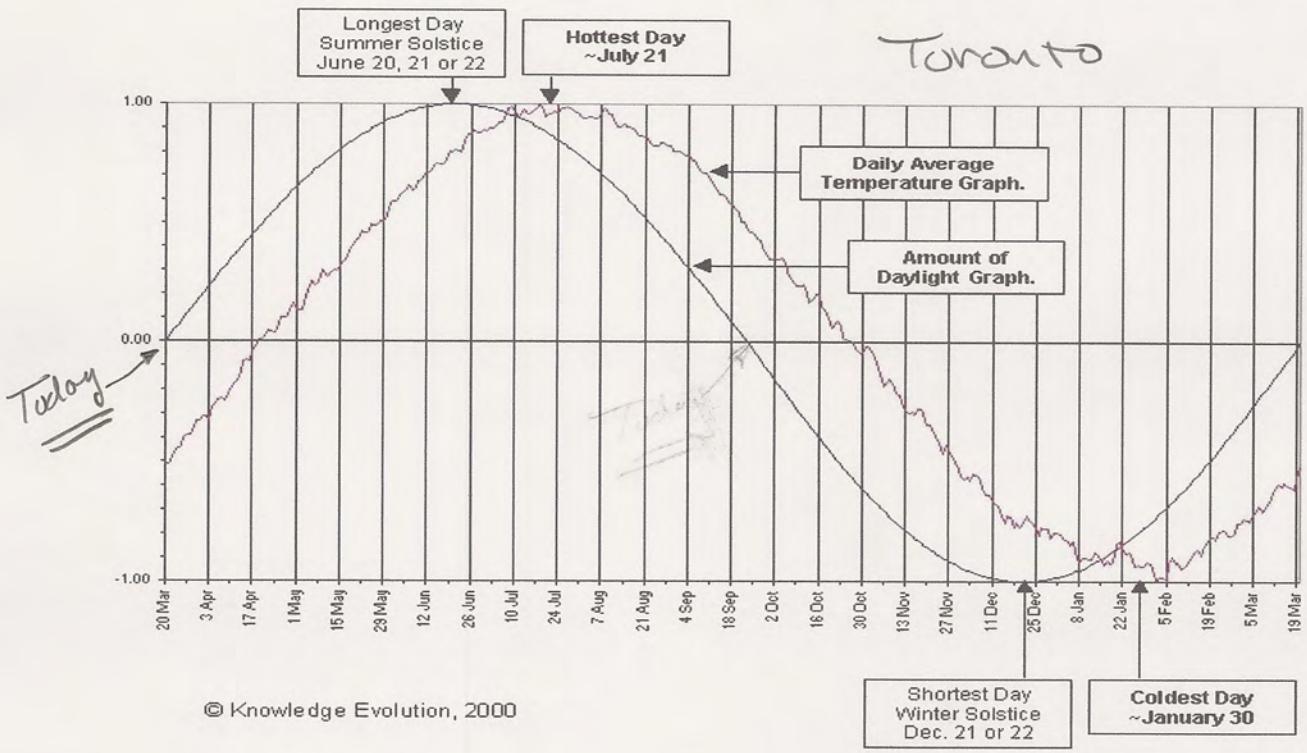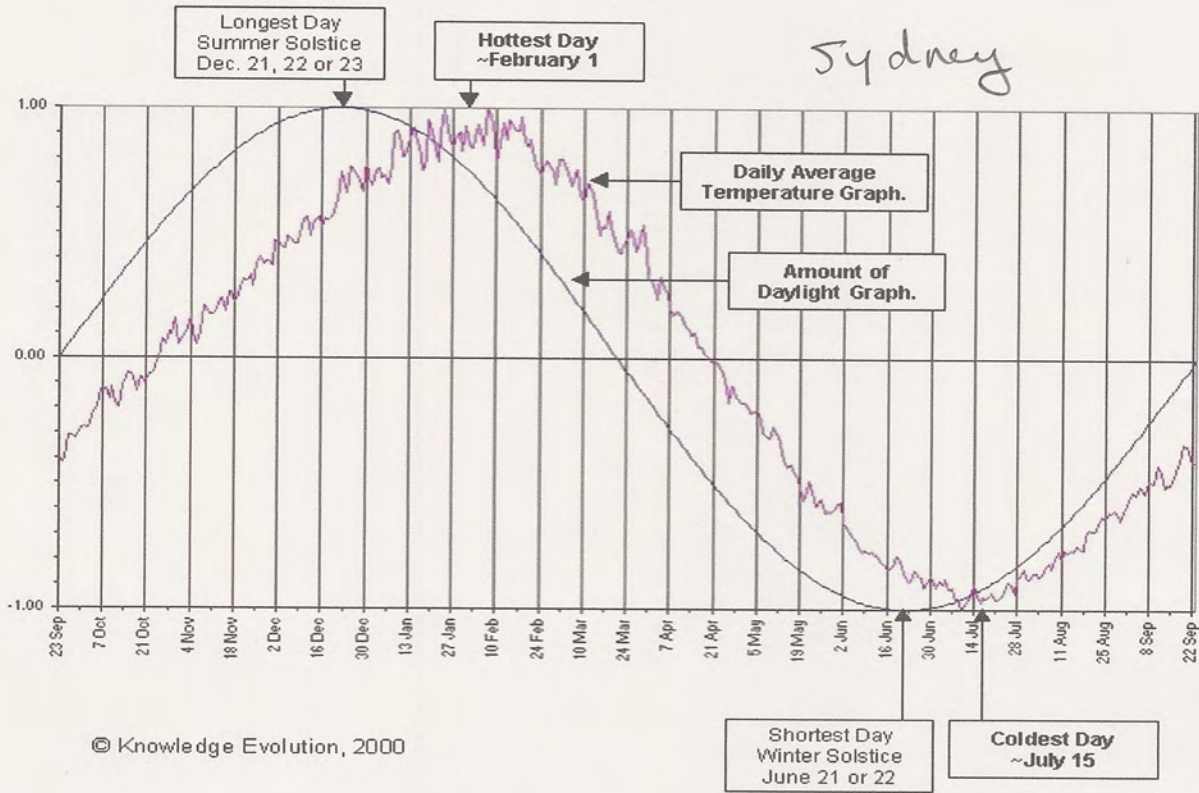



I. Thevenin Equivalent Voltage Source

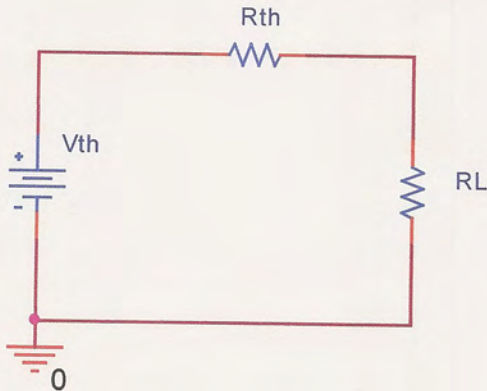



The Thevenin equivalent circuit consists of a voltage source in series with a resistor, which provides a very simple replacement for much more complex circuits. If we have this simple source, analyzing changing loads becomes quite easy.

In this problem, you are to find the Thevenin voltage and resistance for three circuits. The load is to the right of the dashed line in the first two circuits.

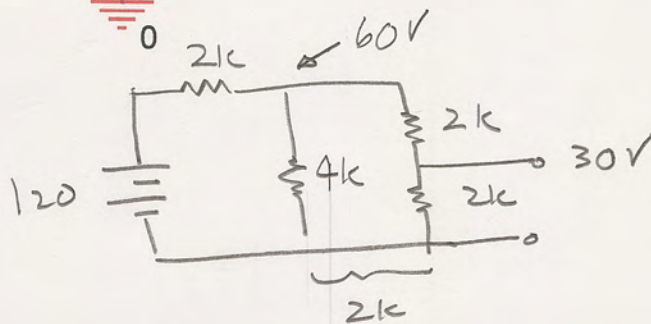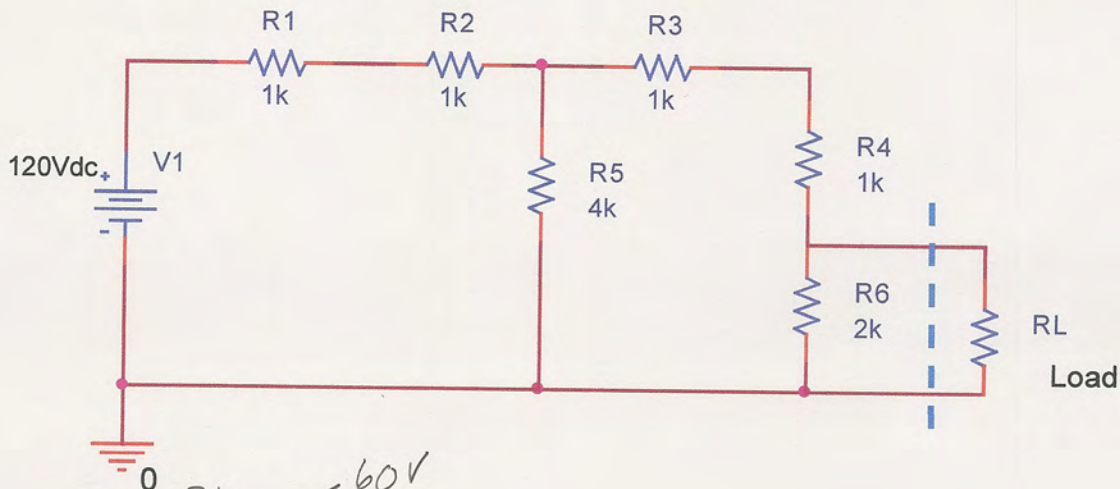Circuit 1: (This is the simplest of the three problems.) {10 pts}



$\Rightarrow V_{TH} = 30V$

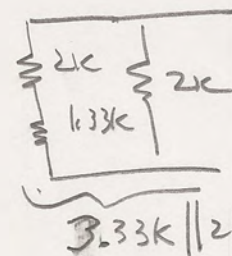
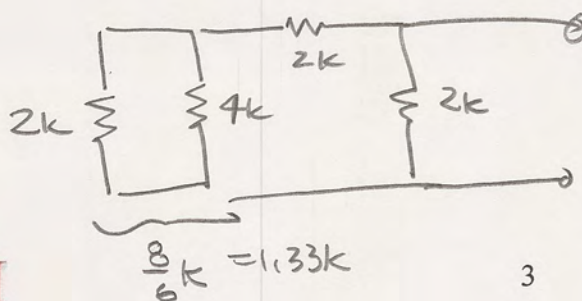


$3.33k \parallel 2k = \frac{6.66k}{5.33} = 1.25k$


EI

$R_{TH} = 1.25k$

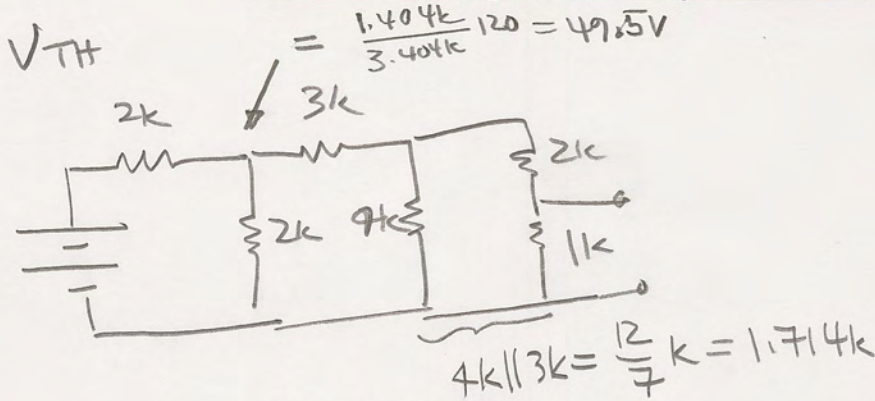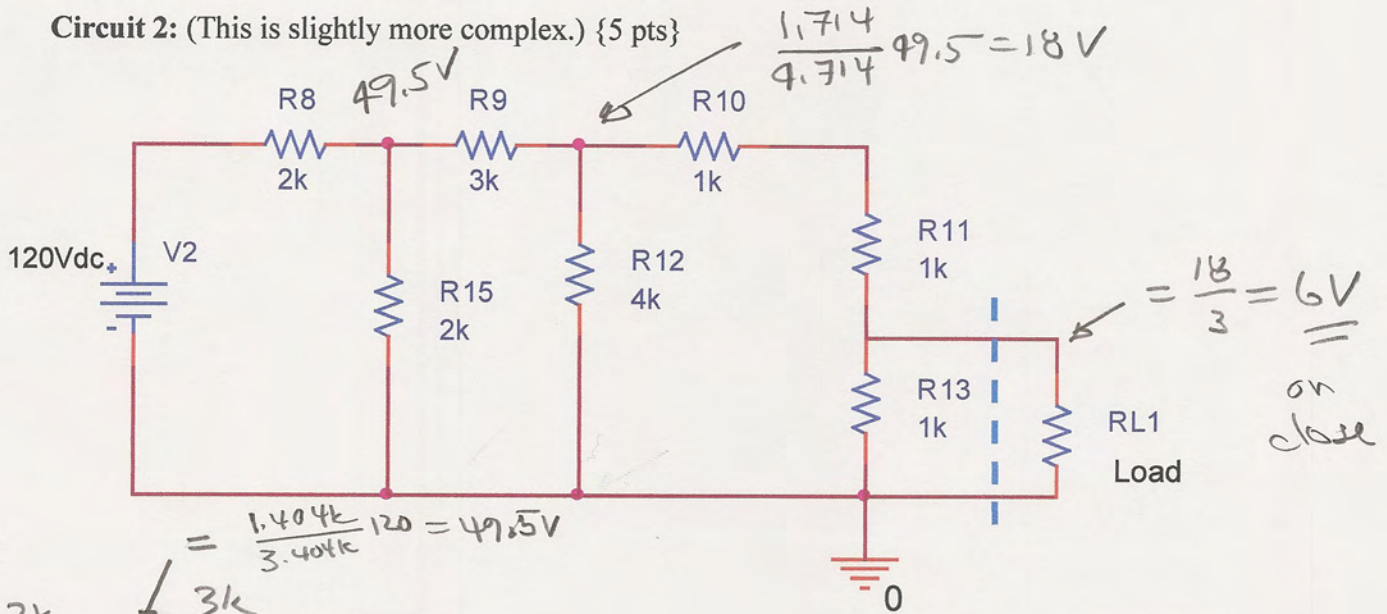Circuit 2: (This is slightly more complex.) {5 pts}



$V_{TH} = 6V$

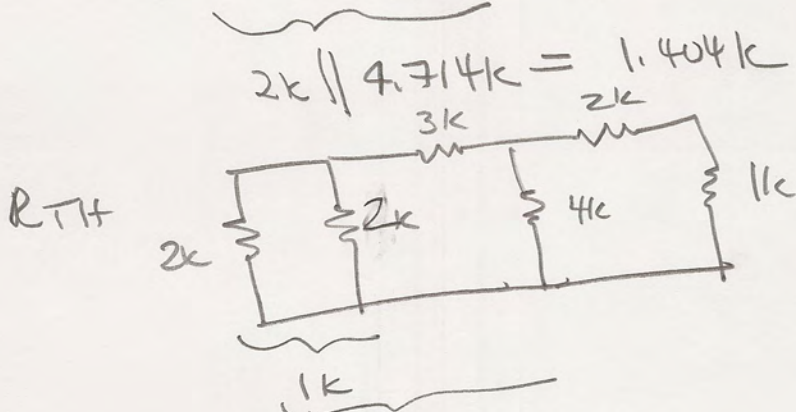


$R_{TH} = 800$

$$4k \parallel 4k = 2k$$

$$4k \parallel 1k = \frac{4}{5}k = 800\Omega$$



Circuit 3:

The 3rd circuit is significantly more complicated than the other two. Rather than analyze it from first principles, we will use the results from a PSpice simulation. In the first plot, the load resistor is very large (10MΩ) while in the second the load resistor is much smaller (1kΩ). Using the given voltages at each of the nodes for an open circuit load (RL1 is the load) and for a 1kΩ load, determine V_{th} and R_{th} . {10 pts}

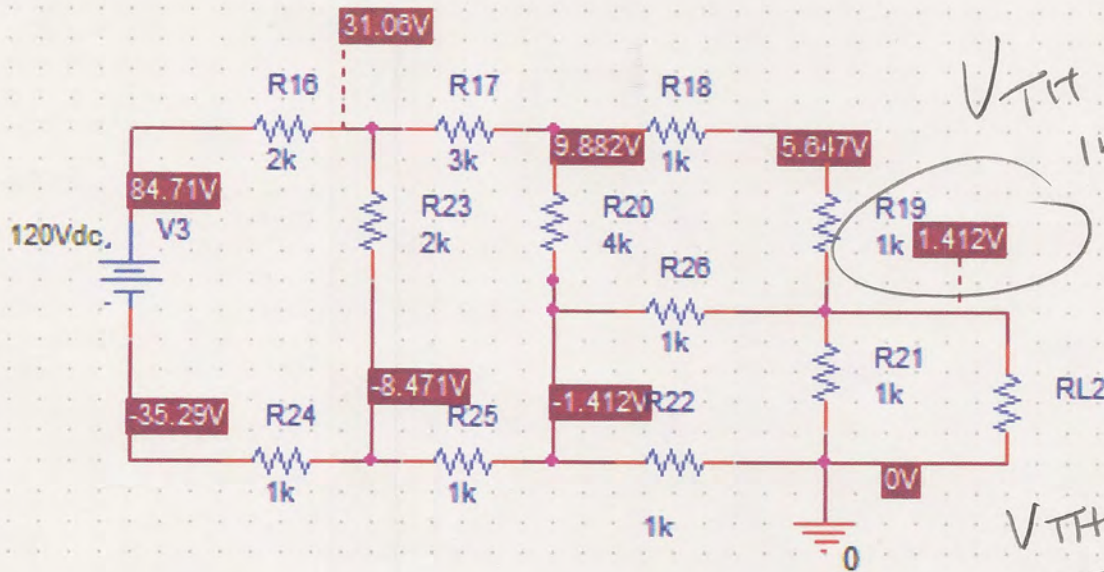

V_{TH} by inspection

$V_{TH} = 1.412V$

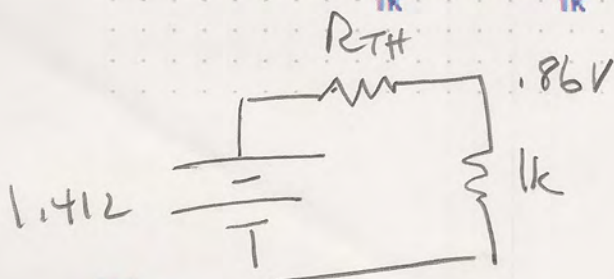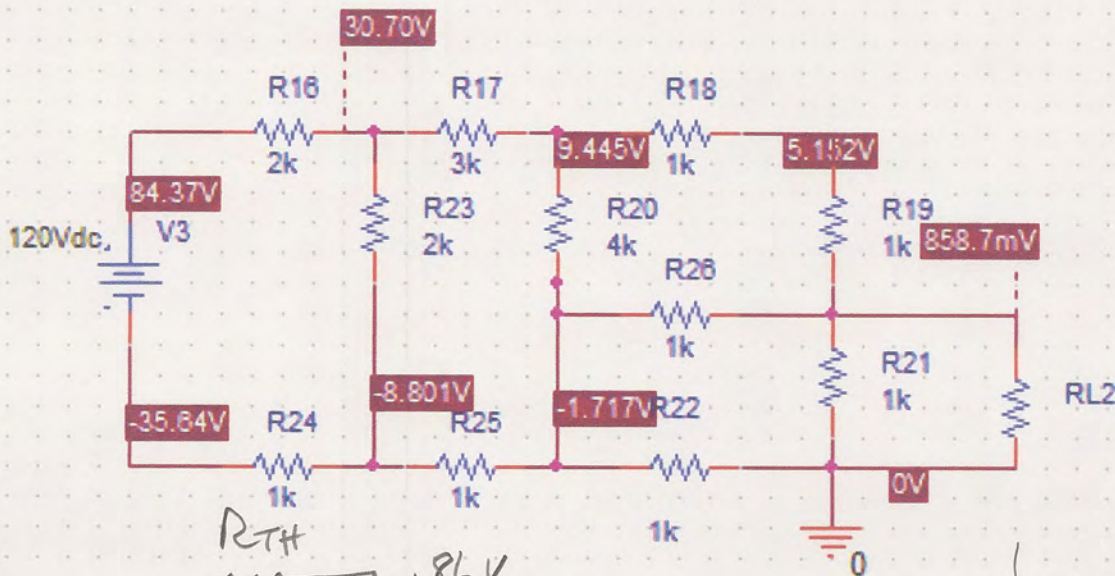


$$V_{out} = 0.86 = \frac{1.412}{1 + R_{TH}}$$

$$R_{TH} = \left(\frac{1.41}{0.86} - 1 \right) k = \underline{\underline{640 \Omega}}$$

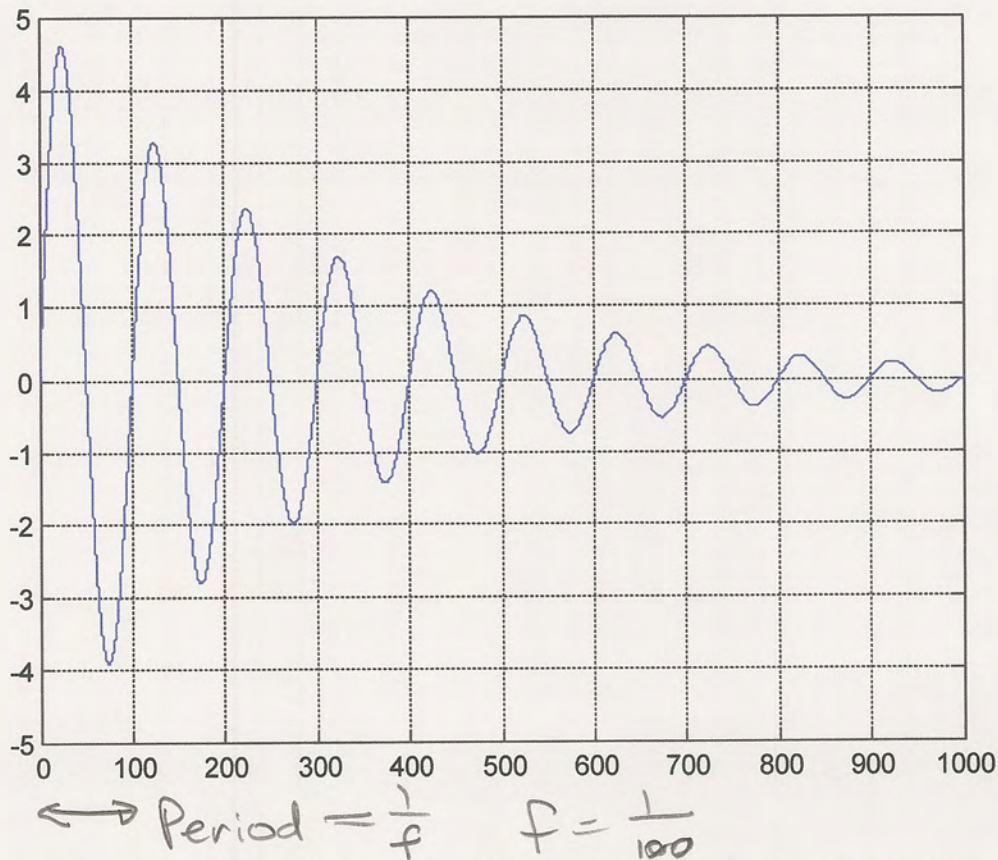II. Harmonic Oscillators

The velocity measured for an oscillating cantilever beam is shown in graphical form as:



where the horizontal scale is time (100 sec per division) and the vertical scale is velocity (1 m/s per division).

- a. Find the decay constant α and the angular frequency ω for this function. {6 pts}

$$\omega = 2\pi f = \frac{2\pi}{100} = \frac{\pi}{50} = 0.063$$

Very Small

$$5e^{-\alpha t} = 1 \text{ for } t \approx 470$$

$$-\alpha 470 = \ln(0.2) \Rightarrow \alpha = \frac{1}{300}$$

- b. Write the mathematical expression for the velocity in the form $v(t) = Ae^{-\alpha t} \sin \omega t$. Use real values for the constants and provide units where appropriate. {4 pts}

$$v = 5 e^{-t/300} \sin\left(\frac{\pi}{50} t\right)$$

- c. Find the acceleration $a(t)$ of the beam from your answer to part b. Again, use real values for the constants and provide units where appropriate. {6 pts}

$$a = 5 \left(-\frac{1}{300}\right) e^{-t/300} \sin\left(\frac{\pi}{50} t\right) + 5 e^{-t/300} \left(\frac{\pi}{50}\right) \cos\left(\frac{\pi}{50} t\right)$$

- d. Assume that you would like to build an LC oscillator circuit that operates at the same frequency and the beam above. You have a $100\mu\text{F}$ capacitor and need to make an inductor. What value of inductance is necessary to achieve this frequency? {4 pts}

$$\omega = \frac{\pi}{50} = \frac{1}{\sqrt{LC}} \quad L = \left(\frac{50}{\pi}\right)^2 \frac{1}{C}$$

$$= \left(\frac{50}{\pi}\right)^2 \frac{1}{10^{-4}}$$


$$\approx 25 \text{ MH}$$

Very unrealistic


- e. What is the primary color of the Mobile Studio board? {5 pts ... really!}

Red - But any answer is ok for 5 pts
(I am curious to see your answer)

III. Operational Amplifiers

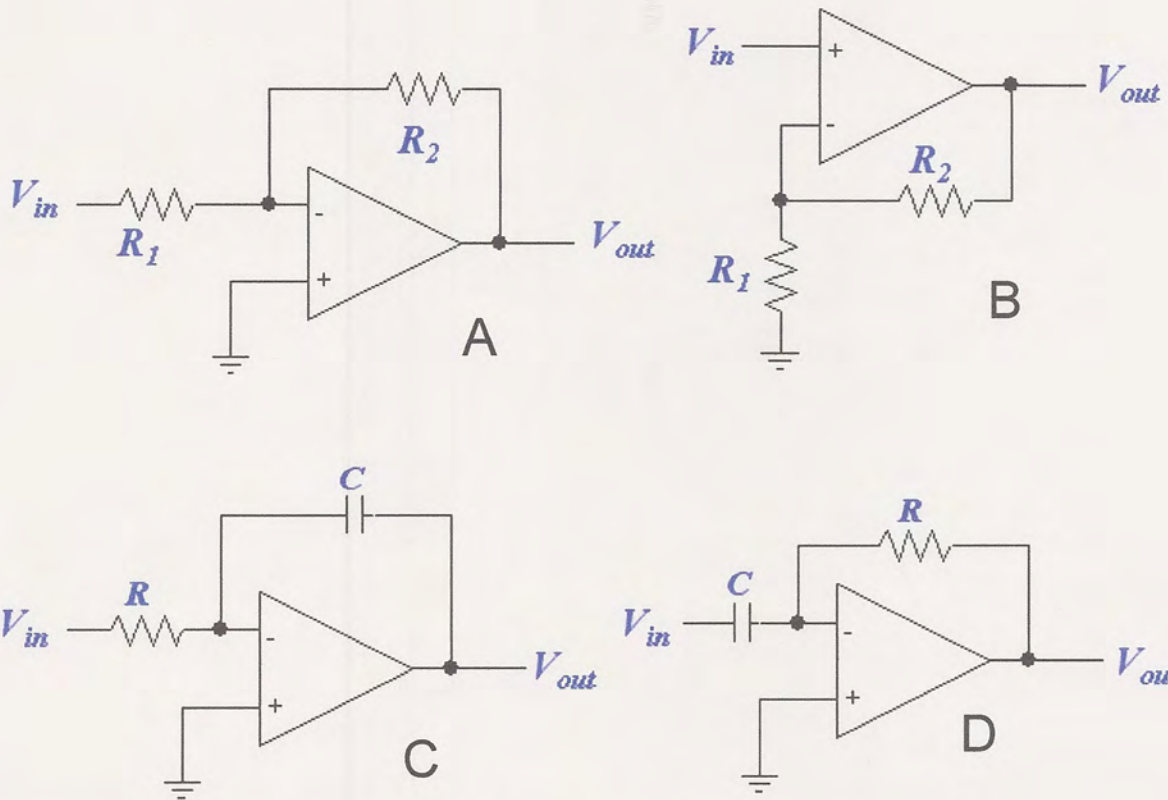

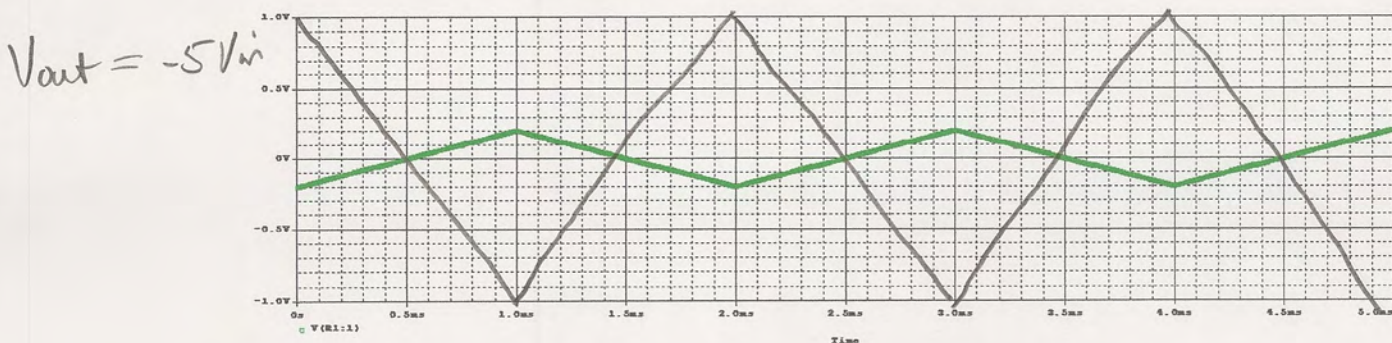
- a. {4 pts} What type of amplifier is each circuit?
 - a. A
 - b. B
 - c. C
 - d. D
- b. {4 pts} The input voltage is shown below. Solve for and sketch the output voltage for circuit A with $R_1=1k\Omega$ and $R_2=5k\Omega$.



The vertical scale is -1V to +1V and the horizontal scale is from 0 to 5ms.

- c. {4 pts} The input voltage is shown below. Solve for and sketch the output voltage for circuit B with $R_1=1k\Omega$ and $R_2=4k\Omega$.


$V_{out} = 5V_{in}$

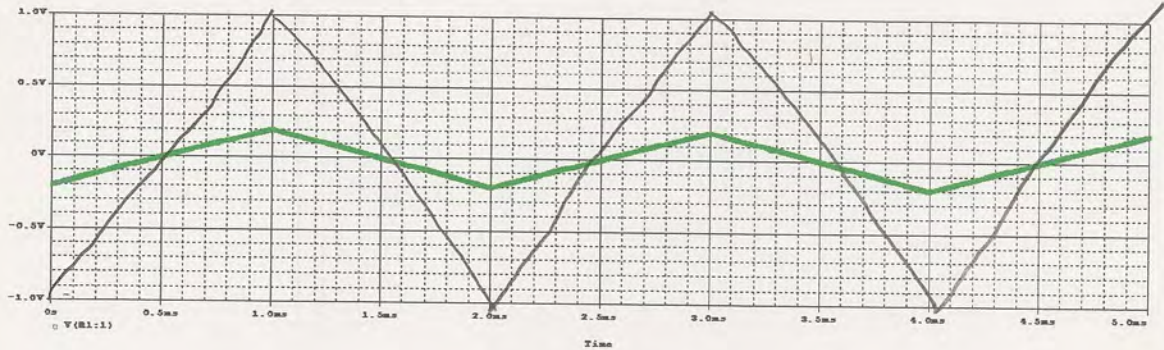

- d. {4 pts} The input voltage is shown below. Solve for and sketch the output voltage for circuit C with $R=2k\Omega$ and $C=0.047\mu F$. (Extra Credit)

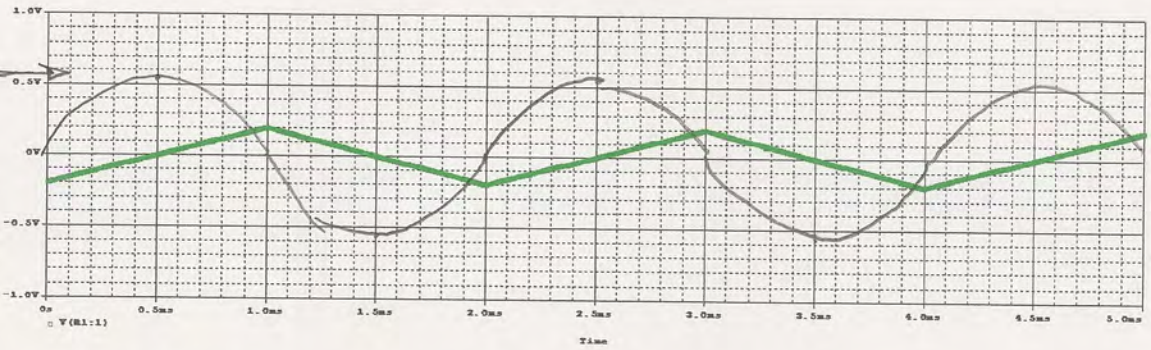0.53


$V_{out} = \frac{1}{1 + 2.25 \times 10^6 \frac{s}{s}}$



- e. {4 pts} The input voltage is shown below. Solve for and sketch the output voltage for circuit D with $C=.33\mu F$ and $R=6k\Omega$.

0.8

-0.8

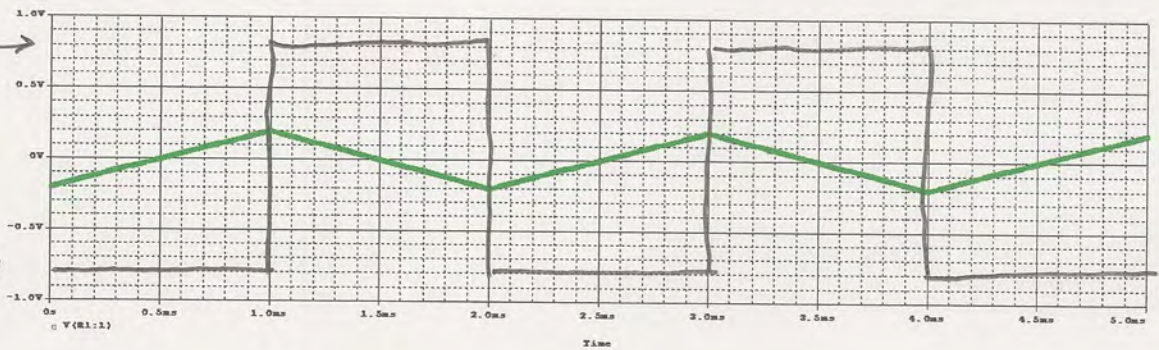

$V_{out} = \frac{1}{1 + 0.8 \frac{s}{s}}$

Space for the analysis of the circuits above:

$$A \quad V_{out} = -\frac{5k}{1k} V_{in} = -5V_{in}$$

$$B \quad V_{out} = \left(1 + \frac{4k}{1k}\right) V_{in} = 5V_{in}$$

$$C \quad V_{out} = -\frac{1}{RC} \int V_{in} dt$$

$$= -\frac{1}{(2k)(.047\mu)} \int V_{in} dt$$

$$= -(10640)(400) \int t dt$$

$$= -4.25 \times 10^6 \frac{t^2}{2}$$

$$V_{in} = \pm at$$

↑
slope


$$\frac{4V}{1ms} = 400$$

for $t = .5ms$ V_{out} changes by $530ms$


$$D \quad V_{out} = -RC \frac{dV_{in}}{dt} = (133\mu F)(6k) \frac{d(\pm 400t)}{dt}$$

$$\approx -7.8$$

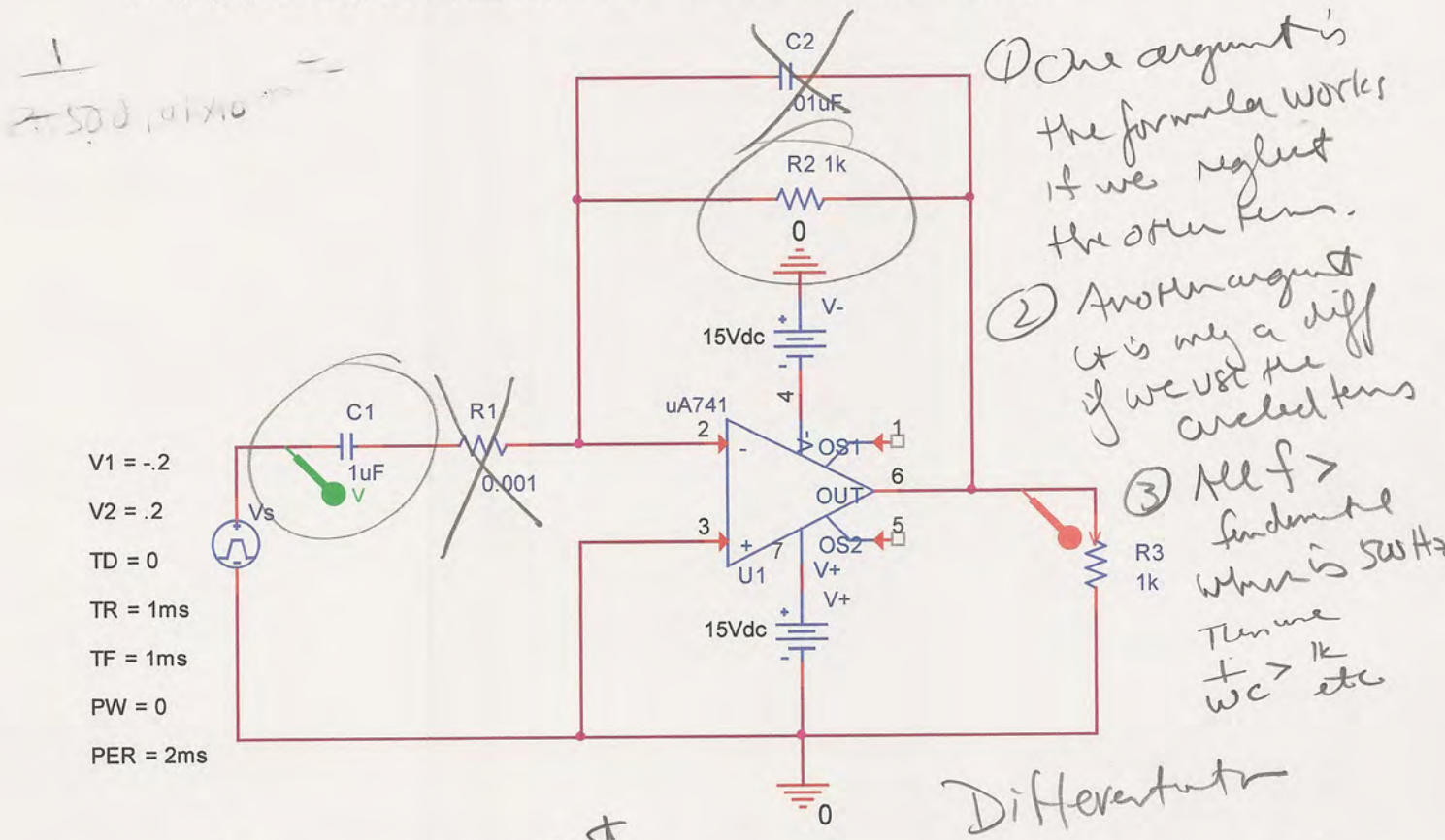f. {9 pts} The response of the circuit below has been simulated using PSpice.



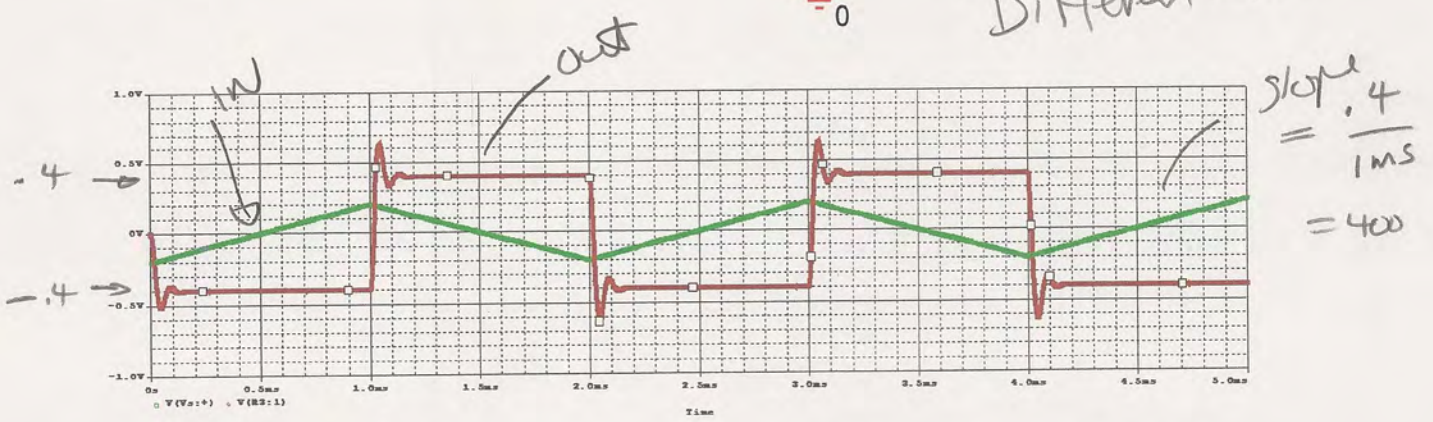V1 = -.2
 V2 = .2
 TD = 0
 TR = 1ms
 TF = 1ms
 PW = 0
 PER = 2ms



Label the input voltage and the output voltage on the plot showing the signals. {2 pts} The circuit configuration does not look exactly like any of the ideal op-amp circuits. However, it largely provides the functionality of one of the ideal circuits. From the input and output voltages, identify what kind of circuit this is {3 pts}, indicate the circuit components that you can neglect in your analysis and why, and verify mathematically that it is working at least approximately the way it should. {4 pts}


$$V_{out} = -RC \frac{dV_{in}}{dt} = -(1000)(10^{-6})(400) = -0.4$$

IV. Concepts, Troubleshooting and Data Analysis

a. {5 pts} Today's date is 3-20-2013. Because the date consists of three numbers, how would you represent each number with the resistor color code, if indeed it can be done? If it can be, give the color code. If it cannot be, cross out the number.

- a. 3 3 orange 030 = 3×10^0 \Rightarrow Black Orange Black
- b. 20 2 violet 200 = 20×10^0 \Rightarrow Red Black Blue
- c. ~~2013~~ Too many digits

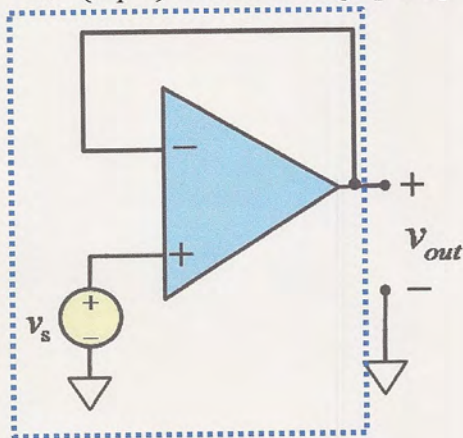
b. {5 pts} The following op-amp circuit is built. What kind of an amplifier circuit is it?



Determine the Thevenin equivalent voltage V_{TH} and the Thevenin equivalent resistance R_{TH} for this circuit including the source v_s (that is, everything inside the dashed box).

$V_{oc} = V_{out} = V_s$
 $R_{TH} = 0$ Because V_{out} does not depend on the load.

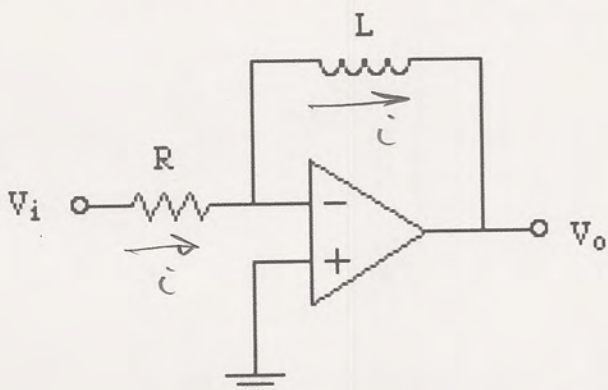c. {5 pts} An ideal op-amp circuit is configured with an inductor in the feedback loop and an input resistor, as shown below. What mathematic operation will this circuit perform? Derive the expression for V_o in terms of V_i .



$$i = \frac{V_i}{R} = V_{out} = -L \frac{di}{dt}$$

$$\Rightarrow V_{out} = -L \frac{d}{dt} \left(\frac{V_i}{R} \right)$$

$$= -\frac{L}{R} \frac{d}{dt} V_{in}$$

Differentiator

