

## ENGR-2300: Electronic Instrumentation


## Quiz 3

Spring 2016

Name Solution (Temporary)Section     Question I (20 Points)                     Question II (20 Points)                     Question III (20 Points)                     Question IV (20 Points)                     Question V (20 Points)                     Total (100 Points)                     

On all questions: **SHOW ALL WORK.** BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for answers that appear without justification. Also, if there is a small flaw in your reasoning, we will not know and not be able to give you credit for what you have correct if you do not provide information on how you solved the problem. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

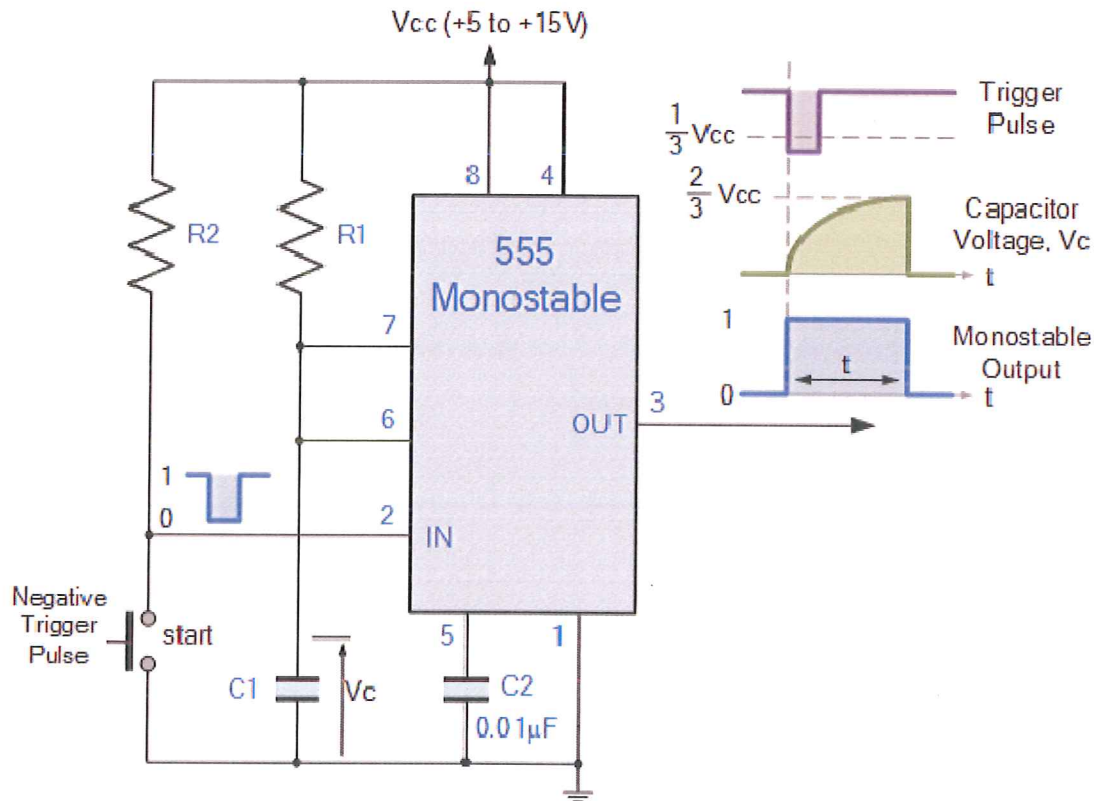
Monostable 555 Timer (From <http://www.electronics-tutorials.ws/>)



When a negative ( 0V ) pulse is applied to the trigger input (pin 2) of the Monostable configured 555 Timer oscillator, the internal comparator, (comparator No1) detects this input and “sets” the state of the flip-flop, changing the output from a “LOW” state to a “HIGH” state. This action in turn turns “OFF” the discharge transistor connected to pin 7, thereby removing the short circuit across the external timing capacitor, C1.

This action allows the timing capacitor to start to charge up through resistor R1 until the voltage across the capacitor reaches the threshold (pin 6) voltage of  $\frac{2}{3}V_{cc}$  set up by the internal voltage divider network. At this point the comparators output goes “HIGH” and “resets” the flip-flop back to its original state which in turn turns “ON” the transistor and discharges the capacitor through pin 7 to ground. This causes the output to change its state back to the original stable “LOW” value awaiting another trigger pulse to start the timing process over again. Then, the Monostable Multivibrator has only “ONE” stable state.

The **Monostable 555 Timer** circuit triggers on a negative-going pulse applied to pin 2 and this trigger pulse must be much shorter than the output pulse width allowing time for the timing capacitor to charge and then discharge fully. Once triggered, the 555 Monostable will remain in this “HIGH” unstable output state until the time period set up by the  $R_1 \times C_1$  network has elapsed. The amount of time that the output voltage remains “HIGH” or at a logic “1” level, is determined by the time it takes to charge capacitor C1 to  $\frac{2}{3}$  of  $V_{cc}$ .

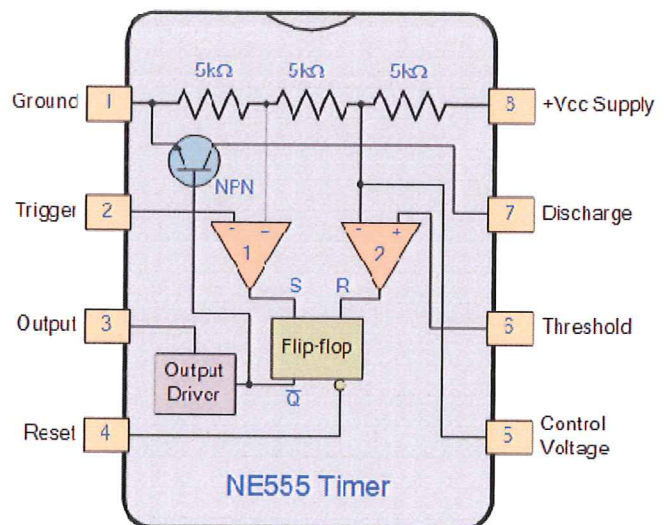


## Some Typical LED Operating Info:

|   | Wavelength (nm) | Color Name           | Fwd Voltage (Vf @ 20ma) | Intensity 5mm LEDs | Viewing Angle | LED Dye Material   |
|---|-----------------|----------------------|-------------------------|--------------------|---------------|--|
|   | 940             | Infrared             | 1.5                     | 16mW @50mA         | 15°           | GaAlAs/GaAs -- Gallium Aluminum Arsenide/Gallium Arsenide          |
|   | 880             | Infrared             | 1.7                     | 18mW @50mA         | 15°           | GaAlAs/GaAs -- Gallium Aluminum Arsenide/Gallium Arsenide          |
|   | 850             | Infrared             | 1.7                     | 26mW @50mA         | 15°           | GaAlAs/GaAs -- Gallium Aluminum Arsenide/Gallium Aluminum Arsenide |
|   | 660             | Ultra Red            | 1.8                     | 2000mcd @50mA      | 15°           | GaAlAs/GaAs -- Gallium Aluminum Arsenide/Gallium Aluminum Arsenide |
|   | 635             | High Eff. Red        | 2.0                     | 200mcd @20mA       | 15°           | GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide          |
| ★ | 633             | Super Red            | 2.2                     | 3500mcd @20mA      | 15°           | InGaAlP - Indium Gallium Aluminum Phosphide                        |
|   | 620             | Super Orange         | 2.2                     | 4500mcd @20mA      | 15°           | InGaAlP - Indium Gallium Aluminum Phosphide                        |
|   | 612             | Super Orange         | 2.2                     | 6500mcd @20mA      | 15°           | InGaAlP - Indium Gallium Aluminum Phosphide                        |
|   | 605             | Orange               | 2.1                     | 160mcd @20mA       | 15°           | GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide          |
|   | 595             | Super Yellow         | 2.2                     | 5500mcd @20mA      | 15°           | InGaAlP - Indium Gallium Aluminum Phosphide                        |
| ★ | 592             | Super Pure Yellow    | 2.1                     | 7000mcd @20mA      | 15°           | InGaAlP - Indium Gallium Aluminum Phosphide                        |
|   | 585             | Yellow               | 2.1                     | 100mcd @20mA       | 15°           | GaAsP/GaP - Gallium Arsenic Phosphide / Gallium Phosphide          |
|   | 4500K           | "Incandescent" White | 3.6                     | 2000mcd @20mA      | 20°           | SiC/GaN -- Silicon Carbide/Gallium Nitride                         |



|   |       |                       |     |                 |     |  |
|---|-------|-----------------------|-----|-----------------|-----|--|
|   | 6500K | Pale White            | 3.6 | 4000mcd @20mA   | 20° | SiC/GaN -- Silicon Carbide/Gallium Nitride     |
| ★ | 8000K | Cool White            | 3.6 | 6000mcd @20mA   | 20° | SiC/GaN - Silicon Carbide / Gallium Nitride    |
|   | 574   | Super Lime Yellow     | 2.4 | 1000mcd @20mA   | 15° | InGaAlP - Indium Gallium Aluminum Phosphide    |
|   | 570   | Super Lime Green      | 2.0 | 1000mcd @20mA   | 15° | InGaAlP - Indium Gallium Aluminum Phosphide    |
|   | 565   | High Efficiency Green | 2.1 | 200mcd @20mA    | 15° | GaP/GaP - Gallium Phosphide/Gallium Phosphide  |
|   | 560   | Super Pure Green      | 2.1 | 350mcd @20mA    | 15° | InGaAlP - Indium Gallium Aluminum Phosphide    |
|   | 555   | Pure Green            | 2.1 | 80mcd @20mA     | 15° | GaP/GaP - Gallium Phosphide/ Gallium Phosphide |
| ★ | 525   | Aqua Green            | 3.5 | 10,000mcd @20mA | 15° | SiC/GaN - Silicon Carbide / Gallium Nitride    |
|   | 505   | Blue Green            | 3.5 | 2000mcd @20mA   | 45° | SiC/GaN - Silicon Carbide / Gallium Nitride    |
|   | 470   | Super Blue            | 3.6 | 3000mcd @20mA   | 15° | SiC/GaN - Silicon Carbide / Gallium Nitride    |
|   | 430   | Ultra Blue            | 3.8 | 100mcd @20mA    | 15° | SiC/GaN - Silicon Carbide / Gallium Nitride    |

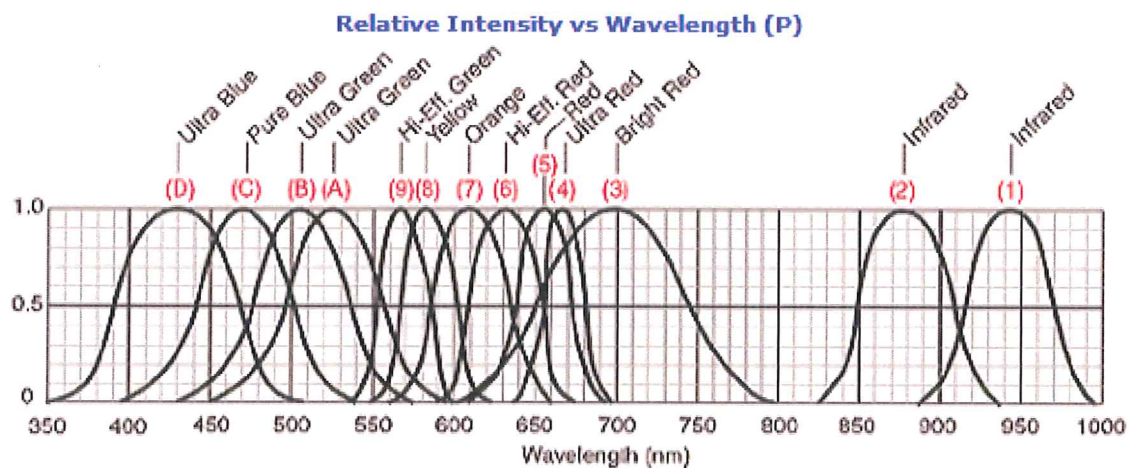

From Wikipedia: A **Zener diode** is a diode which allows current to flow in the forward direction in the same manner as an ideal diode, but also permits it to flow in the reverse direction when the voltage is above a certain value known as the breakdown voltage, "zener knee voltage", "zener voltage", "avalanche point", or "peak inverse voltage".

| Type Number | Nominal Zener Voltage $V_Z$ @ $I_{ZT}^{(1)}$ (Volts) | Test Current $I_{ZT}$ (mA) | Maximum Zener Impedance $Z_{ZT}$ @ $I_{ZT}^{(1)}$ ( $\Omega$ ) | Maximum Regulator Current $I_{ZM}^{(2)}$ (mA) | Maximum Reverse Leakage Current   |  |
|-------------|--|----------------------------|--|---|---|--|
|             |  |                            |  |   | $T_A = 25^\circ\text{C}$<br>$I_R$ @ $V_R = 1\text{V}$ ( $\mu\text{A}$ ) | $T_A = 150^\circ\text{C}$<br>$I_R$ @ $V_R = 1\text{V}$ ( $\mu\text{A}$ ) |
| 1N746A      | 3.3  | 20                         | 28   | 110   | 10  | 30   |
| 1N747A      | 3.6  | 20                         | 24   | 100   | 10  | 30   |
| 1N748A      | 3.9  | 20                         | 23   | 95  | 10  | 30   |
| 1N749A      | 4.3  | 20                         | 22   | 85  | 2   | 30   |
| 1N750A      | 4.7  | 20                         | 19   | 75  | 2   | 30   |
| 1N751A      | 5.1  | 20                         | 17   | 70  | 1   | 20   |
| 1N752A      | 5.6  | 20                         | 11   | 65  | 1   | 20   |
| 1N753A      | 6.2  | 20                         | 7  | 60  | 0.1   | 20   |
| 1N754A      | 6.8  | 20                         | 5  | 55  | 0.1   | 20   |
| 1N755A      | 7.5  | 20                         | 6  | 50  | 0.1   | 20   |
| 1N756A      | 8.2  | 20                         | 8  | 45  | 0.1   | 20   |
| 1N757A      | 9.1  | 20                         | 10   | 40  | 0.1   | 20   |
| 1N758A      | 10   | 20                         | 17   | 35  | 0.1   | 20   |
| 1N759A      | 12   | 20                         | 30   | 30  | 0.1   | 20   |

| Standard Resistor Values ( $\pm 5\%$ ) |    |     |      |     |      |      |
|--|----|-----|------|-----|------|------|
| 1.0                                    | 10 | 100 | 1.0K | 10K | 100K | 1.0M |
| 1.1                                    | 11 | 110 | 1.1K | 11K | 110K | 1.1M |
| 1.2                                    | 12 | 120 | 1.2K | 12K | 120K | 1.2M |
| 1.3                                    | 13 | 130 | 1.3K | 13K | 130K | 1.3M |
| 1.5                                    | 15 | 150 | 1.5K | 15K | 150K | 1.5M |
| 1.6                                    | 16 | 160 | 1.6K | 16K | 160K | 1.6M |
| 1.8                                    | 18 | 180 | 1.8K | 18K | 180K | 1.8M |
| 2.0                                    | 20 | 200 | 2.0K | 20K | 200K | 2.0M |
| 2.2                                    | 22 | 220 | 2.2K | 22K | 220K | 2.2M |
| 2.4                                    | 24 | 240 | 2.4K | 24K | 240K | 2.4M |
| 2.7                                    | 27 | 270 | 2.7K | 27K | 270K | 2.7M |
| 3.0                                    | 30 | 300 | 3.0K | 30K | 300K | 3.0M |
| 3.3                                    | 33 | 330 | 3.3K | 33K | 330K | 3.3M |
| 3.6                                    | 36 | 360 | 3.6K | 36K | 360K | 3.6M |
| 3.9                                    | 39 | 390 | 3.9K | 39K | 390K | 3.9M |
| 4.3                                    | 43 | 430 | 4.3K | 43K | 430K | 4.3M |
| 4.7                                    | 47 | 470 | 4.7K | 47K | 470K | 4.7M |
| 5.1                                    | 51 | 510 | 5.1K | 51K | 510K | 5.1M |
| 5.6                                    | 56 | 560 | 5.6K | 56K | 560K | 5.6M |
| 6.2                                    | 62 | 620 | 6.2K | 62K | 620K | 6.2M |
| 6.8                                    | 68 | 680 | 6.8K | 68K | 680K | 6.8M |
| 7.5                                    | 75 | 750 | 7.5K | 75K | 750K | 7.5M |
| 8.2                                    | 82 | 820 | 8.2K | 82K | 820K | 8.2M |
| 9.1                                    | 91 | 910 | 9.1K | 91K | 910K | 9.1M |



## MC14584B

ELECTRICAL CHARACTERISTICS (Voltages Referenced to V<sub>SS</sub>)

| Characteristic   | Symbol                        | V <sub>DD</sub><br>Vdc | - 55°C  |       | 25°C |                    |       | 125°C |       | Unit |      |
|--|-------------------------------|------------------------|---|-------|------|--------------------|-------|-------|-------|------|------|
|  |                               |                        | Min   | Max   | Min  | Typ <sup>(2)</sup> | Max   | Min   | Max   |      |      |
| Output Voltage<br>V <sub>in</sub> = V <sub>DD</sub><br><br>V <sub>in</sub> = 0   | "0" Level                     | V <sub>OL</sub>        | 5.0   | -     | 0.05 | -                  | 0     | 0.05  | -     | 0.05 | Vdc  |
|  |                               |                        | 10  | -     | 0.05 | -                  | 0     | 0.05  | -     | 0.05 |      |
|  |                               |                        | 15  | -     | 0.05 | -                  | 0     | 0.05  | -     | 0.05 |      |
|  | "1" Level                     | V <sub>OH</sub>        | 5.0   | 4.95  | -    | 4.95               | 5.0   | -     | 4.95  | -    | Vdc  |
|  |                               |                        | 10  | 9.95  | -    | 9.95               | 10    | -     | 9.95  | -    |      |
|  |                               |                        | 15  | 14.95 | -    | 14.95              | 15    | -     | 14.95 | -    |      |
| Output Drive Current<br>(V <sub>OH</sub> = 2.5 Vdc)<br>(V <sub>OH</sub> = 4.6 Vdc)<br>(V <sub>OH</sub> = 9.5 Vdc)<br>(V <sub>OH</sub> = 13.5 Vdc)<br><br>(V <sub>OL</sub> = 0.4 Vdc)<br>(V <sub>OL</sub> = 0.5 Vdc)<br>(V <sub>OL</sub> = 1.5 Vdc) | Source                        | I <sub>OH</sub>        | 5.0   | -3.0  | -    | -2.4               | -4.2  | -     | -1.7  | -    | mAdc |
|  |                               |                        | 5.0   | -0.64 | -    | -0.51              | -0.88 | -     | -0.36 | -    |      |
|  |                               |                        | 10  | -1.6  | -    | -1.3               | -2.25 | -     | -0.9  | -    |      |
|  | Sink                          | I <sub>OL</sub>        | 5.0   | 0.64  | -    | 0.51               | 0.88  | -     | 0.36  | -    | mAdc |
|  |                               |                        | 10  | 1.6   | -    | 1.3                | 2.25  | -     | 0.9   | -    |      |
|  |                               |                        | 15  | 4.2   | -    | 3.4                | 8.8   | -     | 2.4   | -    |      |
| Input Current  | I <sub>in</sub>               | 15                     | -   | ±0.1  | -    | ±0.00001           | ±0.1  | -     | ±1.0  | μAdc |      |
| Input Capacitance<br>(V <sub>in</sub> = 0)   | C <sub>in</sub>               | -                      | -   | -     | -    | 5.0                | 7.5   | -     | -     | pF   |      |
| Quiescent Current<br>(Per Package)   | I <sub>DD</sub>               | 5.0                    | -   | 0.25  | -    | 0.0005             | 0.25  | -     | 7.5   | μAdc |      |
|  |                               | 10                     | -   | 0.5   | -    | 0.0010             | 0.5   | -     | 15    |      |      |
|  |                               | 15                     | -   | 1.0   | -    | 0.0015             | 1.0   | -     | 30    |      |      |
| Total Supply Current <sup>(3) (4)</sup><br>(Dynamic plus Quiescent,<br>Per Package)<br>(C <sub>L</sub> = 50 pF on all outputs, all<br>buffers switching)   | I <sub>T</sub>                | 5.0                    | I <sub>T</sub> = (1.8 μA/kHz) f + I <sub>DD</sub> |       |      |                    |       |       |       | μAdc |      |
|  |                               | 10                     | I <sub>T</sub> = (3.6 μA/kHz) f + I <sub>DD</sub> |       |      |                    |       |       |       |      |      |
|  |                               | 15                     | I <sub>T</sub> = (5.4 μA/kHz) f + I <sub>DD</sub> |       |      |                    |       |       |       |      |      |
| Hysteresis Voltage   | V <sub>H</sub> <sup>(5)</sup> | 5.0                    | 0.27  | 1.0   | 0.25 | 0.6                | 1.0   | 0.21  | 1.0   | Vdc  |      |
|  |                               | 10                     | 0.36  | 1.3   | 0.3  | 0.7                | 1.2   | 0.25  | 1.2   |      |      |
|  |                               | 15                     | 0.77  | 1.7   | 0.6  | 1.1                | 1.5   | 0.50  | 1.4   |      |      |
| Threshold Voltage<br>Positive-Going<br><br>Negative-Going  | V <sub>T+</sub>               | 5.0                    | 1.9   | 3.5   | 1.8  | 2.7                | 3.4   | 1.7   | 3.4   | Vdc  |      |
|  |                               | 10                     | 3.4   | 7.0   | 3.3  | 5.3                | 6.9   | 3.2   | 6.9   |      |      |
|  |                               | 15                     | 5.2   | 10.6  | 5.2  | 8.0                | 10.5  | 5.2   | 10.5  |      |      |
|  | V <sub>T-</sub>               | 5.0                    | 1.6   | 3.3   | 1.6  | 2.1                | 3.2   | 1.5   | 3.2   | Vdc  |      |
|  |                               | 10                     | 3.0   | 6.7   | 3.0  | 4.6                | 6.7   | 3.0   | 6.7   |      |      |
|  |                               | 15                     | 4.5   | 9.7   | 4.6  | 6.9                | 9.8   | 4.7   | 9.9   |      |      |

**Question 1 (20 Points) A Little Thevenin, Voltage Divider, System Design, etc.**


- a. (6 Pts) This problem helps to define the context for other questions. Identify at least 4 devices and functions located in the same cell in each table by circling the cells and numbering them from 2 to 5. An example is shown for the NOT GATE in column 2, row 6 as is its function 'Change True to False or False to True' and it is numbered 1.

| DEVICE             |                         |                     |
|--------------------|-------------------------|---------------------|
| VOLTAGE DIVIDER    | HIGH-PASS FILTER        | INVERTING AMPLIFIER |
| DC VOLTAGE SOURCE  | NON-INVERTING AMPLIFIER | CAPACITOR           |
| FUNCTION GENERATOR | BAND-PASS FILTER        | INDUCTOR            |
| RESISTOR           | OP-AMP                  | OR GATE             |
| PHOTOTRANSISTOR    | FULL-WAVE RECTIFIER     | 555 TIMER           |
| BAND REJECT FILTER | NOT GATE                | AND GATE            |
| NAND GATE          | TRANSFORMER             | NOR GATE            |
| TRANSFORMER        | OSCILLOSCOPE            | LOW-PASS FILTER     |
| DIODE              | TRANSISTOR SWITCH       | HALF WAVE RECTIFIER |
| PHOTODIODE         | LED                     | PHOTOCELL           |

| Function   |   |  |
|--|---|--|
| Make Voltage Smaller   | Convert AC Voltages to DC Voltages                                    | Match Impedance  |
| Block Current in One Direction Only  | Store Energy  | Block DC with a Single Component                                 |
| Output an Electrical Signal  | ON-OFF Switch   | Store Energy   |
| Increase Voltage, Power and Current while reversing Polarities                                     | Deciding a Process is True if Any Monitored Conditions are False      | Block a Small Range of Frequencies but Pass Others               |
| Increase Voltage without an External Power Supply  | Convert Light Energy into Electrical Energy                           | Block High Frequencies with a Single Components                  |
| Deciding a Process is True Only if All Monitored Conditions are True                               | Change True to False or False to True                                 | Deciding a Process is True if Any Monitored Conditions are False |
| Pass a Small Range of Frequencies but Block Others   | Increase Voltage, Power and Current while keeping Polarities the Same | Deciding a Process is True if Any Monitored Conditions are True  |
| Increase Current Without an External Power Supply  | Measure Voltage vs Time   | Convert Electrical Energy into Heat                              |
| Produce an Output Voltage at least Thousands of Time Larger than the Difference between Two Inputs | Produce a Sequence of Square Voltage Pulses                           | Make the Output Voltage Larger than the Input Voltage            |
| Produce a Single Square Pulse  | Convert Electrical Energy into Light                                  | Convert Light Energy into Electrical Energy                      |

The following configuration behaves like parts of circuits encountered in Experiments 6 and 7.

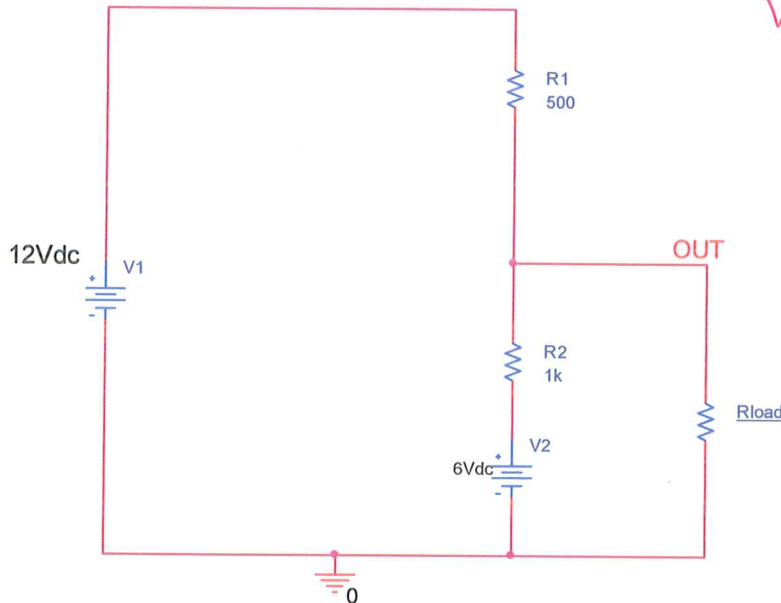- b. (6 Pts) Consider the very basic circuit – the voltage divider – in one of its slightly more complicated forms. Determine the Thevenin Voltage  $V_{TH}$  and Resistance  $R_{TH}$  for this configuration.



$$V_{out} = 6 + \frac{1}{1.5} (12 - 6)$$

$$= 6 + \frac{2}{3} 6 = 10 \text{ V}$$



$$= V_{TH}$$

$$R_{TH} = 500 \parallel 1k$$

$$= \frac{(500)(1000)}{1500}$$

$$= \frac{1000}{3} = 333 \Omega$$

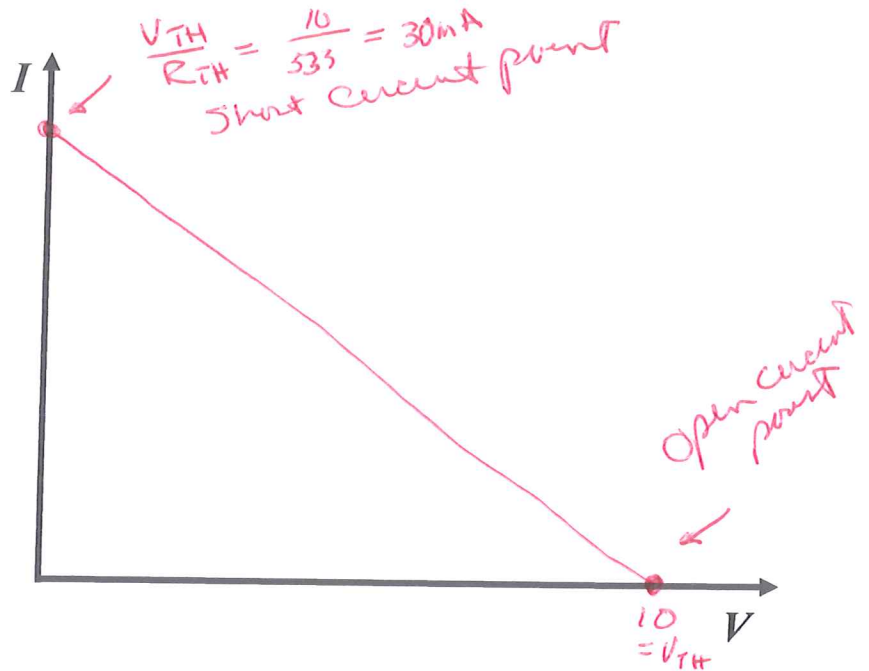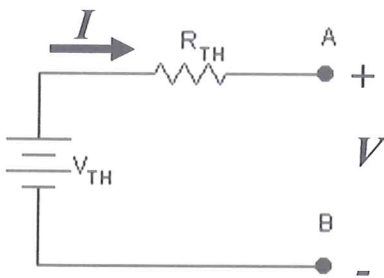
- c. (4 Pts) Plot  $I$  vs  $V$  voltage for the Thevenin equivalent source determined in part b. Pay close attention to the polarities indicated in the figure, and fully label your plot. *Hint: Plot a representative set of points for loads from a short circuit to an open circuit and then connect the dots.*






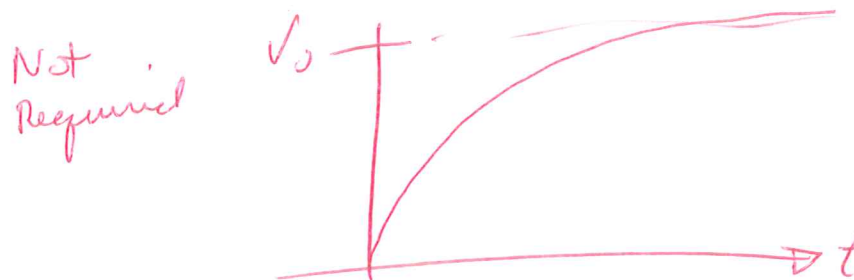- d. (4 Pts) A capacitor  $C$  is charged to a voltage  $V_0$  through a resistor  $R$ . Assuming the capacitor is originally uncharged, write the mathematical expression for the capacitor voltage as a function of time.  $V_C(t) = ?$  Hint: It involves an exponential function of time and a time constant and, when plotted, looks like the Capacitor Voltage plot for the Monostable circuit shown on page 2.

$$V_C(t) = V_0 (1 - e^{-t/\tau})$$
$$\tau = RC$$



Question 2 (20 Points) 555 Timer

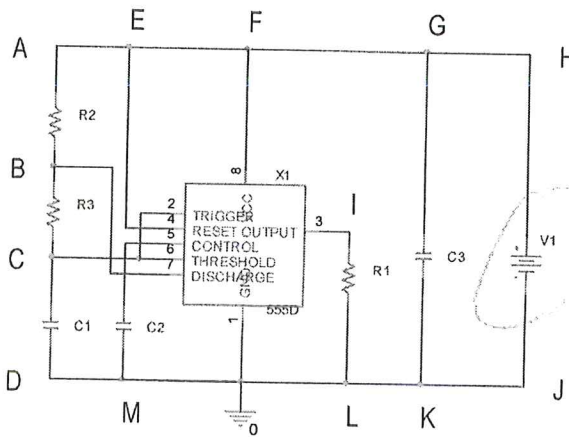

A 555 timer, astable multivibrator is built with:

- R1 = 1kΩ
- R2 = 5kΩ → R1 on C1/b
- R3 = 2kΩ → R2 on C1/b
- V1 = 15V
- C3 = 50uF
- C2 = 0.1uF
- C1 to be determined → C1 on C1/b


a. (6pt) The measured frequency of the astable multivibrator is 320Hz. Determine the value of C1, determine the Duty Cycle and determine the period:

$$f = \frac{1.44}{(R2 + 2R3)C1} \quad C1 = \frac{1.44}{(5k + 2 \cdot 2k) \cdot 320} = 0.5 \mu F \quad C1 = 0.5 \mu F$$


$$D = \frac{T1}{T} = \frac{0.693(R2 + R3)C1}{0.693(R2 + 2R3)C1} = \frac{7k}{9k} = 78\% \quad \text{Duty Cycle} = 78\%$$

$$\text{Period} = \frac{1}{f} = \frac{1}{320} = 3.125 \mu s$$

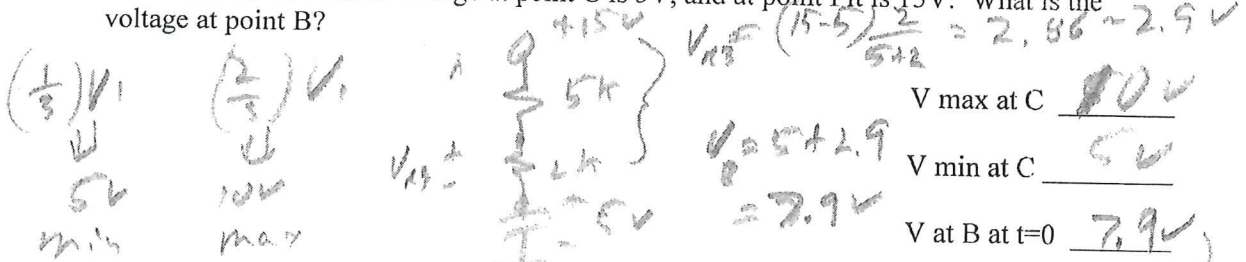b. (2pt) What are the minimum and maximum values for the voltage at point C? At t=0 it is found that the measured voltage at point C is 5V, and at point I it is 15V. What is the voltage at point B?



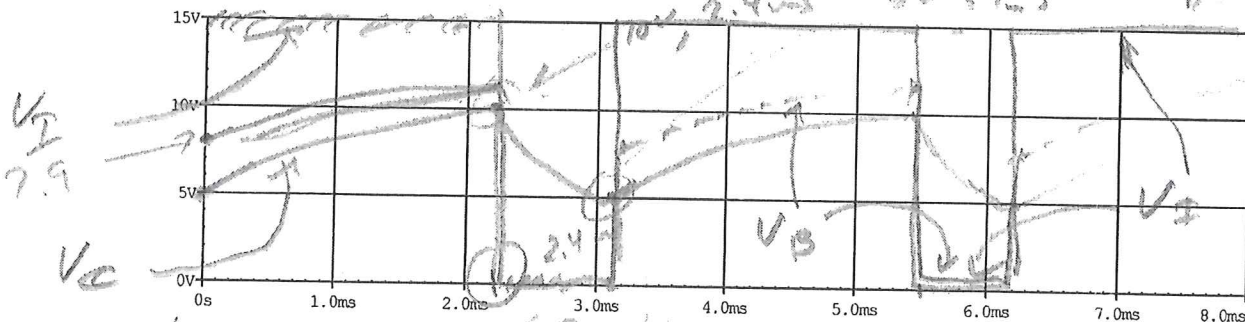c. (6pts) On the plot below, sketch and label the voltages at points C, B and I. Start with V at point C=5V at t=0. Label important voltages and times.



$$t_{on} = T1 = 0.693(5k + 2k)0.5 \mu F = 2.4 \mu s$$

EI

Soln

Question 2 continued:

- d. (4pts) It is desired to keep the frequency of the circuit in part a. the same (320Hz) but now a 60% duty cycle is needed. Leave the value of C1 the same and determine new values of R2 and R3 that meet these requirements.

$$D = \frac{T_1}{T} = \frac{0.693(R_2 + R_3)C_1}{0.693(R_2 + 2R_3)C_1} = \frac{R_2 + R_3}{R_2 + 2R_3} = 0.6$$

$$R_2 + R_3 = (0.6)(R_2 + 2R_3)$$

$$(2) = 5.4k$$

$$T = 0.693(R_2 + 2R_3)C_1 = \text{constant}$$

$$R_2 + 2R_3 = 9k \quad (1)$$

$$(1) - (2) \Rightarrow R_3 = (9 - 5.4)k$$

$$R_3 = 3.6k\Omega$$

$$R_2 + R_3 = 5.4k \quad | \quad R_2 = 1.8k$$

- e. (2pts) Your partner wants to build an astable multivibrator that runs at 320Hz and has an output duty cycle of 40%. Can the circuit in this problem do this by only changing resistor and/or capacitor values?

If you answer yes, give the new values:

If you answer no, state what component that you used in the labs that could be added to the circuit to achieve the requirements. (You don't need to draw the circuit.)

No, Duty Cycle always  $> 50\%$

→ component → any one of


- transistor
- Inverter
- relay



**Question 3 (20 Points) Combinational & Sequential Logic Circuits**

*Soln.*

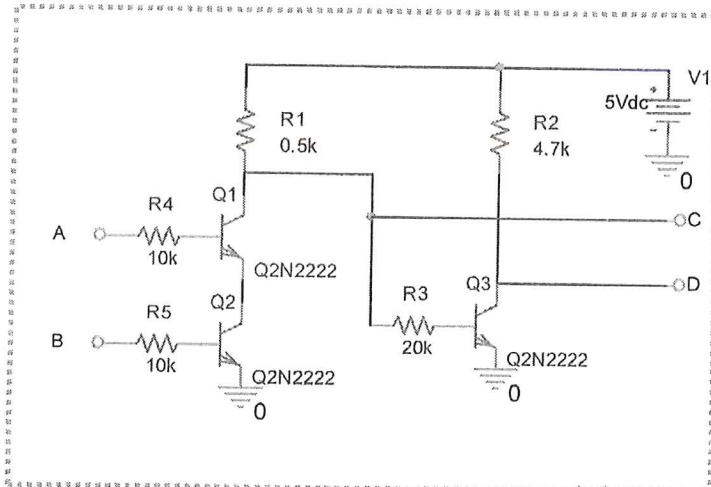- a. The circuit below shows how a simple logic gate can be built out of transistors and resistors. The circuit is inside the dashed box and has two inputs and two outputs. Voltages above 2.5V are logic high and voltages below 2.5V are logic low. A and B are inputs. C and D are outputs.



- i. Complete the table below using logic levels of 0 and 1, not the actual voltages. Suggestion: Do C first then complete column D. (6pts)

*Need both Q1 & Q2 on to pull down voltage*

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

*Inversion of C*

- ii. What type of logic gate does output C represent? What type of logic gate does output D represent? (2pts)

*C ⇒ NAND  
D ⇒ AND*


- b. A 4-bit counter had an initial state shown in the table below and then received a string of 5 clock pulses. What are QA, QB, QC and QD after 5 additional clock pulses? Clearly indicate the state of each signal. (2pts)

|                      | QD | QC | QB | QA |
|----------------------|----|----|----|----|
| Start state          | 0  | 1  | 0  | 0  |
| State after 5 counts | 1  | 0  | 0  | 1  |

*OR 0100 + 0101 = 1001*


*0100  
0101  
0110  
0111  
1000  
1001*

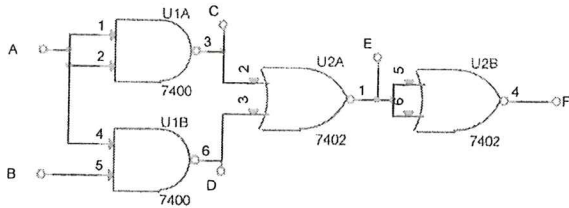- c. The following circuit is configured using **NAND and NOR gates**. A and B are inputs, C, D, E and F are outputs. **Fill in columns C and F** in the truth table for this circuit. Columns D, E, and are for your convenience. (4 Pts)




| A | B | C | D | E | Output F |
|---|---|---|---|---|----------|
| 0 | 0 | 1 | 1 | 0 | 1        |
| 0 | 1 | 1 | 1 | 0 | 1        |
| 1 | 0 | 0 | 1 | 0 | 1        |
| 1 | 1 | 0 | 0 | 1 | 0        |

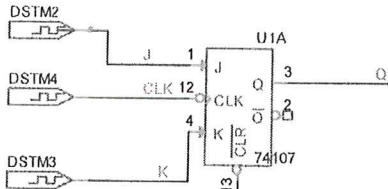- d. For this problem, plot the output Q for the timeline shown. The J-K flip-flop function table is listed on the crib sheet but a slightly different version is also shown here. This one emphasizes that the output transitions occur when the clock pulse transitions from high to low. Both the crib sheet table and this one are valid. (6pts)



74107A  
FUNCTION TABLE


| INPUTS |     |   |   | OUTPUTS        |             |
|--------|-----|---|---|----------------|-------------|
| CLR    | CLK | J | K | Q              | $\bar{Q}$   |
| L      | X   | X | X | L              | H           |
| H      | L   | L | L | Q <sub>0</sub> | $\bar{Q}_0$ |
| H      | L   | H | L | H              | L           |
| H      | L   | L | H | L              | H           |
| H      | L   | H | H | TOGGLE         | TOGGLE      |
| H      | H   | X | X | Q <sub>0</sub> | $\bar{Q}_0$ |

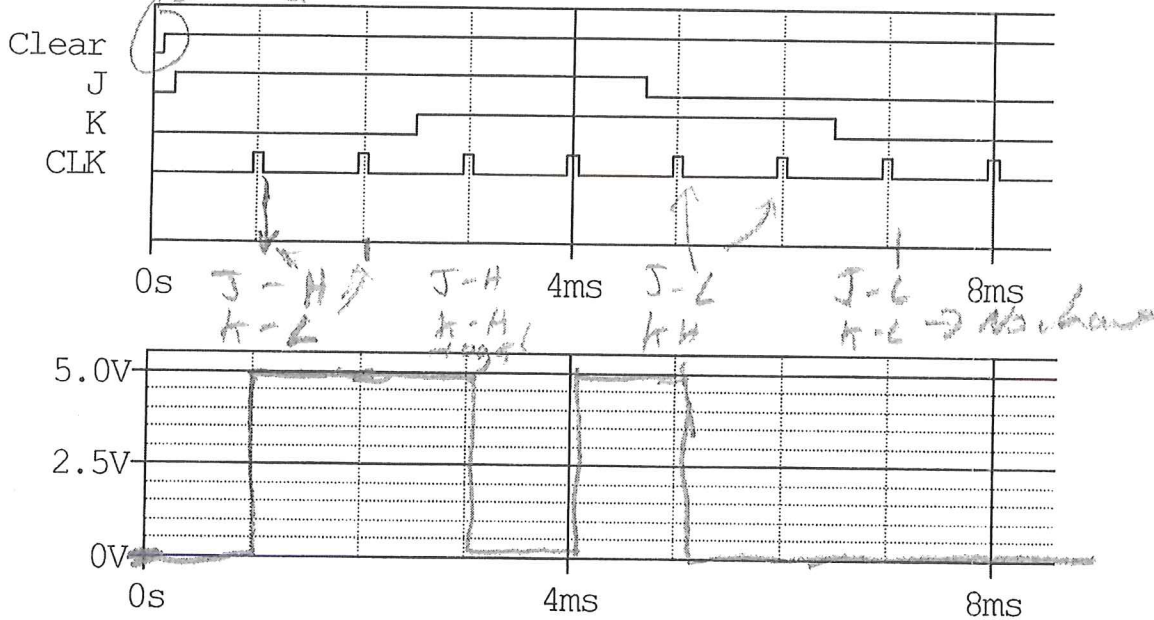


Plot Q, use 0V for logic low and 5V for logic high.

Parts of solution for Q3

555 timer problem:

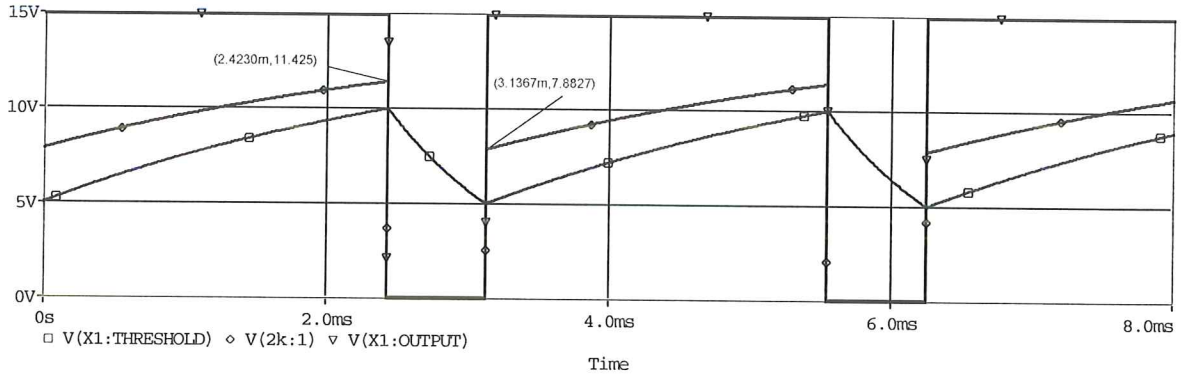


V

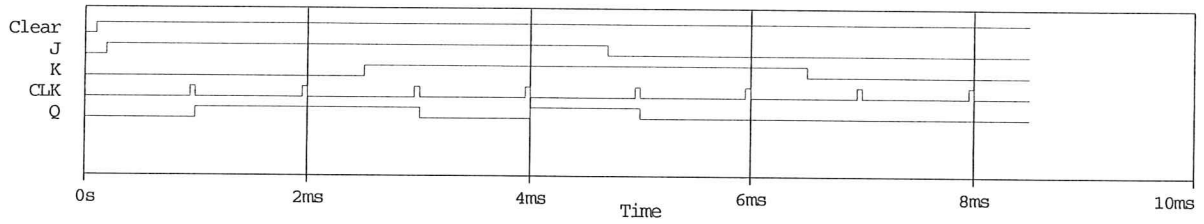



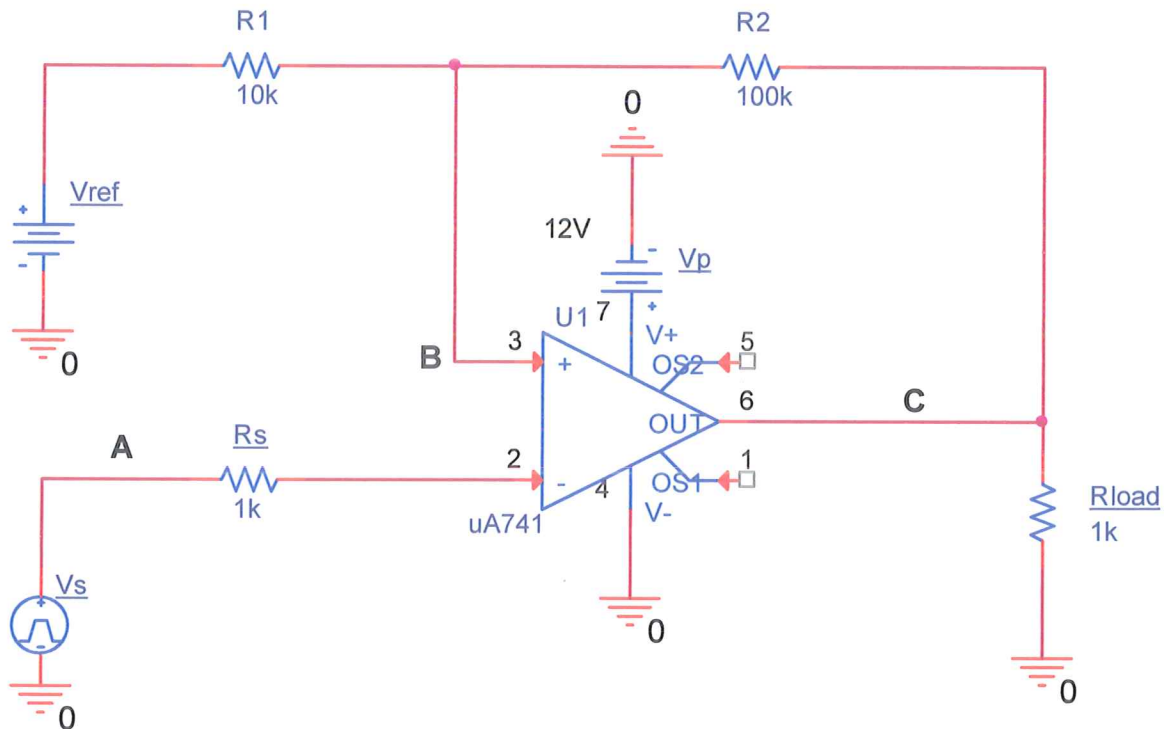**Question 4 (20 Points) Schmitt Trigger**

In this problem, we investigate a Schmitt Trigger made from a 741 op-amp. Note that the op-amp has only a single DC power supply of  $V^+ = 12V$ . The negative power supply connection  $V^-$  is connected to ground. The reference voltage  $V_{ref}$  is unspecified. Make any reasonable assumptions when answering the questions below.



- a. What are the two possible output voltages at point C in this circuit? So we can refer to them without confusion, call the two values  $V_C^{HI}$  and  $V_C^{LO}$ , for the higher (maximum) and lower (minimum) values, respectively. (2 Pts)

$$V_C^{HI} = 12V \quad \text{from power supply connections}$$

$$V_C^{LO} = 0V$$

- b. The voltage at point B is a function of both the output voltage at point C and  $V_{ref}$ . Determine the value of  $V_{ref}$  for which the voltage at B will be 5V when the output voltage is at its lower value  $V_C^{LO}$ . (3 Pts)



$$5 = \frac{R_1}{R_1 + R_2} (0 - V_{ref}) + V_{ref}$$

$$= \left(-\frac{1}{11} + 1\right) V_{ref} \Rightarrow V_{ref} = 5.5V$$

- c. Using your answer  $V_{ref}$  from part b, determine the voltage at B when the output voltage is at its higher value  $V_C^{HI}$ . (4 Pts)


$$V_B = \frac{1}{11} (12 - 5.5) + 5.5 = 6.1 \checkmark$$

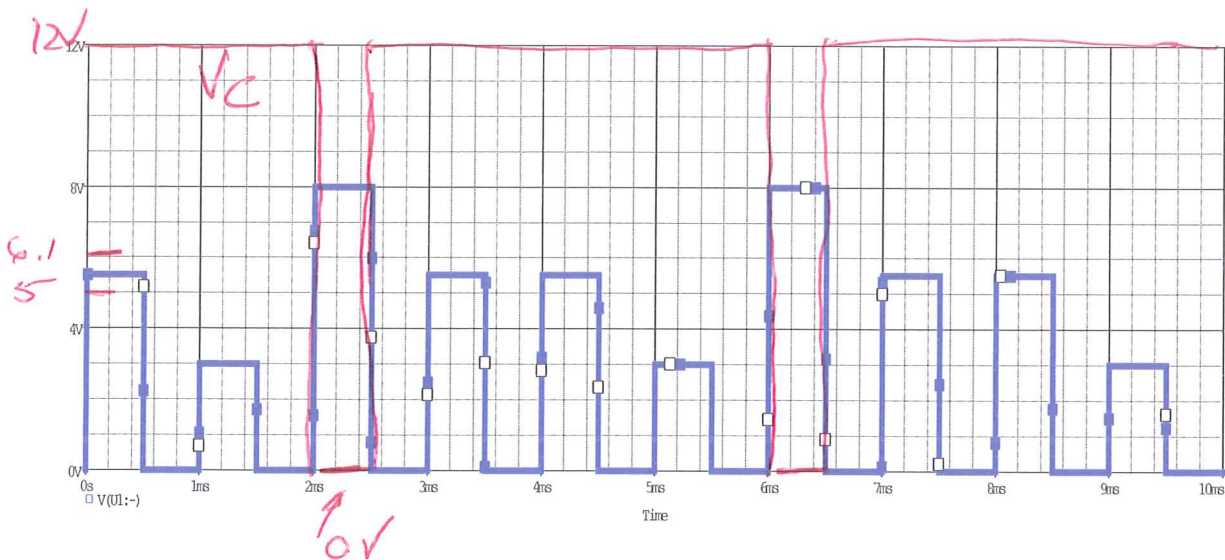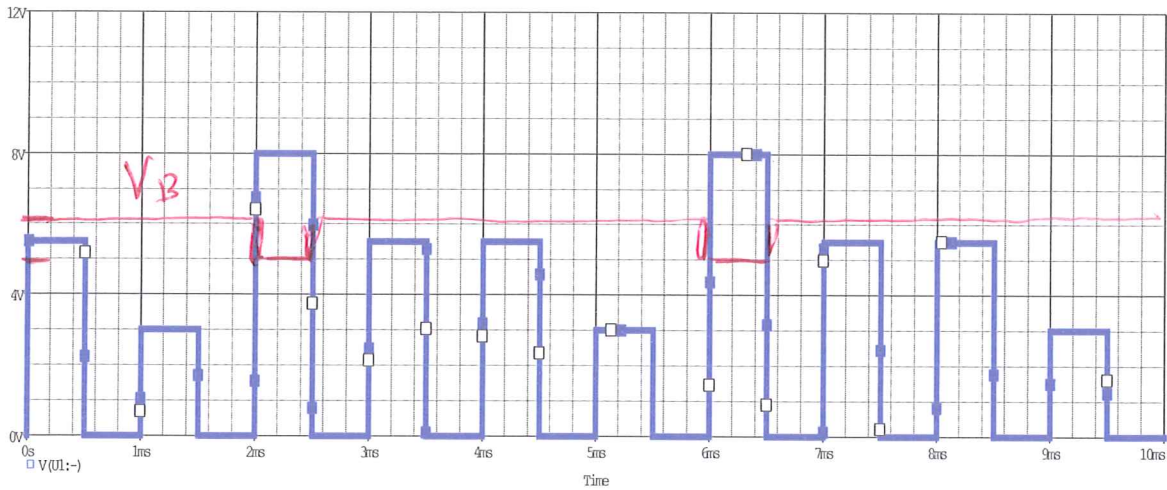- d. On the following plots, the input at point A is shown. On both plots, mark the upper and lower thresholds of the hysteresis (2 pts), and Sketch and label the voltage at point B on the first plot for the input shown. (4 pts) Sketch and label the voltage at point C on the second plot for the input shown (4 Pts) Be sure to clearly label the plots so they can be easily recognized by the grader. Indicate key values for each voltage signal. The vertical scale is 1V/div. The values 0V, 4V, and 8V are labeled. The horizontal scale goes from 0 to 10ms.




**Question 5 (20 Points) Diode Circuits**

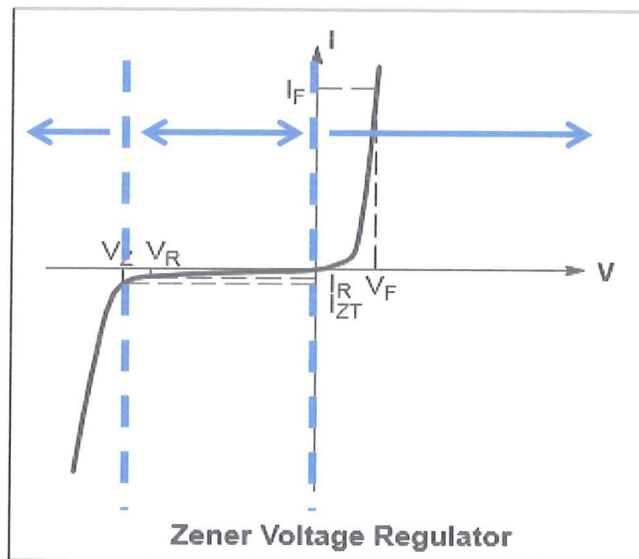- a. (3 Pts) We wish to regulate a 12V DC power supply using a Zener Diode from the table at the beginning of this quiz. Like all Zeners, this diode has three voltage ranges shown in its I-V curve below: the Breakdown Region, The Forward Bias Region and the Reverse Bias Region. Assuming ideal conditions for this diode, complete the following
- i. The voltage across the diode is  $V_D \approx 0.7V$  in the Forward Bias Region
  - ii. The voltage across the diode is  $V_D \approx 12V$  in the Breakdown Region
  - iii. The current through the diode is  $I_D \approx 0A$  in the Reverse Bias Region




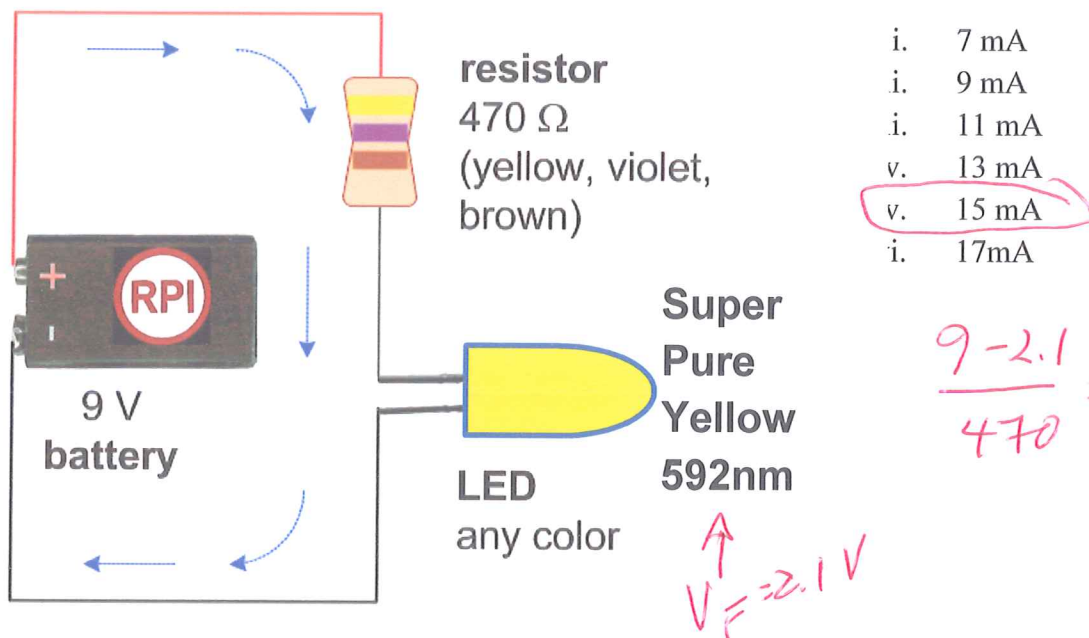
- b. (3 Pts) What is the current through the LED below, if we use the specified yellow LED? (Choose the closest answer.)





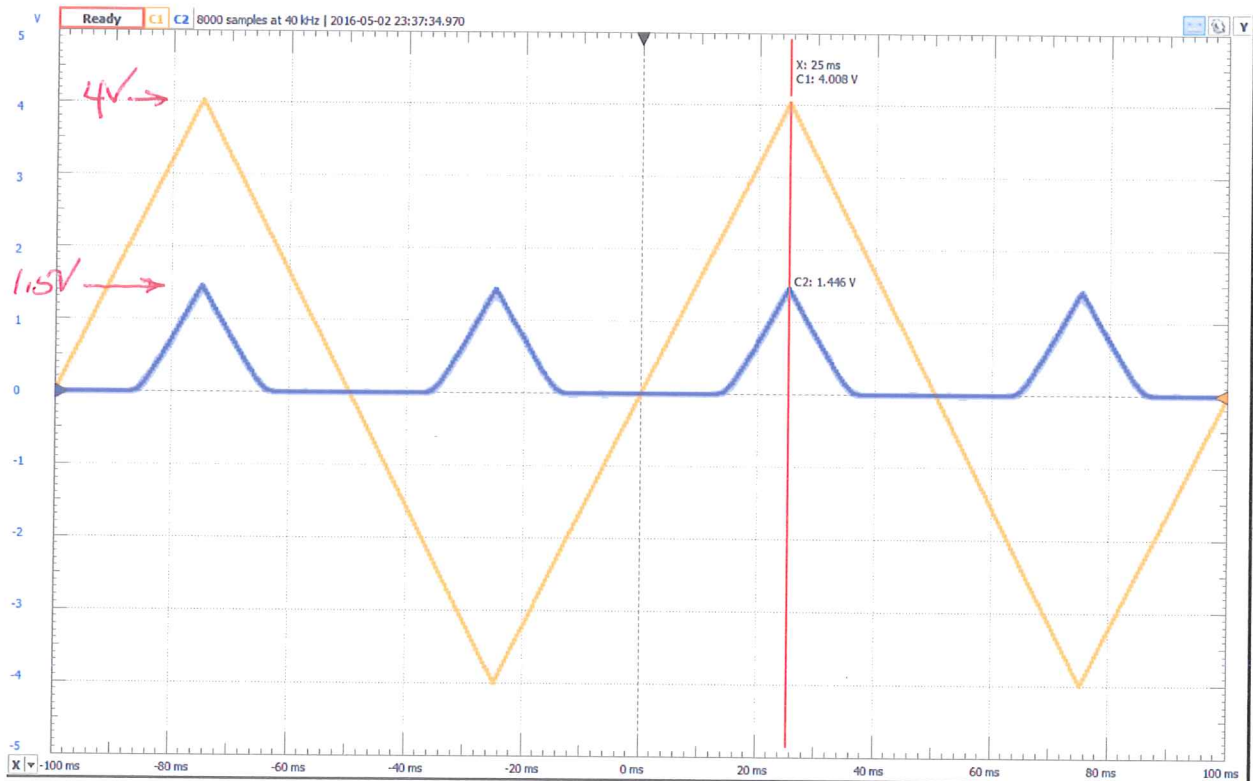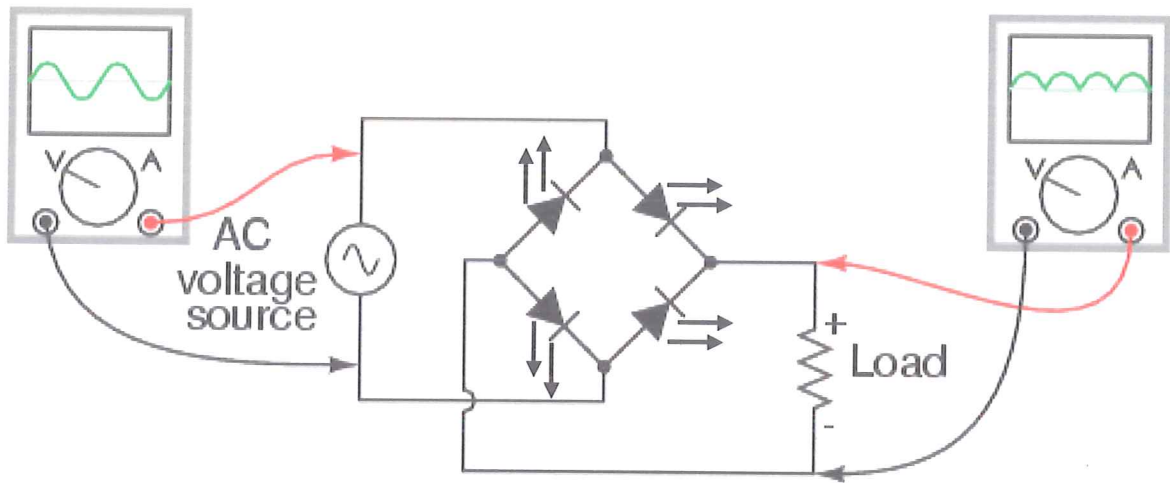- c. (4 Pts) This problem is similar to the full wave rectifier task from Experiment 8 with a triangular wave input voltage, except that infrared (IR) LEDs were used in place of standard diodes (see first figure below). The voltage source is connected to the top and bottom nodes and monitored with a scope. The output voltage across the load resistor is also measured with a scope. Both signals are shown in the second figure. The vertical

*Full-wave rectifier circuit (bridge design)*





scale is 1V/div and the horizontal scale is 20ms/div. Answer the following questions.

- i) (3 Pts) Using the information in the plot, determine an approximate value for the forward voltage of this LED.



2 diodes are on  $\frac{1}{2}$  Drop  $4 - 1.5 = 2.5V$   
 $\Rightarrow V_F = \frac{2.5}{2} = 1.25V$  which is  
 consistent with the values in the table

- ii) (1 Pt) Since the diodes are LEDs, what pattern of light would you see if you observed this circuit in action?

None - Cannot see IR  
 Also OK  Also 

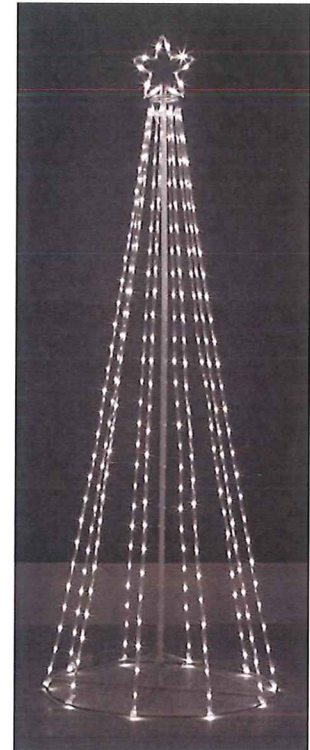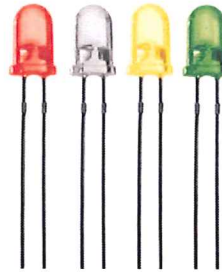- d. (5 Pts) We now want to use multiple LEDs in several long strings of holiday lights. For this purpose, we will use four different color LEDs: Red, Green, Yellow and White. We will use the four LEDs marked with a ★ in the table above. The figure at the right shows only white LEDs, but you should assume all four colors are used and that there are 15 of each for a total of 60 lights in each string.

Assuming that you have a 180V DC supply to power the LEDs, what resistor do you need in series with the 60 LEDs to achieve a desired operating current of 50mA or 20mA. Either OK



$V_F \Rightarrow 2.2, 2.1, 3.6, 3.5$


Sum = 11.4V

60 lights  $\Rightarrow 15 \times 11.4 = 171V$


$\frac{180 - 170}{.05} = 180\Omega$   
 or  $\frac{180 - 170}{.02} = 450\Omega$

Both OK

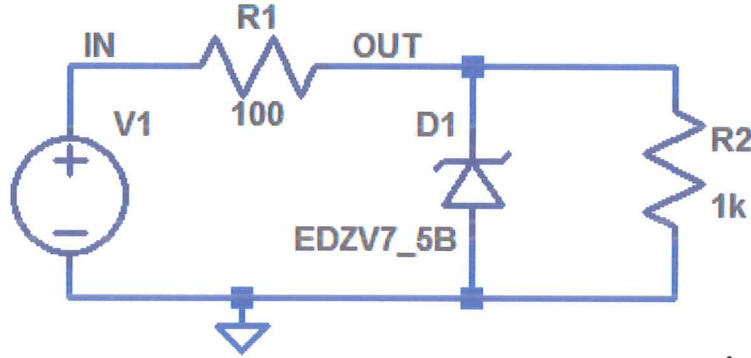- e. (5 Pts) Shown below is a Zener diode working to regulate the voltage across one resistor in a voltage divider. The voltage source is a 1kHz sine wave with amplitude 6V and offset 4V.



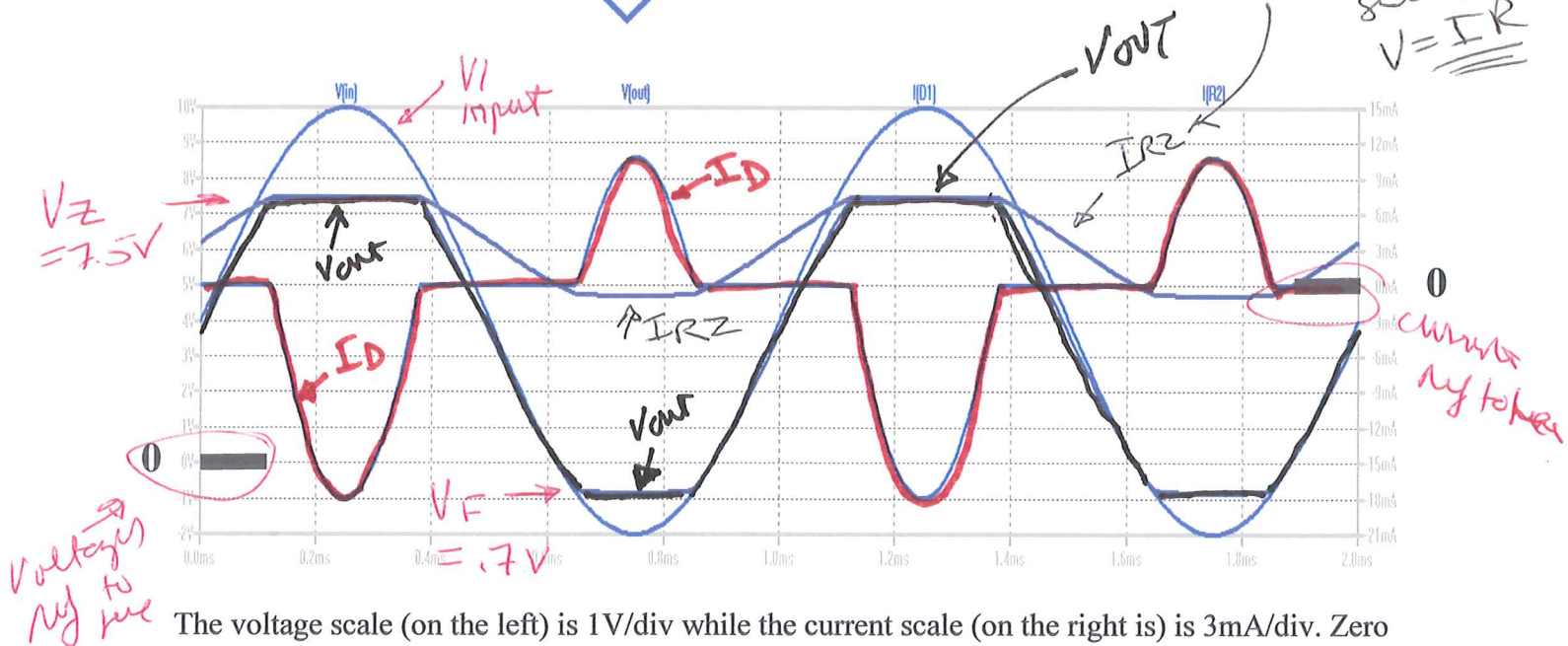*IR<sub>Z</sub> looks like V<sub>out</sub>*  
*since V = IR*



The voltage scale (on the left) is 1V/div while the current scale (on the right) is 3mA/div. Zero is indicated for both scales. Four signals are plotted:  $V_{IN}$ ,  $V_{OUT}$ ,  $I_D$  for the Zener, and  $I_R$  for the 1k resistor. Identify and label each signal and also annotate any significant voltages or currents. In particular, label the forward voltage  $V_F$  and the Zener voltage  $V_Z$  of the Zener diode. *Hint: Remember the general shape of the Zener I-V characteristic as shown in part a above. Also, the name of the diode might offer a clue as to its properties. Make any reasonable assumptions.*

$V_Z = 7.5\text{ V}$

$V_F \approx 0.7\text{ V}$

19 + 22 +