

ENGR-4300
Spring 2009
Test 4

Name **SOLUTION**

Section 1(MR 8:00) 2(TF 2:00) 3(MR 6:00)
(circle one)

Question I (20 points) _____

Question II (20 points) _____

Question III (15 points) _____


Question IV (25 points) _____

Question V (20 points) _____

Total (100 points): _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification.

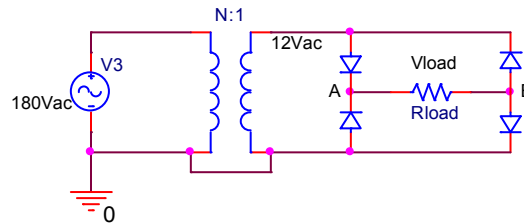Question I – Diode Rectifier Circuits (20 points)



1. Designing a low-voltage DC power source from a 180Vpeak AC supply, requires a transformer and rectifier bridge.

a) (3pt) What should the transformer turns ratio $N:1$ be to output 12Vpeak on the secondary side from the 180Vpeak on the primary?

$$N_2/N_1 = V_2/V_1 \quad N = N_1 = V_1 \times N_2/V_2 = 180 \times 1/12 = 15$$


b) (3pt) Given the rectifier bridge circuit with 4 diodes (0.6V turn-on), what will be the peak voltage V_{load} across the load resistor R_{load} ?


$$V_{load} = 12V_{peak} - 0.6V - 0.6V = 10.8V$$

c) (1pt) Which side, **A** or **B**, of R_{load} is the positive (high) voltage of V_{load} ?


A

d) (4pt) With 12Vac applied to the rectifier bridge circuit shown on the plot below, sketch V_{load} , the voltage across R_{load} .

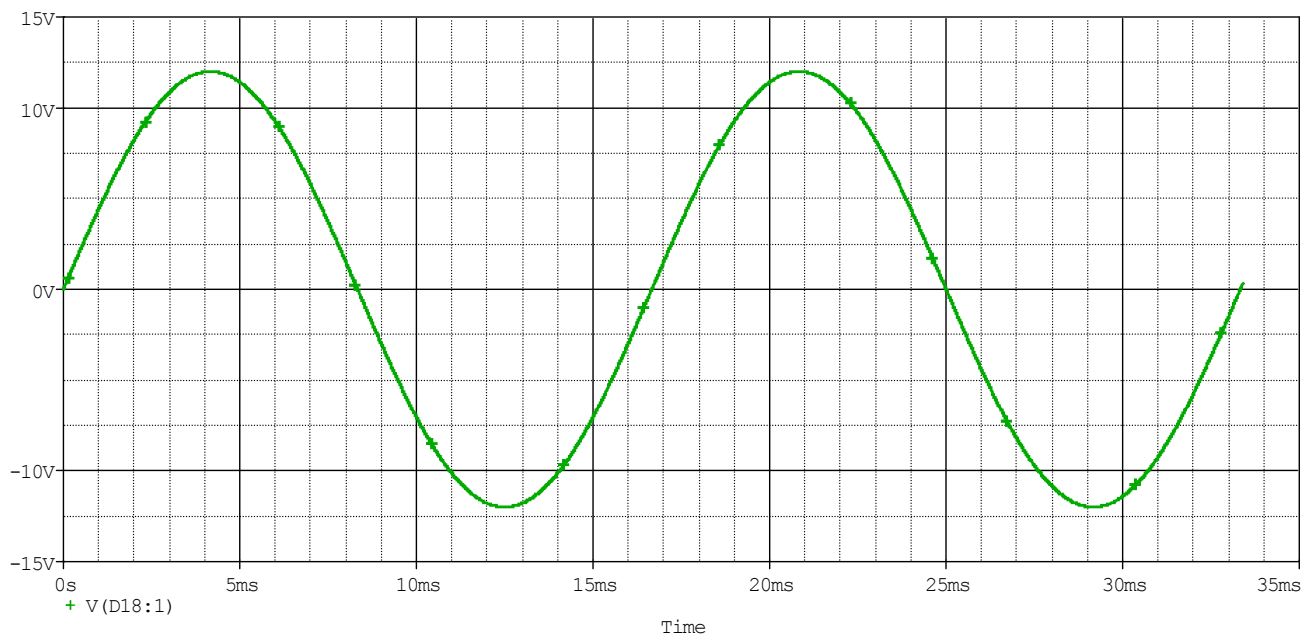


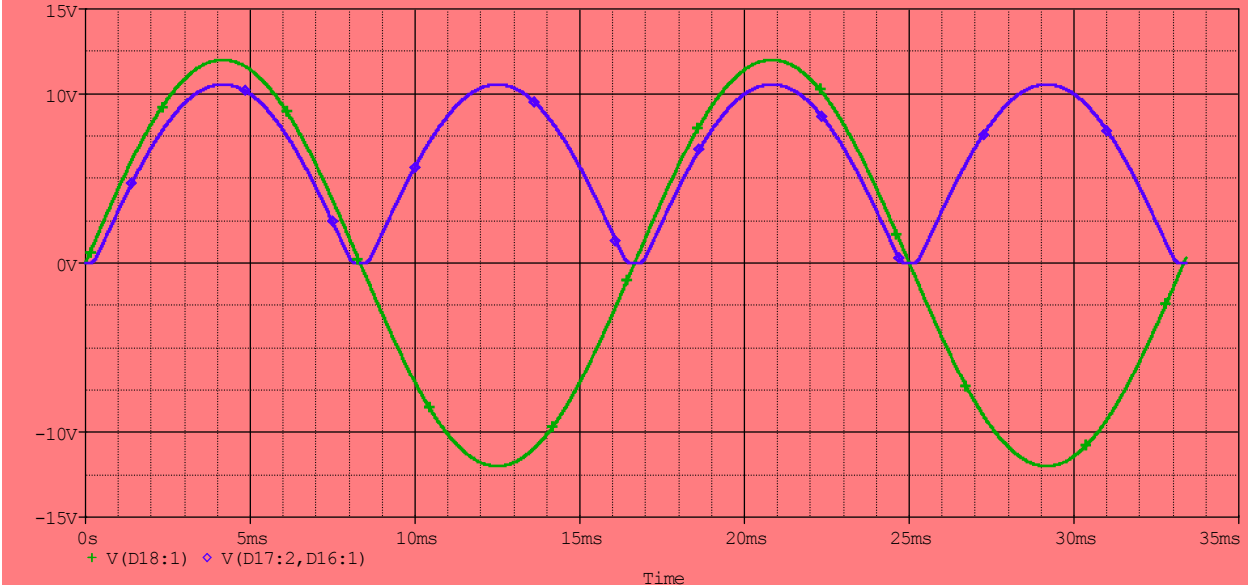

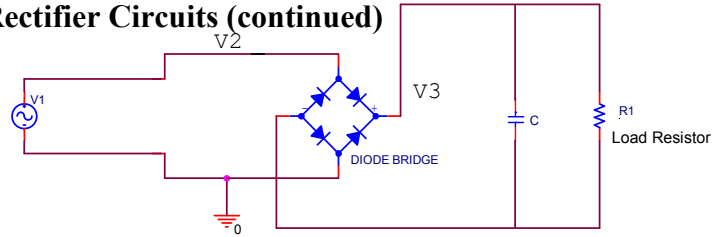
Question I – Diode Rectifier Circuits (continued)



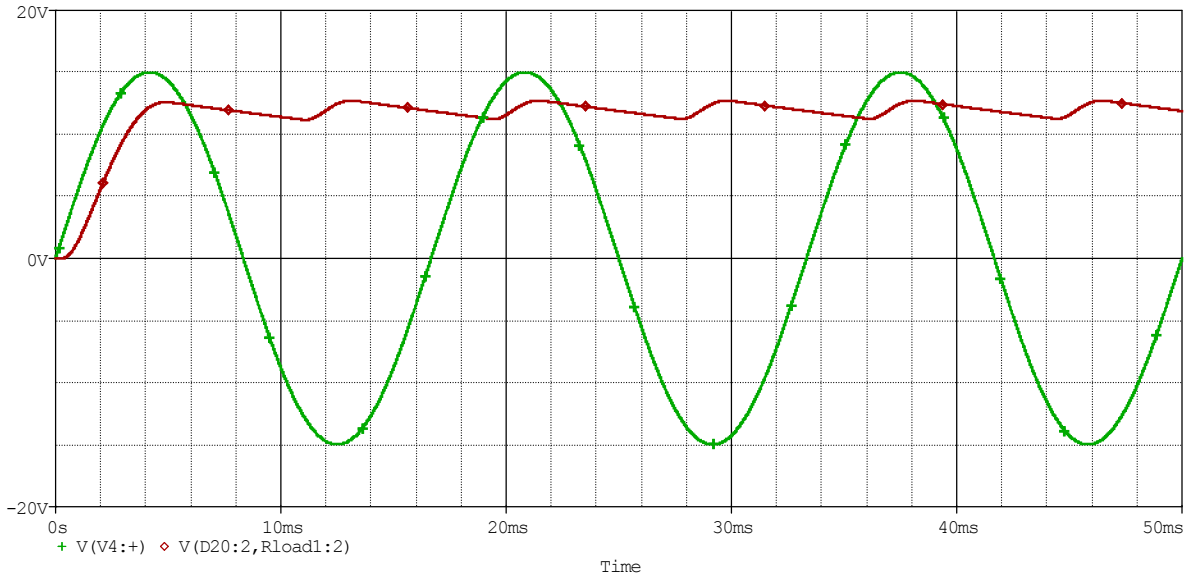2. For the following full-wave rectifier above, with $R_{load} = 100\Omega$ and $C = 500\mu F$, the plot below shows the input voltage and the voltage across the load.



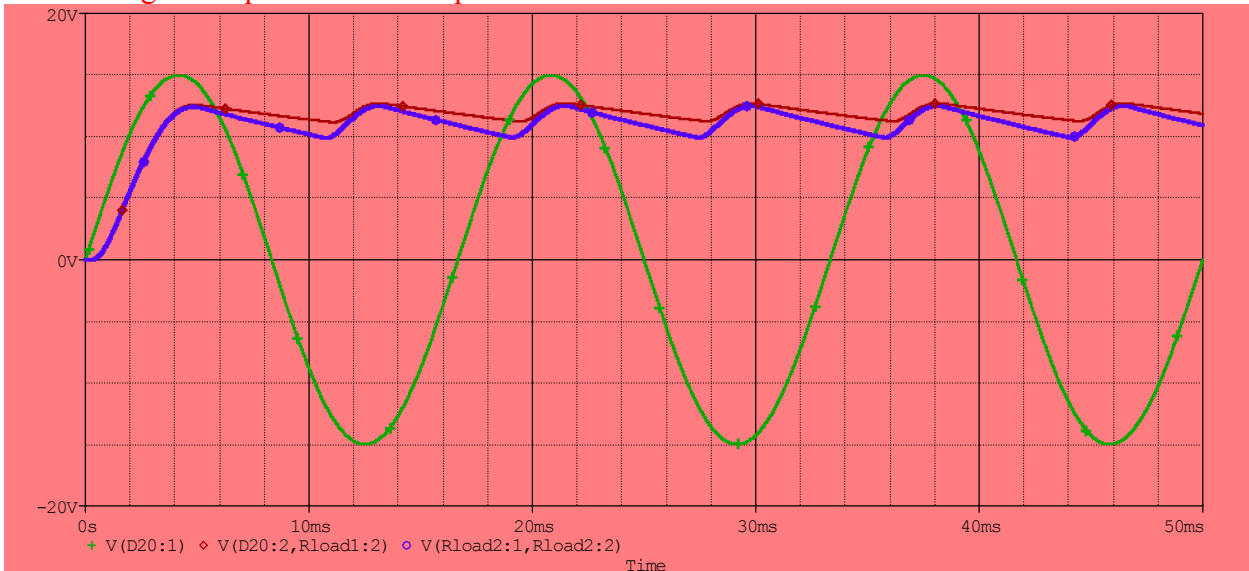a) (3pt) On the plot, show how the voltage across the load would change if R_{load} is reduced to 50Ω .
Voltage Droop is about twice previous or $\sim 2.5V$




b) (2pt) What new value for C would restore the voltage waveform back to its original form when R_{load} was 100Ω ?

$$RC = R'C'$$


$$100 \times 500\mu = 50 \times C'$$

$$C' = (100/50)500\mu = 1000\mu F$$

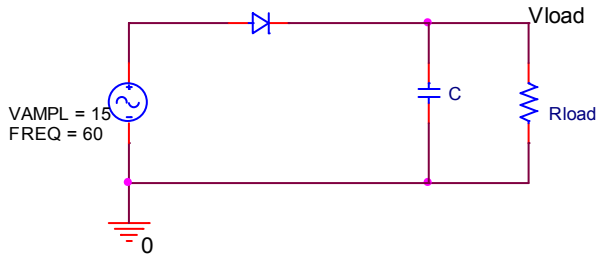
Question I – Diode Rectifier Circuits (continued)



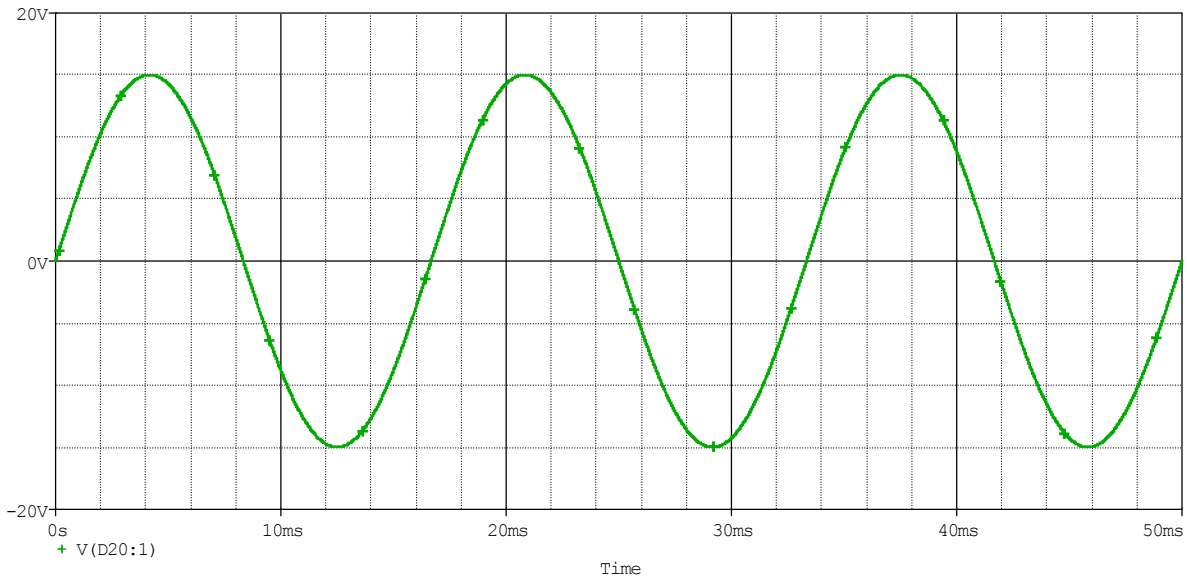c) (4pt) For an essentially equivalent half-wave rectifier circuit replacing the full-wave above, with $R_{load} = 100$ and $C = 500\mu F$ as in the circuit in 1, sketch the voltage across R_{load} on the 15V input voltage plotted below.





Voltage Droop ~ 4V (Actual $V_{max} = 12 - 0.6 = 11.4V$ but not required)

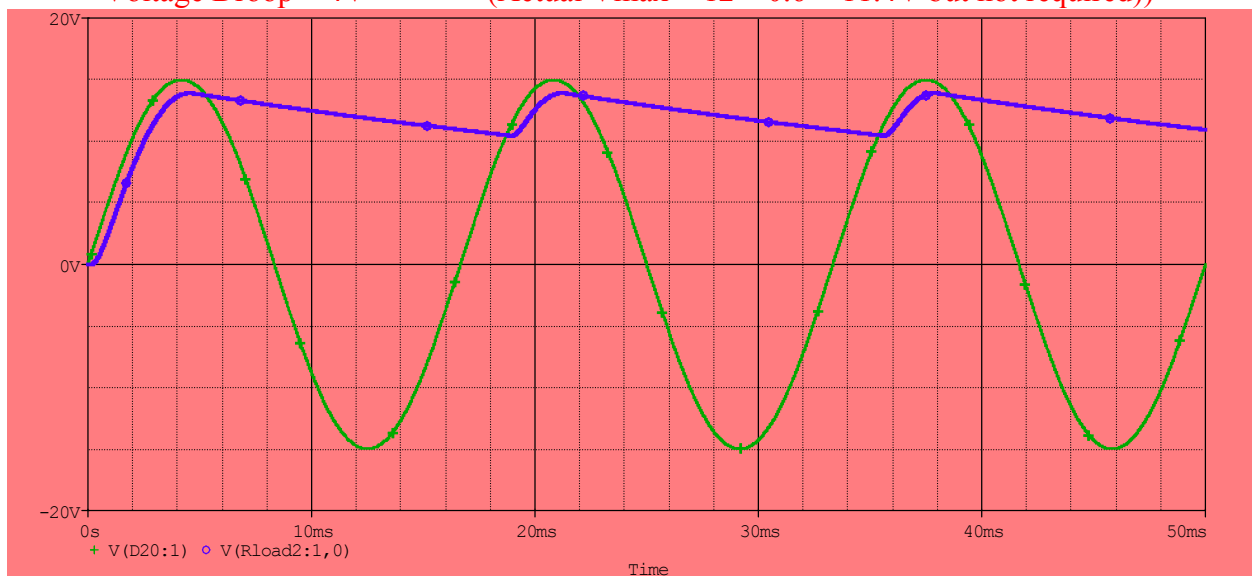


Question II – Diode Limiter Circuits (20 points)

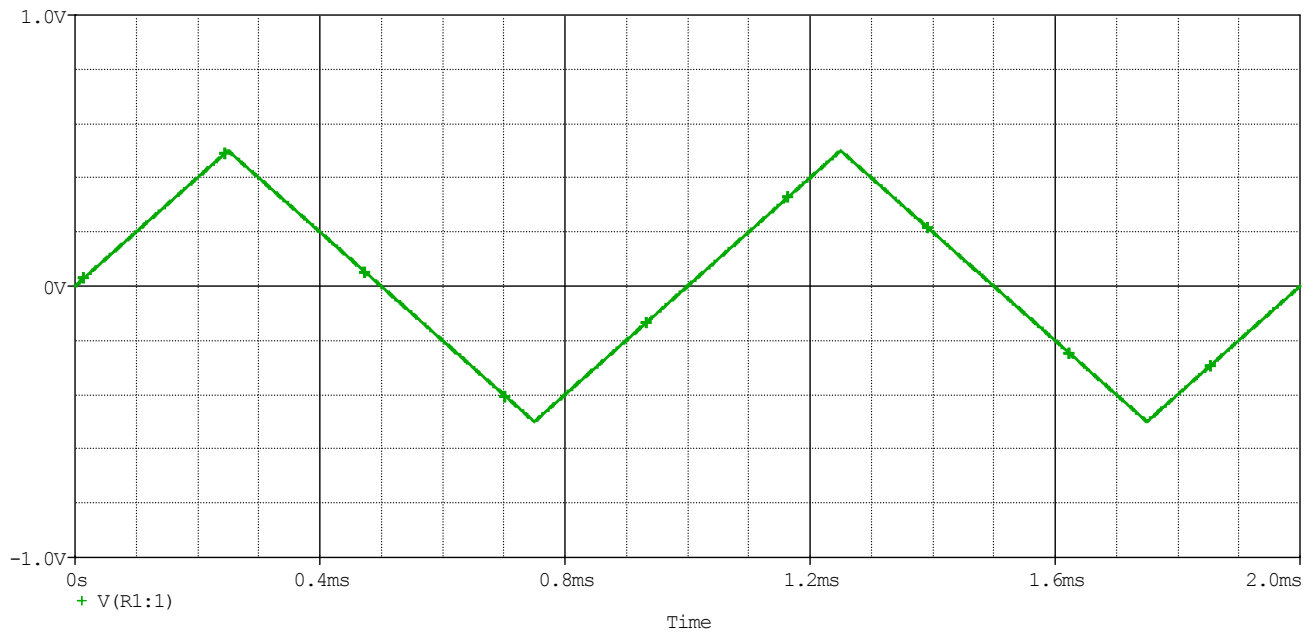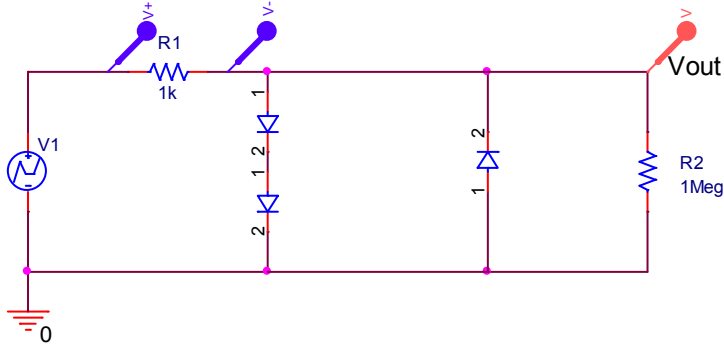1. (6pt) Draw and label V_{out} and V_r (the voltage across R1) on the plot below showing V_1 . The diodes turn on at 0.5V. (Label the maximum and minimum of the output.)





R2 at 1Meg is too large to have any visible effect on the output. $V_r = 0V$, $V_{out} = V_1$

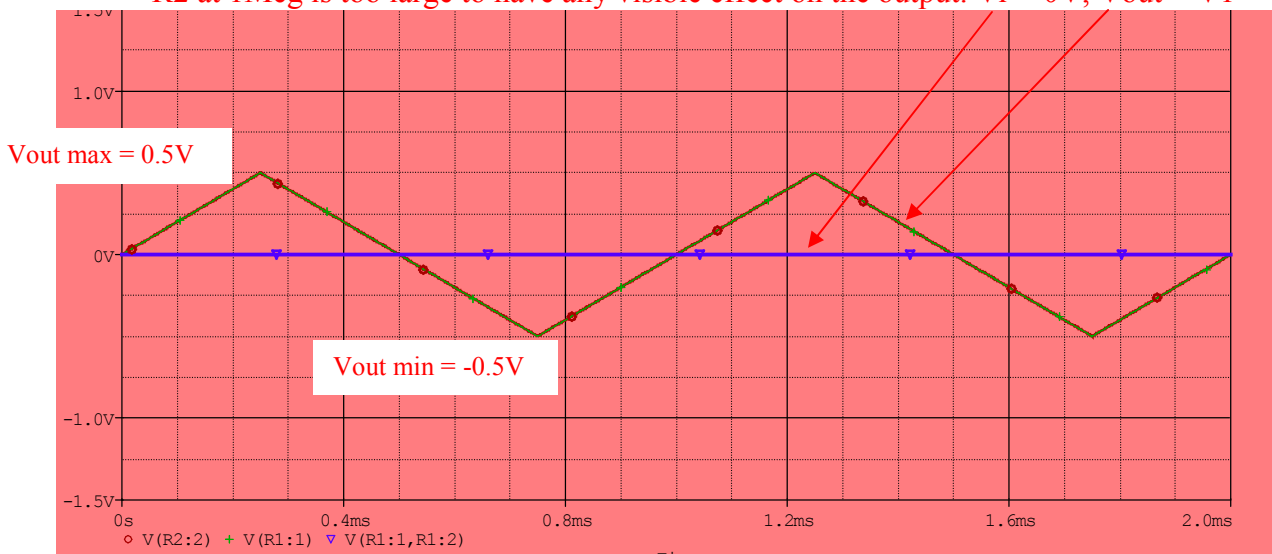



Question II – Diode Limiter Circuits (continued)

2. (6pt) Draw V_{out} and V_r on the plot below with V_1 increased to $2V_{p-p}$. (Label the maximum and minimum of the output.)

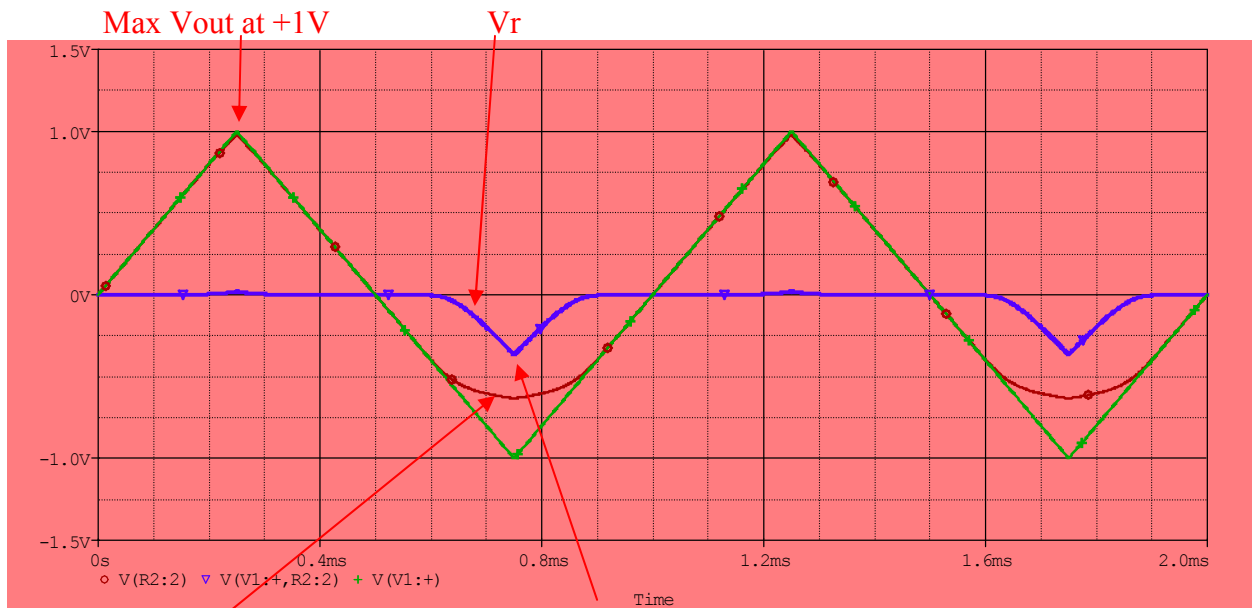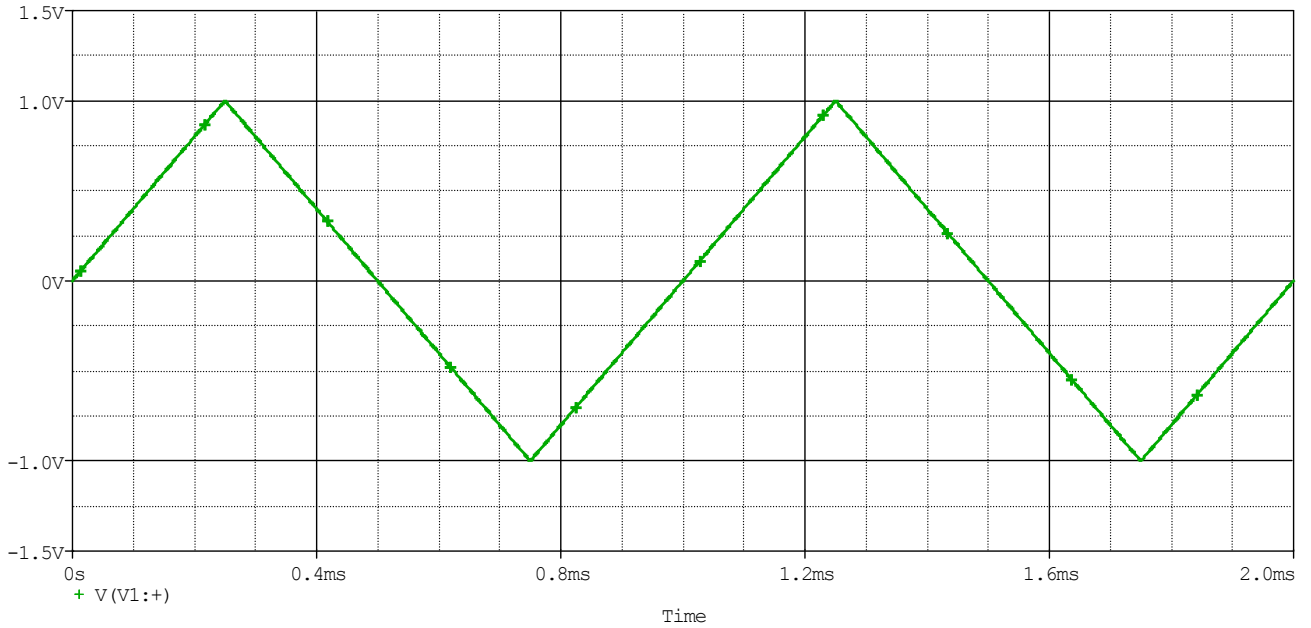

Question II – Diode Limiter Circuits (continued)

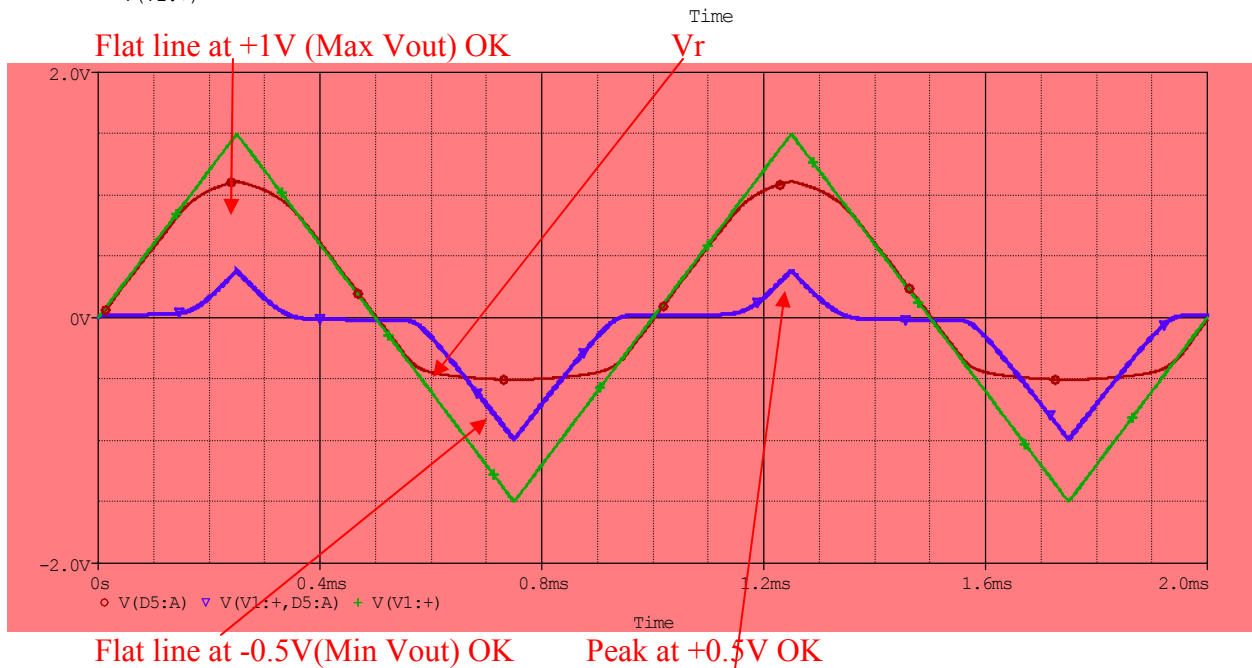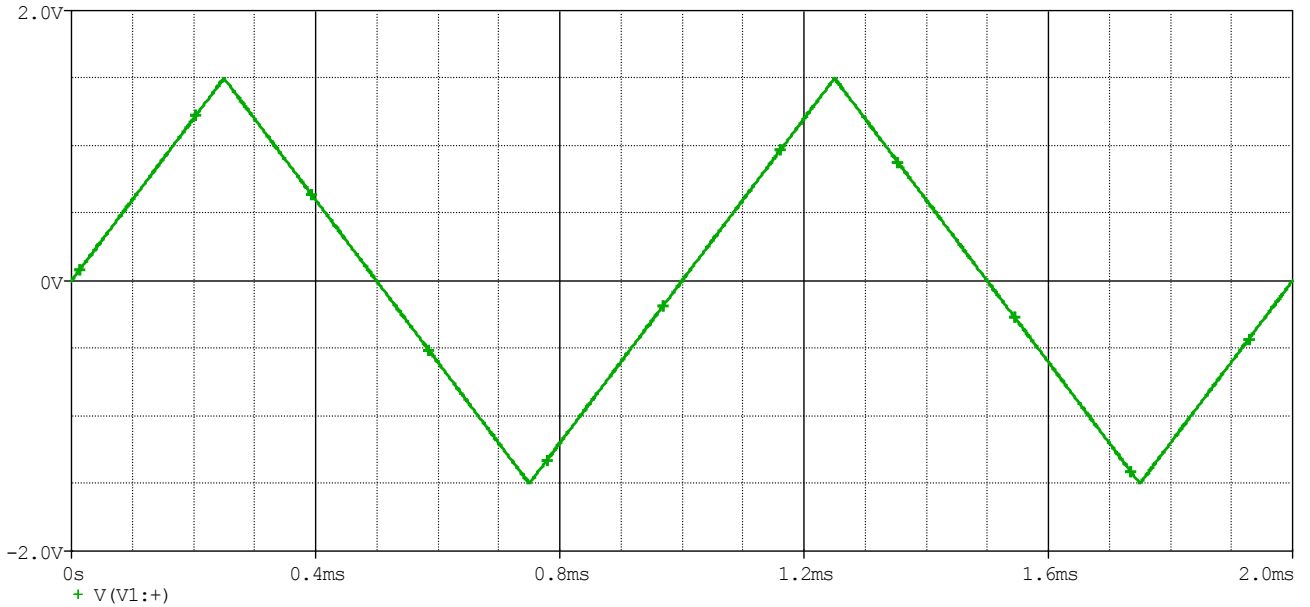
3. (6pt) Draw V_{out} and V_r on the plot below with V_1 increased to $3V_{p-p}$. (Label the maximum and minimum of the output.)



4. (2pt) TRUE or FALSE: With a diode that turns on at 0.7V and one that turns on at 0.6V, it is possible to build a limiter circuit that turns on at 0.1V by wiring them in series, but switching the 0.6V diode's connections around.



FALSE, no current will flow through the series combination since one diode will always be off.

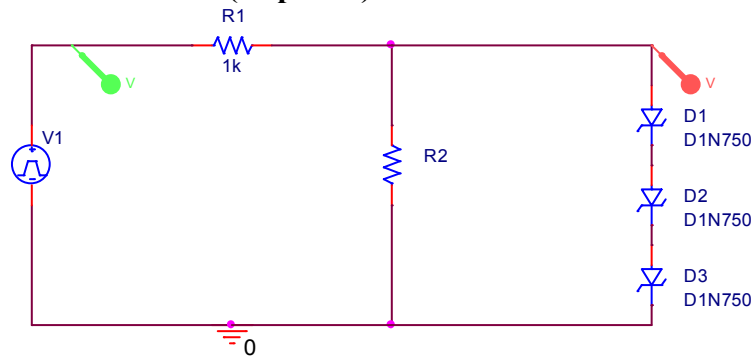Question III – Zener Diode Circuits (15 points)




The circuit above is a zener diode voltage regulator. Three Zener diodes are used to regulate the voltage across the load resistor R2 in the circuit below. Three different values of R2 are tried (100Ω, 1kΩ, and 10kΩ) Draw the voltage on the output probe above D1. **Calculate your answers.**

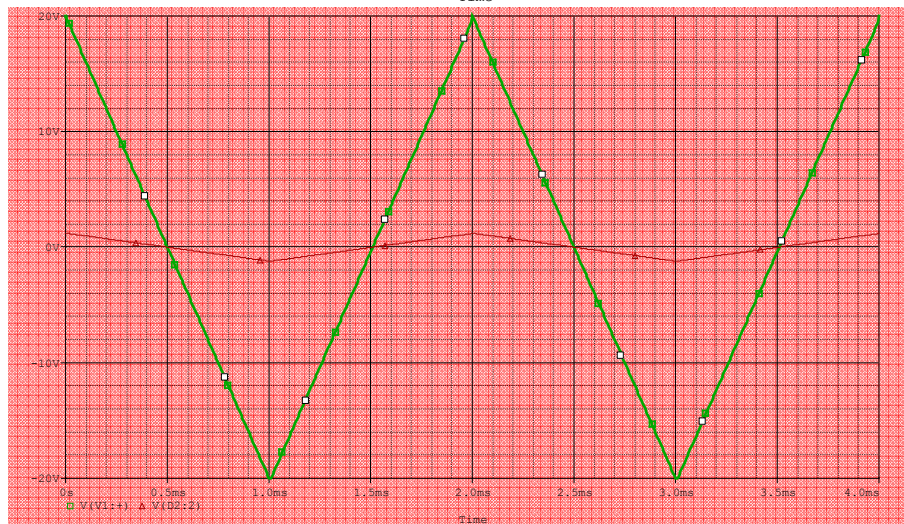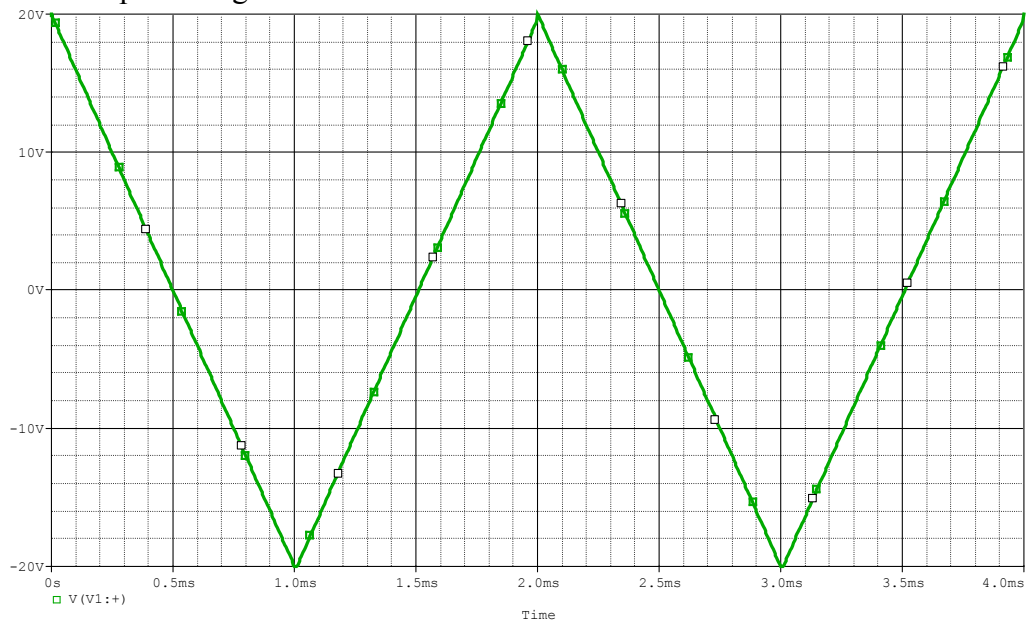
1. (3pt) Plot the output voltage when R2 = 100Ω




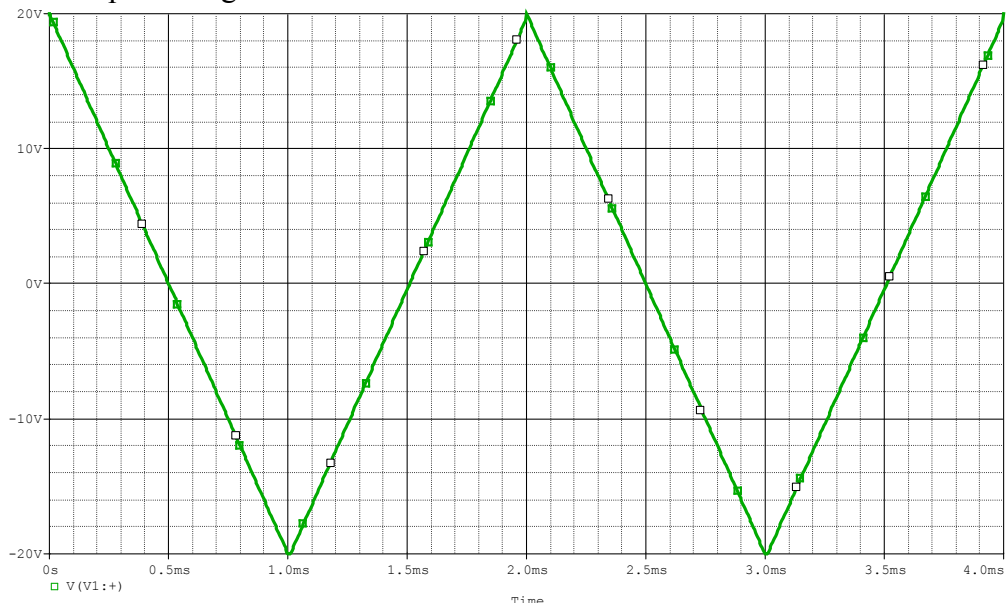2. (3pt) Plot the output voltage when $R2 = 1k\Omega$



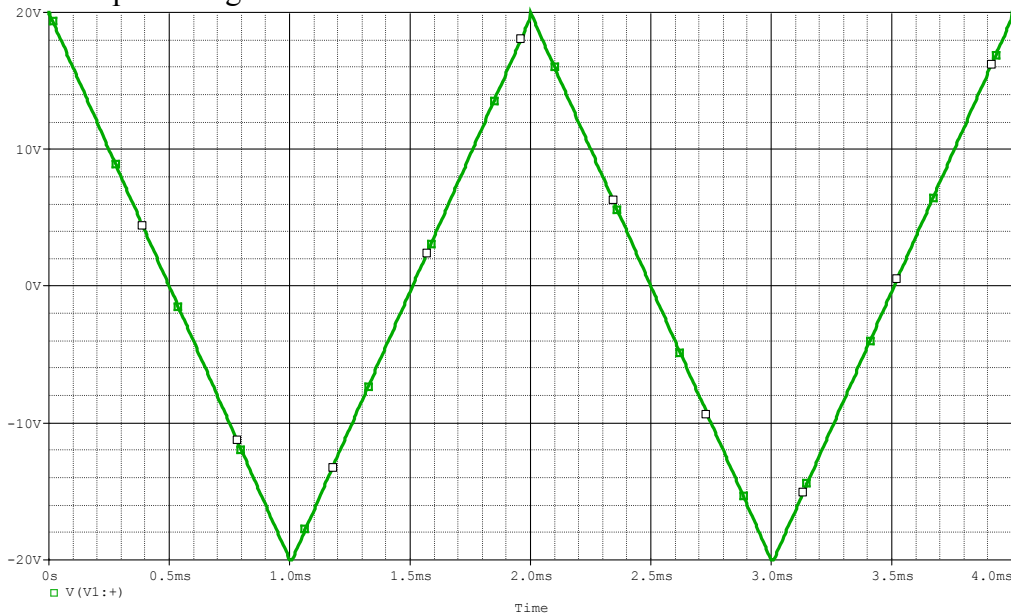3. (3pt) Plot the output voltage when $R2 = 10k\Omega$



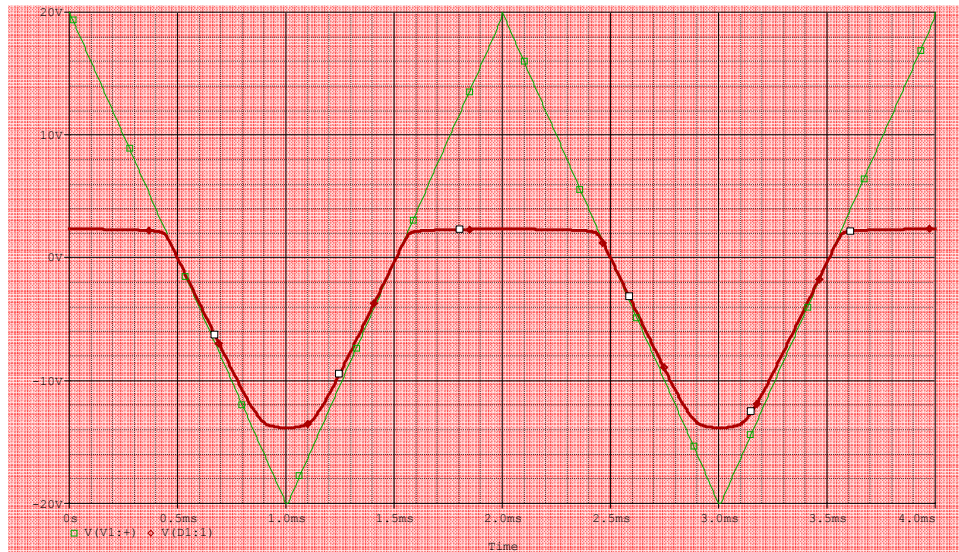

4. (3pt) What is the voltage across R2 when R2 is 10k Ω and the input voltage is 5V?

The voltage divider makes the voltage 4.5 V which is above the limit at 2.1 V. Therefore the voltage is held at 2.1V.

5. (2pt) What is the current through R2 when R2 is 10K and the input voltage is -17V?

Voltage divider voltage is -15.4 which is above -14.1 so it is held at -14.1V
 $i = V_{load}/R_{load} = -14.1/10k\Omega = -1.41 \text{ mA}$


6. (1pt) Which of the 4 Electronic Instrumentation projects could have benefited most from a voltage regulated circuit? (*A major component was highly sensitive to voltage in this project*)

The Accelerometer modules in Project 2 would have been better protected by the circuit above, which would prevent larger voltages than the module can withstand from being applied to it.

Question IV - LEDs and Phototransistor Circuits (25 points)

A high brightness LED is driven by a standard DC source. The source we have available is a 10 Volt wall wart capable of producing up to 5 Watts. We need a forward bias voltage of 4V and a current of 50 mA.

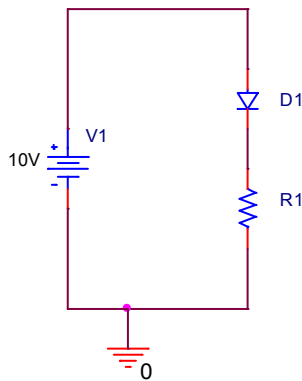1. (5pt) Using the 10 Volt supply, determine the resistance R1 necessary to achieve the desired operation conditions for the diode. Also determine the total power dissipated in the circuit.




$$R_1 = \frac{10 - 4}{.05} = 120\Omega$$

$$P_{diode} = 4 \times 0.05 = 0.2W$$

$$P_{res} = 6 \times 0.05 = 0.3W$$

$$P_{total} = 0.2W + 0.3W = 0.5W \quad (= 10V \times 50mA)$$

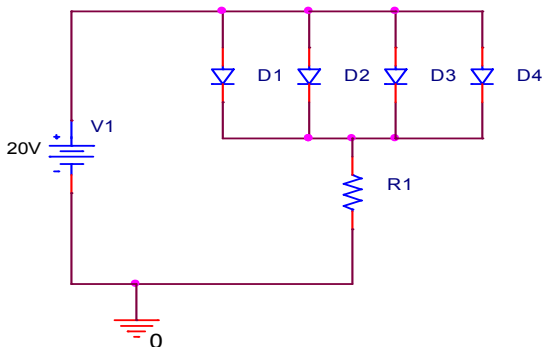2. (10pt) We now want multiple LEDs like a short string of Christmas lights. **Find R1 for both circuits below.** Choose the circuit below that will operate with a 20 Volt wall wart capable of producing 4.5 Watts. The LEDs need 4V and 50 mA of current each to operate. **You may also choose neither or both. Explain with calculations of current, voltage, and power limits in your answer.**




$$R_1 = \frac{20 - 4}{0.05 \times 4} = 80\Omega$$

Meets voltage requirement only takes 4V to light them
Meets current requirement $4.5Watts/20V=225mA$ total in circuit
diodes use 200mA

Total Power requirements $P_{diode} = 4 \times 4 \times 0.05 = 0.8Watts$

$P_{res} = 16 \times .2 = 3.2Watts$ $P_{total} = 3.2 + 0.8 = 4Watts \leq 4.5Watts$

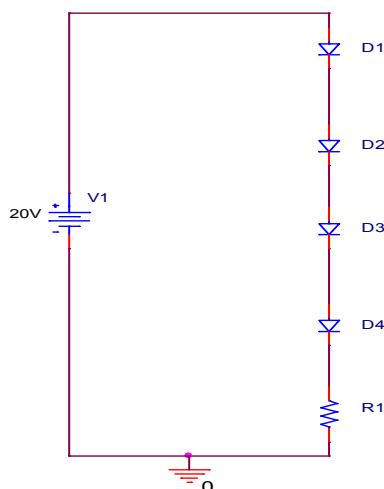Meets power requirement (circle this circuit)



$$R_1 = \frac{(20 - (4 \times 4))}{0.05} = 80\Omega$$

Much less than current limit: 50 mA throughout and can use 225 mA

Voltage limit $4 \times 4 = 16V < 20V$ so meets voltage requirement

$P_{diode} = 4 \times 4 \times 0.05 = 0.8Watts$

$P_{res} = (20 - 16) \times .05 = 0.2Watts$

$P_{total} = 0.2 + 0.8 = 1Watt \leq 4.5Watts$ Meets power requirement


Circle this one too

Question IV - LEDs and Phototransistor Circuits (continued)

3. (4pt) If you add one more diode in parallel to the parallel circuit above, which of the limits (current, voltage, and/or power) will it surpass? *This can be in addition to the limit it may surpass in the previous problem; mention all that apply now.*

Current limit and power limit (5 leds will now require 250mA. The max is 225 mA. The power limit is also surpassed with 1W from the diode and 4W from the LED. This is a total of 5W which is above 4.5 W from the source.)

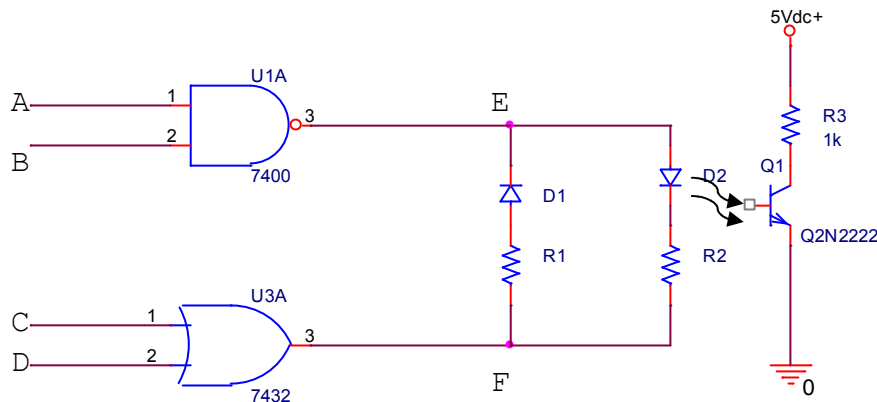
4. (6pt) Given the logic circuit below, fill in the chart using **ON and OFF for D1 and D2**. **Mark the collector voltage in Volts**. Assume that 0 is a low enough voltage to turn the diodes off, 1 is a high enough voltage to turn the diodes on, and the output voltages are identical for both logic gates.



A	B	C	D	E	F	D1	D2	collector
0	0	0	0					
0	1	0	1					
1	0	1	0					
1	1	1	1					

A	B	C	D	E	F	D1	D2	collector(V)
0	0	0	0	1	0	OFF	ON	0V
0	1	0	1	1	1	OFF	OFF	5V
1	0	1	0	1	1	OFF	OFF	5V
1	1	1	1	0	1	ON	OFF	0V

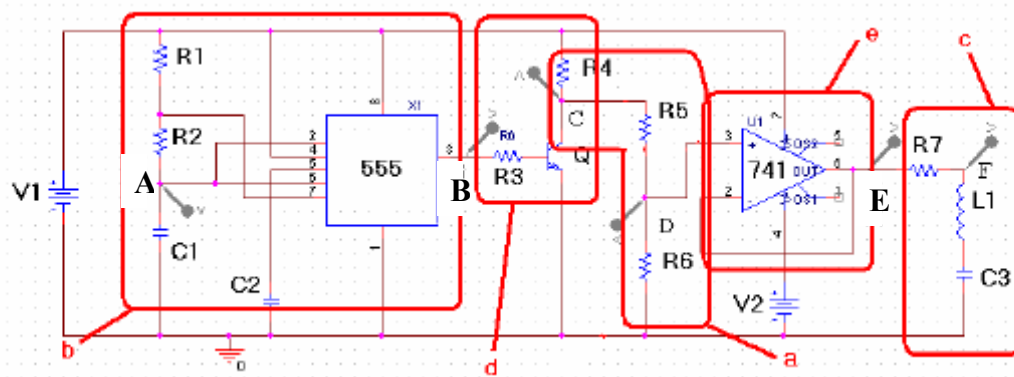Question V – Signal Modulation and Functionality (20 points)



Assume the components have the following values:

- C1=0.2 μ F, C2=0.02 μ F, C3=0.068 μ F
- R1=1k Ω , R2=5k Ω , R3=1k Ω , R4=1k Ω , R5=6k Ω , R6=1k Ω , R7=50 Ω
- L1=5mH
- V1=+15V
- V2=-15V

1. (5pt) Identify the function of each of the blocks in the signal conditioning circuit above. Some blocks may match more than one function name and some function names may not be used.

- Monostable multivibrator circuit _____
- Voltage divider _____
- Inverting amplifier _____
- Comparator _____
- Buffer amplifier (voltage follower) _____
- Schmitt trigger _____
- Voltage divider _____
- RL circuit _____
- A transistor circuit _____
- Astable multivibrator circuit _____
- RLC circuit _____

- Monostable multivibrator circuit N/A
- Voltage divider a
- Inverting Amplifier N/A
- Comparator N/A
- Buffer amplifier (voltage follower) e
- Schmitt Trigger N/A
- RL Circuit N/A
- A transistor circuit d
- Astable multivibrator circuit b
- RLC Circuit c

Question V – Signal Modulation and Functionality (continued)

2. (2pt) What is the general purpose of the circuit circled in e?

It is to keep the impedance of two different parts of the circuit from affecting each other.

3. (3pt) Calculate the frequency of the circuit in b in Hz

$$f = 1/[0.693(R1+2R2)C1] = 1/[0.693(1k+2*5k)*0.2\mu] = 656 \text{ Hz}$$

4. (10pt) Fill in the voltages in the chart below based on the theoretical behavior of the circuit during normal astable (oscillating) operating mode. What are the min and max voltages that appear at each of the given points?

Voltage at pin 3	Point A	Point B	Point C	Point D	Point E
LOW					
HIGH					

Point A: This is the top of the capacitor at pin 2 and 6. Connected to the voltage divider thresholds. $V_a = 1/3(V1) = 1/3*15 = 5V$ low and $V_a = 2/3(V1) = 1/3(15) = 10V$ high

Point B: The output pulses vary between 0 and $V1 = 0V$ and 15V

Point C: When the output of the timer is low, the switch is open and $V_c = 15*(R5+R6)/(R4+R5+R6) = 15(7K)/8K = 13.1V$

When the output of the timer is high the switch is closed = 0V

**Point D: When $V_c = 13.1V$, $V_D = V_c * R6 / (R5 + R6) = 13.1 * 1K / (7K) = 1.88V$
When $V_c = 0$ $V_d = 0V$**

Point E: It is a buffer circuit so the voltages will be the same as point D

Voltage at pin 3	Point A	Point B	Point C	Point D	Point E
LOW	5V	0V	13.1V	1.88V	1.88V
HIGH	10V	15V	0V	0V	0V