
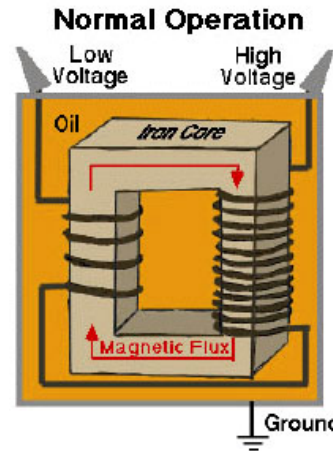


# Electronic Instrumentation


## *Experiment 3*

- Part A: Making an Inductor
- Part B: Measurement of Inductance
- Part C: Simulation of a Transformer
- Part D: Making a Transformer

# Inductors & Transformers

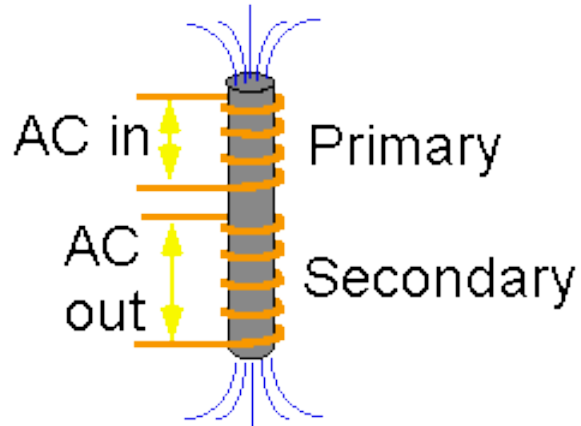

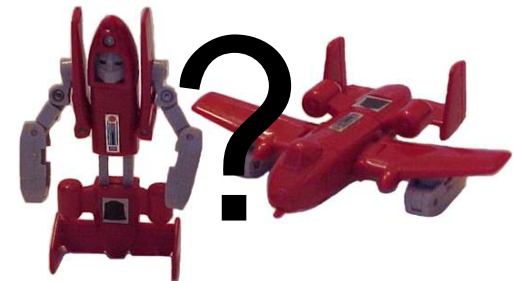- ◆ How do transformers work?
- ◆ How to make an inductor?
- ◆ How to measure inductance?
- ◆ How to make a transformer?



# *Part A*

- ◆ Inductors Review
- ◆ Calculating Inductance
- ◆ Calculating Resistance

# *Inductors-Review*



- ◆ General form of I-V relationship

$$V = L \frac{dI}{dt}$$


- ◆ For steady-state sine wave excitation

$$Z_L = j\omega L \quad V = j\omega LI$$

# *Determining Inductance*

- ◆ Calculate it from dimensions and material properties
- ◆ Measure using commercial bridge (expensive device)
- ◆ Infer inductance from response of a circuit. This latter approach is the cheapest and usually the simplest to apply. Most of the time, we can determine circuit parameters from circuit performance.

# *Making an Inductor*

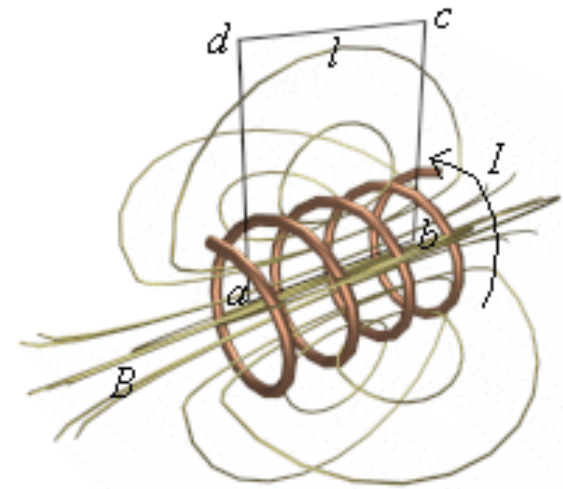


- ◆ For a simple cylindrical inductor (called a solenoid), we wind  $N$  turns of wire around a cylindrical form. The inductance is ideally given by

$$L = \frac{(\mu_0 N^2 \pi r_c^2)}{d} \text{Henries}$$

where this expression only holds when the length  $d$  is very much greater than the diameter  $2r_c$

# *Making an Inductor*

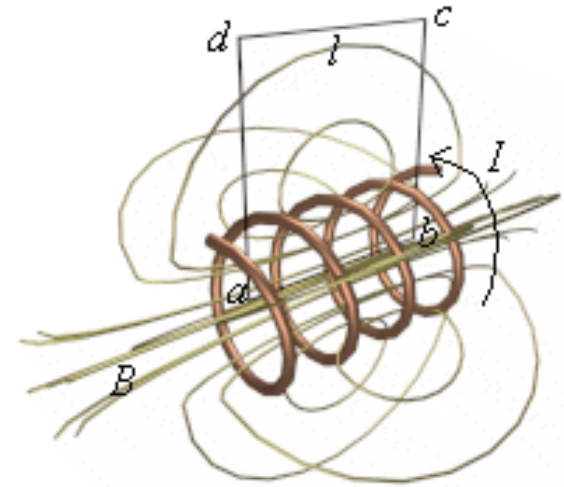


- ◆ Note that the constant  $\mu_o = 4\pi \times 10^{-7}$  H/m is required to have inductance in Henries (named after Joseph Henry of Albany)
- ◆ For magnetic materials, we use  $\mu$  instead, which can typically be  $10^5$  times larger for materials like iron
- ◆  $\mu$  is called the permeability

# *Some Typical Permeabilities*

- ◆ Air  $1.257 \times 10^{-6}$  H/m
- ◆ Ferrite U M33  $9.42 \times 10^{-4}$  H/m
- ◆ Nickel  $7.54 \times 10^{-4}$  H/m
- ◆ Iron  $6.28 \times 10^{-3}$  H/m
- ◆ Ferrite T38  $1.26 \times 10^{-2}$  H/m
- ◆ Silicon GO steel  $5.03 \times 10^{-2}$  H/m
- ◆ supermalloy 1.26 H/m




# Making an Inductor

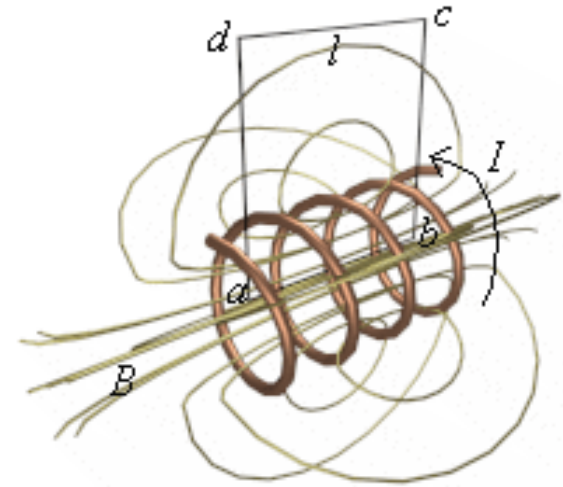

- ◆ If the coil length is much smaller than the diameter ( $r_w$  is the wire radius)

$$L \cong \mu N^2 r_c \left\{ \ln\left(\frac{8r_c}{r_w}\right) - 2 \right\}$$

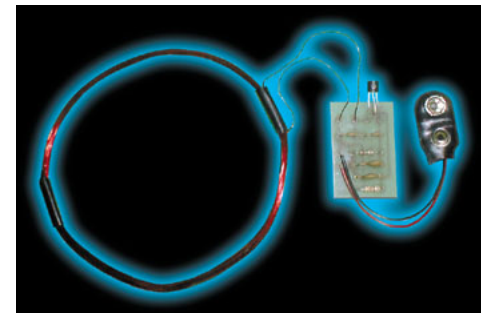Such a coil is used in the metal detector at the right



# Calculating Resistance

- ◆ All wires have some finite resistance. Much of the time, this resistance is negligible when compared with other circuit components.

- ◆ Resistance of a wire is given by 
$$R = \frac{l}{\sigma A}$$

$l$  is the wire length

$A$  is the wire cross sectional area ( $\pi r_w^2$ )

$\sigma$  is the wire conductivity


# *Some Typical Conductivities*

- ◆ Silver  $6.17 \times 10^7$  Siemens/m
- ◆ Copper  $5.8 \times 10^7$  S/m
- ◆ Aluminum  $3.72 \times 10^7$  S/m
- ◆ Iron  $1 \times 10^7$  S/m
- ◆ Sea Water 5 S/m
- ◆ Fresh Water  $25 \times 10^{-6}$  S/m
- ◆ Teflon  $1 \times 10^{-20}$  S/m


*Siemen = 1/ohm*
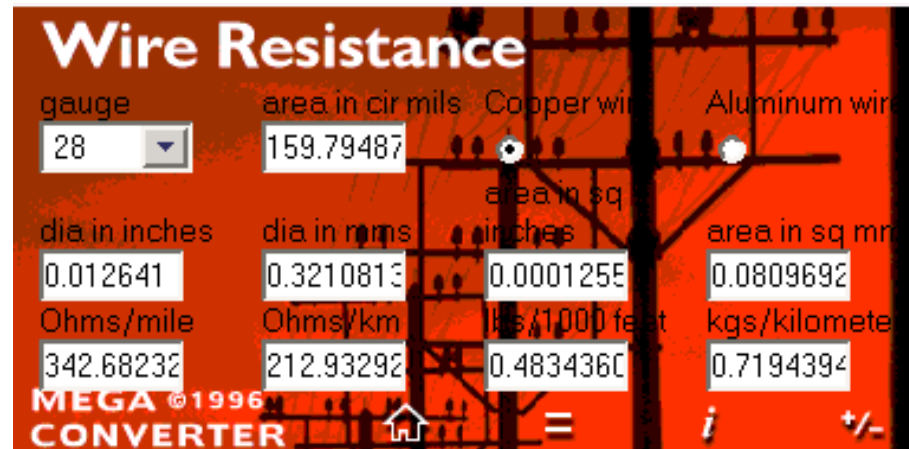
# Wire Resistance

- ◆ Using the Megaconverter at <http://www.megaconverter.com/Mega2/>  
(see course website)



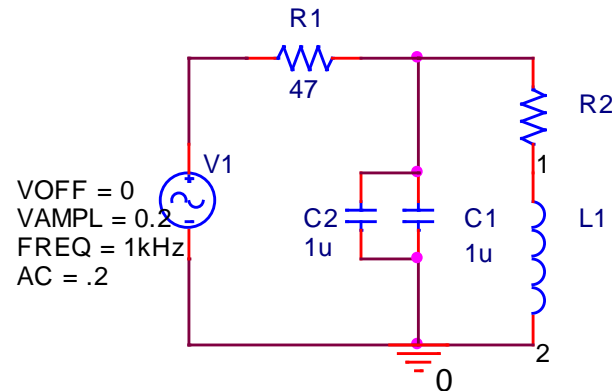
## Part B: Measuring Inductance with a Circuit



- ◆ For this circuit, a resonance should occur for the parallel combination of the unknown inductor and the known capacitor. If we find this frequency, we can find the inductance.

# Determining Inductance

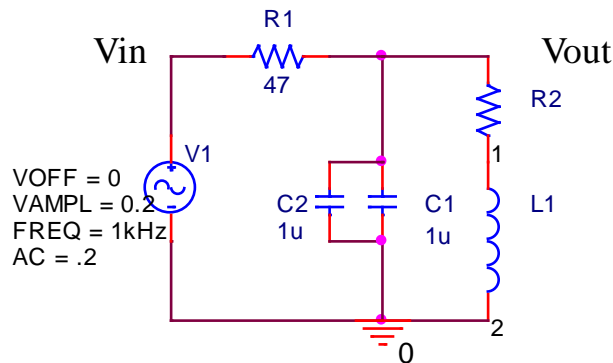

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

- ◆ **Reminder**—The parallel combination of  $L$  and  $C$  goes to infinity at resonance. (Assuming  $R2$  is small.)

$$Z_{\parallel} = \frac{j\omega L \left( \frac{1}{j\omega C} \right)}{j\omega L + \left( \frac{1}{j\omega C} \right)} = \frac{j\omega L}{1 - \omega^2 LC}$$



# Determining Inductance

$$H = \frac{Z_{\parallel}}{R1 + Z_{\parallel}}$$

$$H = \frac{j\omega L}{R1(1 - \omega^2 LC) + j\omega L}$$



$$H_{HI} = H_{LO} = \frac{j\omega L}{R1} = \textit{small}$$
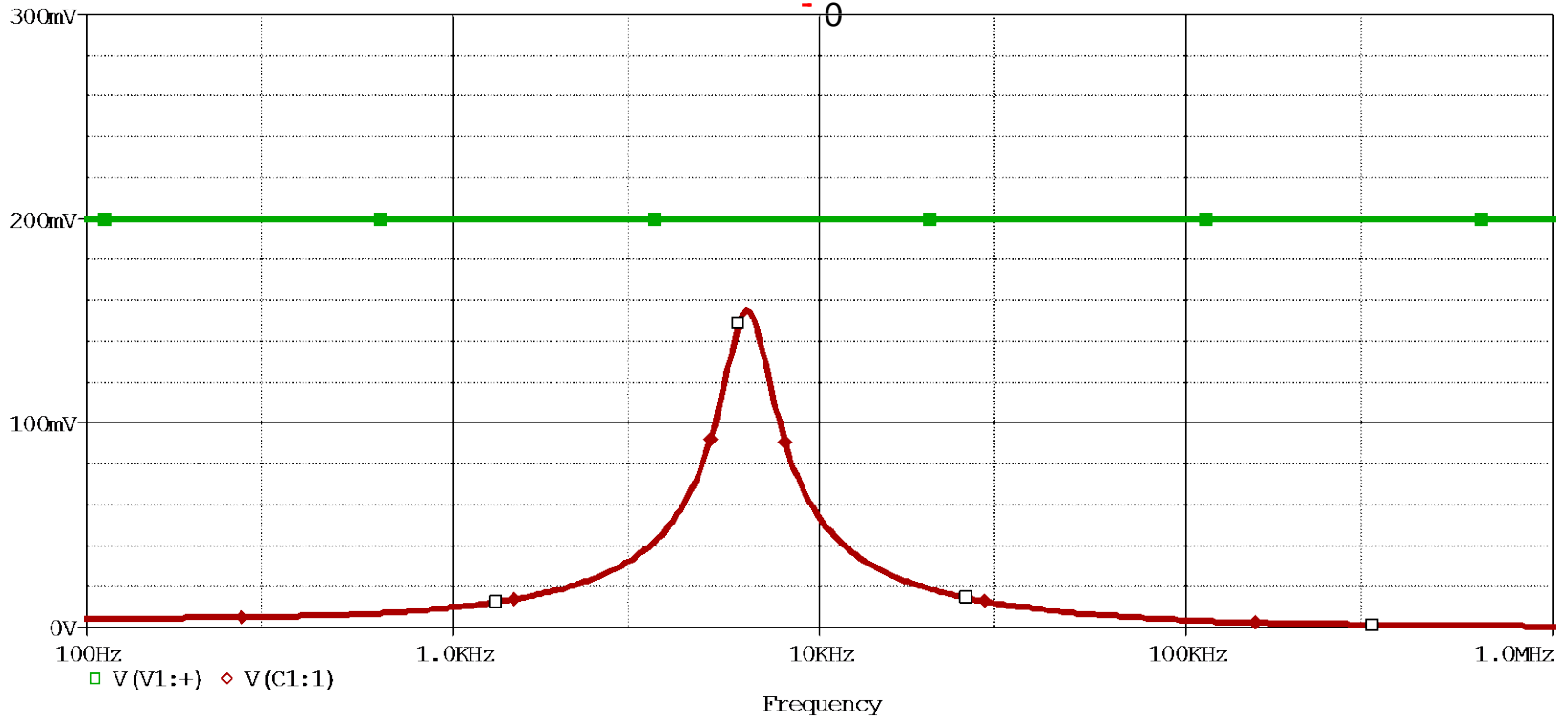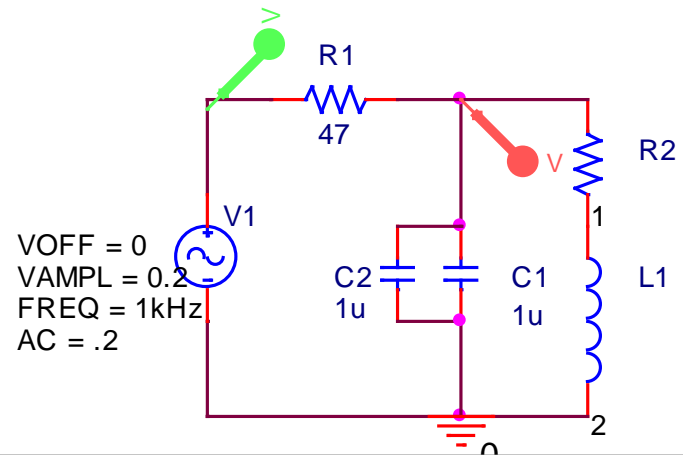
$$\textit{at resonance, } \omega_0, \quad H_0 = \frac{j\omega L}{j\omega L} = 1$$





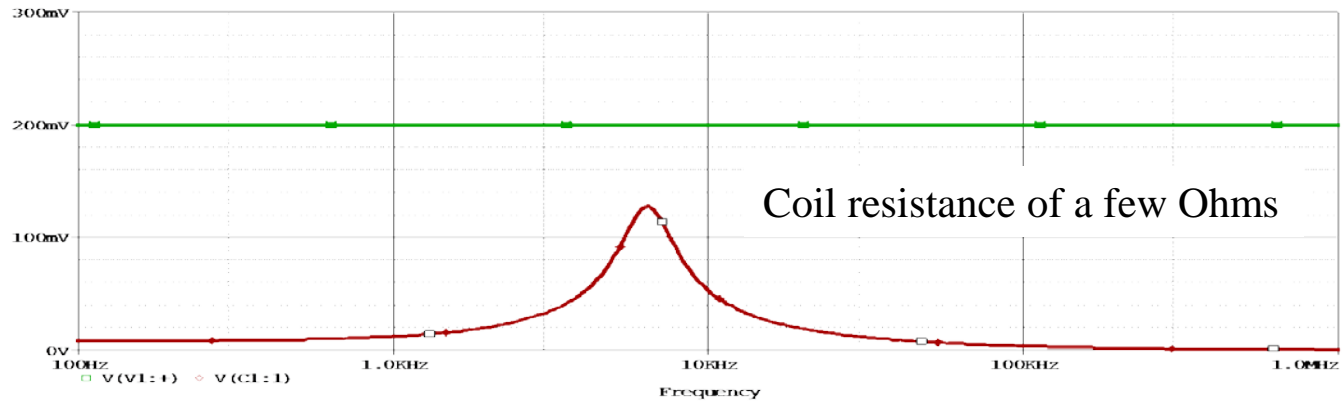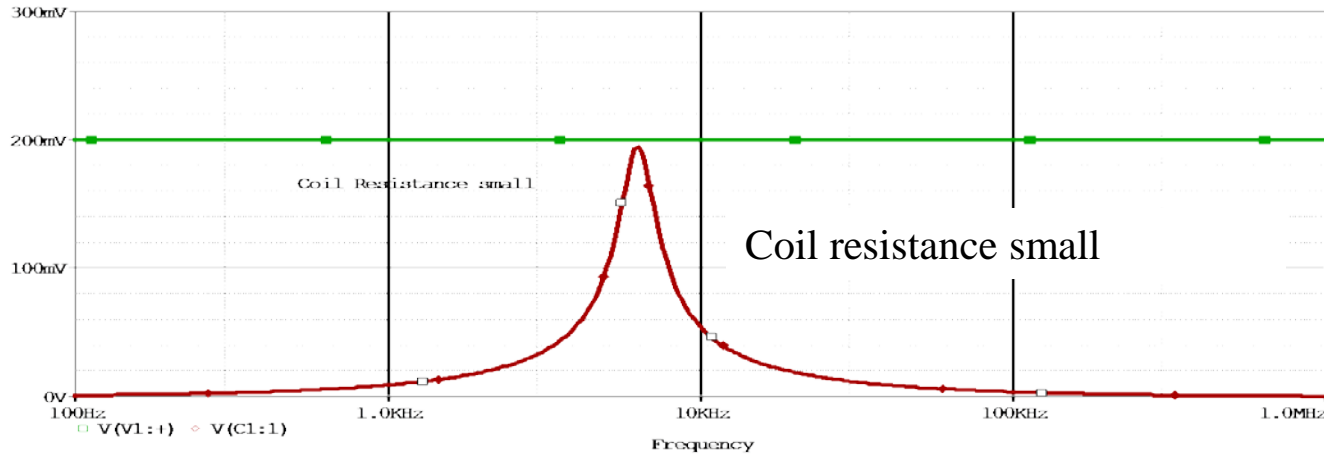- ◆ Even 1 ohm of resistance in the coil can spoil this response somewhat






# *Part C*


- ◆ Examples of Transformers
- ◆ Transformer Equations

# Transformers

- ◆ Cylinders (solenoids)
- ◆ Toroids

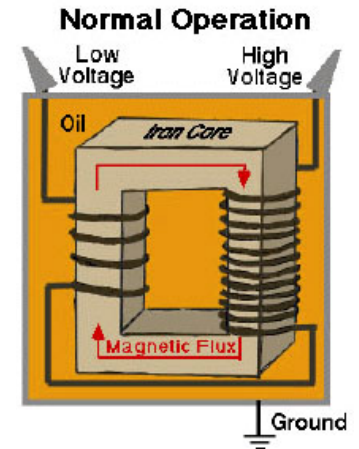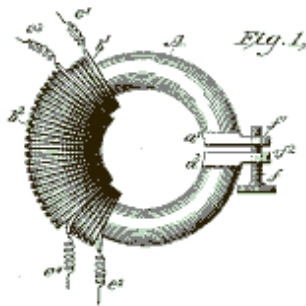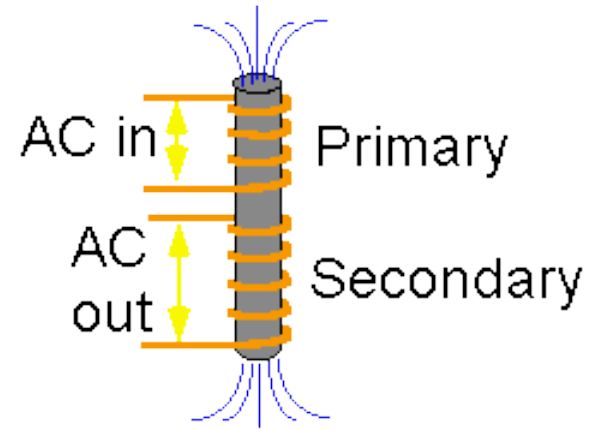

# Transformer Equations

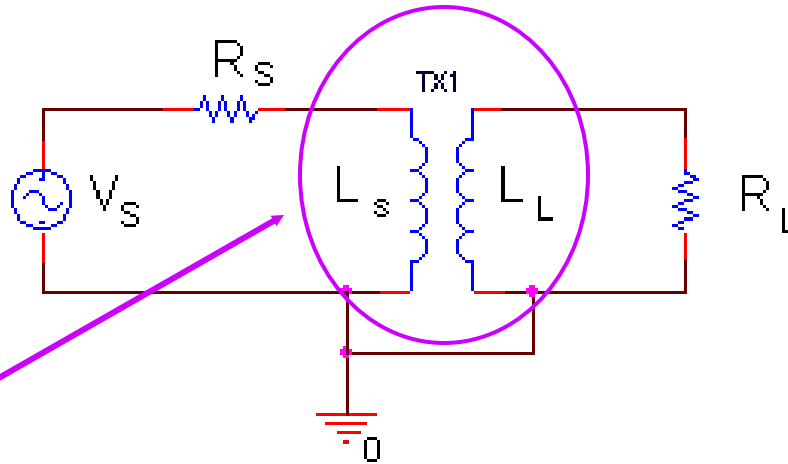


Symbol for  
transformer


$$a = \frac{N_L}{N_S} = \frac{V_L}{V_S} = \sqrt{\frac{L_L}{L_S}} = \frac{I_S}{I_L} \quad Z_{in} = \frac{R_L}{a^2}$$
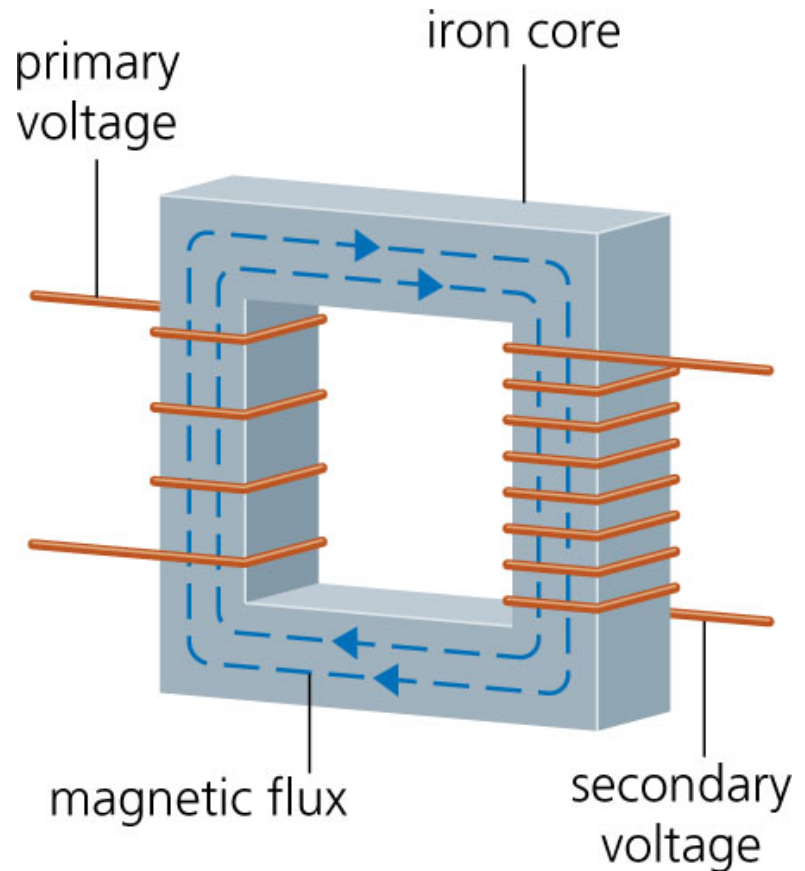
# Deriving Transformer Equations

- ◆ Note that a transformer has two inductors. One is the primary (source end) and one is the secondary (load end):  $L_S$  &  $L_L$
- ◆ The inductors work as expected, but they also couple to one another through their mutual inductance:  $M^2 = k^2 L_S L_L$



# Transformers

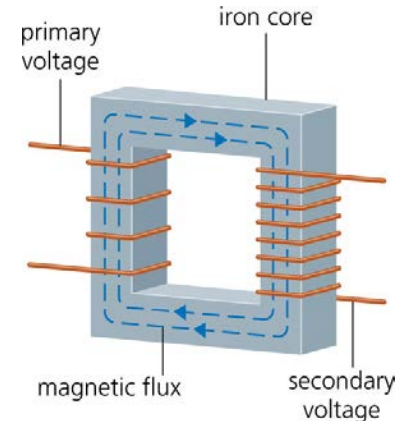


- ◆ Assumption 1: Both Inductor Coils must have similar properties: same coil radius, same core material, and same length.

$$\frac{L_L}{L_S} = \frac{\frac{(\mu_0 N_L^2 \pi r_c^2)}{d}}{\frac{(\mu_0 N_S^2 \pi r_c^2)}{d}} = \frac{N_L^2}{N_S^2} \quad \text{let } a = \frac{N_L}{N_S} \quad \therefore a = \sqrt{\frac{L_L}{L_S}}$$

# Transformers

Note Current Direction

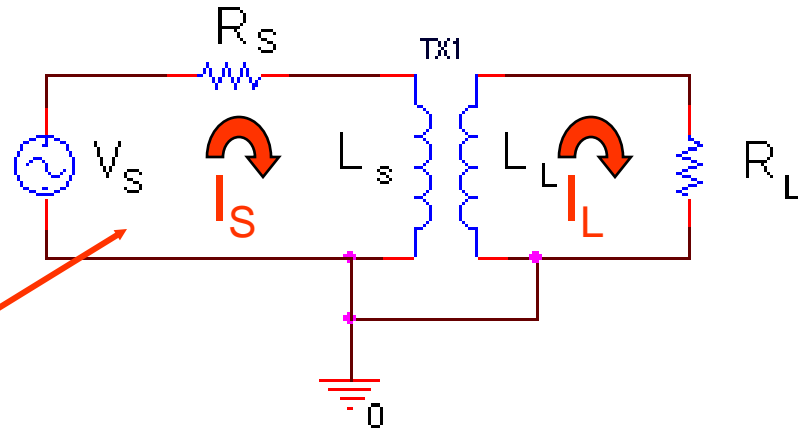


- ◆ Let the current through the primary be  $I_s$
- ◆ Let the current through the secondary be  $I_L$
- ◆ The voltage across the primary inductor is

$$j\omega L I_s - j\omega M I_L$$

- ◆ The voltage across the secondary inductor is

$$j\omega L I_L - j\omega M I_s$$

# Transformers

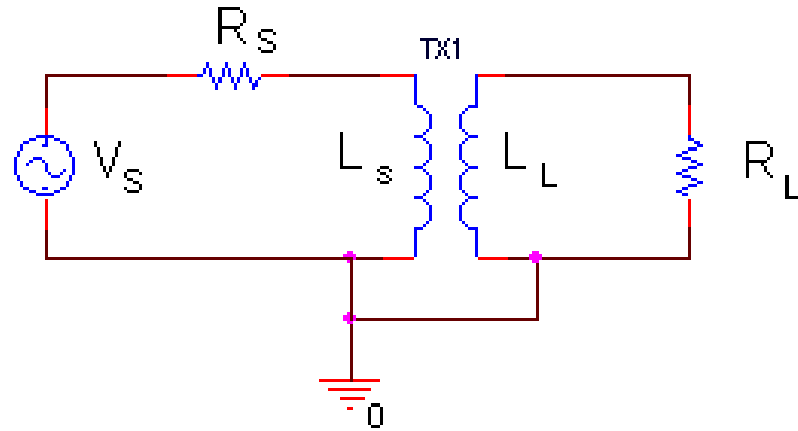

- ◆ Sum of primary voltages must equal the source


$$V_s = R_s I_s + j\omega L_s I_s - j\omega M I_L$$

- ◆ Sum of secondary voltages must equal zero

$$0 = R_L I_L + j\omega L_L I_L - j\omega M I_s$$



# Transformers

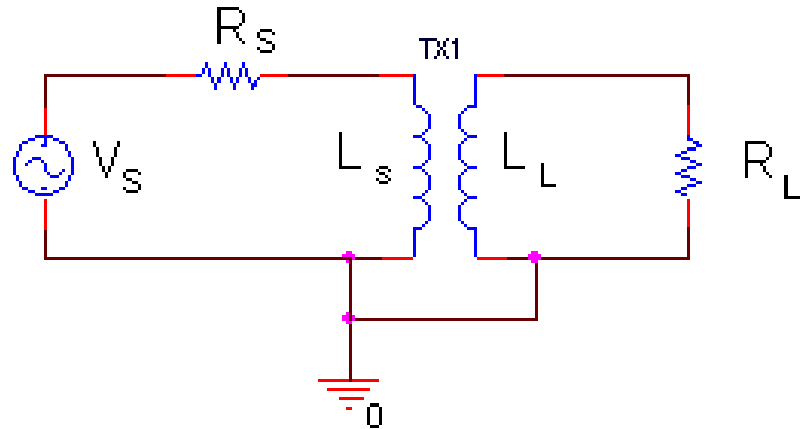


- ◆ Assumption 2: The transformer is designed such that the impedances  $Z = j\omega L$  are much larger than any resistance in the circuit. Then, from the second loop equation

$$0 = \cancel{R_L I_L} + j\omega L_L I_L - j\omega M I_S$$

$$j\omega L_L I_L \approx j\omega M I_S \quad \Rightarrow \quad L_L^2 I_L^2 \approx M^2 I_S^2$$

$$\therefore \frac{I_L}{I_S} \approx \frac{M}{L_L}$$

# Transformers

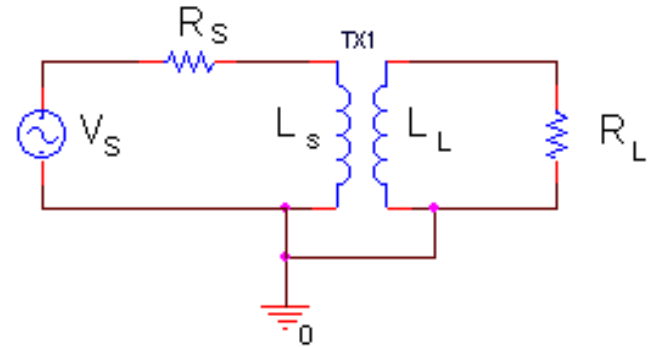


- ◆  $k$  is the coupling coefficient
  - If  $k=1$ , there is perfect coupling.
  - $k$  is usually a little less than 1 in a good transformer.
- ◆ Assumption 3: Assume perfect coupling ( $k=1$ )

We know  $M^2=k^2 L_S L_L = L_S L_L$  and  $a = \sqrt{\frac{L_L}{L_S}}$

Therefore,  $\therefore \frac{I_L}{I_S} \approx \frac{M}{L_L} = \frac{\sqrt{L_S L_L}}{L_L} = \sqrt{\frac{L_S}{L_L}} = \frac{1}{a}$


# Transformers

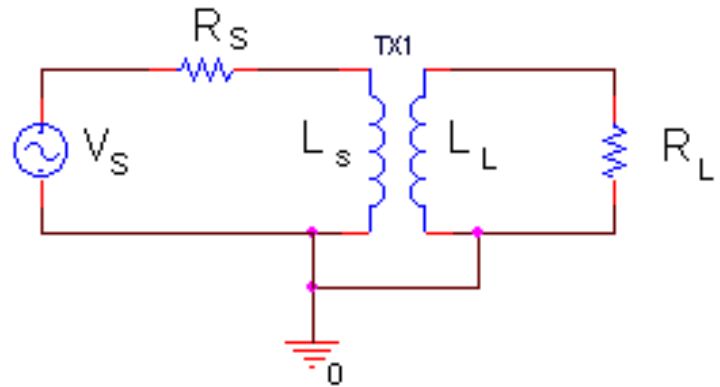

- ◆ The input impedance of the primary winding reflects the load impedance.  $Z_{L_S} = Z_{in} = Z_{total} - R_S$
- ◆ It can be determined from the loop equations
  - 1]  $V_S = R_S I_S + j\omega L_S I_S - j\omega M I_L$
  - 2]  $0 = R_L I_L + j\omega L_L I_L - j\omega M I_S$
- ◆ Divide by 1]  $I_S$ . Substitute 2] and  $M$  into 1]

$$Z_{IN} = \frac{V_S}{I_S} - R_S = j\omega L_S + \frac{\omega^2 L_S L_L}{(R_L + j\omega L_L)}$$

# Transformers

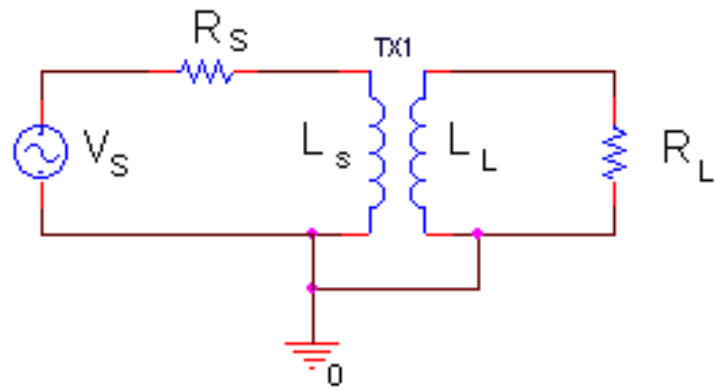


- ◆ Find a common denominator and simplify

$$Z_{IN} = \frac{j\omega L_S R_L}{j\omega L_L + R_L}$$

- ◆ By Assumption 2,  $R_L$  is small compared to the impedance of the transformer, so

$$Z_{IN} = \frac{L_S R_L}{L_L} = \frac{R_L}{a^2}$$

# Transformers

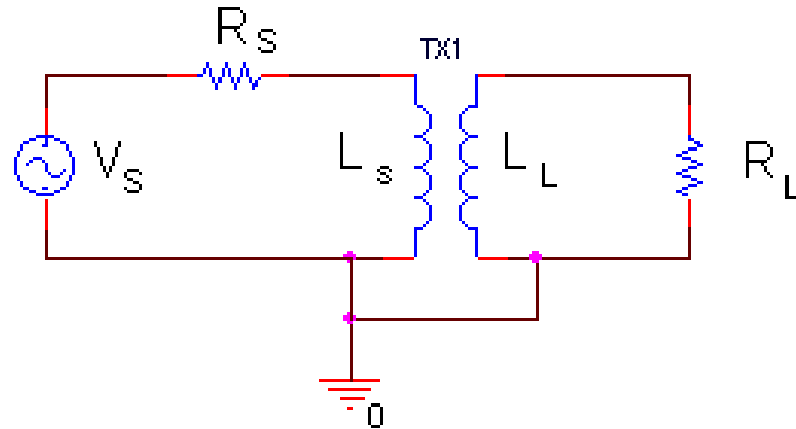


- ◆ It can also be shown that the voltages across the primary and secondary terminals of the transformer are related by

$$N_S V_L = N_L V_S$$

Note that the coil with more turns has the larger voltage.

- ◆ Detailed derivation of transformer equations  
[http://hibp.ecse.rpi.edu/~connor/education/transformer\\_notes.pdf](http://hibp.ecse.rpi.edu/~connor/education/transformer_notes.pdf)

# Transformer Equations

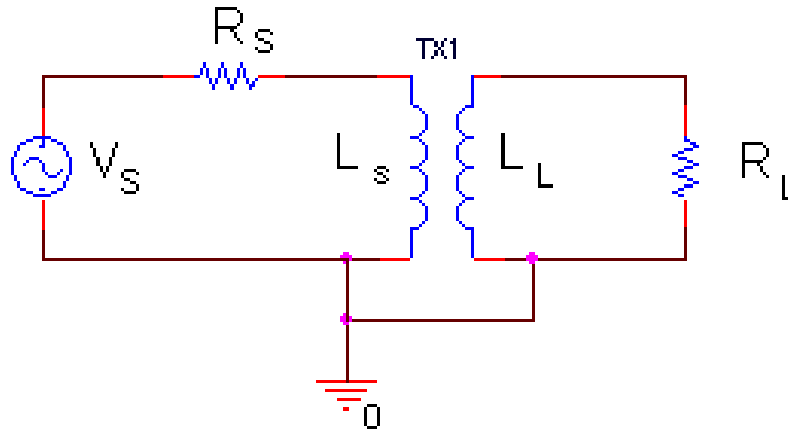

$$a = \frac{N_L}{N_S} = \frac{V_L}{V_S} = \sqrt{\frac{L_L}{L_S}} = \frac{I_S}{I_L} \quad Z_{in} = \frac{R_L}{a^2}$$

# *Part D*

- ◆ Step-up and Step-down transformers
- ◆ Build a transformer

# *Step-up and Step-down Transformers*

Step-up Transformer

$$N_2 > N_1$$

$$V_2 > V_1$$

$$I_2 < I_1$$

$$\sqrt{L_2} > \sqrt{L_1}$$

Step-down Transformer

$$N_2 < N_1$$

$$V_2 < V_1$$

$$I_2 > I_1$$

$$\sqrt{L_2} < \sqrt{L_1}$$

Note that power ( $P=VI$ ) is conserved in both cases.




# *Build a Transformer*

- ◆ Wind secondary coil directly over primary coil
- ◆ “Try” for half the number of turns
- ◆ At what frequencies does it work as expected with respect to voltage? When is  $\omega L \gg R$ ?



$$a = \frac{N_L}{N_S} = \frac{V_L}{V_S}$$

# *Some Interesting Inductors*

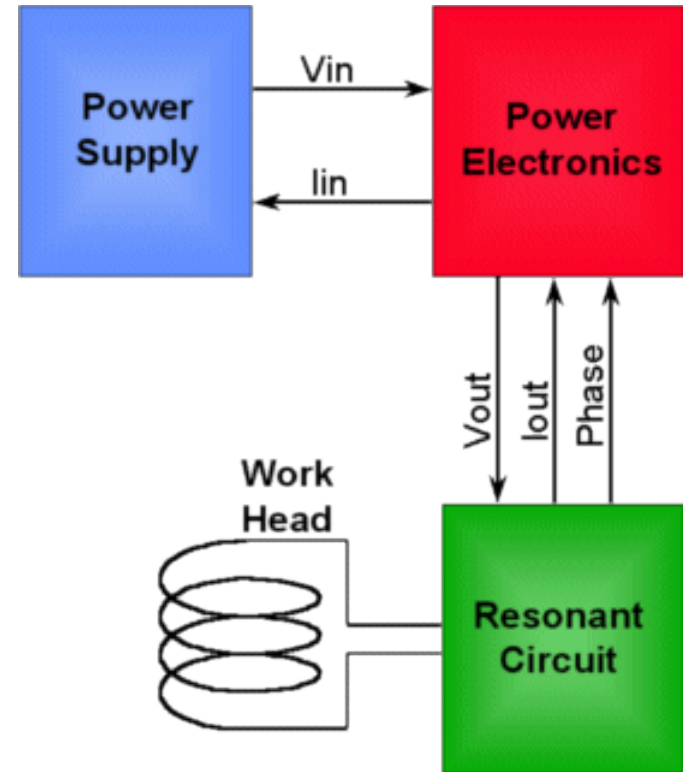



- ◆ Induction Heating

# *Some Interesting Inductors*

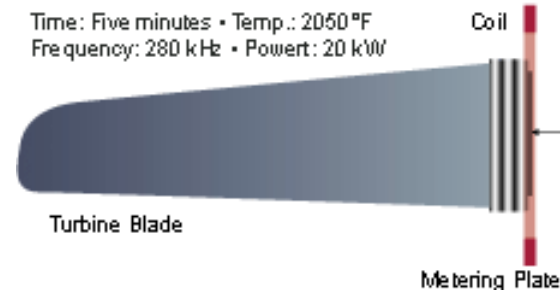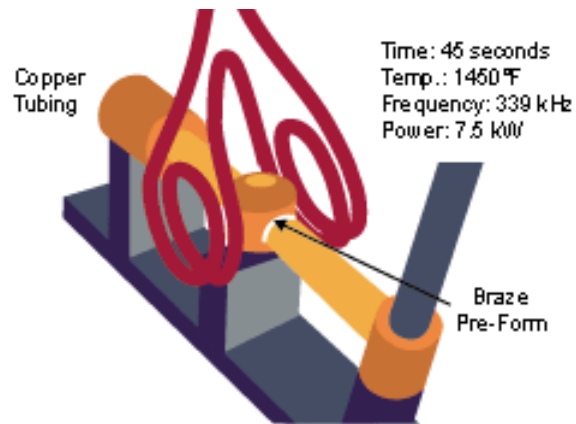

## ◆ Induction Heating in Aerospace

# *Some Interesting Inductors*

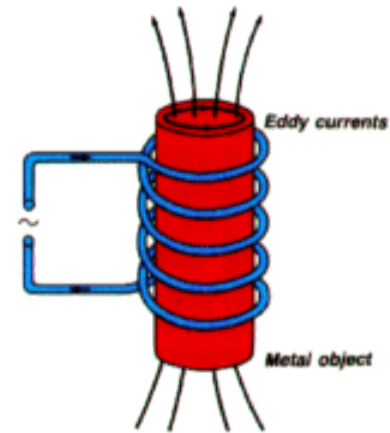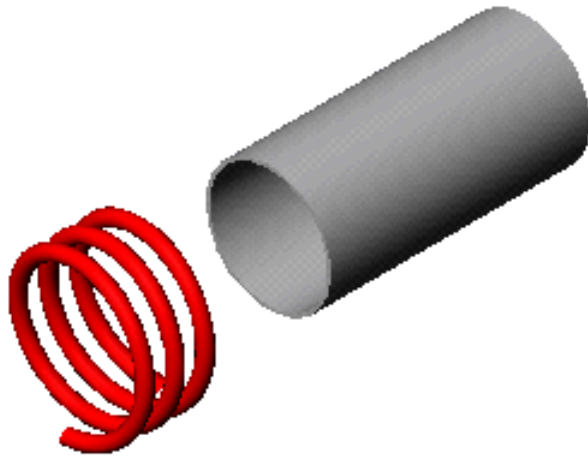


- ◆ Induction Forming


# *Some Interesting Inductors*



Primary  
Coil

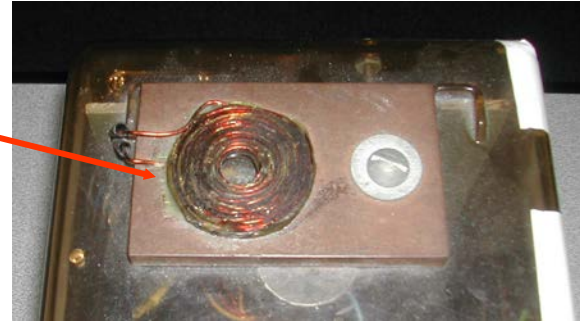

Secondary  
Coil

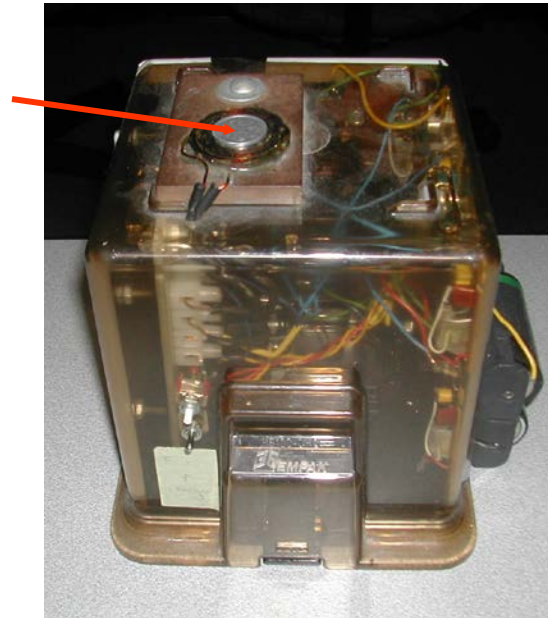

◆ Coin Flipper

# *Some Interesting Inductors*



## ◆ GE Genura Light


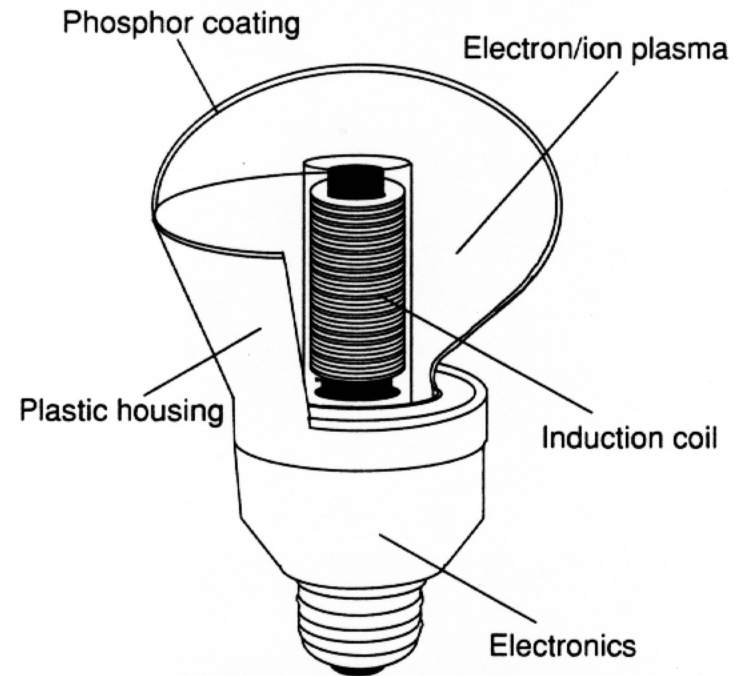


Figure 1. Schematic of the Genura induction lamp. The power supply converts ordinary 60 or 50 hertz current into high-efficiency power that is fed into an electrical coil. The coil excites a gas plasma inside the bulb, releasing UV radiation that strikes the bulb's phosphor coating and is converted into visible light.

Katherine Falk

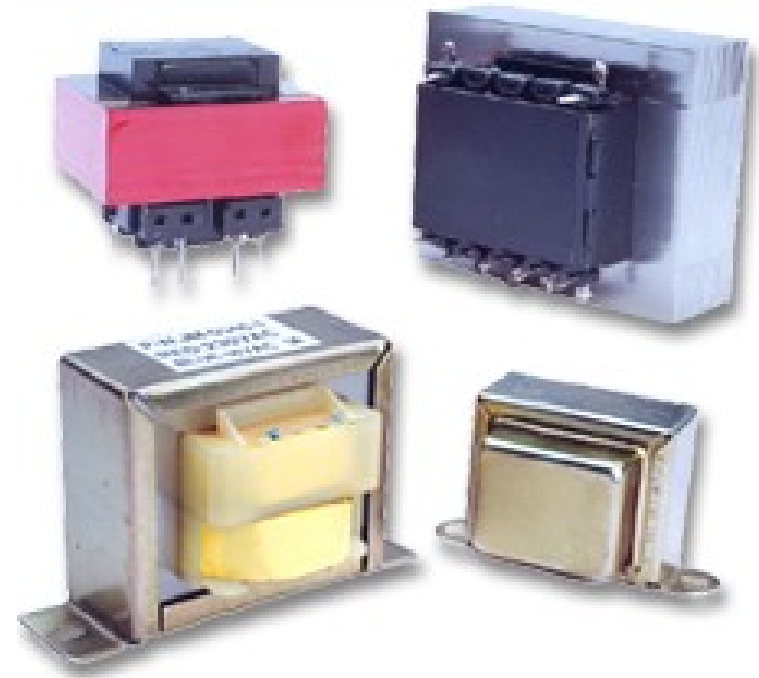


# *Some Interesting Transformers*



- ◆ A huge range in sizes



# *Some Interesting Transformers*

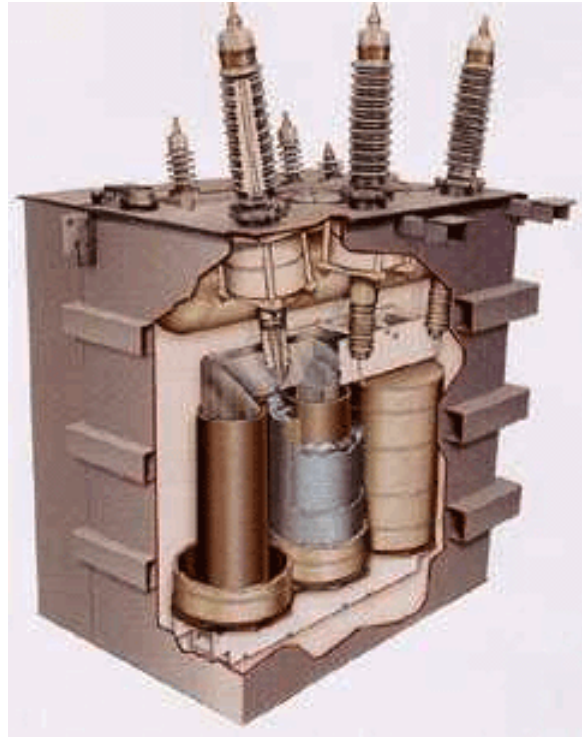

- ◆ High Temperature Superconducting Transformer




# Household Power

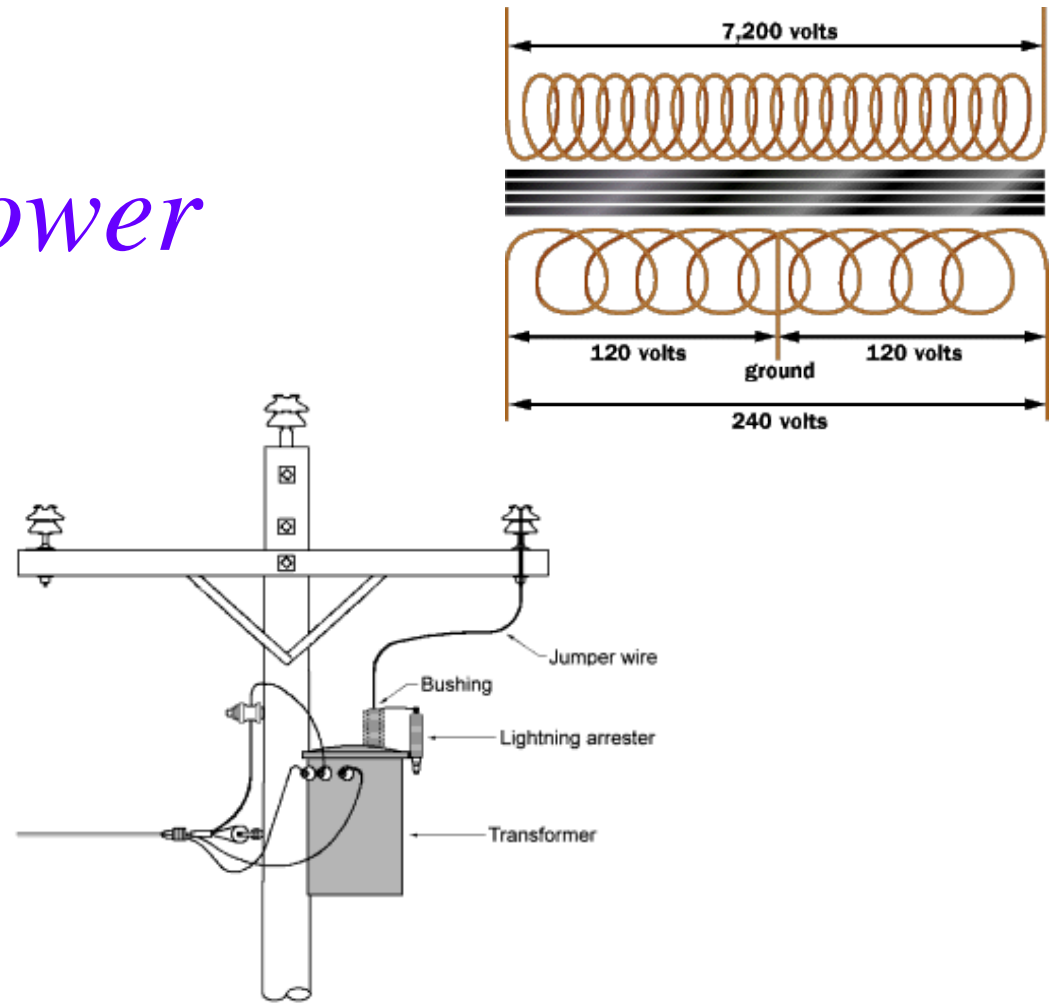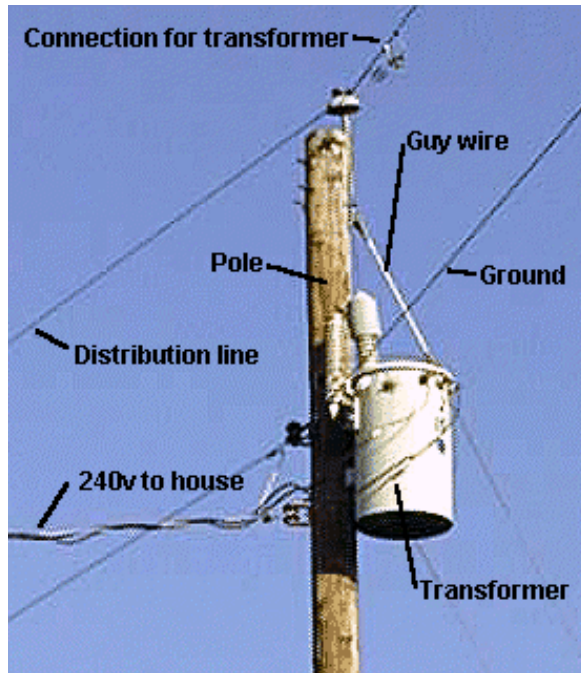

- ◆ 7200V transformed to 240V for household use

# Wall Warts

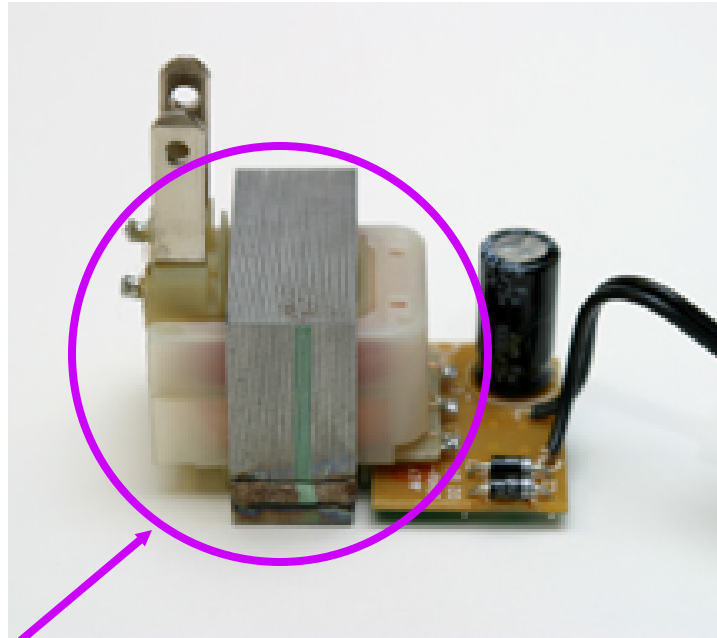

Transformer