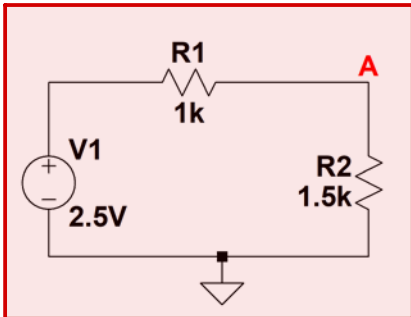


2. Design Problems (15 points)

For the two design problems below, your answers should include a clearly drawn (by hand or LTspice) schematic of the circuit and should also include handwritten work/explanation justifying your design methodology. Indicate which node/nodes satisfy the design criterion.


Part a) (5 points) Design a circuit such that there is a node with voltage 1.5V. Constraint: Use one voltage source of value 2.5 V.



Many correct answers possible.
One simplistic approach presented.

$$V_A = V_1 \left(\frac{1.5K}{1.5K + 1K} \right) = 1.5 V$$

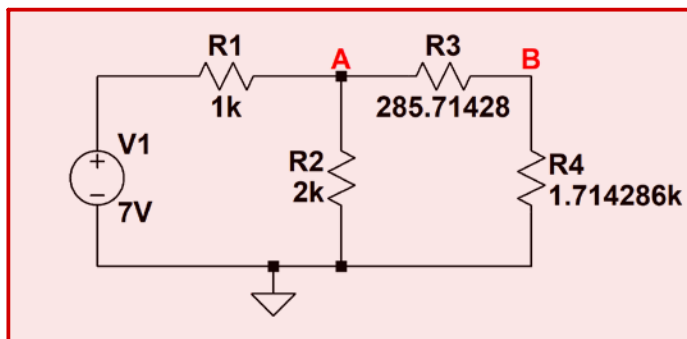Part b) (10 points) Design any circuit (any combination of resistors and source voltages) that has a node with 3.5 V and a node with 3V. Neither of those nodes can be connected to a voltage source.




Many correct answers possible.
One simplistic approach presented.

$$V_A = 3.5 V$$

$$V_B = 3 V$$

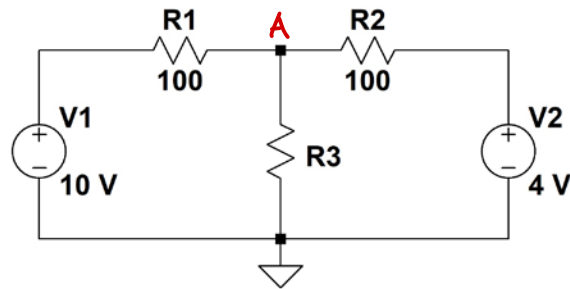3. Nodal Analysis (20 points)

Consider the circuit shown below. The voltage across R3 is 6 V.



Part a) (10 points) Determine the value of resistance R3 using nodal analysis such that the voltage across it is 6 V. Show handwritten work.

KCL @ node A

$$\frac{V_A - V_1}{R_1} + \frac{V_A - V_2}{R_2} + \frac{V_A - 0}{R_3} = 0$$


$$\Rightarrow \frac{V_A - 10}{100} + \frac{V_A - 4}{100} + \frac{V_A}{R_3} = 0$$

$$\Rightarrow V_A - 10 + V_A - 4 + \frac{100 V_A}{R_3} = 0$$

$$\Rightarrow \frac{100 V_A}{R_3} = 14 - 2 V_A$$

$$\Rightarrow R_3 = \frac{100 V_A}{14 - 2 V_A} \stackrel{V_A = 6V}{=} \frac{600}{2} = \boxed{300 \Omega}$$

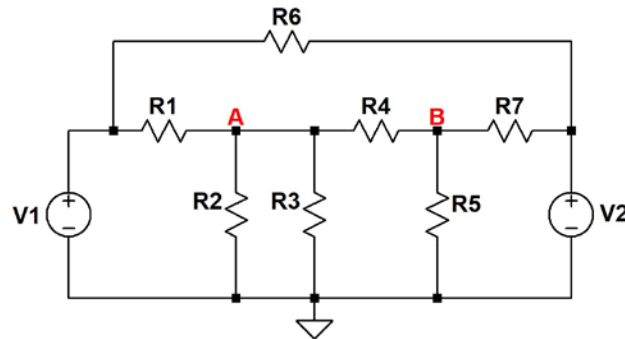Consider a new circuit shown below. Answer part b based on new circuit.



Part b) (10 points) Use nodal analysis to find the matrix equation, $Ax = b$. All your terms should be symbolic (no numbers needed). Your final answer should be expressed as a matrix equation as shown below. V_A and V_B are nodal voltages at nodes A and B respectively.

KCL @ node A

$$\frac{V_A - V_1}{R_1} + \frac{V_A}{R_2} + \frac{V_A}{R_3} + \frac{V_A - V_B}{R_4} = 0$$

$$\Rightarrow V_A \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right] - \frac{V_B}{R_4} = \frac{V_1}{R_1}$$

KCL @ node B

$$\frac{V_B - V_2}{R_7} + \frac{V_B}{R_5} + \frac{V_B - V_A}{R_4} = 0$$

$$-\frac{V_A}{R_4} + V_B \left[\frac{1}{R_7} + \frac{1}{R_5} + \frac{1}{R_4} \right] = \frac{V_2}{R_7}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_4} & \frac{1}{R_7} + \frac{1}{R_5} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} V_1/R_1 \\ V_2/R_7 \end{bmatrix}$$

4. Matrix Solutions (20 points)

Using matrix reductions techniques applied in the experiments, solve (by hand) for the unknown values in the above matrix expression. You must show your matrix reduction work.

$$\begin{bmatrix} -1 & 1 & -4 \\ -2 & 2 & -5 \\ 0 & 2 & 7 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 5 \\ 4 \end{bmatrix}$$

Several ways to solve.

$$R_2 = R_2 - 2 \times R_1$$

$$\begin{bmatrix} -1 & 1 & -4 \\ 0 & 0 & 3 \\ 0 & 2 & 7 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 3 \\ 4 \end{bmatrix}$$


Using 2nd row $\Rightarrow 3x_3 = 3 \Rightarrow x_3 = 1$

Using 3rd row $\Rightarrow 2x_2 + 7x_3 = 4$
 $\Rightarrow 2x_2 = 4 - 7 = -3$
 $\Rightarrow x_2 = -1.5$

Using 1st row $\Rightarrow -x_1 + x_2 - 4x_3 = 1$
 $\Rightarrow -x_1 - 1.5 - 4 = 1$
 $\Rightarrow x_1 = -1.5 - 4 - 1 = -6.5$

5. Voltage Dividers (25 points)

Consider the circuit diagram shown below. The voltage source is a 10 V supply. R_3 is 10 ohms. R_1 , R_2 , and R_4 are unknown resistors. The current through R_3 is i_m as shown.

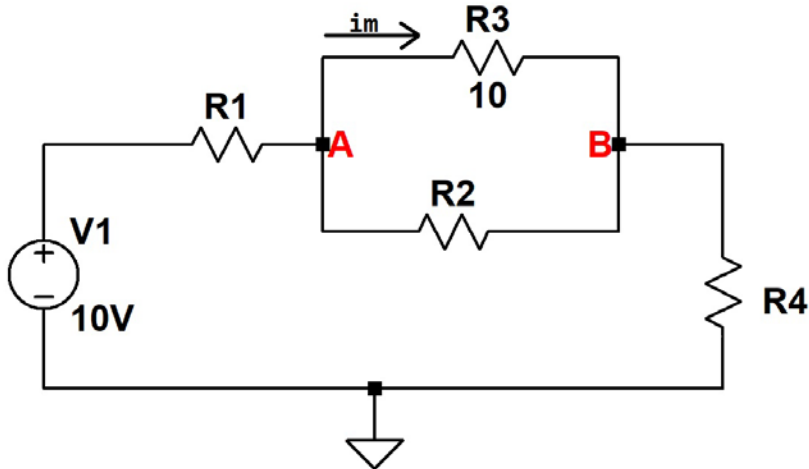

Case 1: Given that when $R_4 = 0$ ohms, the current through resistor R_3 is 2 mA, i.e. $i_m = 2$ mA.

Case 2: Given that when $R_4 = 2000$ ohms, current through resistor R_3 is 1 mA, i.e. $i_m = 1$ mA.

Part a) (3 points) Find voltage between points A and B for each of the cases described above?

$$\text{Case 1: } V_{AB} = i_m R_3 = 20 \text{ mV}$$

$$\text{Case 2: } V_{AB} = i_m R_3 = 10 \text{ mV}$$

Part b) (2 points) What is the equivalent resistance between points A and B, R_{AB} ? (Express in terms of R_2).

$$R_{AB} = R_2 \parallel R_3 = \frac{10 R_2}{10 + R_2}$$

Part c) (5 points) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 1.

$$V_{AB} = 20 \text{ mV} = V_1 \left(\frac{R_{AB}}{R_1 + R_{AB} + R_4} \right)$$

(Handwritten annotations: 10V above the fraction, 0Ω below the denominator)

$$\Rightarrow (R_1 + R_{AB}) 2 \text{ mV} = R_{AB} \cdot 10 \text{ V}$$

$$\Rightarrow R_1 + \frac{10 R_2}{10 + R_2} = \frac{5000 R_2}{10 + R_2} \Rightarrow 10 R_1 - 4990 R_2 + R_1 R_2 = 0$$

Equation 1

Part d) (10 points) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 2.

$$V_{AB} = 10\text{mV} = \underset{\substack{\downarrow \\ 10\text{V}}}{V_1} \left(\frac{R_{AB}}{R_1 + R_{AB} + R_4} \right) \quad \leftarrow 2000\Omega$$

$$\Rightarrow \left(R_1 + \frac{10R_2}{10+R_2} + 2000 \right) 1\text{mV} = \frac{10R_2}{10+R_2}$$

$$\Rightarrow \boxed{10R_1 - 7990R_2 + R_1R_2 = -20000} \quad \text{equation 2}$$

Part e) (5 points) Solve the linear relationships (any method you want) derived in the previous parts, to determine the values of resistors R_1 and R_2 such that both case 1 and 2 are satisfied.

equation 1 - equation 2

$$\Rightarrow 3000R_2 = 20000 \quad \Rightarrow \boxed{R_2 = 6.667 \Omega}$$


Substitute in equation 1.

$$10R_1 - 33268.33 + 6.667R_1 = 0$$

$$\Rightarrow \boxed{R_1 = 1996 \Omega}$$

6. Nodal Analysis – Multiple Sources (20 points)

Consider the circuit shown below.

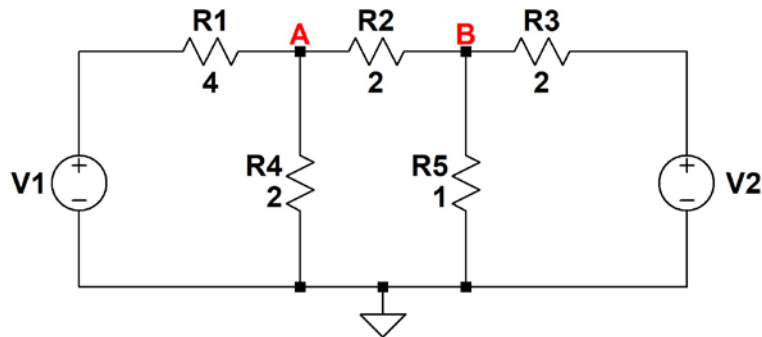

Using nodal analysis techniques, express the voltage at node A and node B in the form, $V_A = aV_1 + bV_2$ and $V_B = cV_1 + dV_2$. In other words, find values for the constants a, b, c, and d.

KCL @ node A

$$\frac{V_A - V_1}{4} + \frac{V_A}{2} + \frac{V_A - V_B}{2} = 0$$

$$\Rightarrow \boxed{1.25 V_A - 0.5 V_B = 0.25 V_1} \quad \text{--- (1)}$$

KCL @ node B

$$\frac{V_B - V_A}{2} + \frac{V_B}{1} + \frac{V_B - V_2}{2} = 0$$

$$\boxed{-0.5 V_A + 2 V_B = 0.5 V_2} \quad \text{--- (2)}$$

From (2). $2V_B = 0.5V_2 + 0.5V_A$

$$\Rightarrow V_B = 0.25V_A + 0.25V_2 \quad \text{--- (3)}$$

Substitute (3) in (1)

$$1.25V_A - 0.125V_A - 0.125V_2 = 0.25V_1$$

$$\Rightarrow 1.125V_A = 0.25V_1 + 0.125V_2$$

$$V_A = \frac{2}{9}V_1 + \frac{1}{9}V_2$$

$\swarrow \rightarrow a$ $\swarrow \rightarrow b$

Substituting V_A in (3)

$$V_B = 0.25 \left[\frac{2}{9}V_1 + \frac{1}{9}V_2 \right] + 0.25V_2$$

$$= \frac{1}{18}V_1 + \frac{1}{36}V_2 + \frac{1}{4}V_2$$

$$V_B = \frac{1}{18}V_1 + \frac{5}{18}V_2$$

$\swarrow \rightarrow c$ $\swarrow \rightarrow d$