

Intro to ECSE

Quiz 2

Fall 2022

1.	/15
2.	/10
3.	/20
Total	/45

Name _____

Notes:

SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Use the backs of pages if there is not enough room on the front.

For partial credit on some questions, you may want to re-draw circuit diagrams as you simplify the circuits.

Many problems can be solved using more than one method. check your answers by using a second method.

At least skim through the entire quiz before you begin and then start with the problems you know best. The proctor will only answer clarification questions where wording is unclear or where there may be errors/typos. No other questions will be responded to.

Problem 1 (15 Points): Nodal Analysis

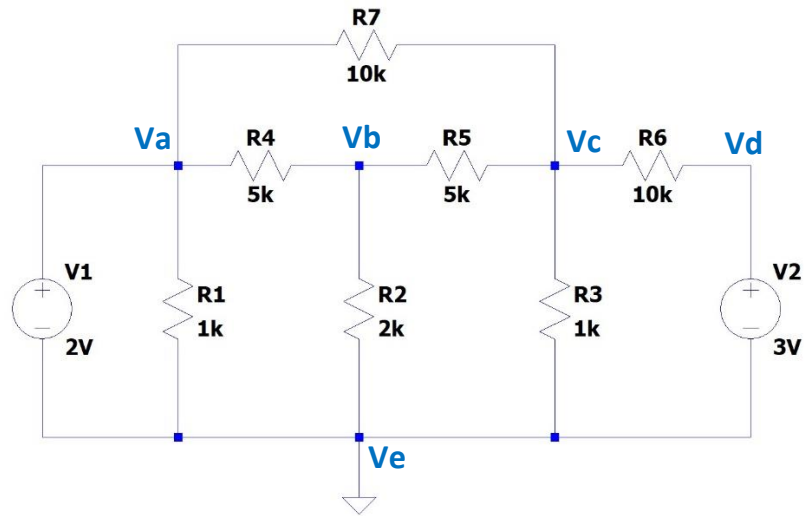


Figure 1

1.1) (2 pts) How many voltage nodes are in this circuit? Label them on the circuit schematic.

There are 5 nodes (1 pt)

Labeled correctly on circuit (1 pt)

1.2) (4 pts) Which of these node voltages are already known (if any)? Write their numerical values on the circuit schematic.

Va = 2V (1 pt)

Vd = 3V (1 pt)

Ve = 0V (1 pt)

Labeled correctly on circuit (1 pt)

1.3) (2 pts) How many linearly-independent equations are needed to solve for all unknowns in this circuit? Why?

of equations = # of nodes - # of voltage sources - 1 = 2 (1 pt)

Explanation (1 pt): There are 5 total nodes. After accounting for voltage sources (2), which each provide a known nodal voltage equal to the individual source voltage, and ground, which provides a known nodal voltage of 0V, only two unknowns are left to solve for, which requires two equations.

1.4) (4 pts) Write down the KCL equation for each node in terms of the nodal voltages you labeled on the schematic in 1.1 and 1.2.

$$\text{At node b: } \frac{Vb-2}{5k} + \frac{Vb-Vc}{5k} + \frac{Vb}{2k} = 0 \quad (2 \text{ pts})$$

$$\text{At node c: } \frac{Vc-Vb}{5k} + \frac{Vc-3}{10k} + \frac{Vc}{1k} + \frac{Vc-2}{10k} = 0 \quad (2 \text{ pts})$$

1.5) (3 pts) Write the equations from 1.4 in matrix form.

In standard form:

$$\text{At node b: } Vb \left(\frac{1}{5k} + \frac{1}{5k} + \frac{1}{2k} \right) + Vc \left(-\frac{1}{5k} \right) = \frac{2}{5k}$$

$$\text{At node c: } Vb \left(-\frac{1}{5k} \right) + Vc \left(\frac{1}{5k} + \frac{1}{10k} + \frac{1}{10k} + \frac{1}{1k} \right) = \frac{2}{10k} + \frac{3}{10k}$$

In matrix form:

$$\begin{matrix} & (1 \text{ pt}) & & (1 \text{ pt}) & & (1 \text{ pt}) \\ \left[\begin{array}{cc} \frac{1}{5k} + \frac{1}{5k} + \frac{1}{2k} & -\frac{1}{5k} \\ -\frac{1}{5k} & \frac{1}{5k} + \frac{2}{10k} + \frac{1}{1k} \end{array} \right] \begin{bmatrix} Vb \\ Vc \end{bmatrix} & = & \begin{bmatrix} \frac{2}{5k} \\ \frac{5}{10k} \end{bmatrix} \end{matrix}$$

Problem 2 (10 pts): Linear and Non-Linear Circuit Elements (Conceptual Questions)

2.1) (2 pts) How can you determine if a circuit element is linear or non-linear?

Explanation (2 pts)

A linear element has an I-V characteristic that is a single straight line for all I and V

OR

A linear element has a single, constant resistance for all I and V


OR

A linear element has a constant resistance that is independent of I and V

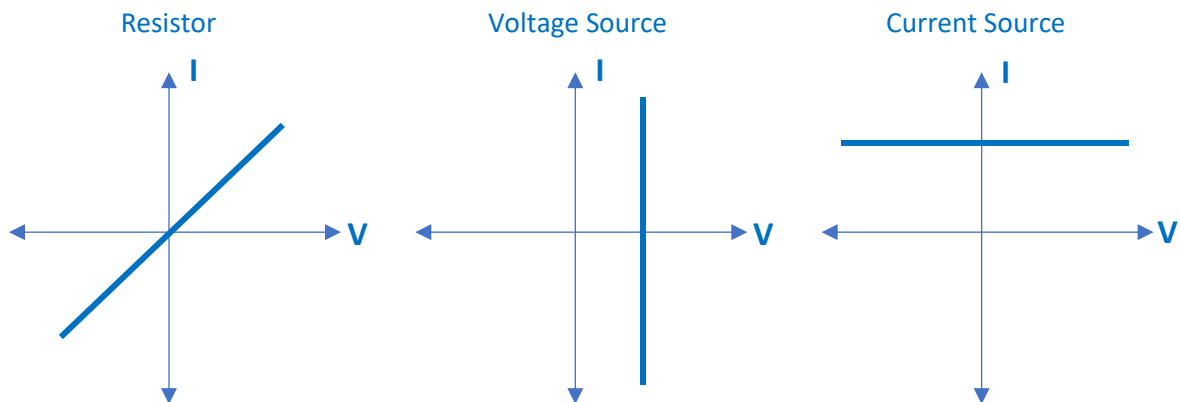2.2) (4 pts) Identify two different linear circuit elements and draw their IV characteristics.

Choose 2 (1 pt each): resistor OR voltage source OR current source

Correct IV characteristic for each chosen circuit element above (1 pt each)



An op-amp circuit is also a valid answer as long as it's a transfer characteristic (V_{out} vs V_{in}) and it is clearly stated/labeled that it must operate in the linear regime.

2.3) (2 pts) The transfer characteristic (V_{out} vs. V_{in}) below belongs to a non-inverting amplifier with a gain of 2. Label the linear region(s) and saturation region(s) of the transfer characteristic.

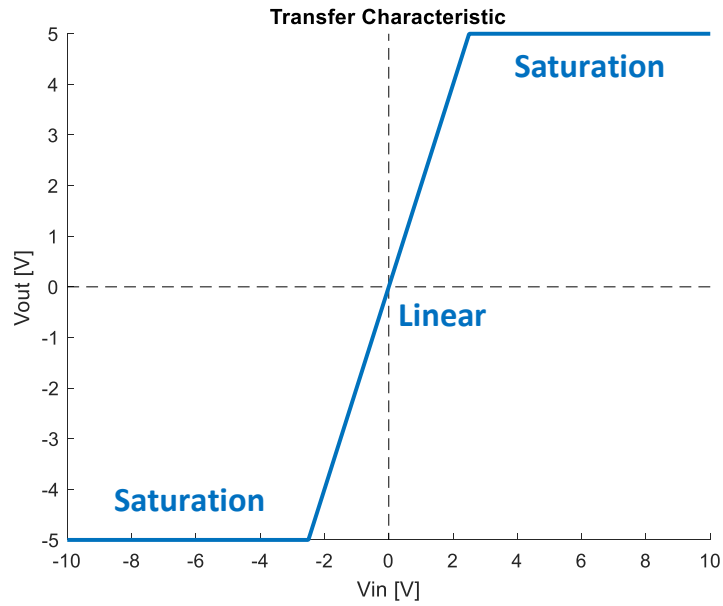


Figure 2

Saturation (1 pt) and linear (1 pt) regions correctly labeled on transfer characteristic.

2.4) (2 pts) A diode is a non-linear circuit element. What does that tell us about its resistance, as opposed to that of linear circuit elements?

Explanation (2 pts): A diode's resistance changes as a function of I and V , so it does not have a constant resistance across all I and V , unlike linear circuit elements.

Problem 3 (20 Pts): Operational Amplifiers

Shown below is a simple circuit for amplifying an audio signal. Assume that U1, U2, and U3 are ideal op-amps. For all parts of this problem, the positive (V_{s+}) and negative (V_{s-}) supply voltages are +5V and -5V. V1 is a sinusoidal wave with an amplitude of 1V.

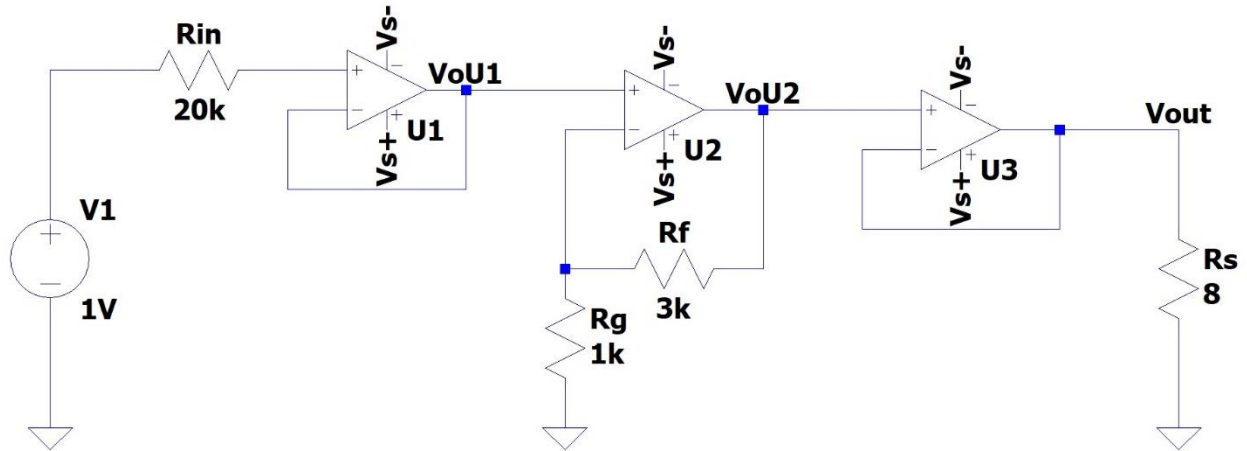


Figure 3

3.1) (3 Pts) What kind of op-amp circuit is stage U1? Write its transfer function both in terms of resistor names (if applicable) and numerically.

Stage U1 is a voltage follower (1 pt)

The transfer function for a voltage follower is $H_1 = 1$ (2 pts)

3.2) (1 Pt) What is the output voltage after stage U1 (V_{oU1})?

$V_{oU1} = H_1 * V_1 = 1 * 1V = 1V$ (1 pt)

3.3) (3 Pts) What kind of op-amp circuit is stage U2? Write its transfer function both in terms of resistor names (if applicable) and numerically.

Stage U2 is a non-inverting amplifier **(1 pt)**

The transfer function for a non-inverting amplifier is: $H2 = \left(1 + \frac{R_f}{R_g}\right)$ **(1 pt)**

$$H2 = \left(1 + \frac{3k}{1k}\right) = 4 \quad \textbf{(1 pt)}$$

3.4) (1 Pt) What is the output voltage after stage U2 (VoU2)?

$$V_{oU2} = H2 * V_{oU1} = 4 * 1V = 4V \quad \textbf{(1 pt)}$$

3.5) (3 Pts) What kind of op-amp circuit is stage U3? Write its transfer function both in terms of resistor names (if applicable) and numerically.

Stage U3 is a voltage follower **(1 pt)**

The transfer function for a voltage follower is $H3 = 1$ **(2 pts)**

3.6) (1 Pt) What is Vout?

$$V_{out} = H3 * V_{oU2} = 1 * 4V = 4V \quad \textbf{(1 pt)}$$

3.7) (2 Pts) What is the overall transfer function H_{total} of the entire circuit in terms of resistor names?

$$H_{total} = H1 * H2 * H3 \quad \textbf{(1 pt)}$$

$$= (1) * \left(1 + \frac{R_f}{R_g}\right) * (1) = \left(1 + \frac{R_f}{R_g}\right) \quad \textbf{(1 pt)}$$

3.8) (3 Pts) Given that $V_{in} = 1V$, what is the maximum gain that stage U2 can have and still ensure that the op-amp circuit does not saturate? If $R_g = 1k\Omega$, what new value of R_f would provide that gain?

$$V_{o,max} = 5V \quad (1 \text{ pt})$$

$$V_{o,max} = V_{in} \left(1 + \frac{R_f}{R_g} \right) \quad (1 \text{ pt})$$

$$5V = 1V \left(1 + \frac{R_f}{1k\Omega} \right) \rightarrow R_f = 4k\Omega \quad (1 \text{ pt})$$

3.9) (3 Pts) Audio systems commonly have an LED indicator that lights up when the audio signal is nearing the maximum voltage that the circuit can output without distorting the signal.

Suppose you are given the following circuit schematic, which compares the input signal (V_{audio}) to a reference voltage (V_{ref}), and are asked to choose resistor values such that the LED (D1) lights up when V_{audio} is greater than V_{ref} and is off when V_{audio} is less than V_{ref} .

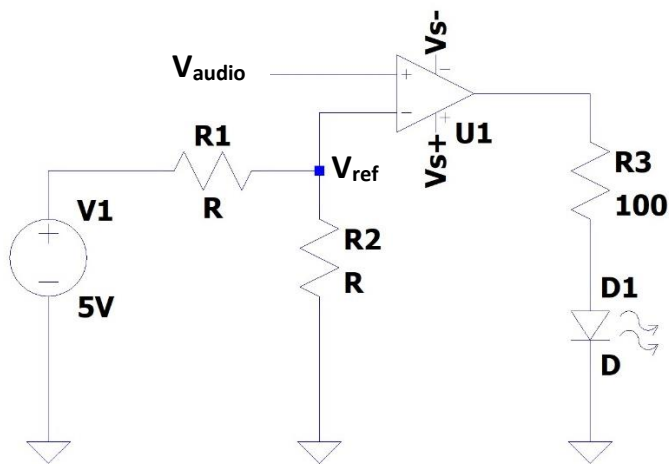


Figure 4

Available Resistors	
1.5kΩ	2.2kΩ
10kΩ	20kΩ

Which values for R_1 and R_2 from the available resistors above would provide a reference voltage of $V_{ref} = 4.5V$ for the circuit? You may use each resistor value only once.

$$V_{ref} = V_1 \frac{R_2}{R_1 + R_2} \quad (1 \text{ pt})$$

$$4.5V = 5V \frac{R_2}{R_1 + R_2} \rightarrow \frac{9}{10} = \frac{R_2}{R_1 + R_2} \rightarrow 9R_1 = R_2$$

Of the possible resistor values, the only two that satisfy the above relationship are $R_2 = 2.2k\Omega$ and $R_1 = 20k\Omega$. (2 pts)

$$\text{Checking the result: } V_{ref} = 5V \frac{20k\Omega}{2.2k\Omega + 20k\Omega} = (5V)(0.901) = 4.50V$$