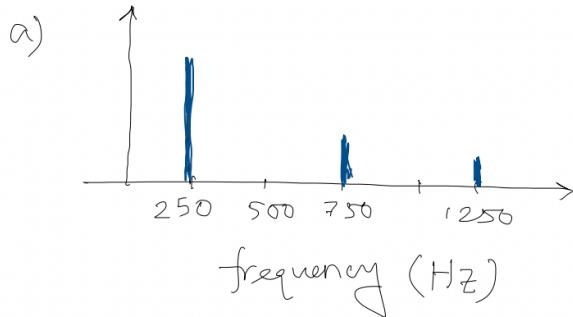


### Problem 1

$$v(t) = \sin(2\pi \cdot \underbrace{250 \cdot t}_{f_1}) + 0.3 \sin(2\pi \cdot \underbrace{750 \cdot t}_{f_2}) \\ + 0.15 \sin(2\pi \cdot \underbrace{1250 \cdot t}_{f_3})$$

1.1




b) The period of  $v(t) = 4 \text{ ms} = 0.004 \text{ s}$

(smallest time after which the signal repeats itself)

$$\therefore \text{fundamental frequency} = \frac{1}{0.004} = 250 \text{ Hz}$$

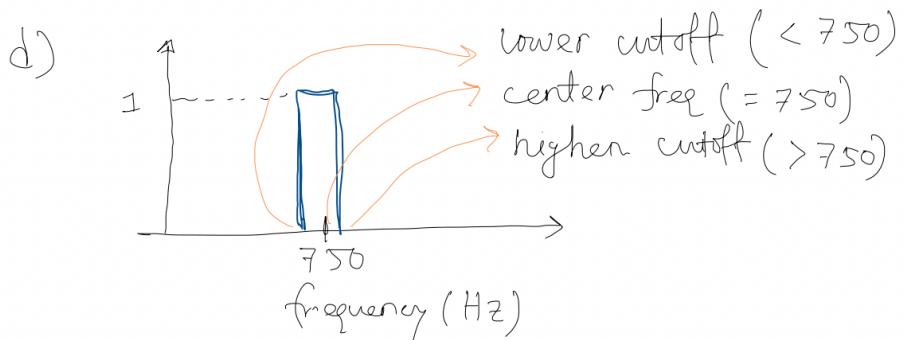c) BPF (band pass filter)


[ because only a band (a frequency for the current case, 750 Hz)  
is being allowed to pass ]



ideal BPF  
= rectangle filter

1.2

Given freq domain representation

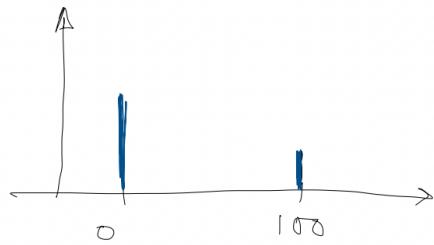


$$\begin{aligned} v(t) &= A_1 \sin(2\pi \cdot 0 \cdot t + \theta_1) \\ &\quad + A_2 \sin(2\pi \cdot 100 \cdot t + \theta_2) \quad \boxed{\checkmark} \\ &= A_1 \sin(\theta_1) + A_2 \sin(200\pi t + \theta_2) \quad \boxed{\checkmark} \\ &= V_{DC} + A_2 \sin(200\pi t + \theta_2) \quad \boxed{\checkmark} \\ &\quad \downarrow \\ &\quad \text{optional} \end{aligned}$$

## Problem 2

2.1

a)

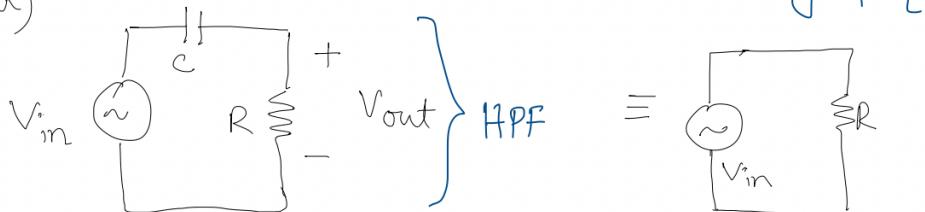

$$b) f_c = \frac{1}{2\pi RC}$$

$$\Rightarrow 6400\pi = \frac{1}{RC}$$


$$\text{when; } C = 10^{-7}; R = 497.359 \Omega$$

$$C = 5 \times 10^{-7}; R = 99.47 \Omega$$

$$C = 10^{-6}; R = 49.73 \Omega$$

so, the closest combination possible
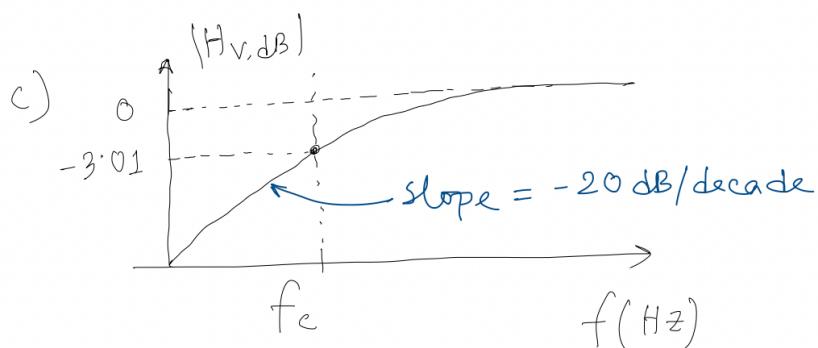
$$\boxed{R = 100 \Omega; C = 5 \times 10^{-7}}$$



$$d) V_{out} = V_{in} \left( \frac{R}{R + \frac{1}{j\omega C}} \right) \quad j\omega = s$$

$$\Rightarrow H(s) = \frac{R}{R + \frac{1}{sC}} = \frac{Rs}{Rs + 1/C}$$

$$\Rightarrow H(s) = \frac{s}{s + \frac{1}{RC}} \quad \& \quad H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}$$

2.2

a)

$$\text{Given: } H(j\omega) = \frac{j\omega}{j\omega + 2 \times 10^3}$$

$$|H(j\omega)| = \sqrt{\left( \frac{j\omega}{j\omega + 2 \times 10^3} \right) \cdot \left( \frac{-j\omega}{-j\omega + 2 \times 10^3} \right)}$$

$$= \sqrt{\frac{\omega^2}{(2 \times 10^3)^2 - (\omega)^2}}$$

$$= \sqrt{\frac{\omega^2}{4 \times 10^6 + \omega^2}}$$

$$b) V_{in} = 2 \sin(\underbrace{1200 t}_{\omega})$$

$$\left| H(1200) \right| = \frac{(1200)^r}{\sqrt{4 \times 10^6 + (1200)^r}}$$

$$= 0.514$$

$$\therefore \text{in decibels} = 20 \log(0.514)$$

$$= -5.772 \text{ dB}$$

$$c) |V_{out}| = |H(1200)| \cdot |V_{in}|$$

$$\Rightarrow |V_{out}| = 0.514 \times 2$$

$$= 1.029 \text{ V}$$

2.3

$$a) V_{out} = V_{in} \cdot \left( \frac{\frac{1}{sC} + sL}{\frac{1}{sC} + sL + R} \right)$$

$$H(s) = \frac{\frac{1}{C} + s^2 L}{\frac{1}{C} + s^2 L + R s}$$


$$= \frac{\frac{1}{LC} + s^2}{\frac{1}{LC} + s^2 + \frac{R}{L} s}$$

$$= \frac{s^2 + \frac{1}{LC}}{s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC}}$$

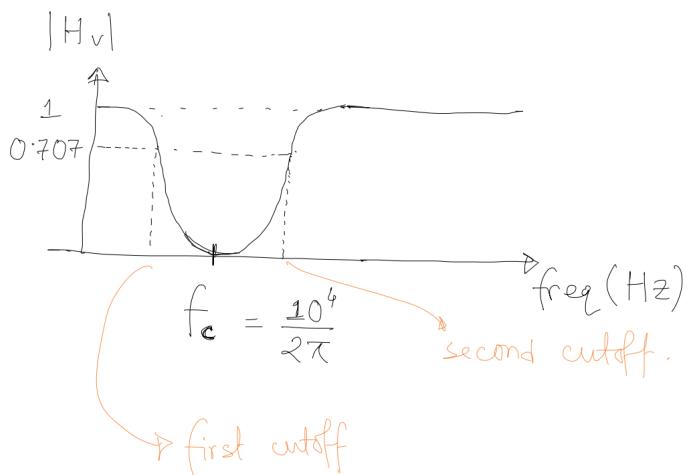b)  $H(s=0) = 1$ ;  $H(s=\infty) = 1$

$$H(s) = 0 \Rightarrow s^2 + \frac{1}{LC} = 0 \Rightarrow \omega^2 = \frac{1}{LC}$$

$$\therefore f_c = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi} \cdot 10^4$$



c) Band stop filter (Notch filter)

### Problem 3

3.1

True  $\rightarrow$  from Fourier series we know this  $\rightarrow$  theoretically True


False  $\rightarrow$  generating sinusoidal waves from -infinity time to 0 time is not practical & impossible.

### 3.2

Square wave consists of infinite amount of sinusoidal waves (from Fourier) having frequencies multiples of the fundamental freq.

Hence; the frequency spectrum of the square wave (signal 1) has more peaks at higher frequencies.


### 3.3

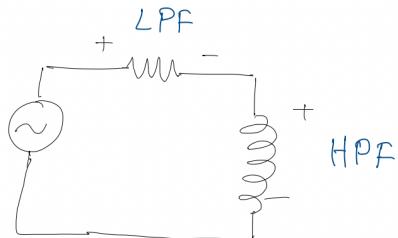

depending on where the  $V_{out}$  is (Across  $R$  or  $L$ ) the circuit can be LPF or HPF

### 3.4

Low Frequency

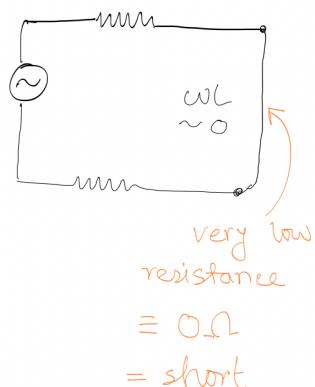

High frequency

