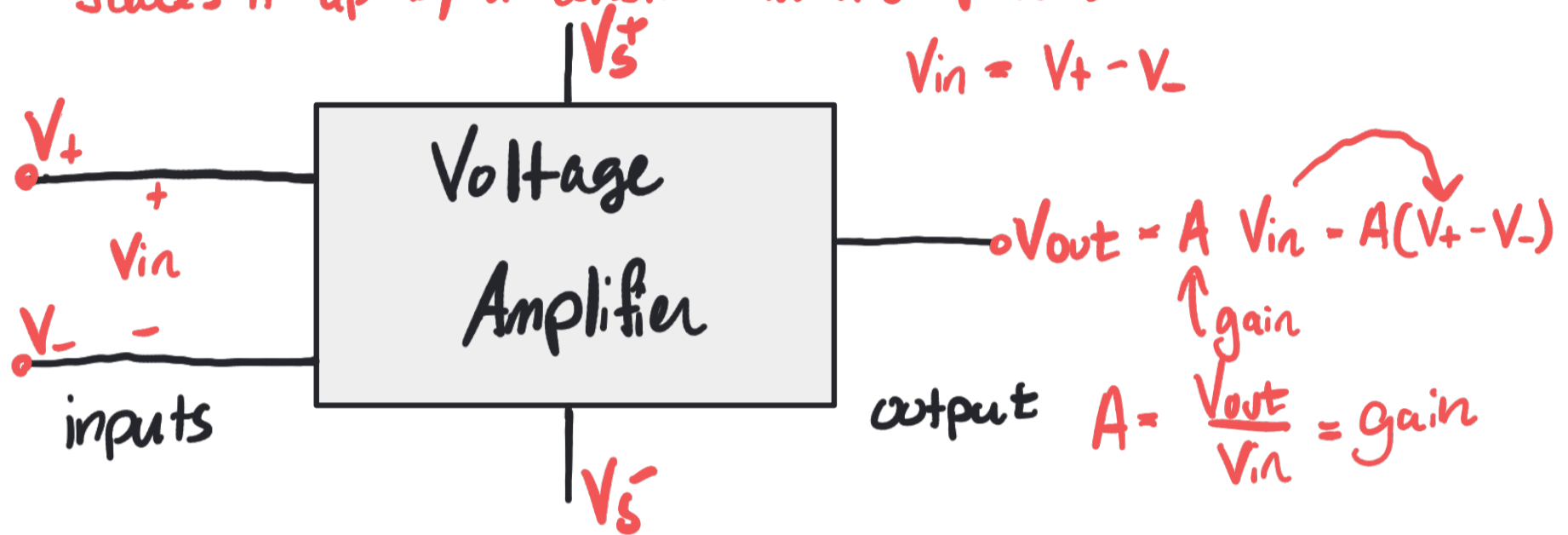


Intro to ECSE Class 14: Operational Amplifiers Pt. 1

1

I] Operational Amplifier (op-amp) Basics


- What is an operational amplifier?
 - **Voltage amplifier**: takes an input voltage, scales it up by a constant and outputs it



- V_s^+ and V_s^- : Supply voltages: give the op-amp the power it needs to amplify a signal
 - you must power your op-amp for it to work (V_s^+ and V_s^- must be connected)

Circuit Symbol

2

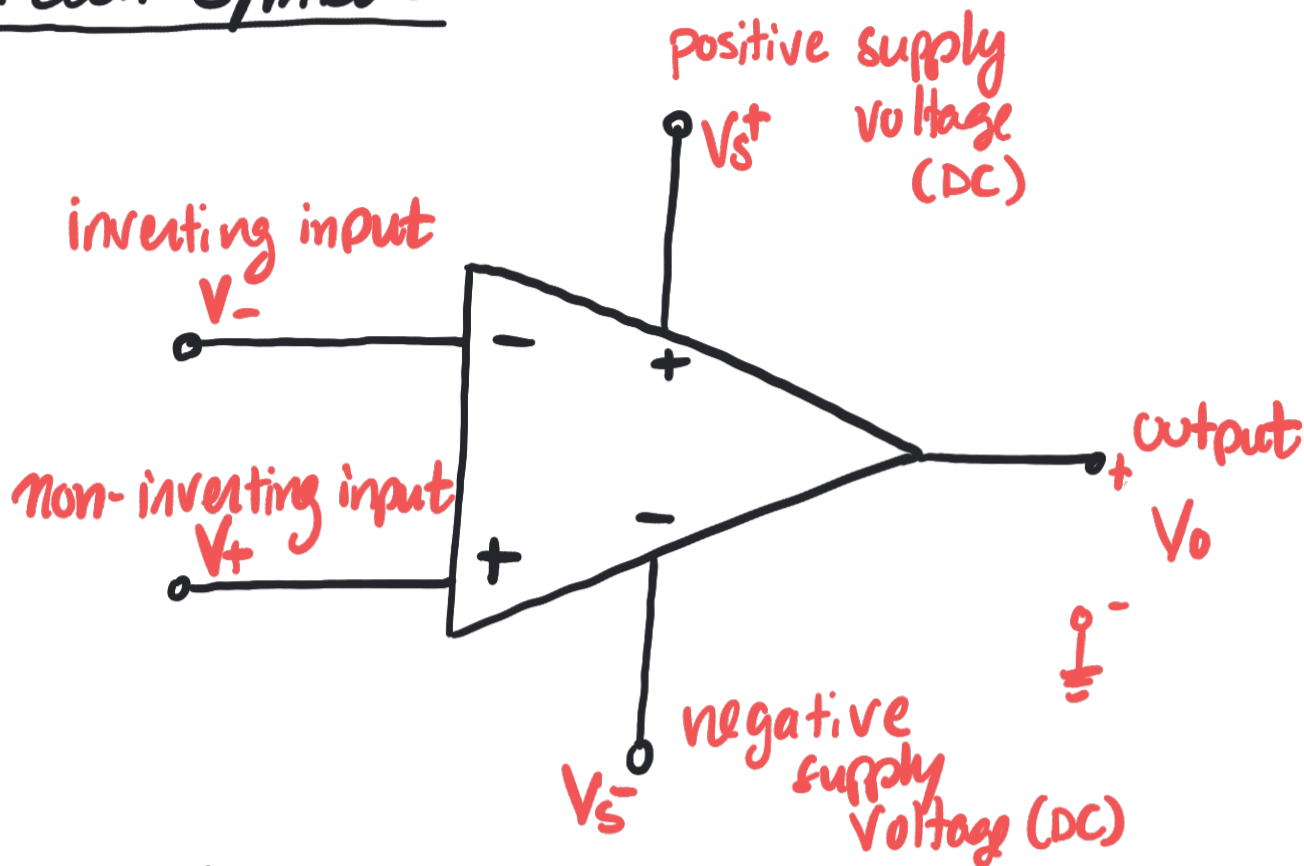


- Inputs/output: $V_{in} = V_+ - V_- \rightarrow V_o = A V_{in}$
Input signal at V_+ and V_- and measure V_o as the output
- Voltage/Power Supply: typically $V_s^- = -V_s^+$ ($V_s^+ = +5V, +9V$
 $V_s^- = -5V, -9V$)
 - some op-amps will allow $V_s^- = 0V$, but you need to check the datasheet
- LTspice: use UniversalOpAmp2 \rightarrow it causes fewer problems

Pinout Diagram


- Specifies which IC (integrated circuit) pins correspond to which terminals on the circuit symbol. Not the same for all op-amps - check the datasheet

LM741 Pinout Diagram

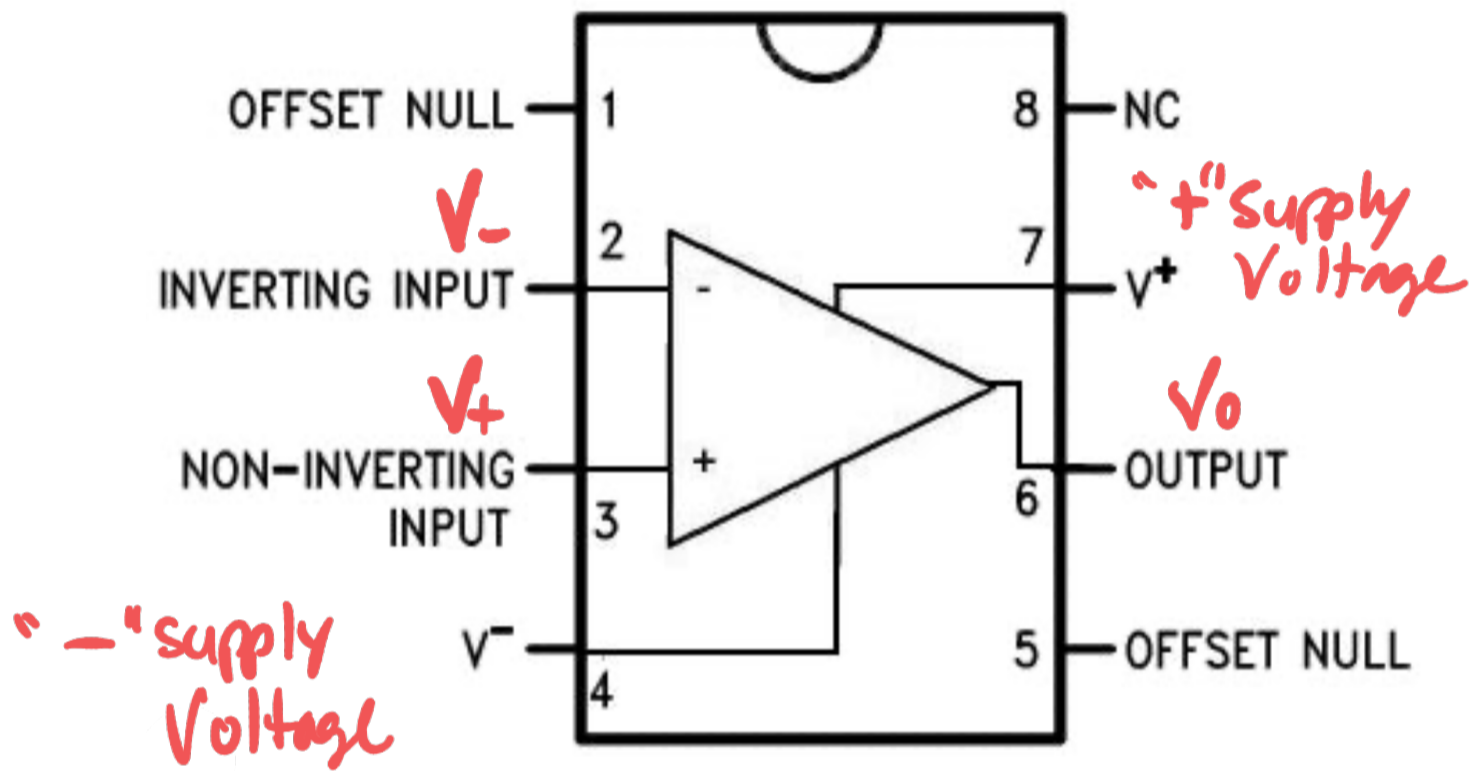


Transfer Characteristic of an open-loop op-amp

- open-loop: no feedback loop

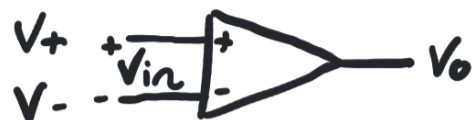

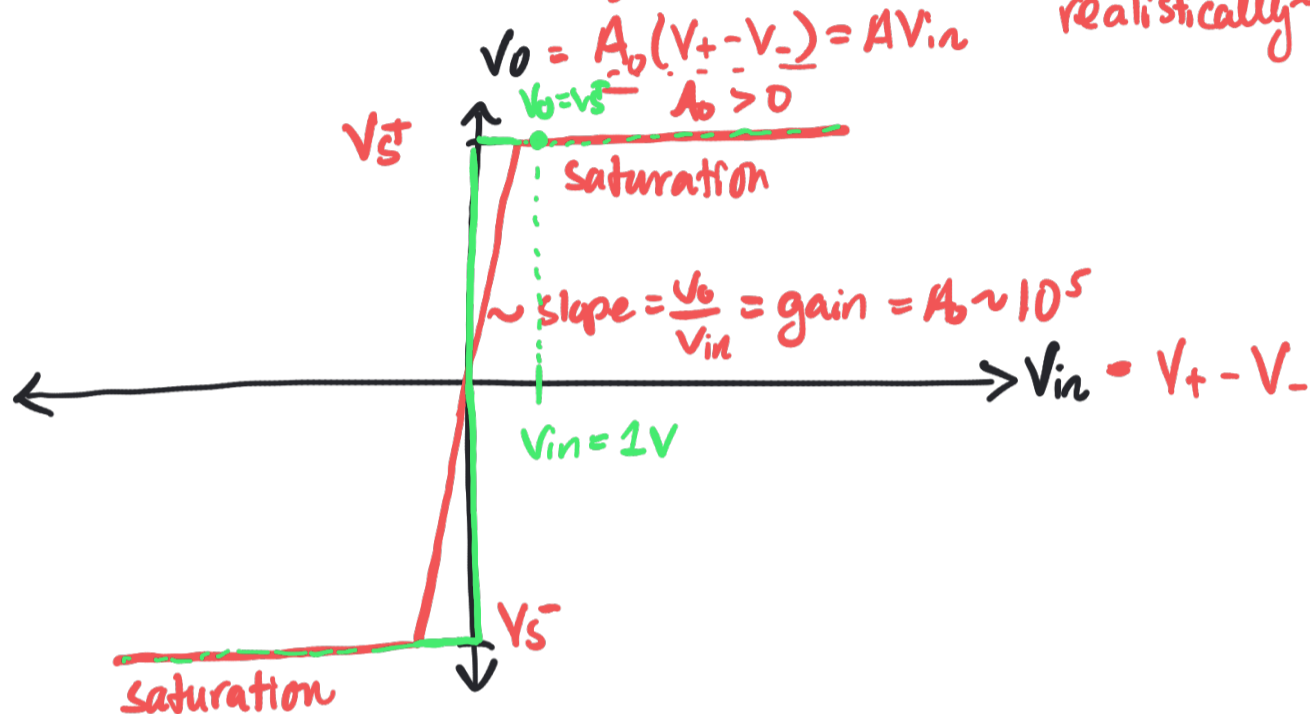- Transfer characteristic: plots V_{out} vs. V_{in}
 "open loop gain" is ideally ∞ , realistically $\sim 10^5$



- Output follows $A_o \times V_{in}$ until we reach V_s^+ or V_s^- , then we say the op-amp "saturates"

- Saturation:** we cannot output voltages larger than V_s^+ or smaller than V_s^-

- What is the function of an open-loop op-amp?

- it functions as a zero-crossing detector (comparator)

- it compares V_+ to V_- (recall $V_{in} = V_+ - V_-$)


- if $V_+ > V_-$, $V_{in} > 0$, $V_o = AV_{in} \rightarrow V_s^+$

- if $V_+ < V_-$, $V_{in} < 0$, $V_o = AV_{in} \rightarrow V_s^-$

- This is a decision-making circuit

The Ideal Op-Amp Model


5

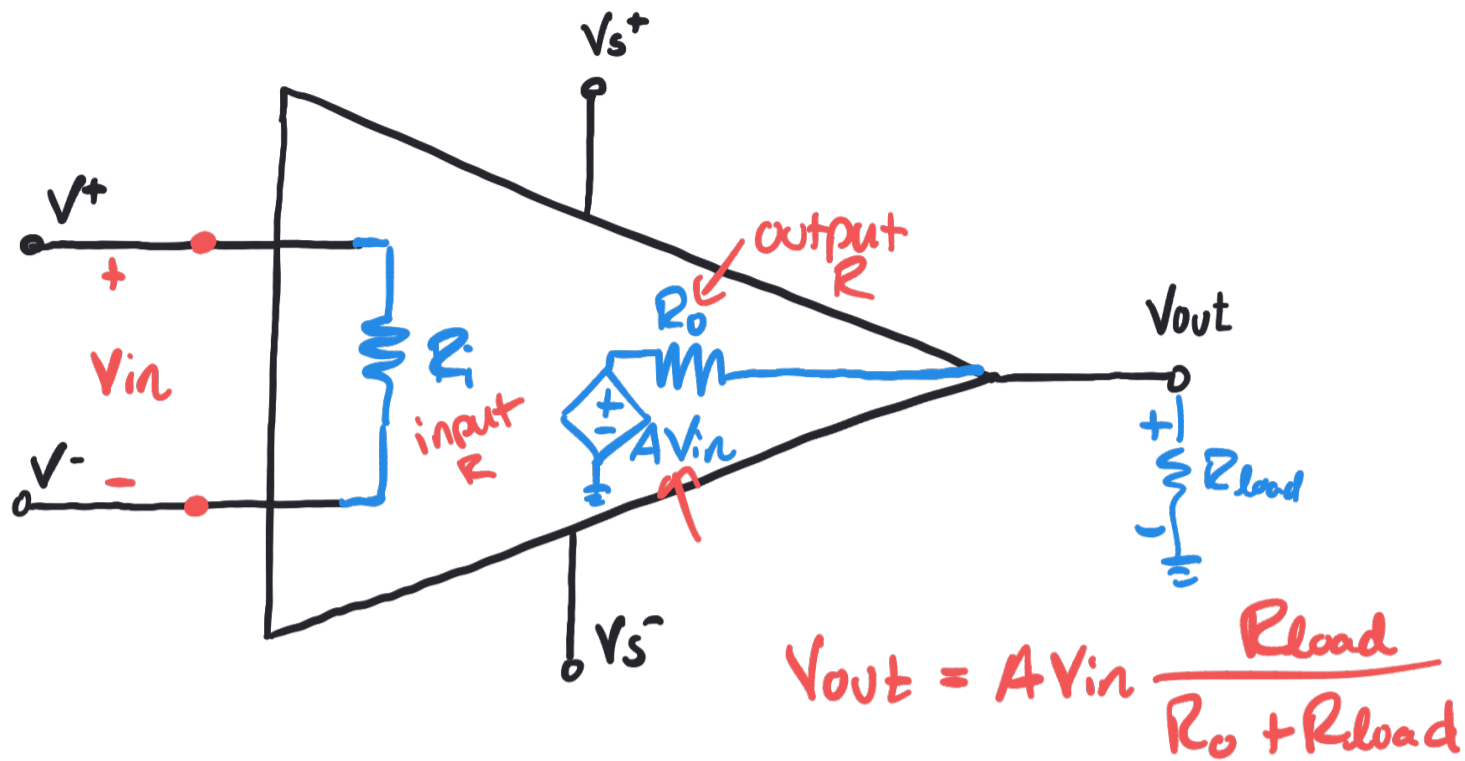

- **Input Resistance (R_i):** resistance that V_{in} "sees"
 - Ideally: $R_i = \infty$
 - Consequence: Golden Rule #1: no current ever flows into the "+" or "-" terminals
 - In Reality: $R_i \sim 2M\Omega$ (check the data sheet)
- **Output Resistance (R_o):** resistance that output terminal "sees"
 - Ideally: $R_o = 0$
 - In Reality: $3\Omega < R_o < 35\Omega$ (check data sheet)
- **Open-loop gain (A_o):** voltage gain of an open-loop op-amp
 - Ideally: $A_o = \infty$
 - Consequence: Golden Rule #2: when an op-amp is configured with negative feedback, $V_+ = V_-$
 - In Reality: $A_o \sim 10^5$ good enough for Golden Rule #2 to hold
- **Negative feedback:** when you connect V_o to V_- : stabilizes the circuit



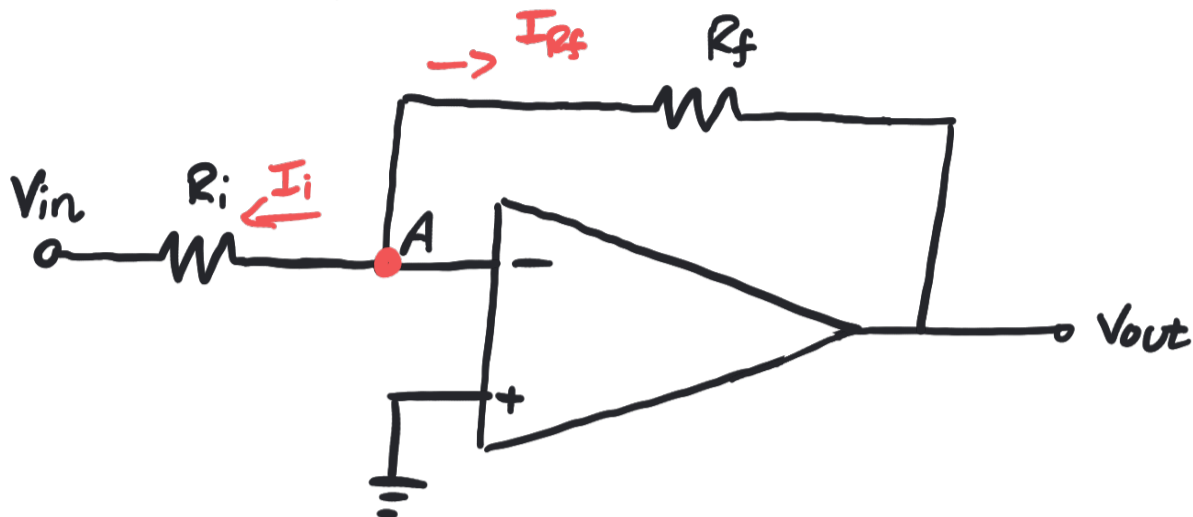Example: Using the properties of an ideal op-amp, determine V_{out} in terms of V_{in} 6



- Assume the op-amp is powered
- Hint #1: the op-amp is configured in a negative feedback loop (can use Golden Rule #2)
- Hint #2: Use KCL at node A

KCL @ A: $I_i + I_{rf} = 0$ Golden Rule #2

$$I_i = \frac{V_A - V_{in}}{R_i} = -\frac{V_{in}}{R_i}$$

$$I_{rf} = \frac{V_A - V_o}{R_f} = -\frac{V_o}{R_f}$$

$$\left. \begin{array}{l} I_i \\ I_{rf} \end{array} \right\} -\frac{V_{in}}{R_i} - \frac{V_o}{R_f} = 0$$

$$\underline{V_o = -\frac{R_f}{R_i} V_{in}} \quad \left. \vphantom{V_o} \right\} \text{inverting amplifier}$$

- #1: what is $(-\frac{R_f}{R_i})$? the gain
- #2: we reduced the gain from $A_o = 10^5$ to $-\frac{R_f}{R_i}$ by using negative feedback

Upcoming Assignment Due Dates

7

1. Mid-Semester Survey *Late Due Date 10/19*
2. Lab 02 Parts A & B *Due Date 10/19*
3. Problem Set 06 *Due Date 10/19*