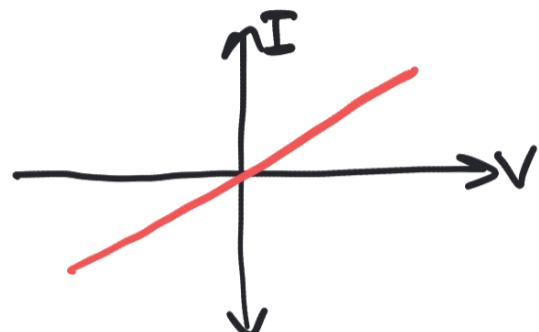


Intro to ECSE Class 16 : Circuit Analysis Method #4: 1 Superposition


I Properties of Linearity: Elements \rightarrow Circuits \rightarrow Systems

- What have we said linearity means so far?
 - + Circuit elements: linear IV characteristic

Resistor



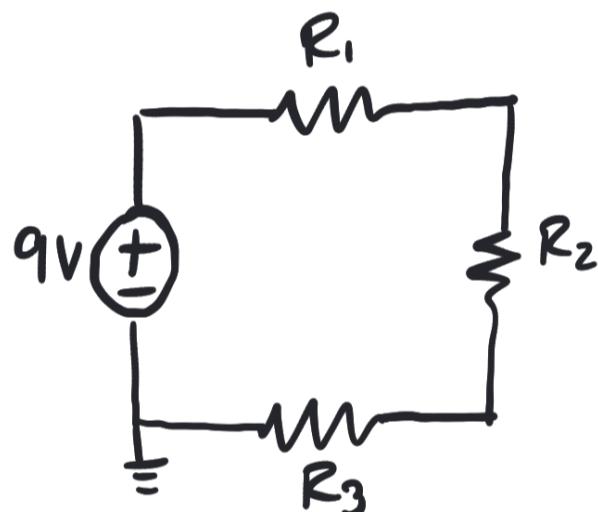- + Circuits: composed of linear circuit elements




- + What sorts of non-linear elements have we encountered so far?

- diodes, LEDs
- op-amps (comparators)
- transistors

• But what does linearity mean for systems in general? 2

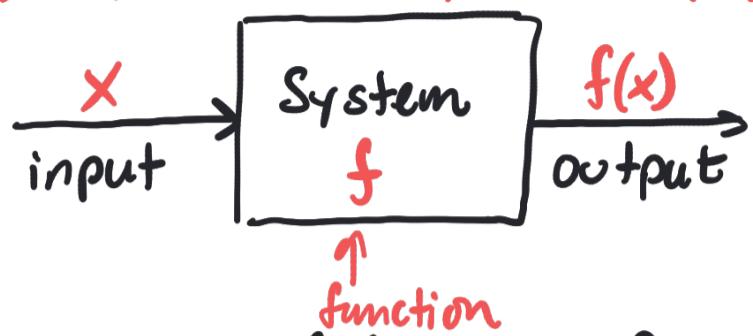- What is a system? something that takes an input, acts on it with a function, then outputs



- And in order to determine if our system is linear, we must determine if the function f is linear

a function is linear is linear
if it satisfies the Superposition Principle

A function satisfies the Superposition Principle if it satisfies the following two properties:

1. Additivity : $f(x_1 + x_2) = f(x_1) + f(x_2)$

This means: if instead of inputting a single input x , we input a sum of inputs $x_1 + x_2$, the output is the sum of the outputs for the individual inputs.

2. Homogeneity : $f(ax) = af(x)$

This means: the output of an input scaled by a constant "a" is "a" times the output for the unscaled input

→ Putting this all together, we have for linear systems:



linear combination

- And in other words: if we send a sum of scaled inputs to our system, the output is the scaled output for each of the individual inputs

• Some examples: are these functions linear?

• 1. Multiplication: amplification, Ohm's law...

$$f(x) = -5x$$

↑ input ↑
output

✓ Additivity: $f(x_1 + x_2) = f(x_1) + f(x_2) \rightarrow \text{inputs } x_1 = 1, x_2 = 2$

linear • $f(x_1 + x_2) = f(1+2=3) = -5(\underline{\cancel{3}}) = -15 \quad \times$

$$\cdot f(x_1) + f(x_2) = -5(1) + -5(2) = -5 - 10 = -15$$

✓ Homogeneity: $f(ax) = af(x), a = 2, x = 3$

$$\cdot f(ax) = f(2x) = -5(2 \cdot 3) = -5 \cdot 6 = -\underline{\cancel{30}}$$

$$\cdot af(x) = 2 \cdot f(3) = 2 \cdot (-5 \cdot 3) = 2 \cdot (-15) = -\underline{\cancel{30}}$$

2. Addition: $f(x) = x + 1$

✗ Additivity: $x_1 = 1, x_2 = 2$

$$\cdot f(x_1 + x_2) = f(1+2) < f(3) = 3+1 = \underline{\cancel{4}} \quad \times$$

Not linear! • $f(x_1) + f(x_2) = f(1) + f(2) = \{1+1\} + \{2+1\} < 2+3 = \underline{\cancel{5}}$


- differentiation and integration are linear

III) Circuit Analysis Method #4: Superposition

4

- What function defines our circuit as a system?

$$V = IR \text{ Ohm's law}$$

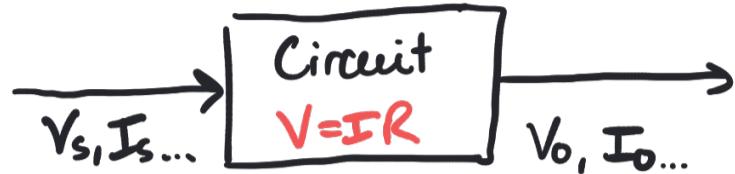

- Our system is governed by Ohm's law \rightarrow multiplication by R or $'/R$ \rightarrow linear!
- What does it look like if we apply the Superposition Principle to our circuit?

$$V_o(V_{in,1} + V_{in,2} + \dots + V_{in,n}) = V_o(V_{in,1}) + V_o(V_{in,2}) + \dots + V_o(V_{in,n})$$

\nwarrow output voltage


- In words: If we have a circuit with multiple sources, we can calculate the output by summing the outputs from individual sources

- But how do we get the output from an individual source?
- We need to turn off all other sources

- Voltage Sources:

on: $V = V_s$

off: $V = 0$

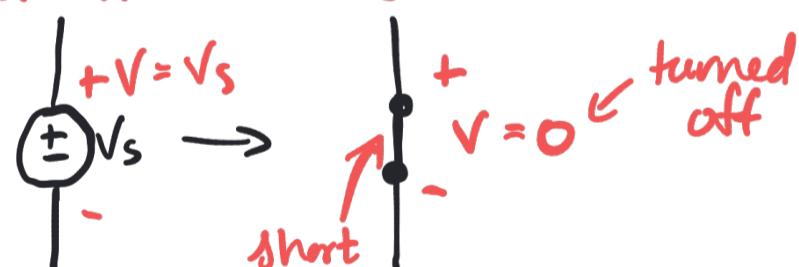


- replace w/ short circuit

- Current Sources:

on: $I = I_s$


off: $I = 0$

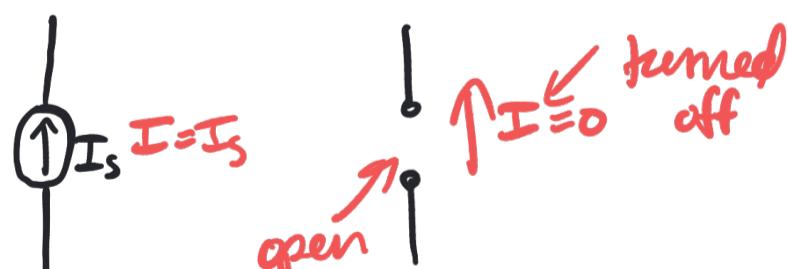

- replace w/ open circuit


- Let's see how this works via an example

5

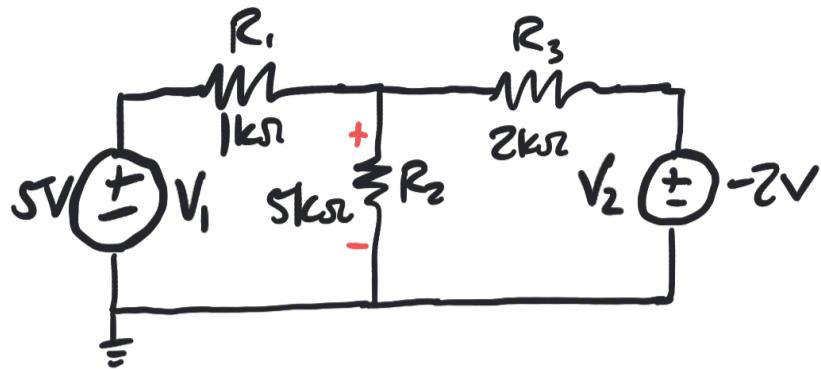

- Solve for V_{R2} using Superposition

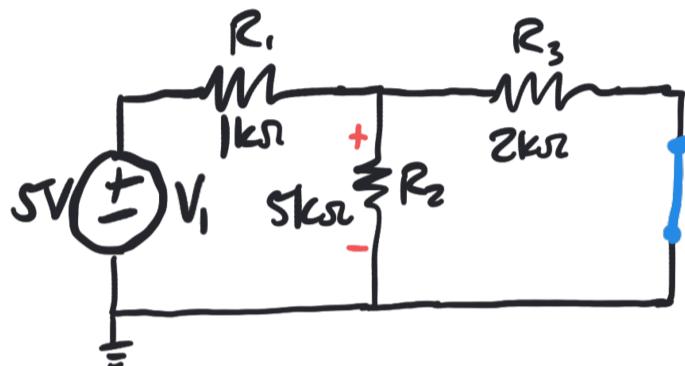
1. Turn off V_2 and solve for V_{R2}, V_1



Using Voltage divider eq.:

$$V_{R2,V1} = SV \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} = SV \cdot \frac{1.429k\Omega}{1k\Omega + 1.429k\Omega} \cdot 2.942V$$

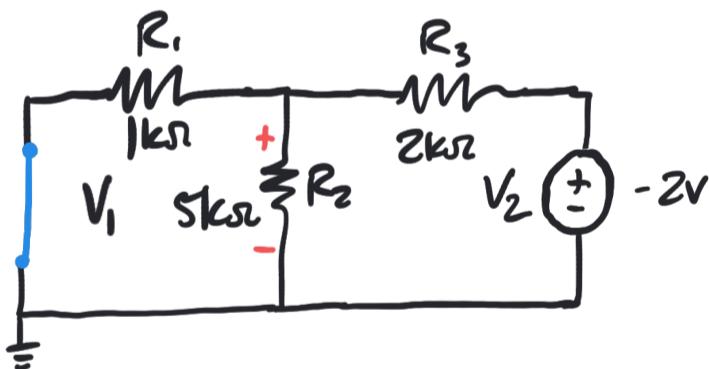2. Turn off V_1 and solve for V_{R2}, V_2




$$V_{R2,V2} = (-2V) \cdot \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} = (-2V) \cdot \frac{0.833k\Omega}{2k\Omega + 0.833k\Omega} = -0.588V$$

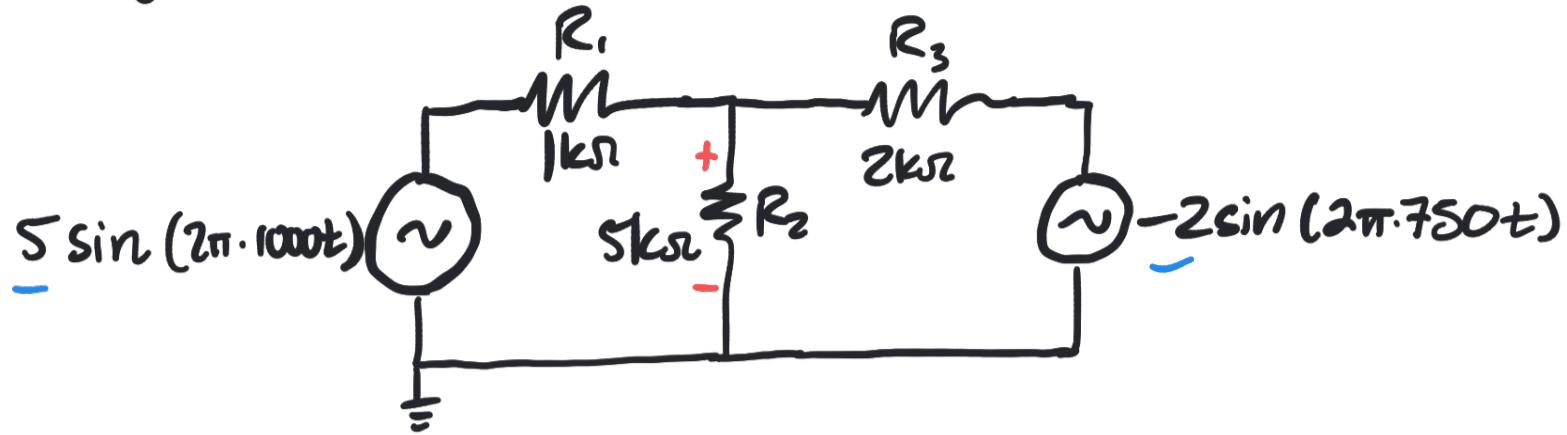3. Add the two results together


$$V_{R2} = V_{R2,V1} + V_{R2,V2} = 2.942V - 0.588V = \underline{\underline{2.354V}}$$

• But why bother with this at all? When is this useful? ^b



• Solve for V_{R2} using Superposition

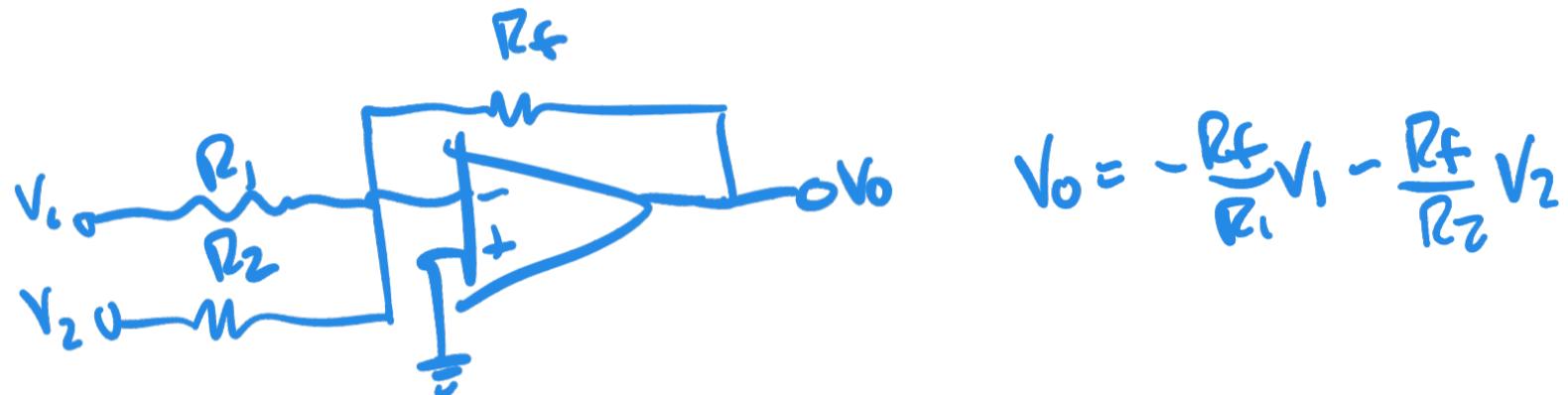
$$\begin{aligned} V_{R2} = V_{R2,V_1} + V_{R2,V_2} &= 2.942 \cdot \sin(2\pi \cdot 1000t) \\ &\quad - 0.568 \sin(2\pi \cdot 750t) \end{aligned}$$




Extra Practice Problem

7

- Find V_{R4} using superposition

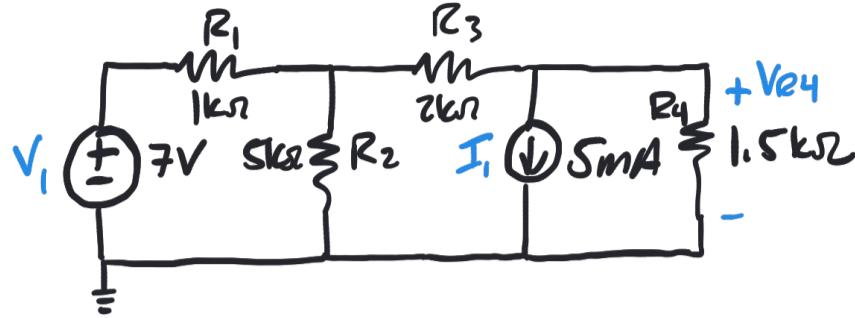

1. V_{R4} due to V_1 :

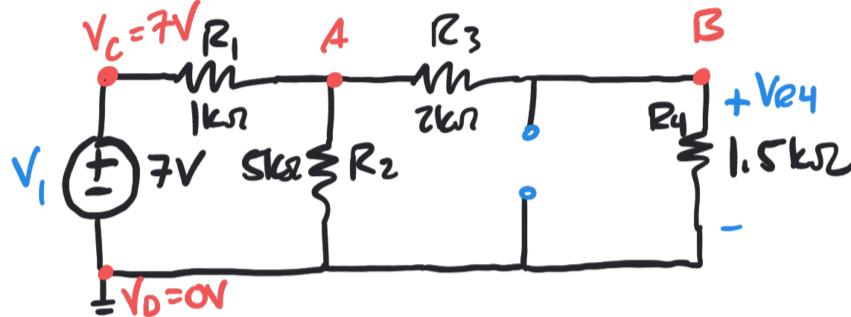


Using nodal analysis

$$\text{Node A: } \frac{V_A - 7V}{1k\Omega} + \frac{V_A}{5k\Omega} + \frac{V_A - V_B}{2k\Omega} = 0 \rightarrow (1/1k\Omega + 1/5k\Omega + 1/2k\Omega)V_A + (-1/2k\Omega)V_B = 7V/1k\Omega$$

$$\text{Node B: } \frac{V_B - V_A}{2k\Omega} + \frac{V_B}{1.5k\Omega} = 0 \rightarrow (-1/2k\Omega)V_A + (1/2k\Omega + 1/1.5k\Omega)V_B = 0$$

$$\begin{bmatrix} (1/1k + 1/5k + 1/2k) & -1/2k \\ -1/2k & (1/2k + 1/1.5k) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 7/1k \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4.712V \\ 2.019V \end{bmatrix}$$

2. V_{R4} due to I_1 :

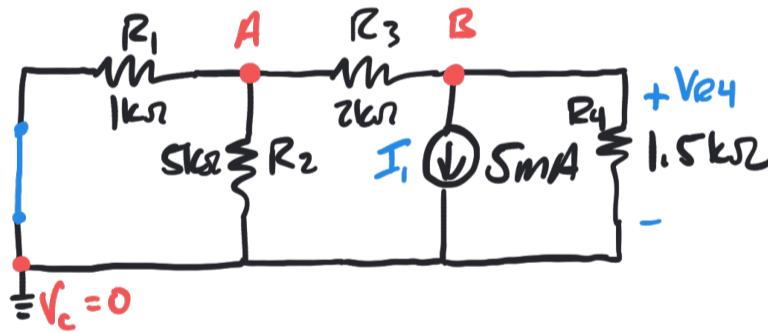

Using nodal analysis

$$\text{Node A: } \frac{V_A}{1k\Omega} + \frac{V_A}{5k\Omega} + \frac{V_A - V_B}{2k\Omega} = 0 \rightarrow (1/1k\Omega + 1/5k\Omega + 1/2k\Omega)V_A + (-1/2k\Omega)V_B = 0$$

$$\text{Node B: } \frac{V_B - V_A}{2k\Omega} + 5 \times 10^{-3}A + \frac{V_B}{1.5k\Omega} = 0 \rightarrow (-1/2k\Omega)V_A + (1/2k\Omega + 1/1.5k\Omega)V_B = -5 \times 10^{-3}A$$

$$\begin{bmatrix} (1/1k + 1/5k + 1/2k) & (-1/2k) \\ (-1/2k) & (1/2k + 1/1.5k) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ -5 \times 10^{-3}A \end{bmatrix} \rightarrow \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} -1.442V \\ -4.904V \end{bmatrix}$$

3. V_{R4} due to $V_1 + I_1$:

$$V_{R4} = 2.019V - 4.904V = \underline{-2.885V}$$

Upcoming Assignments & Due Dates

8

1. lab D1 Optimization Due Date: 10/26