

Name SOLUTIONS

1. _____ (10 pts)
2. _____ (6 pts)
3. _____ (12 pts)
4. _____ (14 pts)
5. _____ (8 pts)

Total _____

For partial credit on some questions, you may want to re-draw circuit diagrams as you simplify the circuits.

Show all of your work. Use the backs of pages if there is not enough room on the front.

Many problems can be solved using more than one method. Check your answers by using a second method.


At least skim through the entire quiz before you begin and then start with the problems you know best.

The proctor will only answer clarification questions where wording is unclear or where there may be errors/typos. No other questions will be responded to.

Problem 1 (12 Points) – Ohm’s Law

A simple voltage source-resistor circuit is shown to the right.

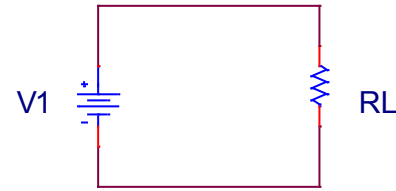- a. Determine the current through R_L (in mAmps) when $V_1=10V$ and $R_L=2k\Omega$. (4 pts)



$$I_{R_L} = \frac{V_1}{R_L} = \frac{10V}{2k\Omega} = 5\text{ mA}$$

- b. For the same circuit, if the voltage increases while the resistance stays constant, the current will (circle one) (1 pt)


Increase

Decrease

- c. For the same circuit, if the resistance increases while the voltage source stays constant, the current will (circle one) (1 pt)

Increase

Decrease

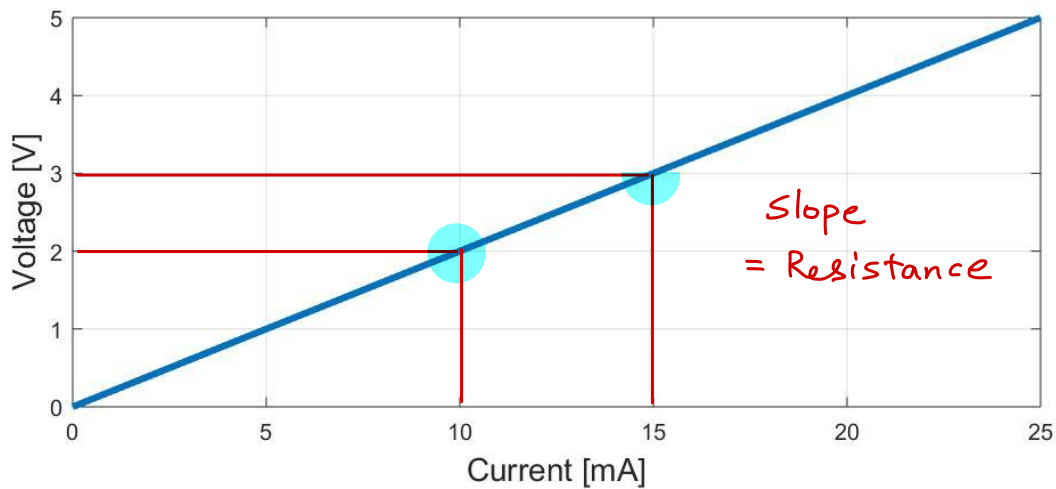


The above linear plot relates voltage and current in a resistor (similar to the circuit at the top of the page).

- d. Based on the plot, determine the value of the resistance. Note, the current is given in mA (10^{-3} A) (4 pts)

$$\text{Slope} = R = \frac{dv}{di} = \frac{3 - 2}{(15 - 10)_m} = \frac{1}{5m} \Omega = 200 \Omega$$

Problem 2 (6 Points) – The Discovery Board

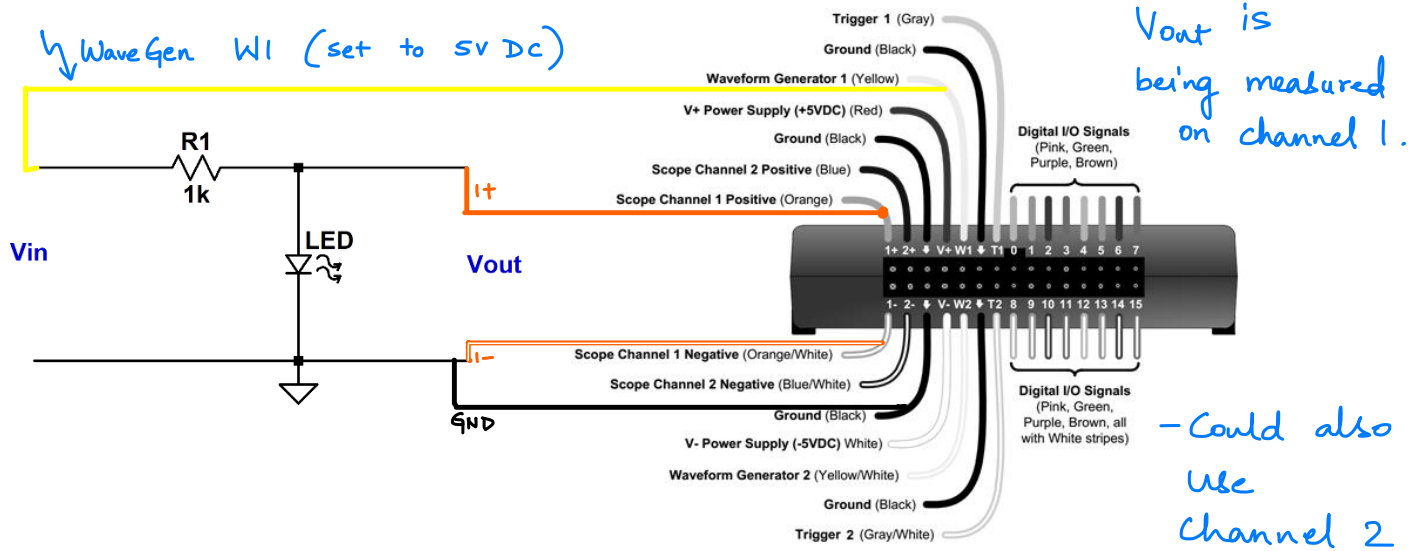- a) In the figure below, draw lines from the Discovery Board to the circuit that represent the wires you need to connect to measure the output voltage V_{out} , i.e. voltage across LED. Additionally, draw lines to provide an input voltage V_{in} of 5V DC to the circuit using the Analog Discovery (no additional instrumentation). Remember, to generate a DC voltage with Wavegen, you need to use two connections from the Discovery Board. (4 pts)




- b) If your measurement for V_{out} is 2.0V (when V_{in} is 5V), find the current that flows through the resistor R_1 . (2 pts)

$$\text{Voltage across } R_1 = V_{in} - V_{out} = 3V$$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{3V}{1K} = 3 \text{ mA}$$

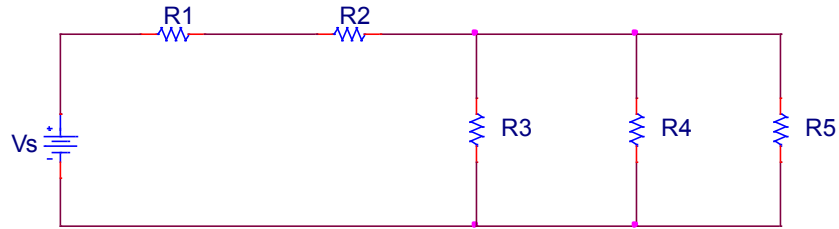
Problem 3 (12 Points) – Resistors in parallel and series



a) For the above circuit, indicate which resistors are in series and which resistors are in parallel.

Series: R1, R2

Parallel: R3, R4, R5

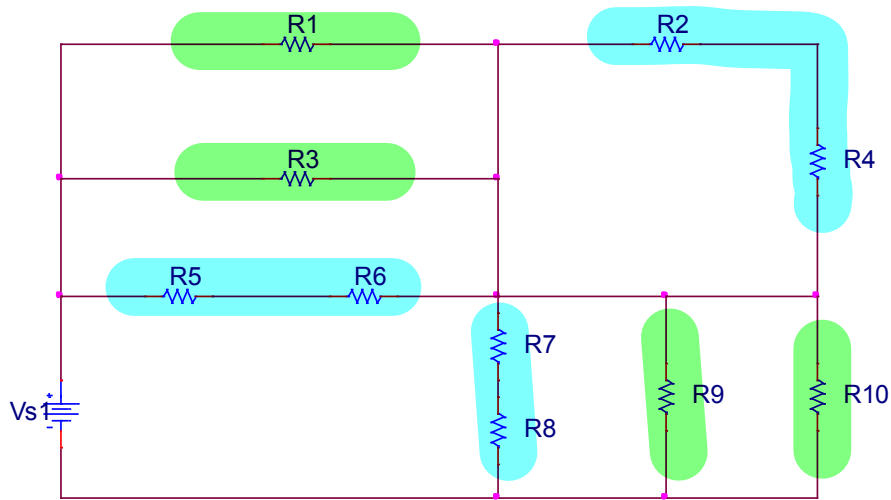

b) For the above circuit, indicate which **pairs** of resistors are in series and which resistors are in parallel. Each line is for a specific pair. There may be more lines than needed. (8 pts)

Series: R5, R6


Series: R7, R8

Series: R2, R4

Parallel: R1, R3

Parallel: R9, R10

Parallel: _____

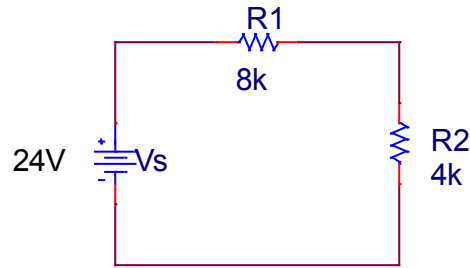Problem 4 (14 Points) – Voltage Dividers – Part 1

- a) For the above circuit, determine the voltages across R1 and R2. (4 pts)

R1:

$$V_{R1} = V_S \left(\frac{R_1}{R_1 + R_2} \right) = 24 \left(\frac{8k}{12k} \right)$$

$$= \boxed{16 \text{ V}}$$

R2:

$$V_{R2} = V_S \left(\frac{R_2}{R_1 + R_2} \right) = 24 \left(\frac{4k}{12k} \right)$$

$$= \boxed{8 \text{ V}}$$

- b) If R2 becomes very large (goes to infinity) and R1 stays the same, what is the maximum voltage across R2? (1 pt)


$$V_{R2} \propto R_2 \Rightarrow \text{As } R_2 \rightarrow \infty, V_{R2} \rightarrow V_S$$

$$\Rightarrow \boxed{V_{R2(\max)} = 24 \text{ V}}$$

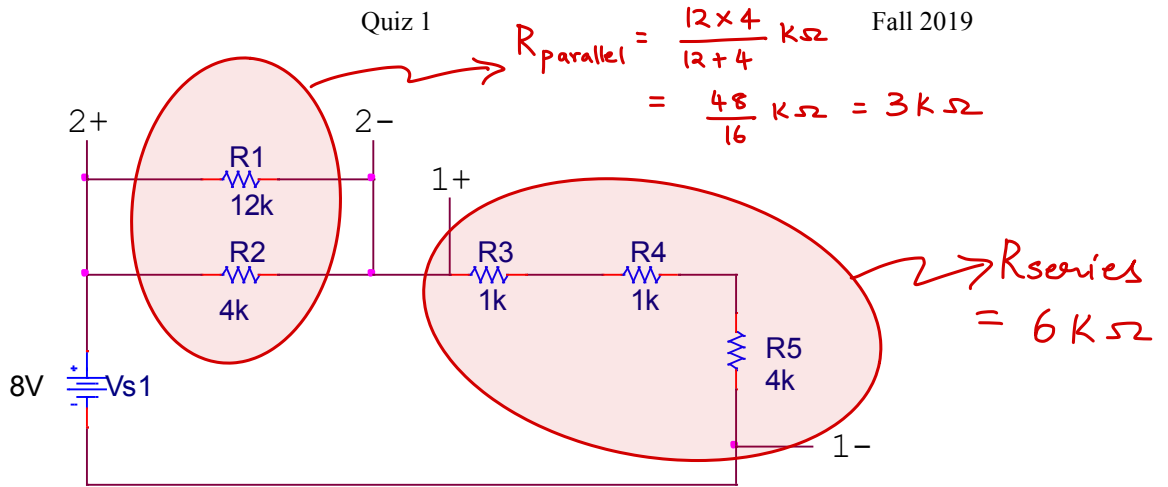
- c) If R1 becomes very large (goes to infinity) and R2 stays the same, what is the minimum voltage across R2? (1 pt)

$$\text{As } R_1 \rightarrow \infty \Rightarrow V_{R1} \rightarrow V_S$$

$$\Rightarrow \boxed{V_{R2(\min)} = 0 \text{ V}}$$



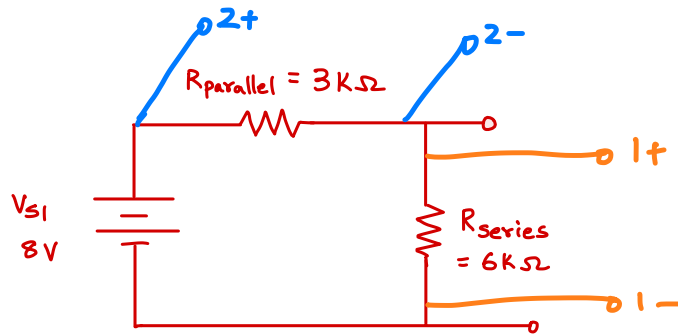d) Apply series and parallel relationships to obtain a simplified two resistor (R_{series} and $R_{parallel}$) circuit. Sketch the new circuit. (4 pts)




e) Use your simplified circuit to determine the voltages across the equivalent resistors, R_{series} and $R_{parallel}$, as indicated by the Channel 1 and 2 connections in the original circuit. (4 pts)

$$V_{ch1} = V_{R_{series}} = V_{s1} \left(\frac{6K}{9K} \right) = \boxed{5.33 V}$$

$$V_{ch2} = V_{R_{parallel}} = V_{s1} \left(\frac{3K}{9K} \right) = \boxed{2.67 V}$$

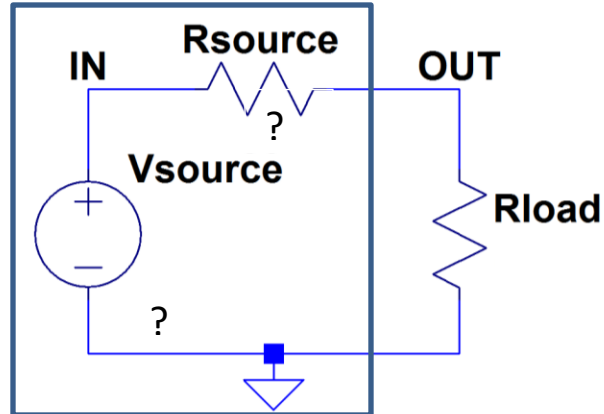Problem 5 (8 Points) – Source Characterization Using a Voltage Divider

Batteries and other voltage sources can generally be modeled by combining an ideal voltage source and a resistor. The circuit at the right is set up to study some kind of a black box DC voltage source. Different load resistors are connected and the voltage $V(\text{OUT})$ is measured. The results of the trials are listed in the table below. *Note that there is more information than you need to find the source voltage and resistance.*



Trial	Rload	V(OUT)
1	1Ω	0.692V
2	2Ω	1.245V
3	10Ω	4.276V
4	20Ω	6.316V
5	100Ω	10.15V
6	200Ω	11.01V
7	1kΩ	11.787V
8	2kΩ	11.892V
9	10kΩ	11.978V
10	20kΩ	11.989V

- a. (4 pts) Determine the source voltage V_{source} (in Volts)

As R_{load} increases, $V(\text{OUT}) \rightarrow 12\text{V}$

$$\Rightarrow \boxed{V_{\text{source}} = 12\text{ V}}$$

- b. (4 pts) Determine the source resistance R_{source} (in Ohms)

Guess for $R_{\text{source}} = 20 - 40\ \Omega$

$$V(\text{OUT}) = V_{\text{source}} \left(\frac{R_{\text{load}}}{R_{\text{load}} + R_{\text{source}}} \right)$$

$$\Rightarrow 6.316 = 12 \left(\frac{20}{20 + R_{\text{source}}} \right) \Rightarrow \boxed{R_{\text{source}} = 18\ \Omega}$$