

2. Design Problems (15 points)


For the two design problems below, your answers should include a clearly drawn (by hand or LTspice) schematic of the circuit and should also include handwritten work/explanation justifying your design methodology. Indicate which node/nodes satisfy the design criterion.

Part a) (5 points) Design a circuit such that there is a node with voltage 1.5V. Constraint: Use one voltage source of value 2.5 V.

Part b) (10 points) Design any circuit (any combination of resistors and source voltages) that has a node with 3.5 V and a node with 3V. Neither of those nodes can be connected to a voltage source.

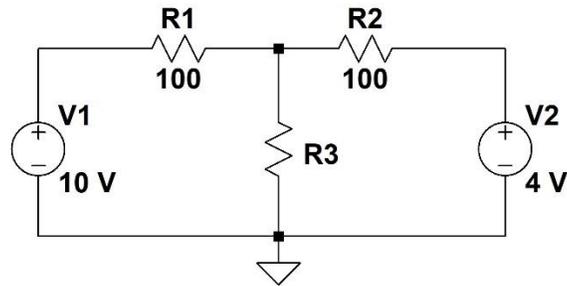3. Nodal Analysis (20 points)

Consider the circuit shown below. The voltage across R_3 is 6 V.



Part a) (10 points) Determine the value of resistance R_3 using nodal analysis such that the voltage across it is 6 V. Show handwritten work.


4. Matrix Solutions (20 points)

Using matrix reductions techniques applied in the experiments, solve (by hand) for the unknown values in the above matrix expression. You must show your matrix reduction work.

$$\begin{bmatrix} -1 & 1 & -4 \\ -2 & 2 & -5 \\ 0 & 2 & 7 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 5 \\ 4 \end{bmatrix}$$

5. Voltage Dividers (25 points)

Consider the circuit diagram shown below. The voltage source is a 10 V supply. R_3 is 10 ohms. R_1 , R_2 , and R_4 are unknown resistors. The current through R_3 is i_m as shown.

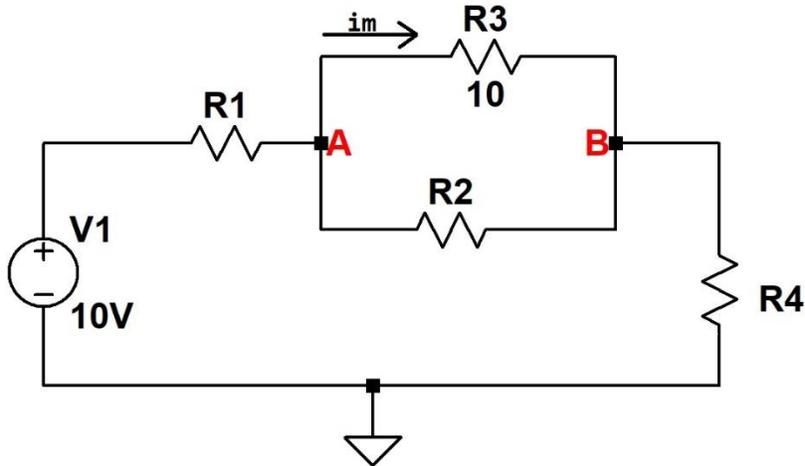

Case 1: Given that when $R_4 = 0$ ohms, the current through resistor R_3 is 2 mA, i.e. $i_m = 2$ mA.

Case 2: Given that when $R_4 = 2000$ ohms, current through resistor R_3 is 1 mA, i.e. $i_m = 1$ mA.

Part a) (3 points) Find voltage between points A and B for each of the cases described above?

Part b) (2 points) What is the equivalent resistance between points A and B, R_{AB} ? (Express in terms of R_2).


Part c) (5 points) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 1.

Part d) (10 points) Using voltage divider and your answer to parts a and b, develop a relationship between R_1 and R_2 for case 2.

Part e) (5 points) Solve the linear relationships (any method you want) derived in the previous parts, to determine the values of resistors R_1 and R_2 such that both case 1 and 2 are satisfied.

6. Nodal Analysis – Multiple Sources (20 points)

Consider the circuit shown below.

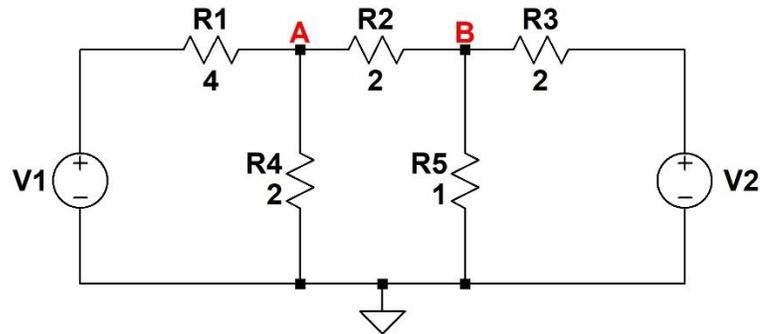

Using nodal analysis techniques, express the voltage at node A and node B in the form, $V_A = aV_1 + bV_2$ and $V_B = cV_1 + dV_2$. In other words, find values for the constants a, b, c, and d.