
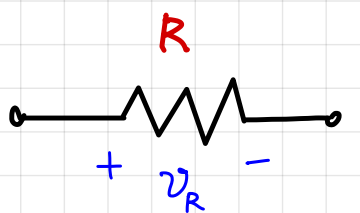
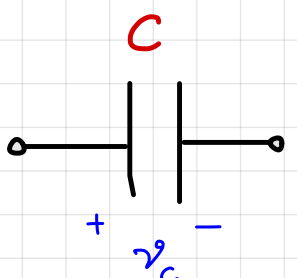
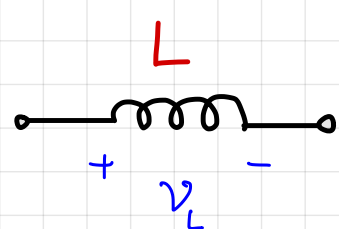


# Series RLC circuits

Second order transient response

# Current - Voltage Relationships

Component	Symbol	$i-v$ relation
Resistor		$v_R = i_R \cdot R$
Capacitor		$i_C = C \frac{dv_C}{dt}$
Inductor		$v_L = L \frac{di_L}{dt}$

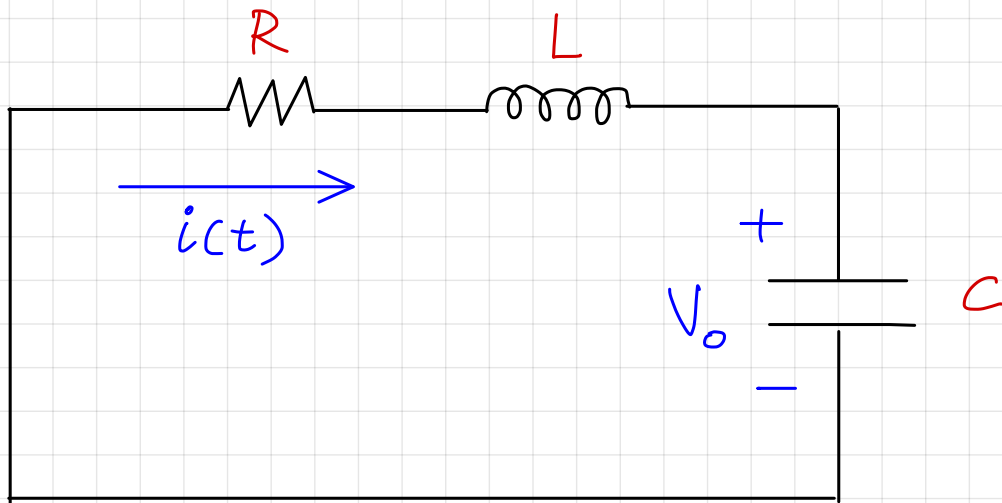

KVL :  $iR + v_L + v_c = 0$

$$v_L = L \frac{di_L}{dt} = L \frac{di}{dt}$$

$$i_c = C \frac{dv_c}{dt} \Rightarrow \int_0^{t'} i(t) dt = C v_c$$

$$\Rightarrow v_c(t) = \frac{1}{C} \int_0^{t'} i dt + V_0$$

$$\Rightarrow i \cdot R + L \frac{di}{dt} + \frac{1}{C} \int_0^{t'} i dt + V_0 = 0$$

Differentiate with respect to 't'.

$$i \cdot R + L \frac{di}{dt} + \frac{1}{C} \int_0^{t'} i dt + V_0 = 0$$

$$R \cdot \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

Divide by 'L'

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

SOLVE  
Differential equation  $\rightarrow$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

Assume  $i(t) = k e^{st}$

then  $\frac{d^2 i}{dt^2} = k s^2 e^{st}$  and  $\frac{di}{dt} = k s e^{st}$

$$\Rightarrow k s^2 e^{st} + \frac{R}{L} k s e^{st} + \frac{1}{LC} k e^{st} = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Characteristic equation.

Solve quadratic equation :  $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

$$s = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

$$= \frac{-\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}{1}$$

next slide: Roots could be real or complex

Define

$\omega_0 =$  Resonant frequency (rad/s)

$$= \frac{1}{\sqrt{LC}}$$

$$\omega_0 = 2\pi f_0$$

radians per second      Hz or  $\text{sec}^{-1}$

$$\alpha = \frac{R}{2L} = \text{attenuation constant}$$

$$\alpha = \frac{1}{\tau}$$

$\tau =$  Time constant

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$\alpha > \omega_0 \rightarrow$  Roots are real

OVERDAMPED  
SYSTEM




$\alpha = \omega_0 \rightarrow$  Roots are real  
and equal

CRITICALLY  
DAMPED



$\alpha < \omega_0 \rightarrow$  Roots are complex  
conjugates

UNDERDAMPED  
SYSTEM

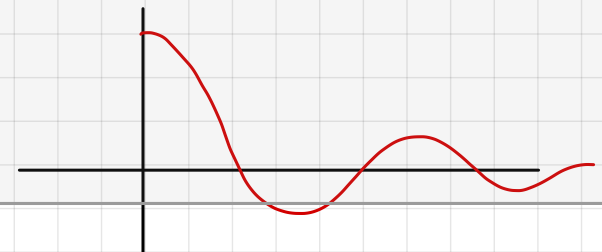

# Damped Frequency $\beta$

$\beta$  = frequency of damped oscillations

$$\beta = \sqrt{\omega_0^2 - \alpha^2}$$

radians per second

resonant frequency

attenuation constant

$$= 2\pi(\text{frequency in Hertz}).$$