

ENGR-2300
Electronic Instrumentation
Quiz 1
Spring 2022

Print Name _____ **RIN** _____

Section ____

I have read, understood, and abided by the Collaboration and Academic Dishonesty statement in the course syllabus. The work presented here was solely performed by me.

Signature: _____

Date: _____

On all questions: **SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS.** No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

Standard Resistor Values ($\pm 5\%$)						
1.0	10	100	1.0K	10K	100K	1.0M
1.1	11	110	1.1K	11K	110K	1.1M
1.2	12	120	1.2K	12K	120K	1.2M
1.3	13	130	1.3K	13K	130K	1.3M
1.5	15	150	1.5K	15K	150K	1.5M
1.6	16	160	1.6K	16K	160K	1.6M
1.8	18	180	1.8K	18K	180K	1.8M
2.0	20	200	2.0K	20K	200K	2.0M
2.2	22	220	2.2K	22K	220K	2.2M
2.4	24	240	2.4K	24K	240K	2.4M
2.7	27	270	2.7K	27K	270K	2.7M
3.0	30	300	3.0K	30K	300K	3.0M
3.3	33	330	3.3K	33K	330K	3.3M
3.6	36	360	3.6K	36K	360K	3.6M
3.9	39	390	3.9K	39K	390K	3.9M
4.3	43	430	4.3K	43K	430K	4.3M
4.7	47	470	4.7K	47K	470K	4.7M
5.1	51	510	5.1K	51K	510K	5.1M
5.6	56	560	5.6K	56K	560K	5.6M
6.2	62	620	6.2K	62K	620K	6.2M
6.8	68	680	6.8K	68K	680K	6.8M
7.5	75	750	7.5K	75K	750K	7.5M
8.2	82	820	8.2K	82K	820K	8.2M
9.1	91	910	9.1K	91K	910K	9.1M

Table 1: Standard resistor values for 5% tolerance resistors.


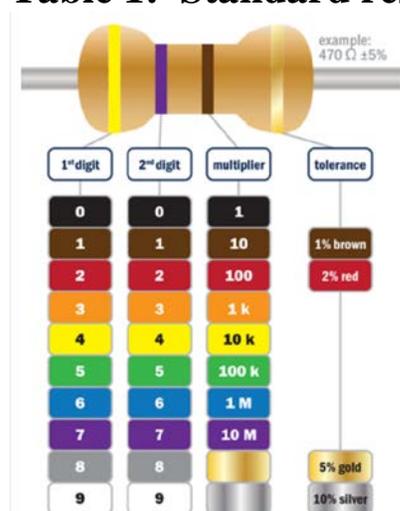



Figure 1: Resistor color and Tolerance bands

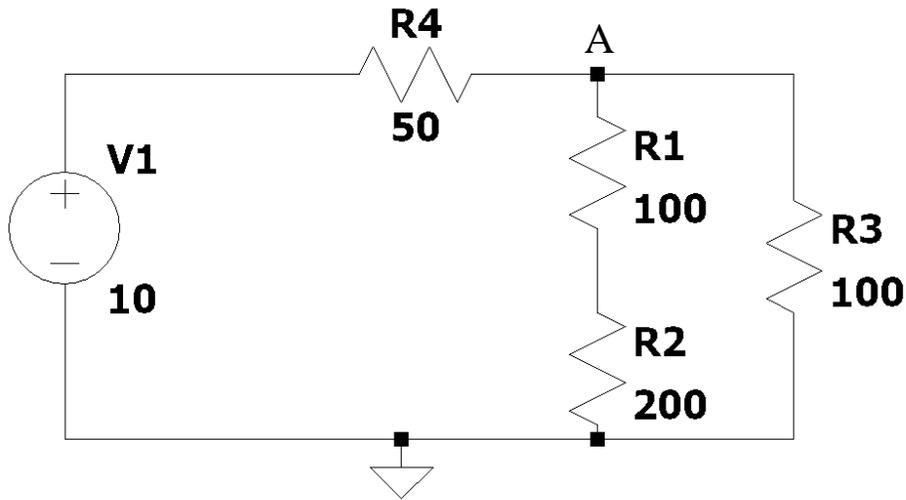- I. **Voltage Dividers (20 points)** As stated on the cover page: Round answers to 3 significant digits. Show formulas first and show your work. No credit will be given for numbers that appear without justification.



- a. (6 pts) What is the voltage at point A in the circuit above?

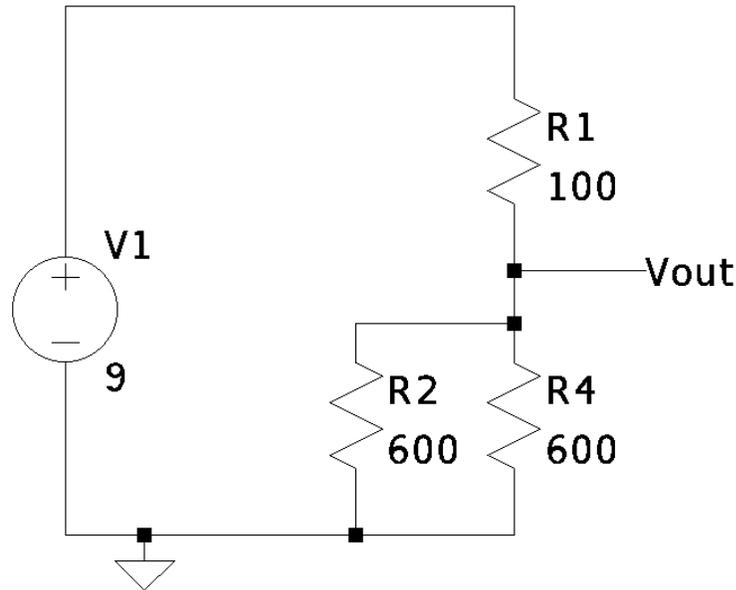- b. (4 pts) What is the current through R4?




- c. (2 pts) In the circuit above, the voltage source represents some 9-volt battery with battery resistance R_{batt} , which is not shown. Draw R_{batt} in the correct location in the circuit above. (This may require you to draw a resistor overtop of a wire.)
- d. (4 pts) You use a voltage probe with a very high input resistance to measure V_{out} and you find it to be 6.4V. What is the value of R_{batt} ?
- e. (2 pts) Suppose that you instead measured V_{out} using a voltage probe with much lower input resistance. How would this affect the voltage measured at V_{out} ?
- f. (2 pts) Name one reason that two 9-volt batteries might have different resistances.

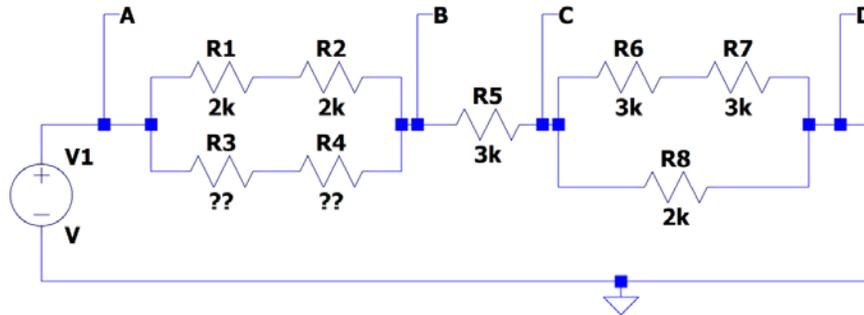II. Resistor Combinations, concepts and miscellaneous (20 points) *Note: Page 2 of this quiz has background information. The crib sheet may also be useful.*

The following circuit consists of 8 resistors and there are 4 voltage markers at points A, B, C, and D. V1 is a DC voltage source which can be created using W1 of the instrumentation board.

Note: several of the following questions are independent of each other, but not all.



- a. (4 pt) It is desired to have the effective **resistance of R3 combined with R4 to be 4.8k Ω** . Using the table on page 2 of this quiz, standard 5% resistor values, **pick resistors for R3 and R4**. State the resistance of each. If these resistors have 5% tolerance, what is the 4-band color code for each resistor? You should note that 4.8k isn't a standard value.

R3 value: _____ Color bands: _____

R4 value: _____ Color bands: _____

- b. (3 pts) If the voltage is measured to be 2.5V at point B, what is the current through R7, R8, and R5? Be sure to include units on all answers.

I(R7) _____

I(R8) _____

I(R5) _____

- c. (2 pts) What is the equivalent resistance between points A and B? Call this R_{AB} . Use part a. for the values of R3 and R4,

R_{AB} _____

d. (2 pts) What is the equivalent resistance between points C and D, Call this R_{CD} .



R_{CD} _____

e. (2 pts) Redraw the circuit with 3 resistors, R_{AB} , R_5 , R_{CD} . Label the resistor values and mark points A, B, C, and D.

f. (2 pts) Using the figure you drew for part e., if $V_1=4V$ what is the voltage at point B?



$V_B =$ _____

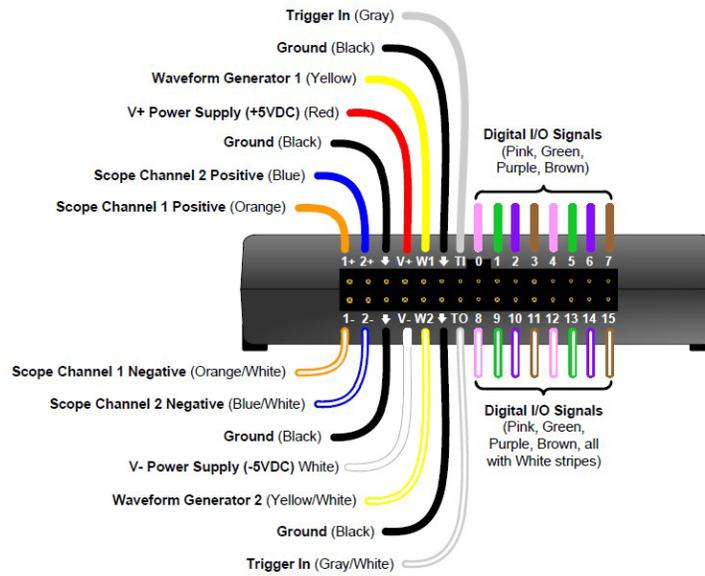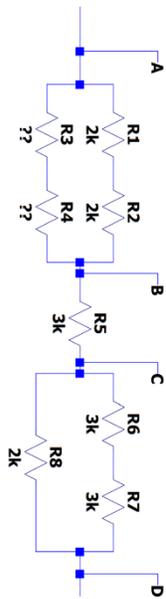- g. (5 pts) Wire this circuit shown for part a. by drawing lines on the figure below. Use the wave gen/signal gen to provide a signal for V1, which is point A. Use channel 1 to measure the signal at point B and use channel 2 to measure the signal at point C.



Draw lines between the 2 figures to indicate wires. Both the M2K and the AD2 have the same wiring and colors. W1 is called Signal Generator on the M2K and Waveform Generator on the AD2.

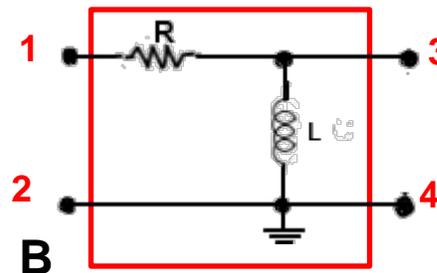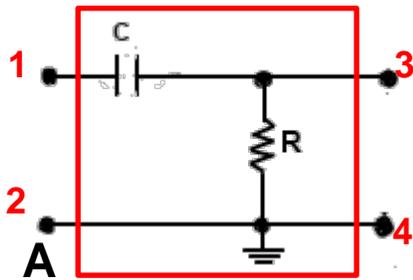III. Filters & Transfer Functions (20 points) For this problem, assume AC steady state.



1) Filters: Use figures A and B above to answer the following questions:

- a) (2pts) Shown above are basic, two-element, passive filter configurations made with CR and RL combinations. Determine the general complex transfer function for each circuit in terms of R, L, C and frequency ω , by modeling each as a voltage divider. This is an AC steady state problem.

A) CR: $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} =$

B) RL: $\frac{V_{OUT}}{V_{IN}} = \frac{V_{34}}{V_{12}} =$

- b) (2pts) For both circuits, what are the magnitude and phase for low but not zero phase?

Circuit A

Circuit B

- c) (2pts) What type of filter is each? Choices are as shown on the Crib Sheet: low pass, high pass, band pass or band reject.

Circuit A

Circuit B


- d) (4pts) Given: $L=40\text{mH}$, $R=2\text{k}\Omega$, and $C=0.20\text{nF}$ Find the corner frequency or this question for each circuit. Give the value of both ω_C and f_C .

Circuit A

Circuit B

2) **Transfer functions:** Use the figure shown to answer the following questions

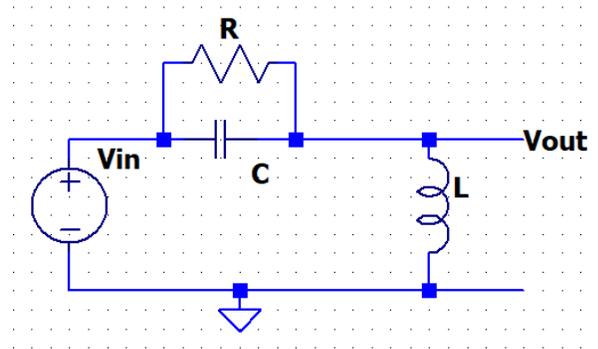
- a. (5 pts) Find the transfer function of the circuit shown. Simplify such that there are no fractions in the numerator or denominator of the transfer function.
 $H(j\omega) = V_{out}(j\omega)/V_{in}(j\omega)$



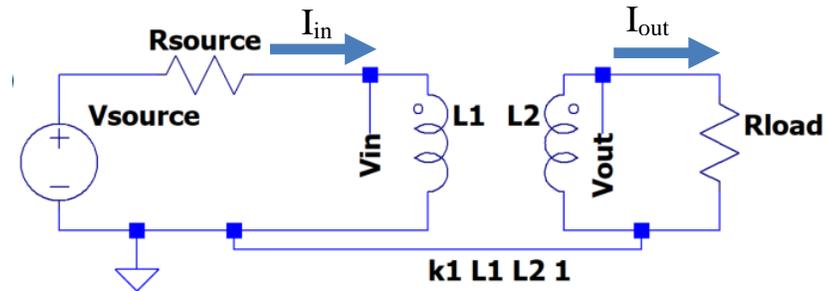- b. (4 pts) What is the magnitude and phase of the transfer function when the frequency is very small (approaches zero)? And what is the magnitude and phase of the transfer function when the frequency is very large (approaches infinity)?
- c. (1 pts) Is it possible for the magnitude of the transfer function to be greater than unity?

Circle one: Yes or No

IV – Phasors and Transformers (20 points)



1) Assume $L1$ and $L2$ form an ideal transformer with full coupling. The transformer has these specifications: $L1=180\text{mH}$, $L2=20\text{mH}$, $R_{source}=90\Omega$, $R_{load}=20\Omega$

a. (8pts) For the given information, determine the turns ratio, a . And determine the ratios V_{out}/V_{in} , I_{out}/I_{in} and the transformer input resistance, R_{in} . (R_{in} is V_{in}/I_{in}) This isn't the resistance seen by V_{source} .

$$a = \underline{\hspace{2cm}}$$

$$V_{out}/V_{in} = \underline{\hspace{2cm}}$$

$$I_{out}/I_{in} = \underline{\hspace{2cm}}$$

$$R_{in} = \underline{\hspace{2cm}}$$

b. (2pts) If V_{source} is a sinewave with a 10V amplitude at 5kHz, what is the amplitude of current I_{in} ? As with all problems, include units and show your work for partial credit.


$$I_{in}(\text{amplitude}) = \underline{\hspace{2cm}}$$

c. (3pts) The ideal transformer model assumes that self-inductance $L1$ and $L2$ are infinite, $|j\omega L1|$ and $|j\omega L2|$ approach infinity. On the practical side the transformer is close to ideal if $|j\omega L1| > 10 \cdot R_{source}$ and $|j\omega L2| > 10 \cdot R_{load}$. Just looking at $L2$, for what range of frequencies will this transformer be close to the ideal?

Conditions on f : $\underline{\hspace{2cm}}$

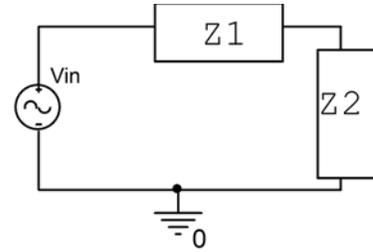2. Phasors: This circuit shown has 2 complex impedances, Z_1 and Z_2 , connected as shown.

Given the polar form of the phasor of V_{in} : $V_{in} = 10V\angle 0^\circ$ where 10 is the amplitude and 0° is the phase angle. And that phasor for V_{Z1} is $V_{Z1} = 4V\angle 30^\circ$ (Again this format is a magnitude and a phase angle.)



- a. (1pts) Give V_{Z1} in Cartesian form, $V_{Z1} = a + jb$, find a and b.
- b. (2pts) If Z_1 is made of just two components, one of which is a resistor, is the other a capacitor or an inductor?
- c. (3pts) Determine V_{Z2} , the voltage across Z_2 in Cartesian and polar form.
3. (1pt) Give the names of 2 of the people teaching this course. This can be first names or last names and can be the professors, teaching assistants, or undergraduate student assistants. Spelling doesn't count. Using their Discord name is also valid.