

ENGR-4300

Fall 2007

Test 2

Name **SOLUTION**

Section 1(MR) 2(TF)
(circle one)

Question I (20 points) _____

Question II (20 points) _____

Question III (15 points) _____

Question IV (20 points) _____


Question V (25 points) _____

Total (100 points): _____




On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification.

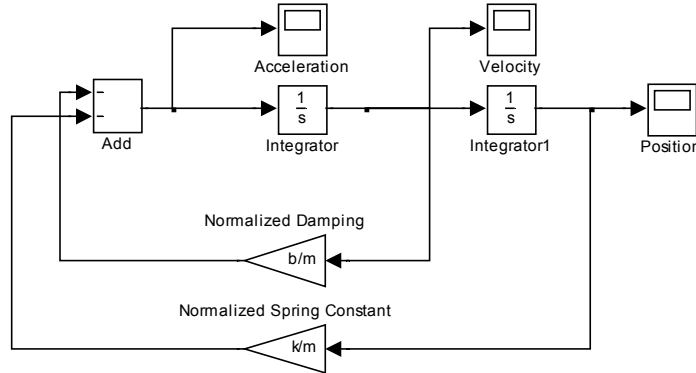Question I – Bridges and Damped Sinusoids (20 points)

One of the most powerful tools we have as engineers is MATLAB, which is especially useful when one does a Simulink model of a system. (The following is provided for completeness. You do not need to know how to work with Simulink to do this problem.) A Simulink model for a cantilever beam is shown below.



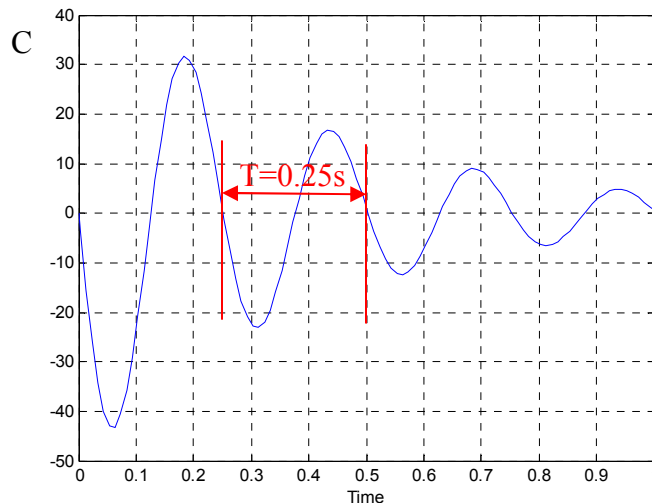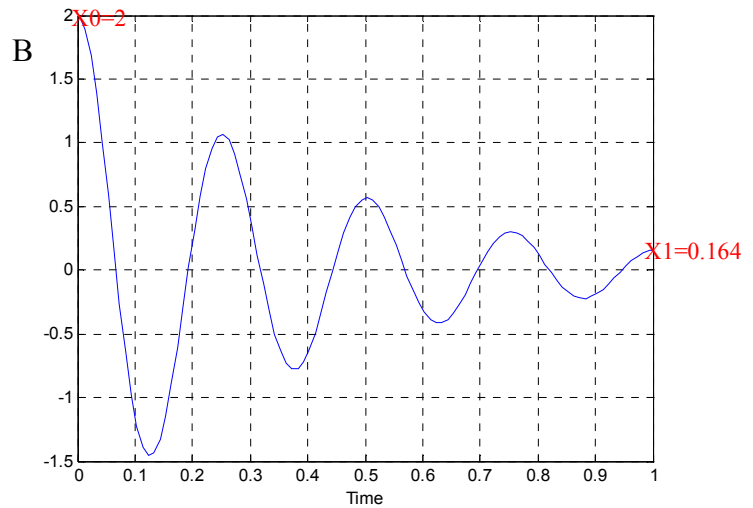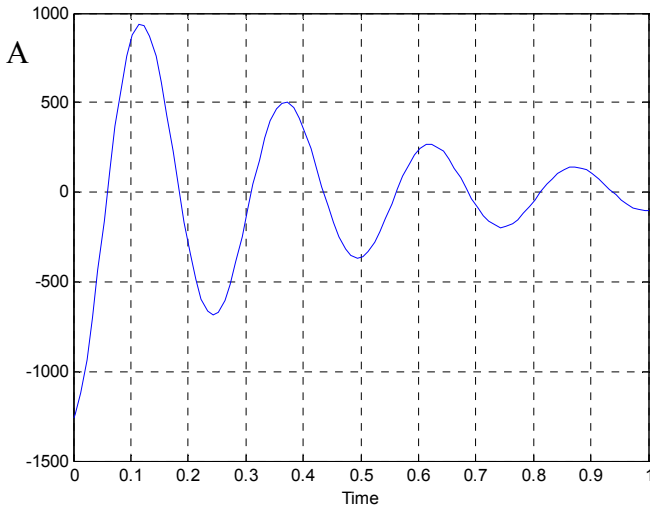The blocks marked Acceleration, Velocity and Position are ‘scopes’ that provide data on the given parameter as a function of time. In no particular order, these three plots follow for a particular set of values for k, b, and m (the spring constant, the damping constant and the mass, respectively).



$$2e^{-\alpha t} = 0.164 \quad @t = 1s$$

$$\alpha = -\ln 0.082$$

$$\alpha = 2.5$$

1) (3pt) Identify which plot is **position**, which is **velocity** and which is **acceleration**. From the plots, what are the initial position, velocity and acceleration? Assume SI units (position in meters, velocity in meters per second, acceleration in meters per second squared).

A: ACCELERATION B: POSITION C: VELOCITY

Initial position: 2m Initial velocity: 0m/s Initial acceleration: 1250m/s²

2) (6pt) Find the frequency f , the period T , and the damping constant α and then evaluate the mathematical expression for each of the three functions – position, velocity and acceleration of the beam. Generically, these expressions are in the form $f(t) = F_0 e^{-\alpha t} \cos(\omega_0 t + \phi_0)$ where F_0 , α , ω_0 and ϕ_0 are constants.

$$T = 0.25\text{s} \quad f = 1/T = 4\text{Hz} \quad \omega = 2\pi f = 25 \text{ rad/s}$$

$$x(t) = 2e^{-2.5t} \cos(25t + 0) \text{ m}$$

$$v(t) = 50e^{-2.5t} \cos(25t + \pi/2) \text{ m/s}$$

$$a(t) = 1250e^{-2.5t} \cos(25t + \pi) \text{ m/s}^2$$

3) (3pt) From these three expressions, determine the mass m , the damping coefficient b and the spring constant k for the cantilever beam being analyzed.

$$\alpha = 2.5 \qquad \omega = 25 \qquad \omega_0 \approx \omega = 25$$

$$\ddot{x}(t) = -\frac{b}{m} \dot{x}(t) - \frac{k}{m} x(t)$$

$$\ddot{x}(t) + \frac{b}{m} \dot{x}(t) + \frac{k}{m} x(t) = 0$$

$$\ddot{x}(t) + 2\alpha \dot{x}(t) + \omega_0^2 x(t) = 0$$


$$\text{Let } m = 1 \Rightarrow b = 2\alpha = 5$$

$$k = \omega_0^2 = 625$$

Grading on this should be based more on the approach than the actual answer; partial credit given for any relevant equations or explanations.

Question I – Bridges and Damped Sinusoids (continued)

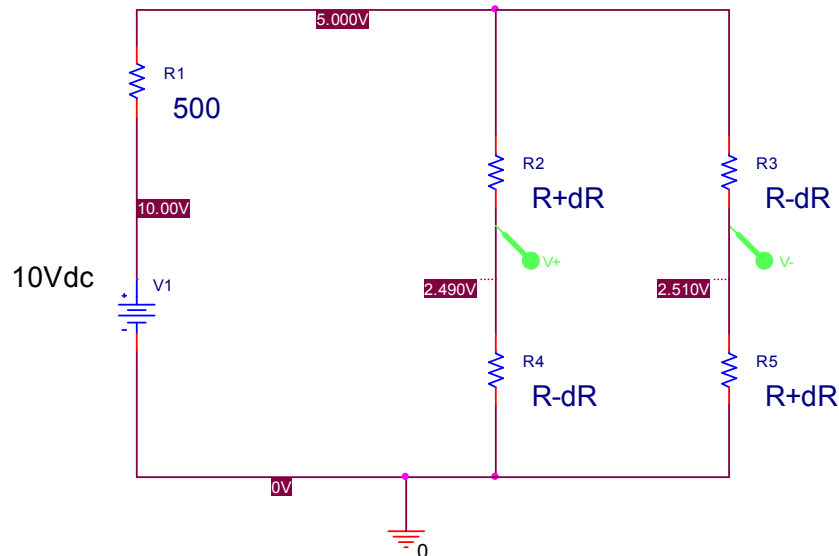4) (6pt) The position of the beam is measured using a bridge circuit consisting of four identical strain gauges, two on the top of the beam and two on the bottom. They are configured with a DC voltage source as shown below. Note that the nominal resistance of each strain gauge is represented as R and the change in the resistance of the strain gauge due to the deflection of the beam is dR . Resistor $R1$ is 500 Ohms and the voltage source is set to $10V$. The voltages observed at each point in the circuit are shown. Since the font is a bit small, they are $10V$, $5V$, $2.49V$ and $2.51V$. Using this information, determine the values of R and dR .



Total resistance in each side of bridge = $R + dR + R - dR = 2R$

Total resistance of combined sides: $2R || 2R = R$

To get the top of the bridge to be 5V, with a voltage divider:

$$10 \frac{R}{R + 500} = 5 \Rightarrow R = 500$$



For left side, to get 2.49V with a voltage divider:

$$5 \frac{R - dR}{R - dR + R + dR} = 2.49 \Rightarrow 5 \frac{R - dR}{2R} = 2.5 + 5 \frac{-dR}{2R} = 2.49$$



$$5 \frac{-dR}{2R} = -0.01 \Rightarrow dR = \frac{2R(0.01)}{5} = \frac{2(500)(0.01)}{5} = 2 \text{ Ohms}$$

Question I – Bridges and Damped Sinusoids (continued)

5) (2pt) Which of the following can be modeled as cantilever beams? Circle the pictures of the appropriate examples and also show where the cantilever is located. **ALL ARE CANTILEVERS**

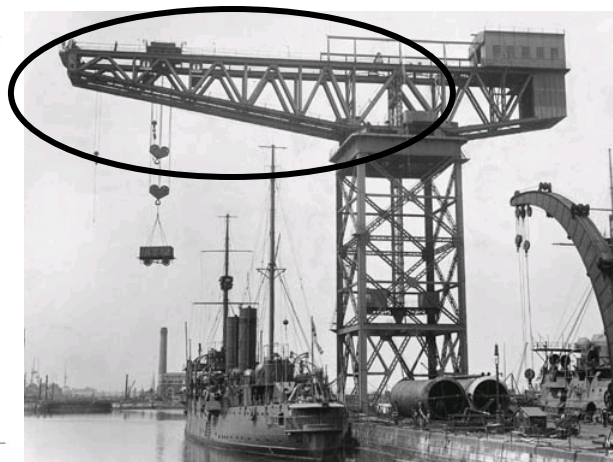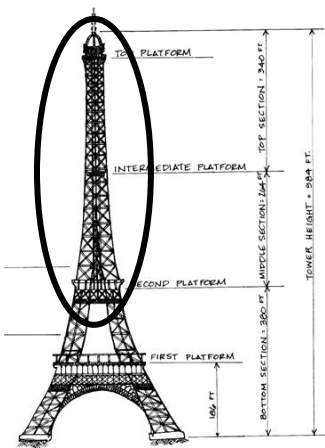

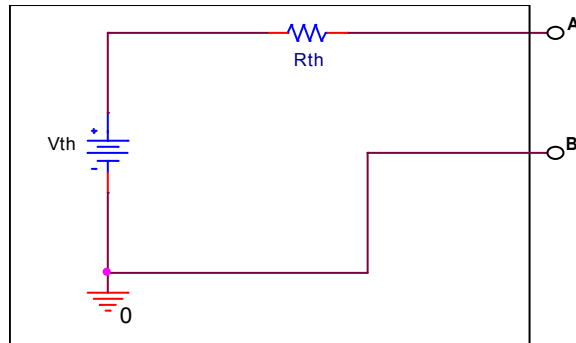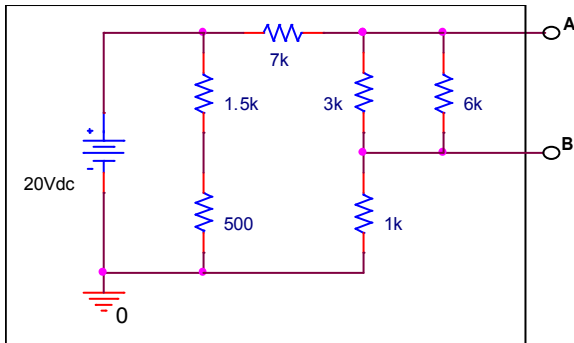Question II – Thevenin Equivalents (20 points)



1) (5pt) Find the Thevenin equivalent voltage with respect to A and B for the circuit shown above left.

$$= 20 \frac{3 \parallel 6}{3 \parallel 6 + 7 + 1} = 20 \frac{2}{2 + 7 + 1} = 4V$$

2) (5pt) Find the Thevenin equivalent resistance with respect to A and B for the circuit shown above left.

$$= 3k \parallel 6k \parallel (7k + 1k) = 2k \parallel 8k = 1.6k \text{ ohms}$$

3) (3pt) What value load resistance added between A and B will have the largest possible **voltage** across it and how much power will be dissipated in the resistor?

Max voltage when $R_{load} = \infty$ ohms (open circuit)

$$P = V \times I = 4V \times 0A = 0W$$

4) (3pt) What value load resistance added between A and B will have the largest possible **current** through it and how much power will be dissipated in the resistor?


Max current when $R_{load} = 0$ ohms (short circuit)

$$P = V \times I = 0V \times (4/1.6k)A = 0W$$

5) (4pt) If the DC voltage source is replaced with an AC source and a $1 \mu F$ capacitor is placed across A and B, what is the corner frequency (in radians/s) of the resultant RC filter? Is it a HPF or a LPF?

$$\omega = 1/(RC) = 1/(1.6k \times 1\mu F) = 1/1.6ms = 625 \text{ rad/s} \quad \text{LPF}$$

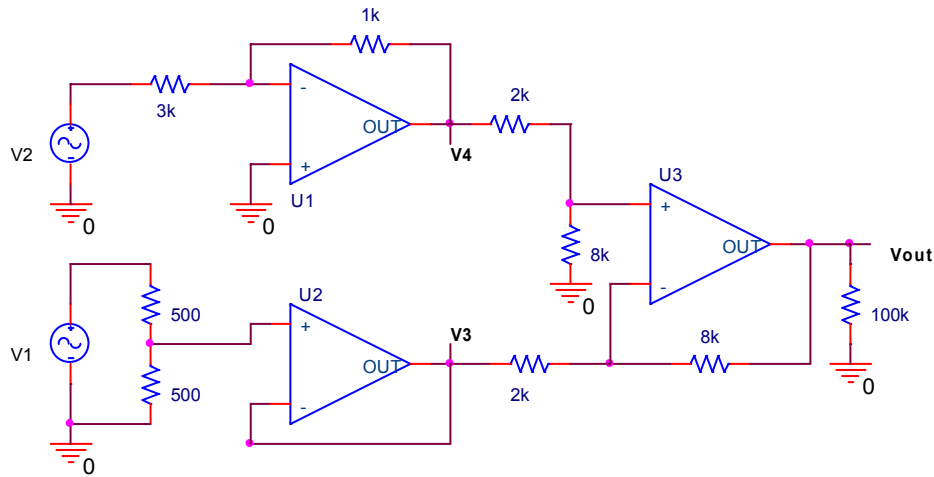Question III – Op-Amp Applications (15 points)



Assume that ± 9 Volt power supplies have been properly connected to all three op-amps in the circuit above.

1) (3pt) The circuit has 3 op-amps labeled as U1, U2, and U3. State what the op-amp circuit is for each. Choices are: 1. Follower/Buffer, 2. Inverting Amp, 3. Non-inverting Amp, 4. Differentiator, 5. Integrator, 6. Adding (Mixing) Amp, 7. Difference (Differential) Amp.

U1 Circuit: INVERTING AMP U2 Circuit: FOLLOWER U3 Circuit: DIFFERENCE AMP

2) (4pt) Determine the voltage, relative to ground, at points V3 and V4 as functions of V1 and V2.

a) Voltage at point V3:

$$V3 = V1 \frac{500}{500 + 500} = \frac{V1}{2}$$

b) Voltage at point V4:

$$V4 = V2 \left(-\frac{Rf}{Ri} \right) = V2 \left(-\frac{1k}{3k} \right) = -\frac{V2}{3}$$

Question III – Op-Amp Applications (continued)

3) (2pt) Determine the output voltage, V_{out} , as a function of V_3 and V_4 .

$$V_{out} = \left(\frac{R_2}{R_1}\right)(V_4 - V_3) = \left(\frac{8k}{2k}\right)(V_4 - V_3) = 4(V_4 - V_3)$$

4) (2pt) Now find V_{out} as a function of V_1 and V_2 .

$$V_{out} = 4(V_4 - V_3) = 4\left(-\frac{V_2}{3} - \frac{V_1}{2}\right) = -\frac{4}{3}V_2 - 2V_1$$


5) (4pt) If $V_1 = +2$ Volts, how large can V_2 become before the output will no longer match the result given by your answer in 4)?.

$$V_{out} = -9V < -\frac{4}{3}V_2 - 2V_1 = -\frac{4}{3}V_2 - 4V$$

$$-5V < -\frac{4}{3}V_2$$

$$V_2 < \frac{15}{4} \text{ Volts} = 3\frac{3}{4} \text{ Volts}$$

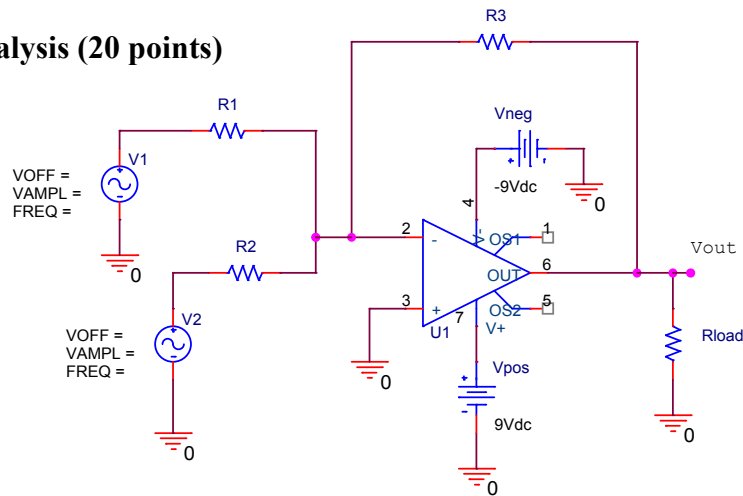Question IV – Op-Amp Analysis (20 points)



Above is a Capture schematic of an op-amp circuit that you should recognize. Assume the op-amp is ideal.


1) (2pt) What type of circuit is it?

Adder

2) (2pt) When assuming that the op-amp is ideal, what are the two golden rules to analyze this circuit?

$V_A = V_B$ or $V_+ = V_-$, $I_A = I_B = 0$ or $I_- = I_+ = 0$

3) (4pt) Use these rules to derive an expression for V_{out} in terms of R_1 , R_2 , R_3 , V_1 and V_2 . (Hint: you may exclude R_{load} .) Redraw the circuit (Remove the op-amp and draw two circuits: one for the + and one for the – input terminals of the op-amp, **draw currents I_1 , I_2 , and I_3 through R_1 , R_2 , and R_3 respectively, on the circuit**).

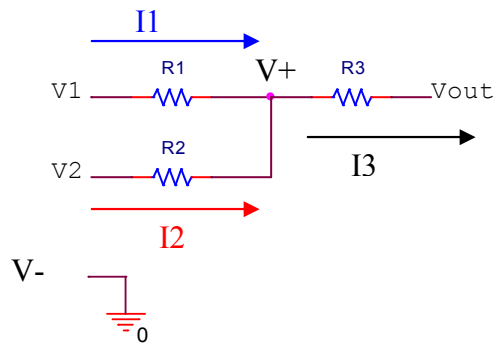

Question IV – Op-Amp Analysis (continued)

4) (4pt) Write equations for the two circuits (use the current relationship).

$$I_3 = I_1 + I_2$$

$$I_1 = \frac{V_1 - V_A}{R_1}$$

$$I_2 = \frac{V_2 - V_A}{R_2}$$

$$I_3 = \frac{V_A - V_{out}}{R_3}$$

$$\frac{V_A - V_{out}}{R_3} = \frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2}$$

Some may apply the $V_- = V_+$ rule first and get the equation in 5) as their answer.

5) (4pt) Simplify using the golden rules and solve for V_{out} .

$$V_A = V_B = 0$$

$$\frac{-V_{out}}{R_3} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$


$$V_{out} = -R_3 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

6) (4pt) If $V_1 = 0.2$ V, $V_2 = 0.3$ V, $R_1 = 3$ k Ω , $R_2 = 3$ k Ω , and $R_3 = 12$ k Ω , what is the value of V_{out} in volts? (Show your work.)

$$V_{out} = \frac{-12k}{3k}(0.2) + \frac{-12k}{3k}(0.3)$$

$$V_{out} = -2V$$

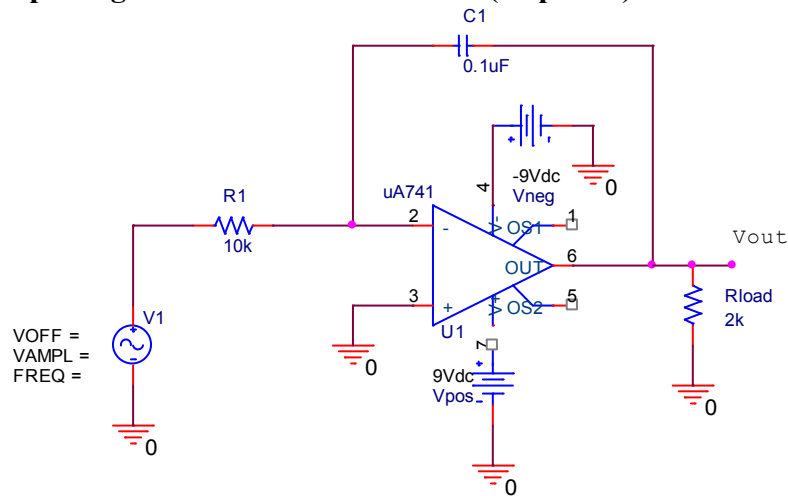Question V – Op-Amp Integrators and Differentiators (25 points)



Assume the op-amp in the circuit above is ideal.

1) (1pt) Above is a Capture schematic of an op-amp circuit that you should recognize. What type of circuit is it?

Ideal integrator

2) (4pt) For this circuit the input is sinusoidal. What is $H(j\omega)$, the transfer function, for this circuit? $H(j\omega) = V_{out}/V_1$. You must use the component values; don't leave the answer in terms of R_1 or C_1 . Simplify your answer.

$$H(j\omega) = \frac{-1}{j\omega R_1 C_1} = \frac{-1}{j\omega(10k)(0.1\mu)} = \frac{-1}{j\omega(0.001)} = \frac{1000j}{\omega}$$


3) (4pt) If a 1k resistor is added in parallel with C_1 , what is the corner frequency in Hertz?

$$f_c = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(1000)(0.1\mu)} = 1,591\text{Hz}$$

4) (1pt) If the input frequency is 10 kHz, will it operate as it should?

Works as an integrator above ω_c so it will operate correctly

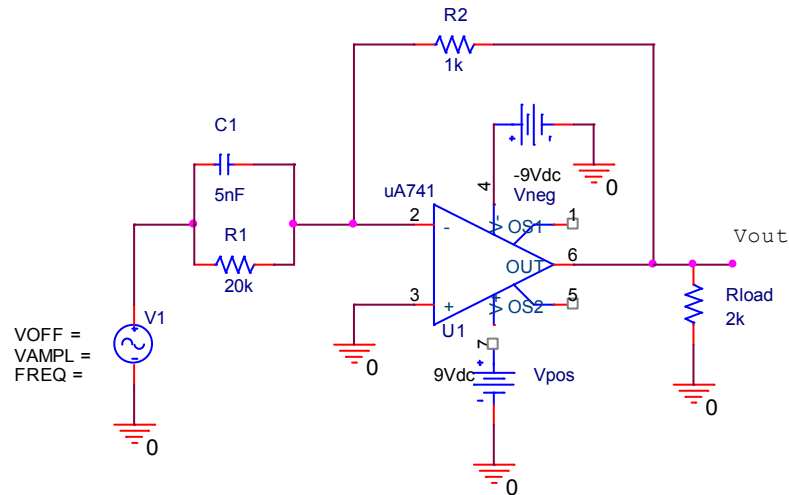Question V – Op-Amp Integrators and Differentiators (continued)



Assume that the input is sinusoidal and we want to find $H(j\omega)$, the transfer function, for this circuit. We know that when the non-inverting terminal of an op amp circuit is grounded, $H(j\omega) = -Z_f/Z_{in}$.

5) (1pt) Find Z_f and substitute values for components.

$$Z_f = R_2 = 1k, \quad Z_f = 1k$$

6) (4pt) Find Z_{in} . Substitute values for the components. Simplify your answer.

$$Z_{in} = \frac{\frac{1}{j\omega C_1} * R_1}{\frac{1}{j\omega C_1} + R_1} = \frac{R_1}{1 + \omega R_1 C_1} = \frac{20k}{1 + \omega(20k)(5n)} = \frac{20k}{1 + j\omega(0.1m)}$$

$$Z_{in} = \frac{20k}{1 + j\omega(0.0001)} = \frac{200M}{10k + j\omega}$$

7) (4pt) Using 5) and 6) determine the transfer function, $H(j\omega)$, for the circuit. Substitute component values. Simplify your answer.

$$H(j\omega) = \frac{-Z_f}{Z_{in}} = \frac{1k}{\frac{20k}{1 + j\omega(0.0001)}} = \frac{1k}{20k} (1 + j\omega(0.0001))$$

$$H(j\omega) = -0.05 - j\omega(0.000005)$$

Question V – Op-Amp Integrators and Differentiators (continued)

8) (3pt) At high frequency this circuit in 5) acts like a _____.
 Fill in the blank using one of the following: a) Inverting Amplifier, b) Non-inverting Amplifier,
 c) Differential Amplifier, d) Adder, e) Integrator, f) Differentiator, g) none of a thru e.

Differentiator

(Also may accept g) none of a through e because the transfer function approaches infinity and won't be a useful differentiator)

9) (3pt) Now assume that V_{in} is a 0.2V DC source. What is V_{out} ?

$$H(j\omega) = -0.05 - j\omega(0.000005)$$

DC input is zero frequency. The transfer function at zero frequency (ω approaches zero) is $H(j\omega) = -0.05$. The phase is π , so the signal is inverted.

$$A_{out} = |H| * V_{in} = 0.05 * 0.2 = 0.01$$

The signal is inverted so $V_{out} = -0.01V$

Also can realize that the capacitor behaves like an open circuit at low frequency. The circuit turns into an inverting amplifier.

$$V_{out} = -R_2/R_1(V_{in}) = -(1k/20k)(0.2) = -0.01V$$