

## 1) Nodal Analysis: Known Voltages

Which of the following nodal voltages do we already know the values of in a circuit?

all voltages in parallel

19%

ground ✓

93%


open circuit voltages

16%

nodes connected to the "+" side of voltage sources ✓

77%

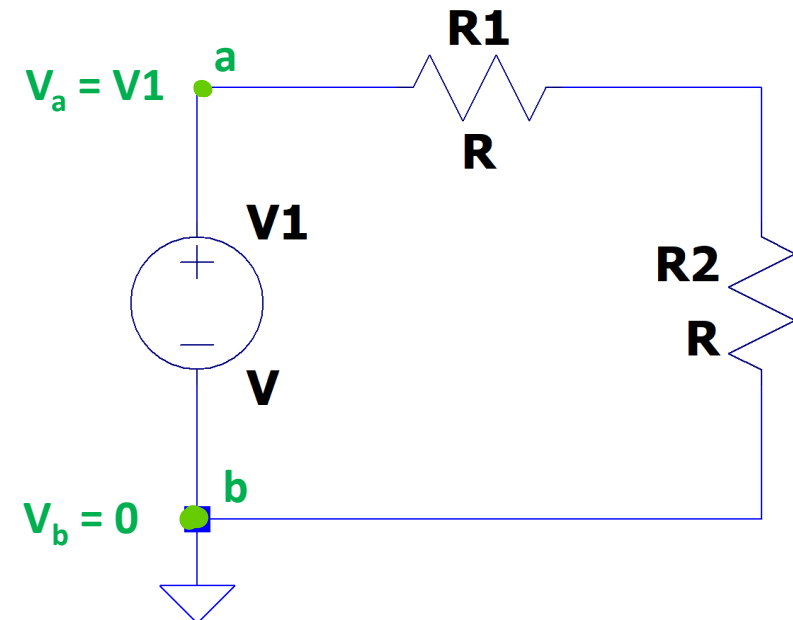- In a circuit, we define ground to be at a potential of  $V = 0V$ , so we always know what the voltage of a node connected to ground is
- When a voltage source is connected between some node and ground, we also know the voltage at that node: it's equal to the voltage that the voltage source supplies.



## 2) Nodal Analysis: Unknown Voltages

When using nodal analysis, what are the unknown variables that we are solving for?

currents at each node

10%

current through each resistor

5%

voltage at each node

77%

voltage across each resistor

8%

- When using the circuit analysis method of nodal analysis, we are solving for the voltages at each of the nodes in the circuit. In this case we have 3 total nodes, 2 nodes at which we already know the voltage ( $V_a = V_1$ ,  $V_b = 0V$ ), and 1 node whose voltage we need to solve for: c.

