

1) Overview of Lab 02: Parts A & B

- Purpose:
- 1) Introduce you to linearity (extremely important)
 - 2) Give you more tools for designing & solving circuits (nodal analysis & some linear algebra)
 - 3) Provide examples of non-linearity as a comparison (diodes & op-amps)

Part A: Defining Linear/Non-Linear Device Characteristics


- today {
- a) Resistors: draw, simulate, and measure IV characteristic
 - b) Diodes: draw, simulate, and measure IV characteristic
 - c) Resistance vs Differential Resistance
 ↓ same for all I and V ↓ R depends on I and V

Part B: Solving Linear Resistive Networks Using Nodal Analysis

- Friday {
- a) Nodal Analysis: solve for the unknown nodal voltages in a circuit by summing currents at nodes (KCL)
 - b) Design circuits using nodal analysis

2) Linear and Non-Linear Current-Voltage (IV) Characteristics

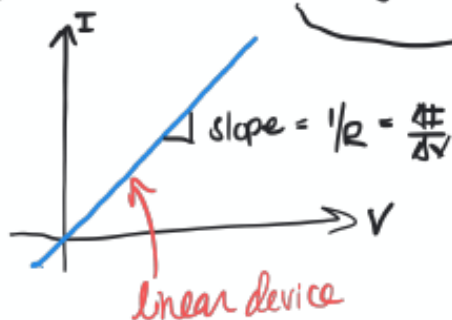i) Resistor: $V = IR$ $y(x) = mx$ $I(V) = V/R$



$$\frac{\Delta I}{\Delta V} = 1/R$$


• slope is the same at all values of V and I (R is constant)

$$R \neq R(I) \neq R(V)$$

ii) Diode: allows current to pass in one direction, but not in the other


a) Simple ideal diode model

circuit symbol :

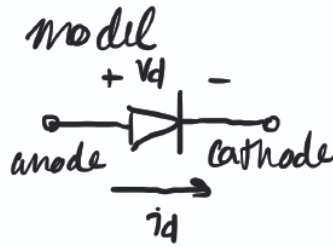


actual appearance :


Si diode

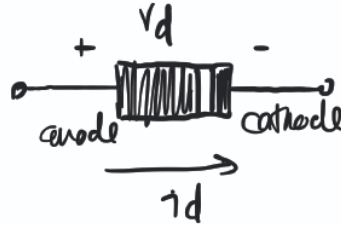

LED

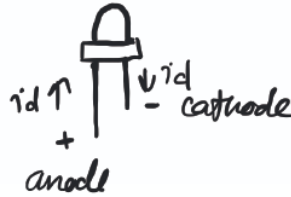

IV Characteristic (simple ideal)

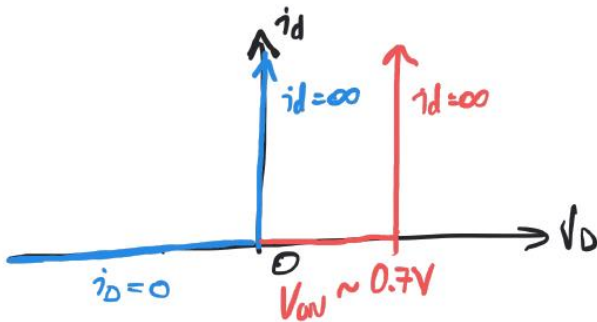

$$i_d = \begin{cases} 0 & \text{for } V_D \leq 0 \\ \infty & \text{for } V_D > 0 \end{cases}$$

acts like a voltage-controlled switch:

- open circuit when $V_D \leq 0$
- short circuit when $V_D > 0$

In reality, diodes have a "turn-on" voltage (V_{on}) - current starts flowing when $V_D > V_{on}$

V_{on} for Si diodes: 0.7V


for LEDs: 1.8V +

$$i_d = \begin{cases} 0 & \text{for } V_D \leq V_{on} \\ \infty & \text{for } V_D > V_{on} \end{cases}$$

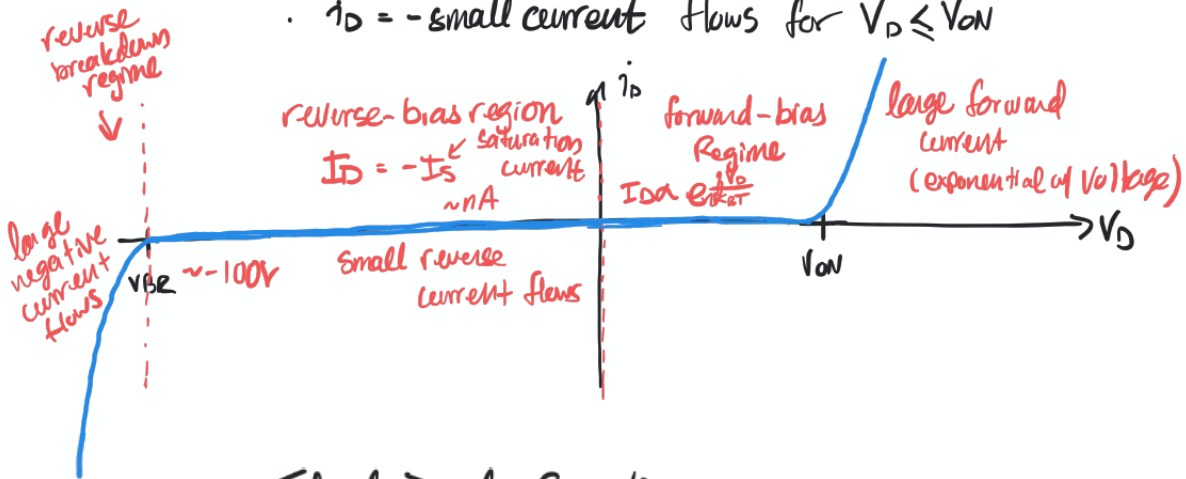b) Model #2: real diode

• Differences:

- $i_D \neq \infty$ for $V_D > V_{ON}$ (curve: resistance is not 0)
- if $V_D < V_{BR}$ (breakdown voltage) a large negative current will flow
- $i_D = -\text{small current}$ flows for $V_D \leq V_{ON}$



Ideal Diode Equation

$$I_D = I_S \left(e^{\frac{qV_D}{n k_B T}} - 1 \right)$$


Annotations for the equation:

- I_S : saturation current
- qV_D : charge diode voltage
- n : ideality factor 1-2
- $k_B T$: Boltzmann's constant
- T : temperature of diode material

- if $V_D \ll 0$, $I_D = I_S (0 - 1) = -I_S$
- if $V_D \geq V_{ON}$, $I_D \sim I_S e^{\frac{qV_D}{k_B T}}$
- Note: This equation does not treat reverse breakdown

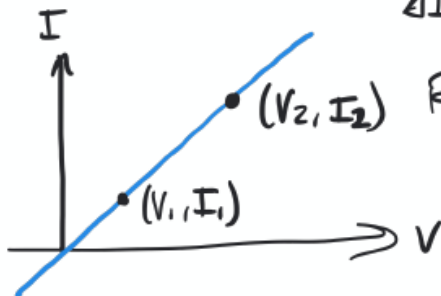iii) Differential Resistance

Via Ohm's Law: $R = \frac{\Delta V}{\Delta I}$



$R = \frac{V_2 - V_1}{I_2 - I_1}$ - This only works for a straight line

Calculus: if ΔV and ΔI are very small:

$\Delta V \rightarrow dV$
 $\Delta I \rightarrow dI$ } Infinitesimal change in V and I → defines slope at a single point

→ we can find slope of any curve

For a general $I-V$ curve:


If $R = \frac{\Delta V}{\Delta I} \rightarrow R_{diff} = \left. \frac{dV}{dI} \right|_{(V_0, I_0)}$

differential resistance at a point (V_0, I_0)


R_{diff} : local measure of resistance: how much does voltage change (dV) for a change in current (dI)?

$dV = R_{diff} \cdot dI$ at a point (V_0, I_0)


Forward-bias regime

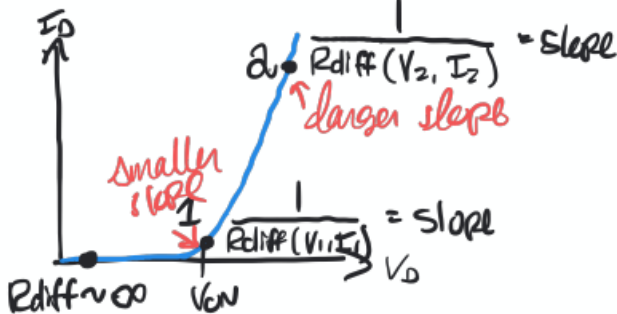

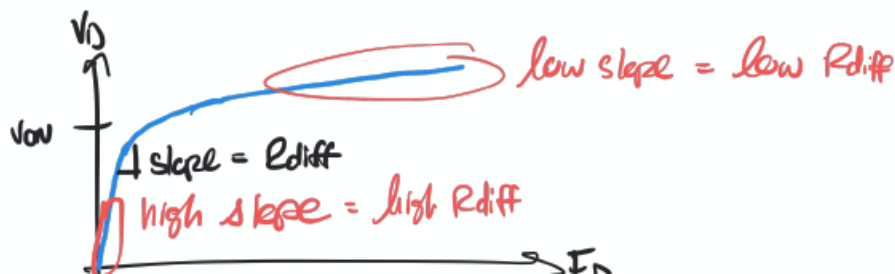Which point has lower R_{diff} ? $R_{diff}(2) < R_{diff}(1)$



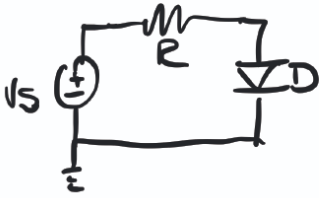iv) Current - Limiting Resistor : R in series with a diode.



why · If current is too high, it will damage the diode. Heat from current destroys the materials. ALWAYS use a resistor in series with a diode

- Diode voltage is insensitive to current changes in forward-bias \rightarrow easier to control a diode using current