

Intro to ECSE: Nodal Analysis 2/17/23

Circuit Analysis Method #3: Nodal Analysis

→ How is it different from KCL/KVL/Ohm's Law?

1) More "efficient": no "guessing" which equations to use and usually fewer equations needed

2) Covers more of the circuit: can handle voltage sources


3) Has an equation to determine # of equations needed

of unknowns → # of linearly independent equations needed = total # of nodes - ^{known nodal voltages} # of voltage sources - 1 _{ground}

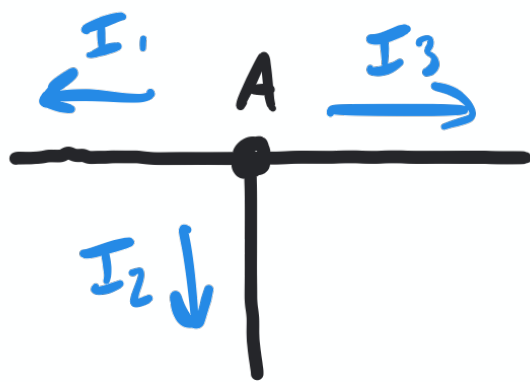4) Passive Sign Convention (Current flow)

→ set direction of current flow first

my convention: ^{KCL} sum of all outgoing currents is 0




$$I_1 + I_2 + I_3 = 0$$

KCL

Nodal Analysis Example

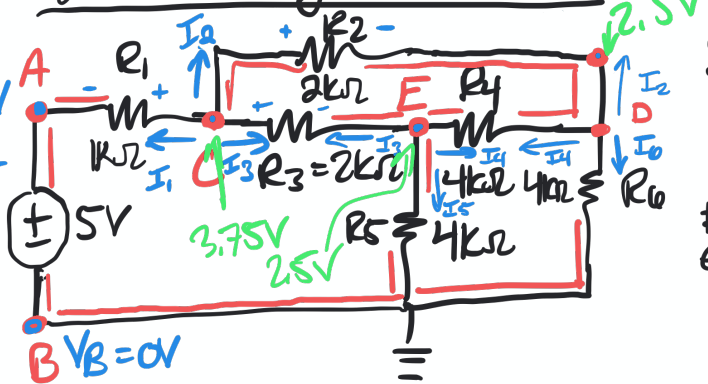Must express in terms of nodal voltages
 $V_A = 5V$
 $I_1 = \frac{V_A - V_C}{R_1} = \frac{V_C - V_A}{R_1}$
 $I_2 = \frac{V_C - V_D}{R_2}$
 $I_3 = \frac{V_C - V_E}{R_3}$



Step 1: How many equations do we need?
 # of eqns = $\frac{\text{total \# nodes}}{\text{\# of v. sources}} - 1 = 5 - 1 - 1 = 3$
 (would need 0 for KVL/KCL)

Step #2: label the nodes and the known nodal voltages

node A voltage
 $V_A = 5V \leftarrow$ voltage source
 $V_B = 0V \leftarrow$ ground

Step #3: Do KCL at each node

Node C: $I_1 + I_2 + I_3 = 0$
 $\frac{V_C - V_A}{R_1} + \frac{V_C - V_D}{R_2} + \frac{V_C - V_E}{R_3} = 0 \leftarrow$ KCL eqn. for node C

Node D: $I_2 + I_4 + I_6 = 0$
 $\frac{V_D - V_C}{R_2} + \frac{V_D - V_E}{R_4} + \frac{V_D - V_B}{R_6} = 0$

Node E: $I_3 + I_4 + I_5 = 0$
 $\frac{V_E - V_C}{R_3} + \frac{V_E - V_D}{R_4} + \frac{V_E - V_B}{R_5} = 0$

Step #4: Put in standard form & simplify

Node C: $V_A \left(-\frac{1}{R_1}\right) + V_B(0) + V_C \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + V_D \left(-\frac{1}{R_2}\right) + V_E \left(-\frac{1}{R_3}\right) = 0$
 source = constant $\rightarrow V_C \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + V_D \left(-\frac{1}{R_2}\right) + V_E \left(-\frac{1}{R_3}\right) = \frac{V_A}{R_1}$

Node D: $V_B \left(-\frac{1}{R_6}\right) + V_C \left(-\frac{1}{R_2}\right) + V_D \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_6}\right) + V_E \left(-\frac{1}{R_4}\right) = 0$

Node E: $V_C \left(-\frac{1}{R_3}\right) + V_D \left(-\frac{1}{R_4}\right) + V_E \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right) = 0$

Step #5: Put in matrix form

$$\begin{matrix} \text{node C} \\ \text{node D} \\ \text{node E} \end{matrix} \begin{matrix} A \\ \\ \\ \end{matrix} \begin{matrix} x \\ \\ \\ \end{matrix} = \begin{matrix} \text{constants} \\ b \\ \\ \end{matrix}$$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} & -\frac{1}{R_3} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_6} & -\frac{1}{R_4} \\ -\frac{1}{R_3} & -\frac{1}{R_4} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_C \\ V_D \\ V_E \end{bmatrix} = \begin{bmatrix} \frac{V_A}{R_1} \\ 0 \\ 0 \end{bmatrix}$$

$V_A = 5V = \text{constant}$

$$\begin{bmatrix} (\frac{1}{1000} + \frac{1}{2000} + \frac{1}{2000}) & (-\frac{1}{2000}) & (-\frac{1}{2000}) \\ (-\frac{1}{2000}) & (\frac{1}{2000} + \frac{1}{4000} + \frac{1}{4000}) & (-\frac{1}{4000}) \\ (-\frac{1}{2000}) & (-\frac{1}{4000}) & (\frac{1}{2000} + \frac{1}{4000} + \frac{1}{4000}) \end{bmatrix} \begin{bmatrix} V_C \\ V_D \\ V_E \end{bmatrix} = \begin{bmatrix} 5/1000 \\ 0 \\ 0 \end{bmatrix}$$

$$A^{-1}b = \begin{bmatrix} V_C \\ V_D \\ V_E \end{bmatrix} = \begin{bmatrix} 3.75 \\ 2.5 \\ 2.5 \end{bmatrix}$$

Matlab