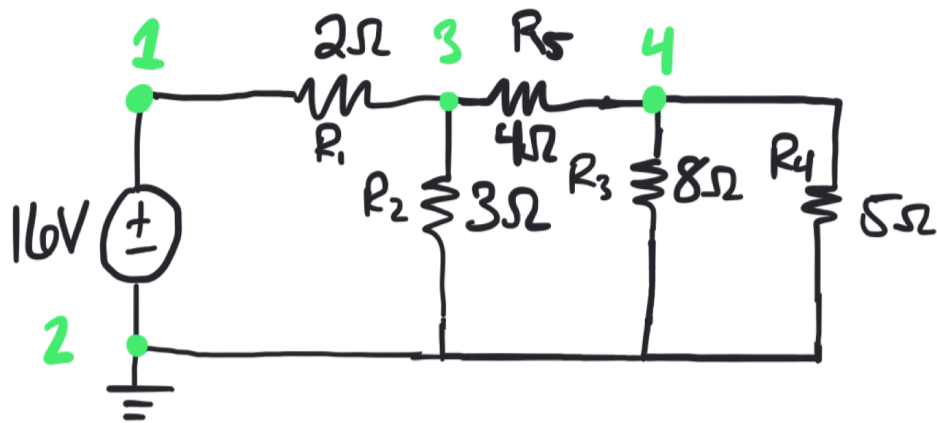



Intro to ECSE: Nodal Analysis Example Problems

1) Multiple Voltage Sources



How many unknowns?
 # nodes total: 4
 # known nodes: 2: node 1: 16V
 node 2: 0V
 # unknown nodes: 2: node 3, node 4

What if we add another voltage source?

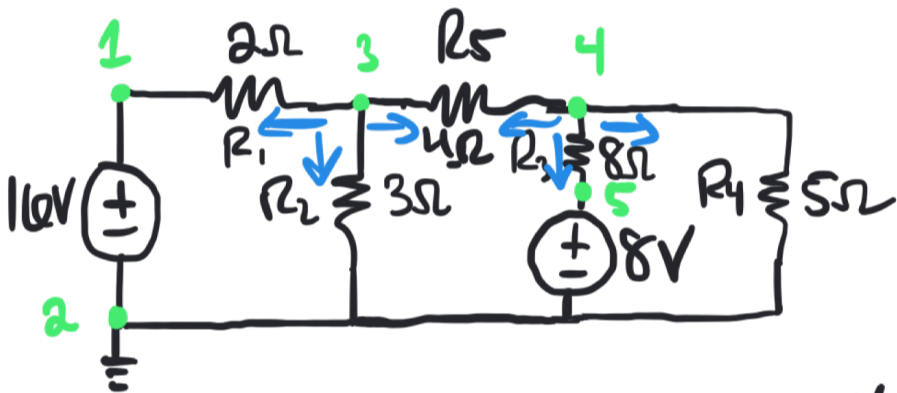

node 3: $\frac{V_3 - 16}{R_1} + \frac{V_3}{R_2} + \frac{V_3 - V_4}{R_3} = 0$

$$V_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + V_4 \left(-\frac{1}{R_3} \right) = \frac{16}{R_1}$$

node 4: $\frac{V_4 - V_3}{R_3} + \frac{V_4 - 8}{R_4} + \frac{V_4}{R_5} = 0$


How many unknowns?
 # nodes total: 5
 # known nodes: 3: node 1, node 2, node 5: 8V
 # unknown nodes: 2: node 3, node 4

$$V_3 \left(-\frac{1}{R_3} \right) + V_4 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{8}{R_4}$$

$$\begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{pmatrix} \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} \frac{16}{R_1} \\ \frac{8}{R_4} \end{bmatrix}$$

$$\begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 8.054 \\ 5.502 \end{bmatrix}$$

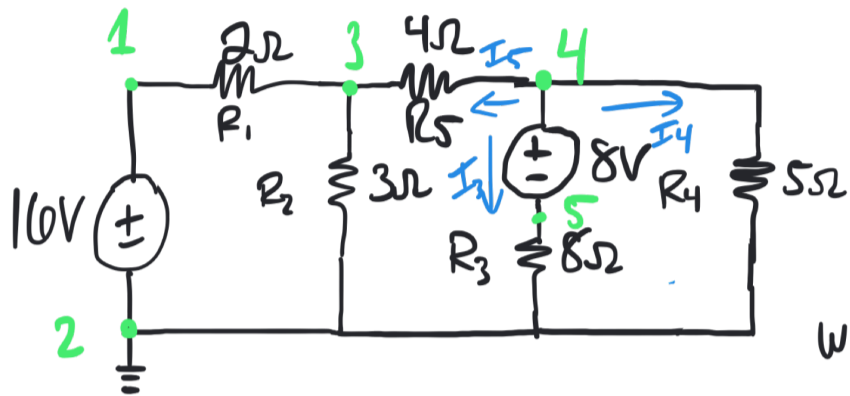What if we place a voltage such that it's not grounded?



Which are the unknown nodes?

Known nodes are: 1: 10V
2: 0V

We also know: $V_4 - V_5 = 8V$

replace all V_5 with $V_5 = V_4 - 8V$

in your equations, then solve as usual

node 3: $\frac{V_3 - 10V}{2\Omega} + \frac{V_3}{3\Omega} + \frac{V_3 - V_4}{4\Omega} = 0$

$$V_3 \left(\frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{4\Omega} \right) + V_4 \left(-\frac{1}{4\Omega} \right) = \frac{10V}{2\Omega}$$

node 4: $\frac{V_4 - V_3}{4\Omega} + \frac{V_5}{8\Omega} + \frac{V_4}{5\Omega} = 0$ $\frac{V_4 - V_3}{4\Omega} + \frac{V_4 - 8V}{8\Omega} + \frac{V_4}{5\Omega} = 0$


$V_3 \left(-\frac{1}{4\Omega} \right) + V_4 \left(\frac{1}{4\Omega} + \frac{1}{8\Omega} + \frac{1}{5\Omega} \right) = \frac{8V}{8\Omega}$
current flowing from 4 to 5 must be the same as from 5 to 2 (series)

$\Delta \text{ so } I_3 = \frac{V_5}{8\Omega} = \frac{V_4 - 8V}{8\Omega}$

node 5: $V_4 - 8V = V_5$


$$\begin{bmatrix} \left(\frac{1}{2\Omega} + \frac{1}{3\Omega} + \frac{1}{4\Omega} \right) & \left(-\frac{1}{4\Omega} \right) \\ \left(-\frac{1}{4\Omega} \right) & \left(\frac{1}{4\Omega} + \frac{1}{8\Omega} + \frac{1}{5\Omega} \right) \end{bmatrix} \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 10V/2\Omega \\ 8V/8\Omega \end{bmatrix} \quad \begin{bmatrix} V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 8.654 \\ 5.502 \end{bmatrix}$$

2) Voltage-dependent voltage sources

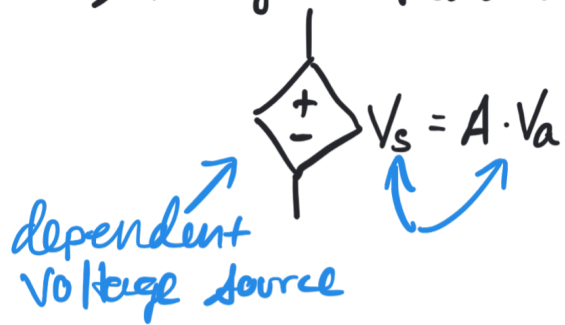

Voltage supplied by source depends on a voltage somewhere else in the circuit
 → op-amps are modeled this way

$$A = 10^5$$

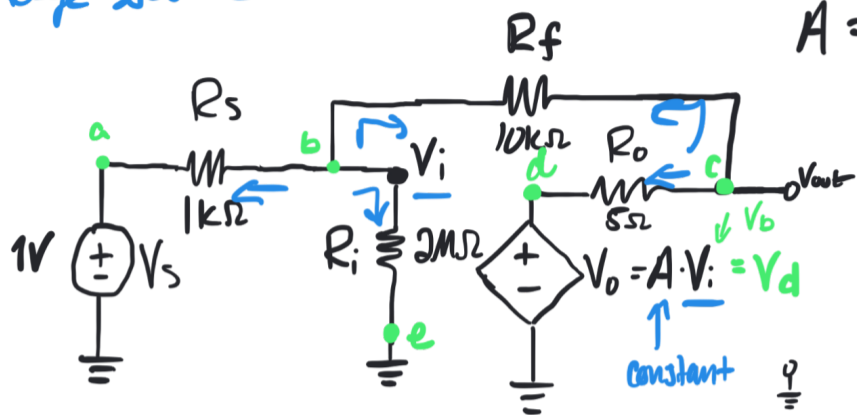

• How many nodes?
 5 total

Known: $V_a = 1V$
 $V_e = 0V$

$$V_d = A V_i = A V_b \quad A = 10^5$$

Unknown: V_b and V_c

at node b:
$$\frac{V_b - 1V}{1k\Omega} + \frac{V_b}{2M\Omega} + \frac{V_b - V_c}{10k\Omega} = 0$$

$$V_b \left(\frac{1}{1k\Omega} + \frac{1}{2M\Omega} + \frac{1}{10k\Omega} \right) + V_c \left(-\frac{1}{10k\Omega} \right) = \frac{1}{1k\Omega}$$

at node c:
$$\frac{V_c - V_d}{5\Omega} + \frac{V_c - V_b}{10k\Omega} = 0$$

$$V_b \left(-\frac{1}{10k\Omega} - \frac{A}{5\Omega} \right) + V_c \left(\frac{1}{5\Omega} + \frac{1}{10k\Omega} \right) = 0$$


$$\begin{bmatrix} \left(\frac{1}{1k\Omega} + \frac{1}{2M\Omega} + \frac{1}{10k\Omega} \right) & \left(-\frac{1}{10k\Omega} \right) \\ \left(-\frac{1}{10k\Omega} - \frac{10^5}{5\Omega} \right) & \left(\frac{1}{5\Omega} + \frac{1}{10k\Omega} \right) \end{bmatrix} \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} \frac{1}{1k\Omega} \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 0 \\ -10 \end{bmatrix}$$

$V_c = V_{out}$
 $V_s = V_{in}$

What does this circuit do? $V_{in} = 1V$

$$V_{out} = -10V$$

op-amp circuit: inverting amplifier

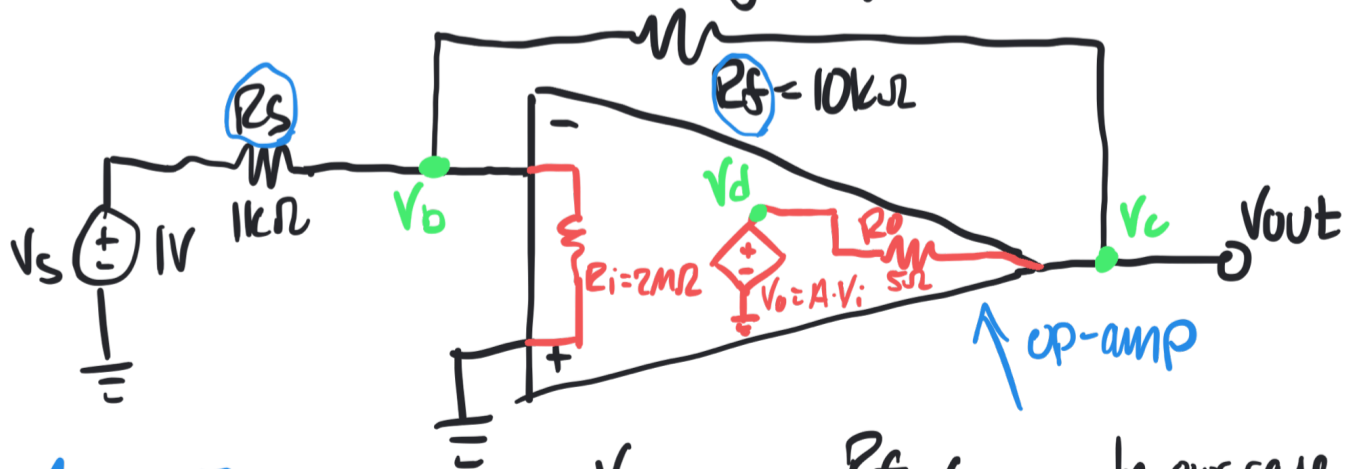

$A = 10^5$
 ↑
 intrinsic gain of the op-amp


$$V_{out} = -\frac{R_f}{R_s} V_{in}$$

In our case

$$V_{out} = -\frac{10k\Omega}{1k\Omega} \cdot 1V = -10V$$

KVL: loop 1: $-2V - 3V + 5V = 0$

loop 2: $-2V - 3V + 5V = 0$

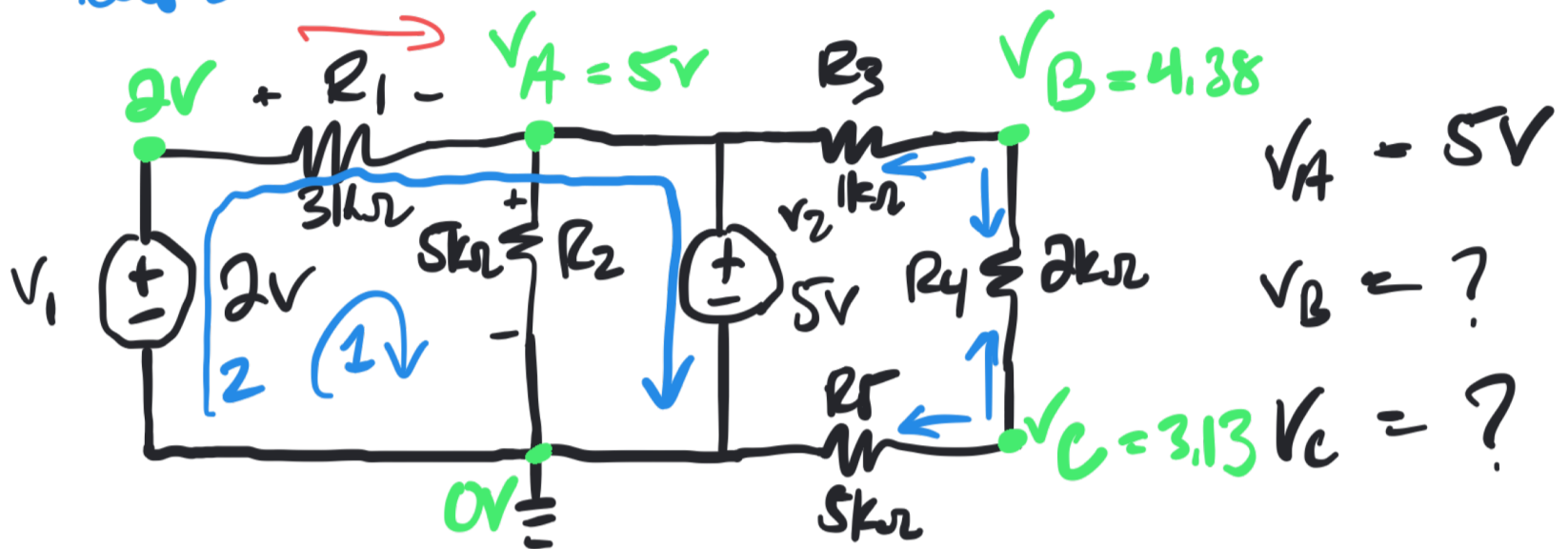

at node B: $\frac{V_B - 5V}{1k\Omega} + \frac{V_B - V_C}{2k\Omega} = 0$

$$V_B \left(\frac{1}{1k\Omega} + \frac{1}{2k\Omega} \right) + V_C \left(-\frac{1}{2k\Omega} \right) = \frac{5V}{1k\Omega}$$

at node C: $\frac{V_C - V_B}{2k\Omega} + \frac{V_C - 0V}{5k\Omega} = 0$

$$V_B \left(-\frac{1}{2k\Omega} \right) + V_C \left(\frac{1}{2k\Omega} + \frac{1}{5k\Omega} \right) = 0$$

$$\begin{bmatrix} \left(\frac{1}{1k\Omega} + \frac{1}{2k\Omega} \right) & \left(-\frac{1}{2k\Omega} \right) \\ \left(-\frac{1}{2k\Omega} \right) & \left(\frac{1}{2k\Omega} + \frac{1}{5k\Omega} \right) \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{5V}{1k\Omega} \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 4.38 \\ 3.13 \end{bmatrix}$$