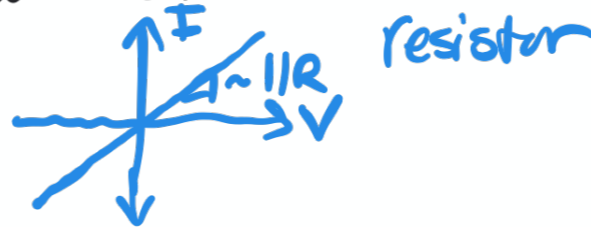


Intro to ECSE Lecture Notes 3/17/23


Properties of Linearity: Devices \rightarrow Circuits \rightarrow Systems

1) What have we said that linearity is so far?


1) circuit elements: I/V characteristics are linear



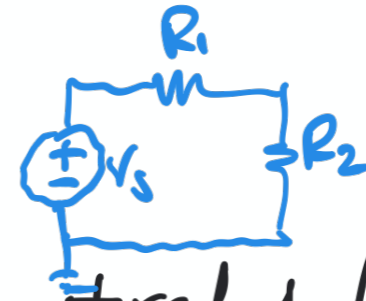2) Circuits: only consists of linear elements




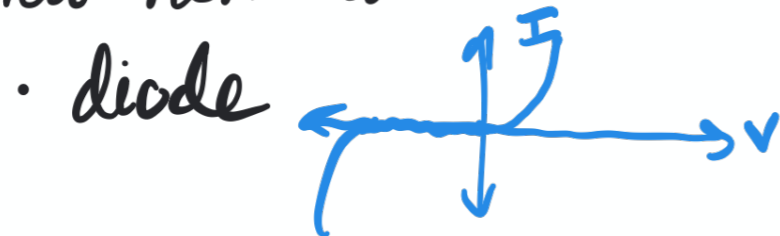• What non-linear circuit elements have you encountered so far?



• (transistors)

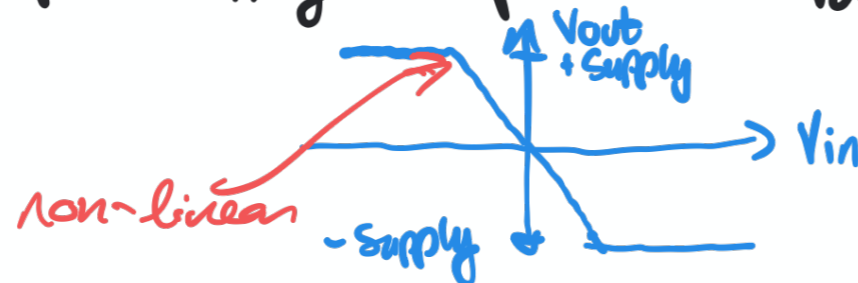• op-amps: voltage amplifiers: V_{out} vs V_{in}




· What does linearity mean for Systems?

· A system is linear if it satisfies the:

Superposition Principle:

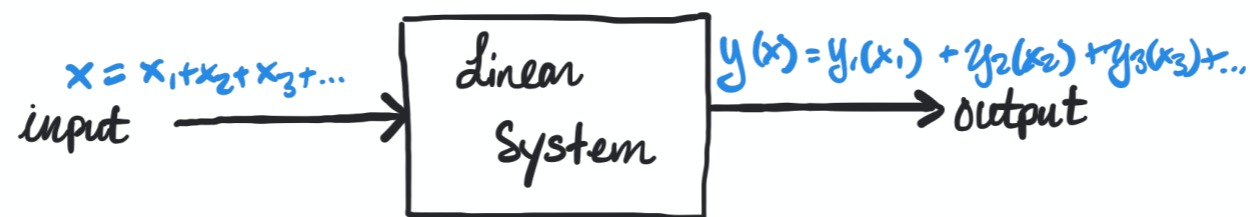+ if you have a sum of inputs: $x = x_1 + x_2 + x_3 + \dots$



· output is the sum of the $x \rightarrow y$ outputs for the individual inputs

· Linear Systems are described by linear functions.

· So, what are linear functions? A function $f(x)$ satisfies superposition via 2 simpler properties:

1) Additivity: $f(x_1 + x_2) = f(x_1) + f(x_2)$

multiplication: $f \rightarrow$ multiplies input by 2

$$x_1 = 2; x_2 = 3 \rightarrow f(x_1 + x_2) = 2 \cdot (2 + 3) = 10$$

2) Homogeneity: $F(\overset{\text{constant}}{c}x) = cF(x)$

$$f(x_1) = 2 \cdot 2 = 4; f(x_2) = 2 \cdot 3 = 6$$

$$f(x_1) + f(x_2) = 10$$

multiplication: same as above

$$f(x) = 2(3 \cdot 2) = 12; c f(x) = 3(2 \cdot 2) = 12$$


· So, if we $\overset{c=3}{\text{said}}$ that a circuit is a linear system, how does it follow Superposition?

2) How do we use superposition in a circuit?

- Find the output due to each **independent source**, with all other independent sources set to zero, then add all of the individual outputs together to find the solution.

- A source set to 0 is called a **dead source** (you "kill" them)




- Dead Voltage source:

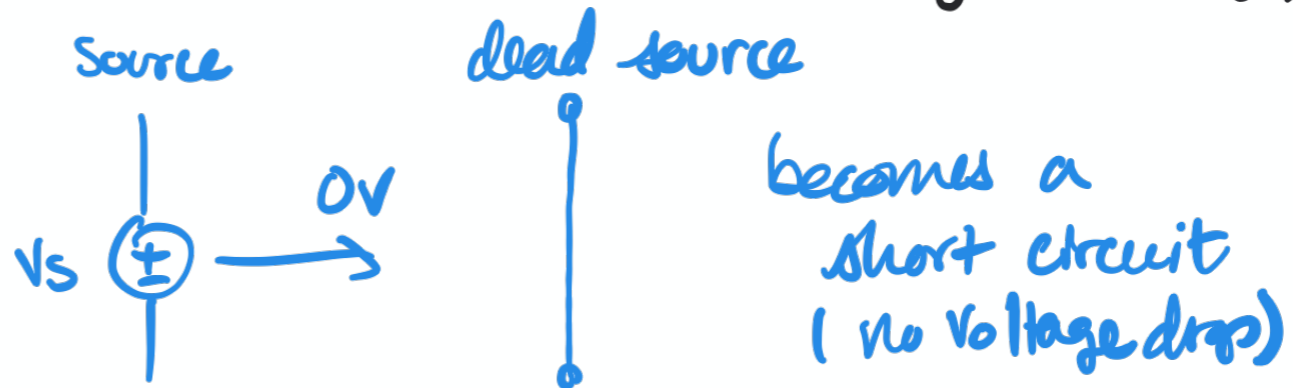

- Dead Current Source:



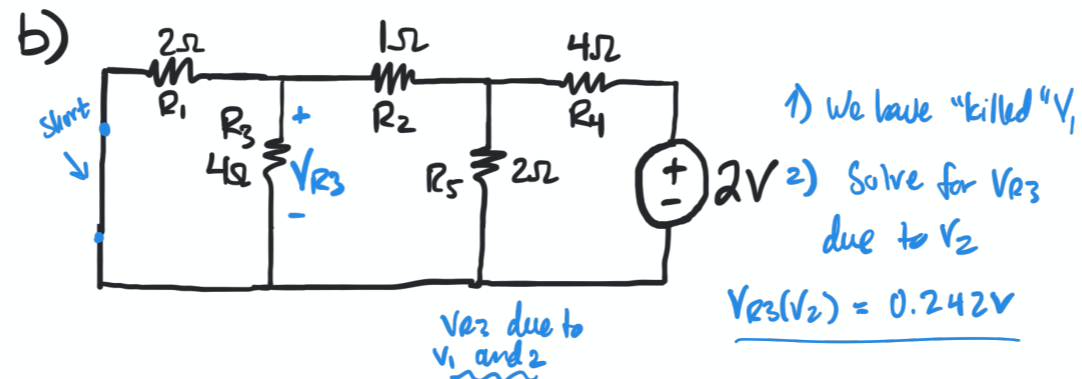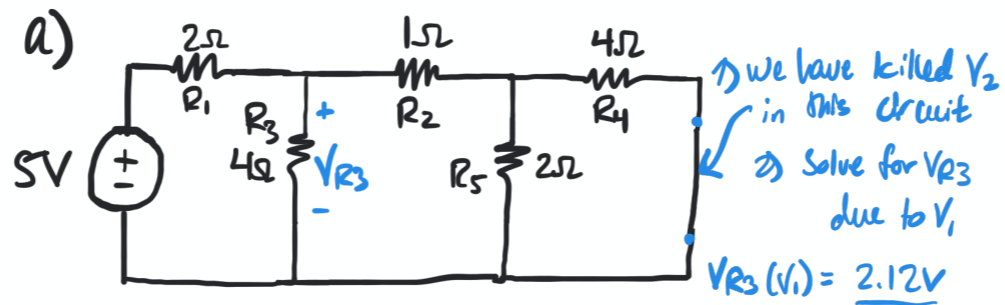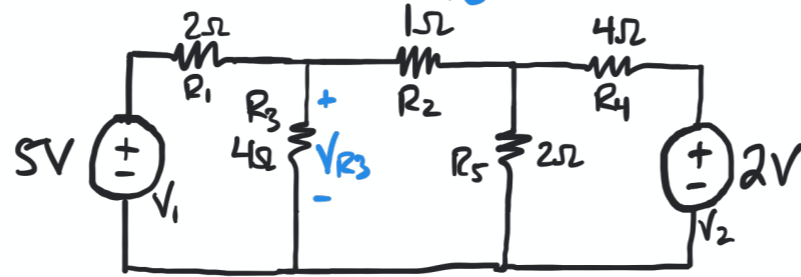Using Superposition to Solve a circuit
Find V_{R3}




Final answer $V_{R3}(V_1 + V_2) = V_{R3}(V_1) + V_{R3}(V_2)$
 $= 2.12V + 0.24V = 2.36V$

If you solve the original circuit with both sources on, you should get $V_{R3} = 2.36V$

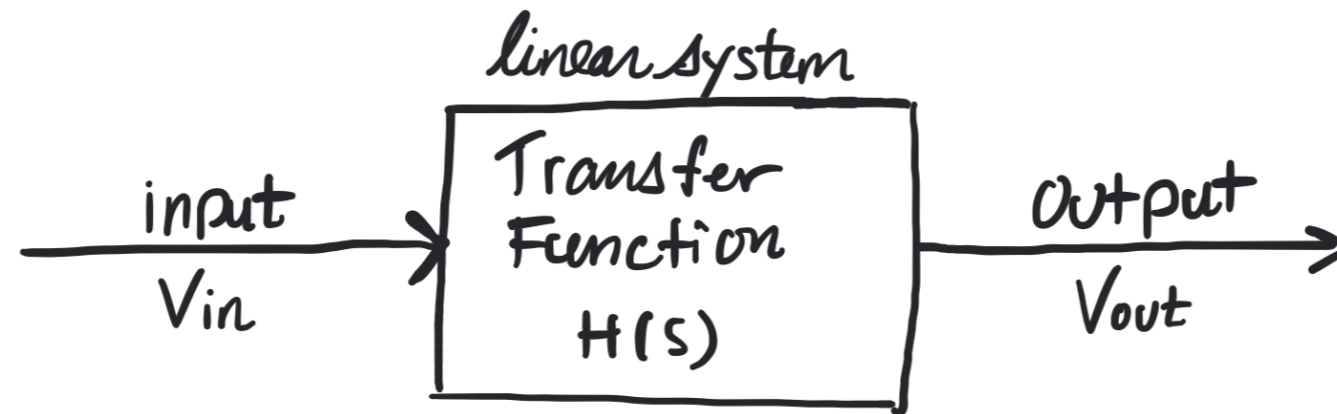3) Transfer Functions

- If a system is linear, we can derive a **transfer function** for it




· Definition: $H = \frac{V_{out}}{V_{in}} = \frac{\text{Output}}{\text{input}}$ ratio

- How do we find V_{out} for a given V_{in} ?

$$V_{out} = H \cdot V_{in} \text{ for any } V_{in}$$

- Once we have the transfer function, we know V_{out} for all possible values of $V_{in} \rightarrow$ H characterizes the system

Example: Inverting Amplifier:

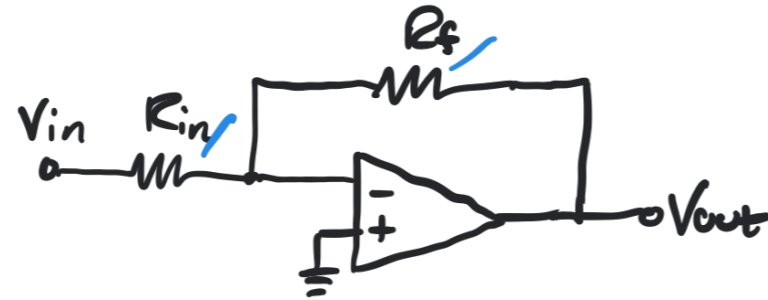


Recall: $V_{out} = -\frac{R_f}{R_{in}} V_{in}$

Knowing $V_{out}(V_{in})$, what is the transfer function for the inverting amplifier?


$$H = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}} \quad \left. \begin{array}{l} \text{if } R_f = 2k\Omega \\ R_{in} = 1k\Omega \end{array} \right\} H = -2$$

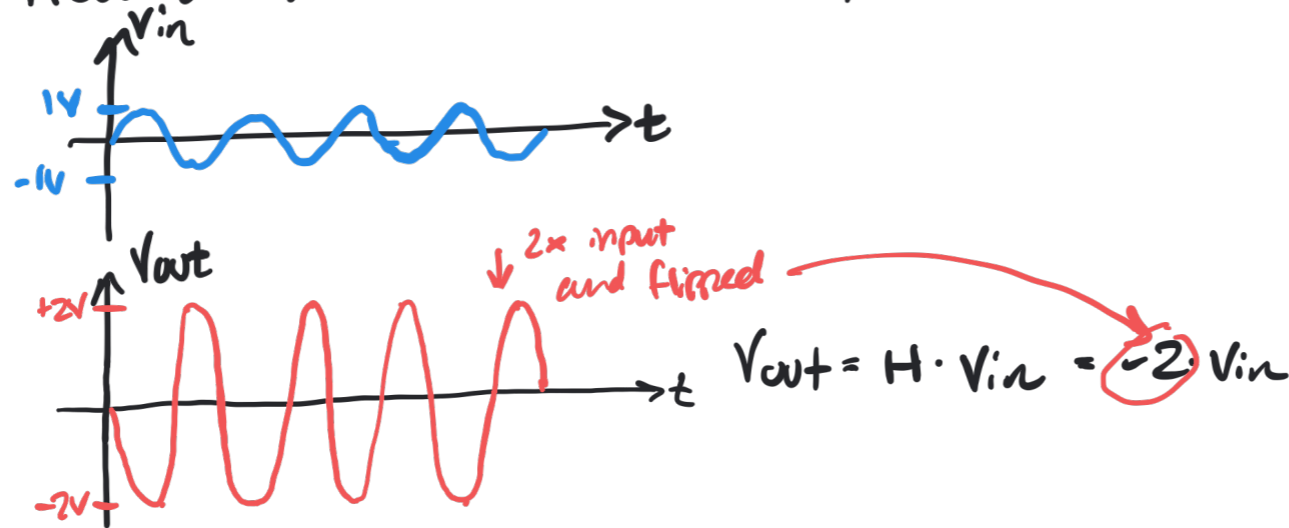How do we use the transfer function? $H = -2$



Almost all op-amp circuits are characterized in terms of their transfer functions, because we can determine V_{out} for any V_{in} .

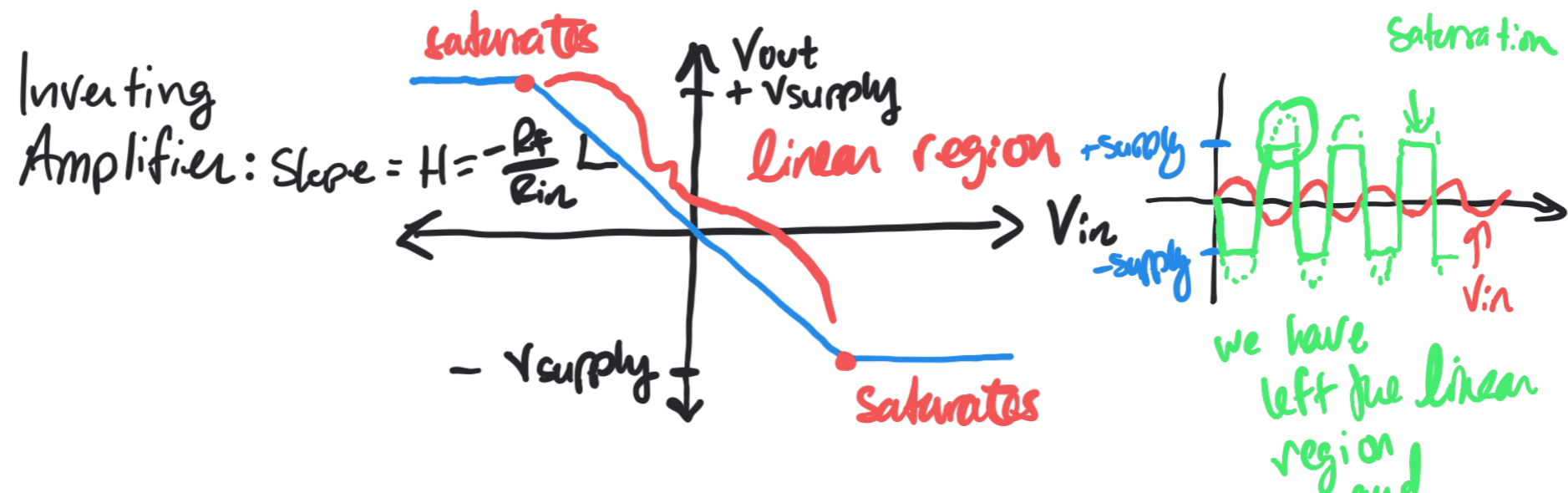- STOP! Didn't we say that op-amp circuits were non-linear because of their non-linear transfer characteristic?!



- We can treat op-amps as linear devices if we operate them in the region where the transfer characteristic is linear. This is also where $V_{out} = H \cdot V_{in}$.