


Intro to ECSE Lecture Notes 3/21/23

1

1) Cascading Op-Amps


- We have seen that most op-amp circuits have a transfer function: $H = \frac{V_{out}}{V_{in}}$

Ex: For a non-inverting amplifier:

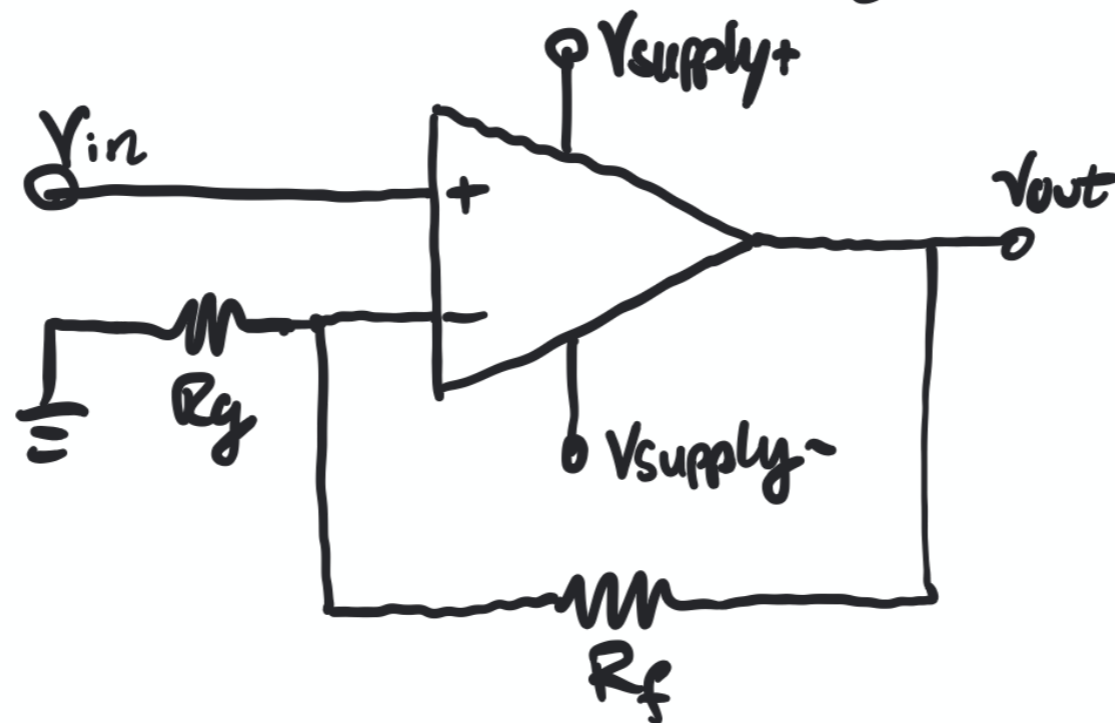


$$H = \frac{V_{out}}{V_{in}} = \left(1 + \frac{R_f}{R_g}\right) = \text{gain}$$

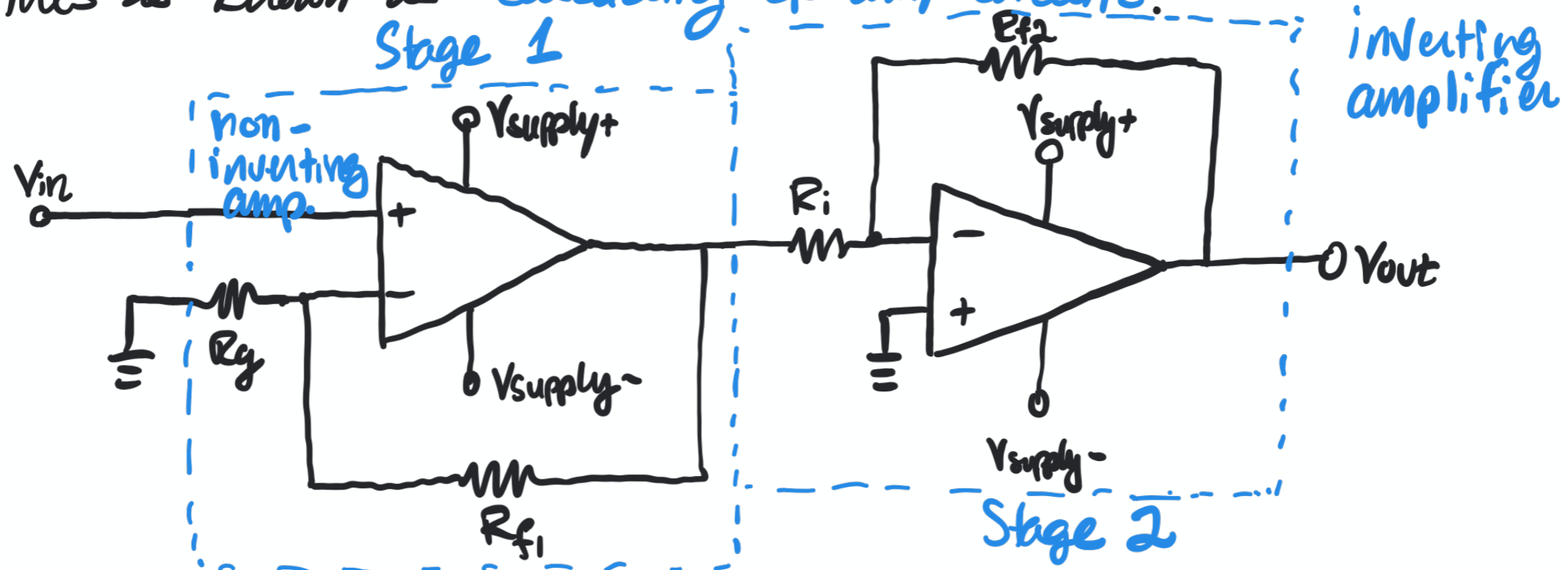• But what if we have multiple op-amp circuits chained together?
 This is known as cascading op-amp circuits.



- How do we analyze this type of circuit?
 - 1) identify stages - draw boxes around / dividing lines between stages
 - 2) identify type of circuit - identify the function of each stage
 - 3) write H for each stage $\rightarrow H_1 = (1 + \frac{R_{f1}}{R_g})$; $H_2 = -\frac{R_{f2}}{R_i}$
 - 4) Write total transfer function $\rightarrow H_{total} = H_1 \times H_2$
 Product of the individual transfer functions
 $= (1 + \frac{R_{f1}}{R_g}) (-\frac{R_{f2}}{R_i})$

Example: What is $H_{total} = \frac{V_{out}}{V_{in}}$?

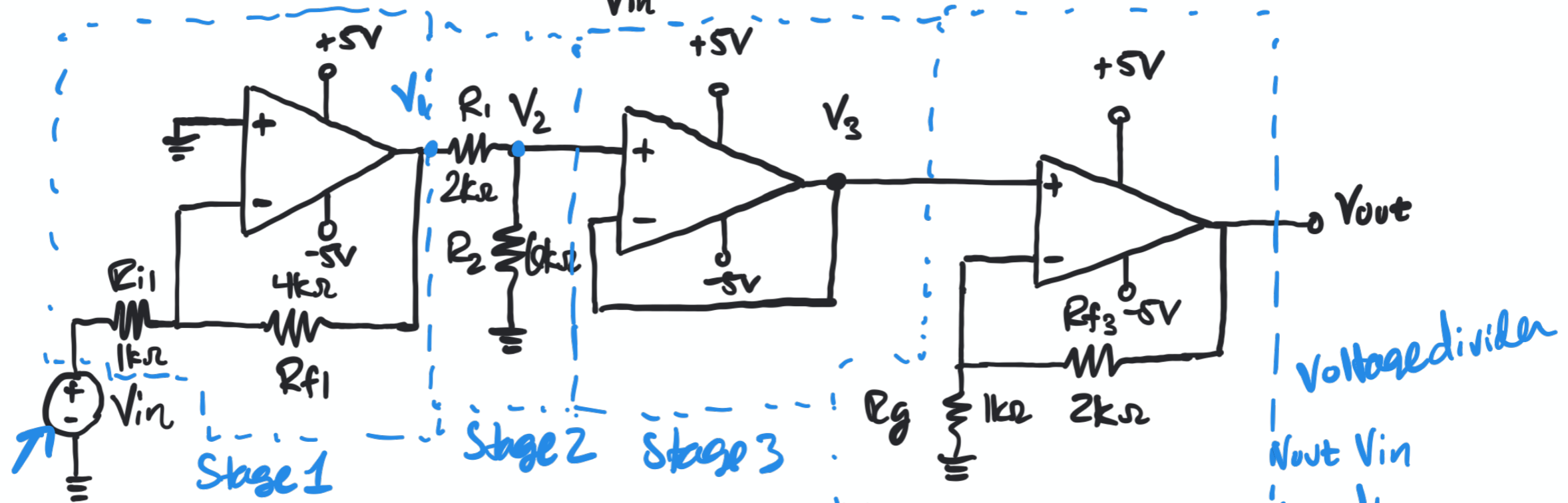

Stage 1: inverting amplifier: $H_1 = -\frac{R_{f1}}{R_{i1}} = -4$


Stage 2: voltage divider: $H_2 = \frac{R_2}{R_1 + R_2} = \frac{6k\Omega}{8k\Omega} = 0.75$

Stage 3: voltage follower (buffer): $H_3 = 1$

Stage 4: non-inverting amplifier: $H_4 = \left(1 + \frac{R_{f3}}{R_g}\right) = \left(1 + \frac{2k\Omega}{1k\Omega}\right) = 3$

Total transfer function $H_{total} = H_1 \cdot H_2 \cdot H_3 \cdot H_4 = (-4)(0.75)(1)(3) = -9 \mid V_{out} = -9V_{in}$

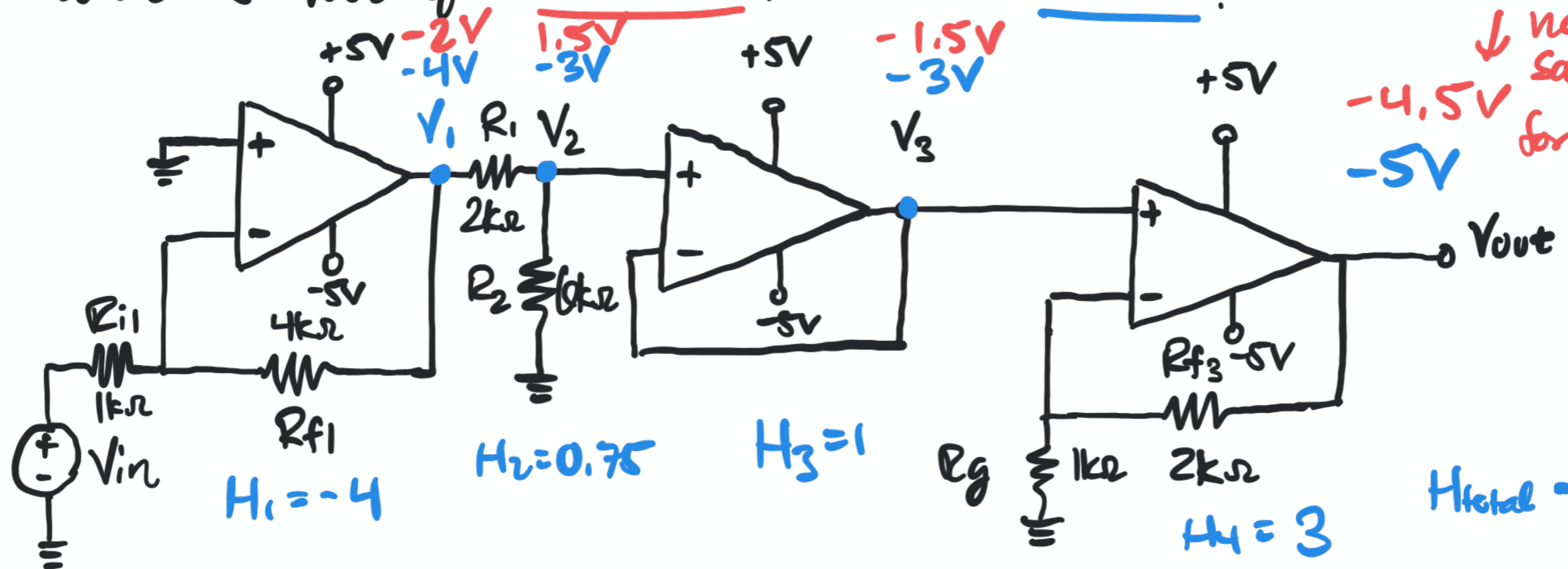Ex: What is V_{out} if $V_{in} = 0.5V$? what if $V_{in} = 1V$?



no saturation for $V_{in} = 0.5V$
 $-4.5V$
 $-5V$

• For $V_{in} = 1$; $V_1 = H_1 \cdot V_{in} = -4V$, $V_{out, max} = H_1 \cdot V_{in, max}$
 $+5V = -4 \cdot V_{in, max} \rightarrow V_{in, max} = -\frac{5}{4}V$

$V_2 = H_2 \cdot V_1 = 0.75 \cdot (-4) = -3V$

$V_3 = H_3 \cdot V_2 = 1 \cdot (-3V) = -3V$

$V_4 = H_4 \cdot V_3 = 3 \cdot (-3V) = -9V \rightarrow$ actually $-5V$

$V_{supply} -$
 \downarrow

signal will be distorted

• For $V_{in} = 0.5V$

$V_{out, max} = H_3 \cdot V_{in, max}$


$-5V = 3 \cdot V_{in, min} \rightarrow V_{in, min} = -\frac{5}{3}V$

2) Setting Thresholds / Reference Levels for Sensors

5

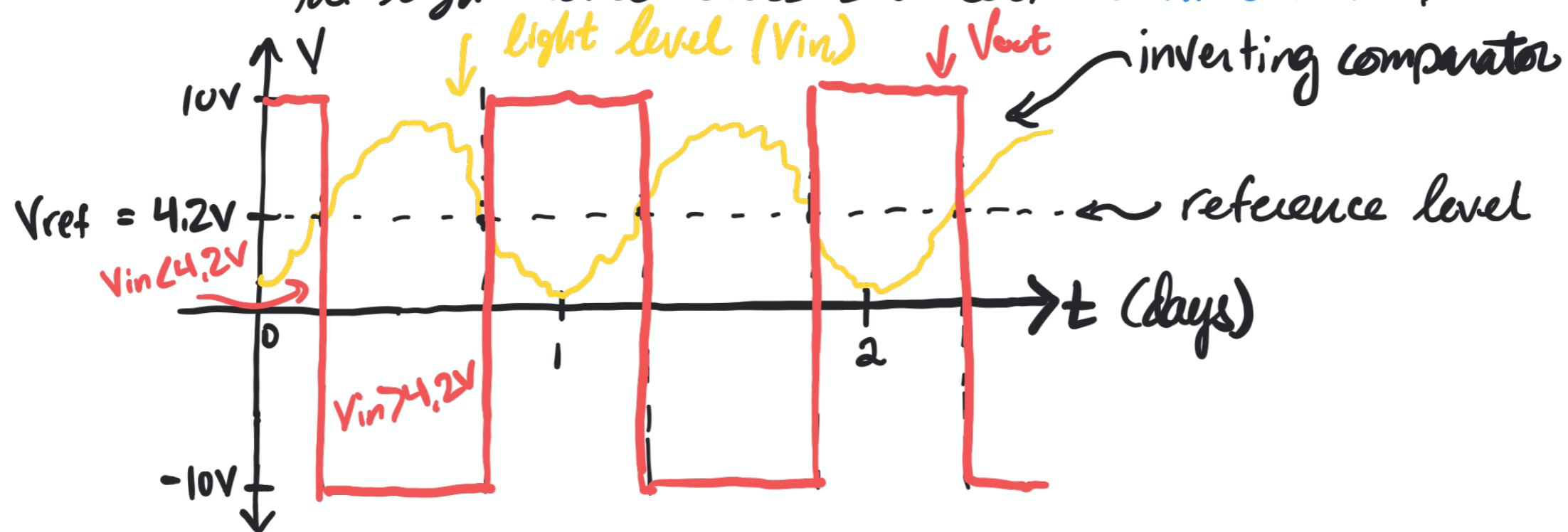
Task: you are given $+10V$ and $-10V$ voltage supplies. Design a circuit that switches the output to $10V$ when the input voltage is less than $4.2V$ and $-10V$ when the input is greater than $4.2V$.

Rationale: **Sensing**. Suppose you have a sensor that changes the voltage it outputs depending on the level of light. You want to do something (say turn on a light) when the light level crosses a certain **threshold**.



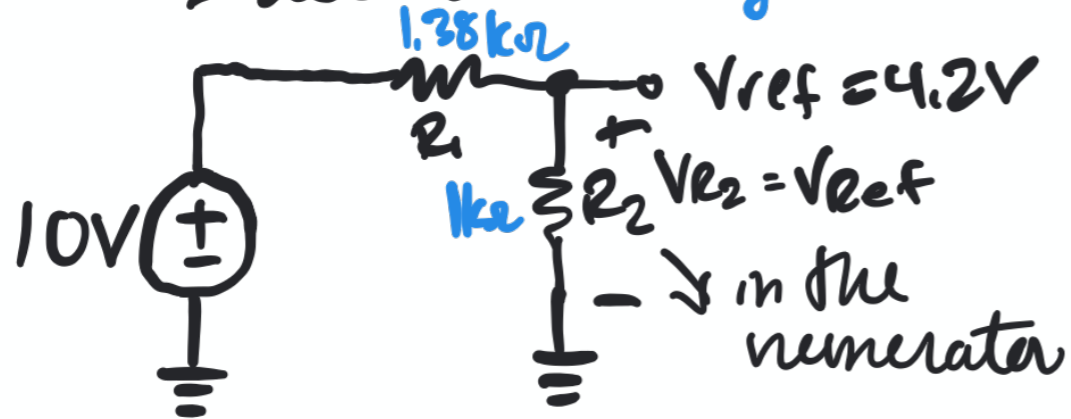1) Generate the reference voltage from the available supply ⁶

↳ use a voltage divider to convert 10V to 4.2V




$$V_{ref} = V_s \frac{R_2}{R_1 + R_2}$$
$$4.2V = 10V \frac{R_2}{R_1 + R_2}$$


Choose $R_2 = 1k\Omega \rightarrow R_1 = 1.38k\Omega$

$$\frac{R_2}{R_1 + R_2} = 0.42$$

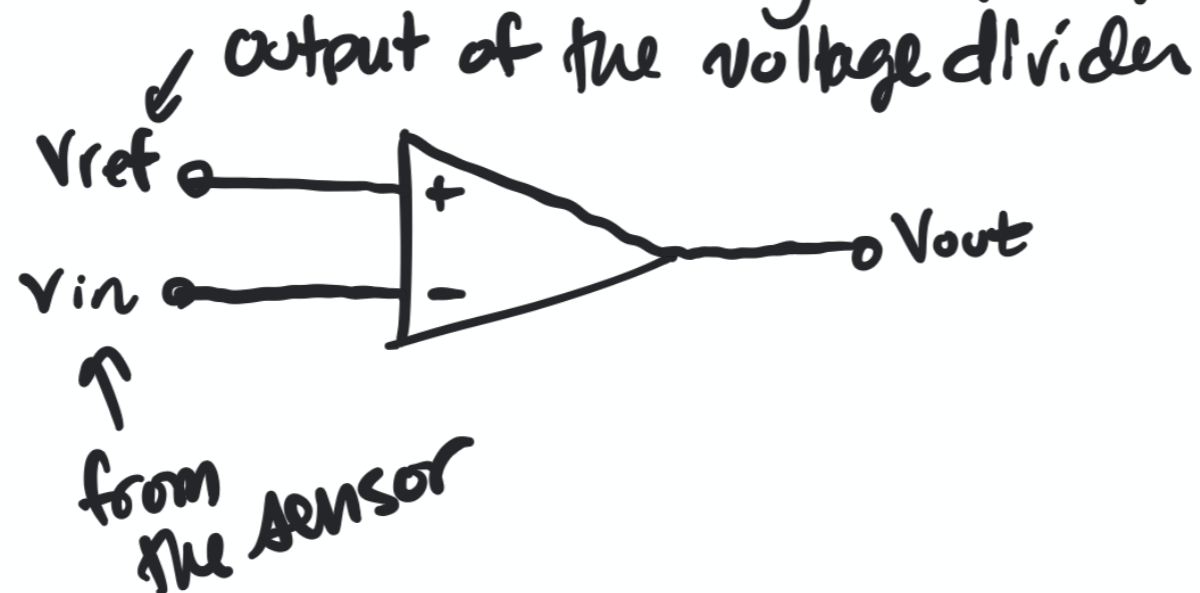2) Setup the circuit (inverting comparator)



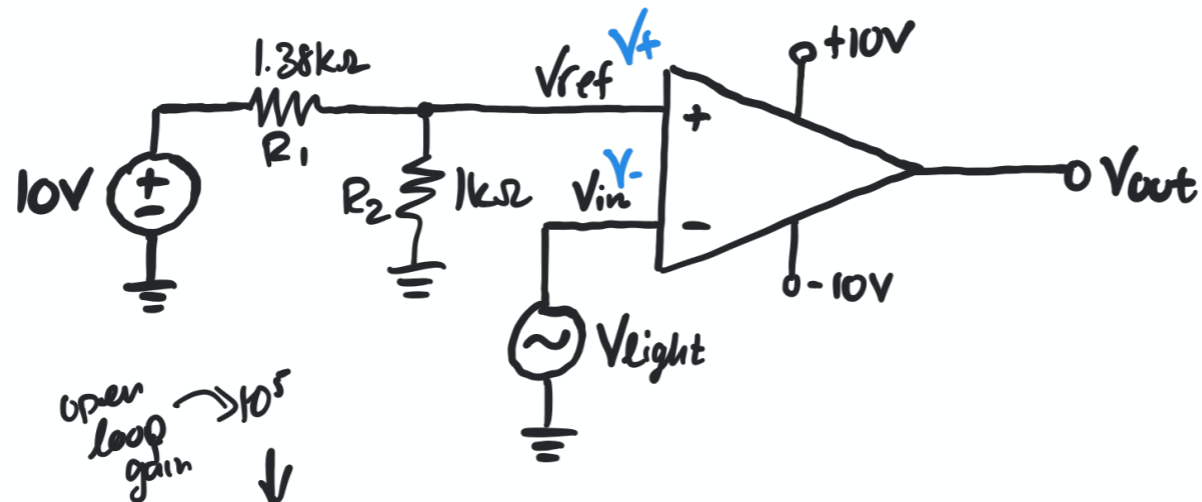2) Use the correct decision-making circuit (comparator) ⁷
 ↳ Inverting Comparator



$$V_{out} = A_o (V_+ - V_-) \rightarrow V_{max, out} = +V_{supply} \Rightarrow V_{out} = \begin{cases} +V_{supply} & \text{when } (V_+ - V_-) > 0 \\ -V_{supply} & \text{when } (V_+ - V_-) < 0 \end{cases}$$

• How do we decide what type of comparator we have?

$$V_{out} = \begin{cases} V_{out} = +V_{supply} & \text{when } (V_{in} - V_{ref}) > 0 \\ V_{out} = -V_{supply} & \text{when } (V_{in} - V_{ref}) < 0 \end{cases} \left. \vphantom{V_{out}} \right\} \text{non-inverting comparator}$$

$$V_+ = V_{in}$$

$$V_- = V_{ref}$$

$$V_{out} = \begin{cases} V_{out} = -V_{supply} & \text{when } (V_{in} - V_{ref}) > 0 \\ V_{out} = +V_{supply} & \text{when } (V_{in} - V_{ref}) < 0 \end{cases} \left. \vphantom{V_{out}} \right\} \text{inverting comparator}$$

$$V_+ = V_{ref}$$

$$V_- = V_{in}$$

(circuit above)

• Which one to choose depends on the application

- How could we use this circuit to make a decision?
 - ↳ Turn on an LED when $V_{light} < 4.2V$

