

Intro to ECSE Lecture Notes 3/24/23

1

1) Quiz 2 topics:

- Linear & Non-linear devices (IV Characteristics)
- Diodes
- Differential Resistance
- Nodal Analysis
- Op-amp basics/properties
- Op-amp circuits/applications
- Properties of linear Devices & Systems
- Superposition (property)
- Superposition (circuit analysis method)
- Transfer functions
- Cascading op-amp circuits
- Setting the reference level for a decision-making circuit

2) Some Example Problems

i) diode circuits



a) If $V_D = 1V$, what is I_{R2} ?

$$\frac{V_{R2}}{R2} = I_{R2} = \frac{1V}{1k\Omega} = 1mA$$

b) What is V_{R1} ?


$$KVL: V_{R1} = V_{in} - V_{R2} = 5V - 1V = 4V$$

detach $\rightarrow n=1$ ← identify factor
 Saturation current
 $I_D = I_S \left(e^{\frac{qV_D}{k_B T}} - 1 \right)$
 $T = 300K$
 $k_B = 1.38 \times 10^{-23} J/K$
 $q = 1.602 \times 10^{-19} C$

c) What is I_D if $I_S = 1 \times 10^{-18} A$?


$$I_D = I_S \left(e^{\frac{qV_D}{k_B T}} - 1 \right) = 0.0039 A$$

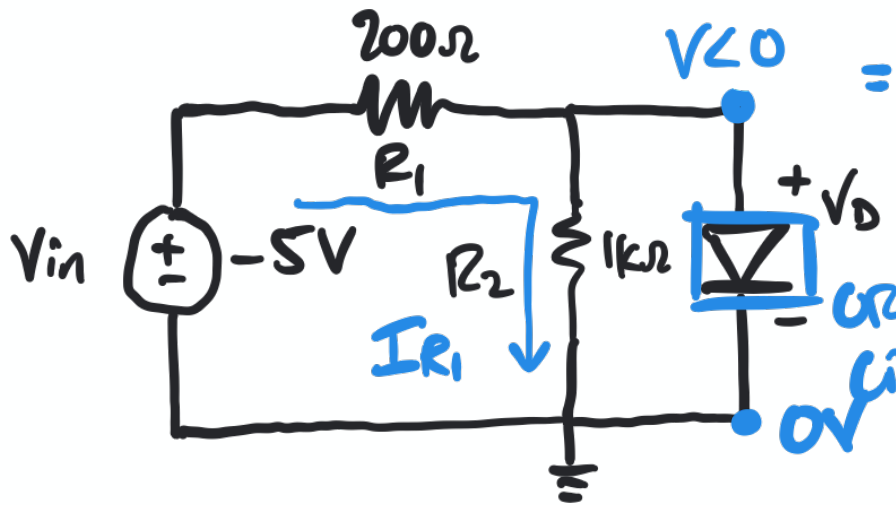d) If $V_{in} = -5V$, what is the current through R_1 ? Assume the IV characteristic above





$$I_{R1} = \frac{V_{in}}{R1 + R2} = \frac{-5V}{1.2k\Omega} = -4.17mA$$

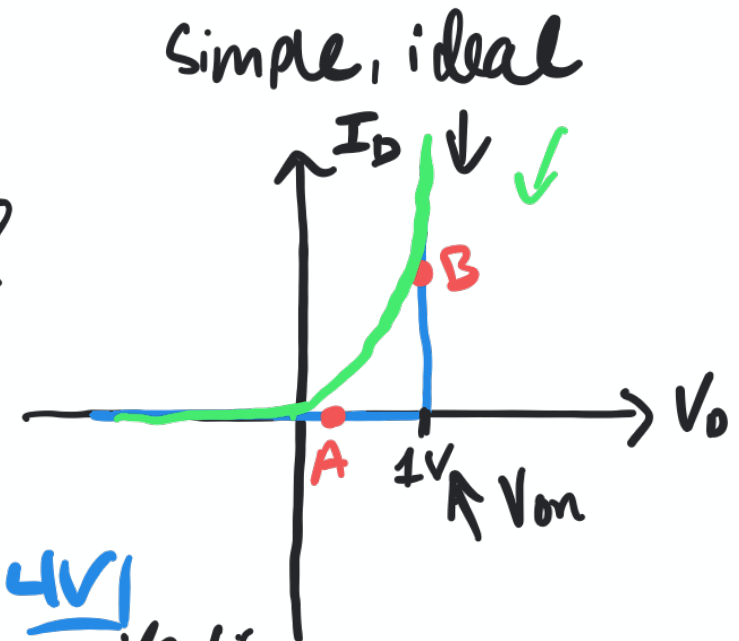e) What is the differential resistance of the diode at A and B? $R = \frac{\Delta V}{\Delta I} \rightarrow A: slope = 0 \mid R_A = \infty$
 $B: slope = \infty \mid R_B = 0$



ii) op-amp basics/properties

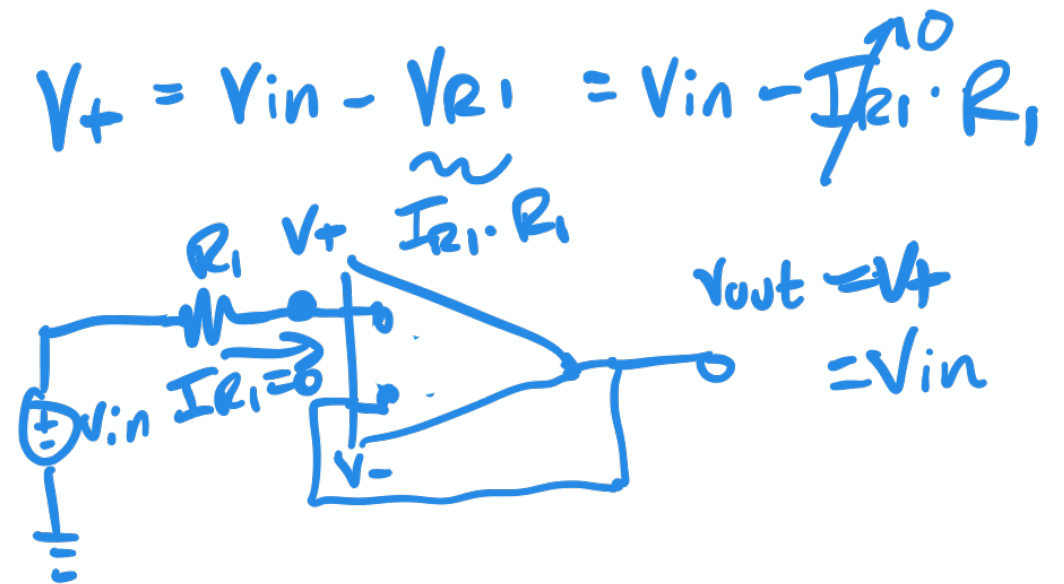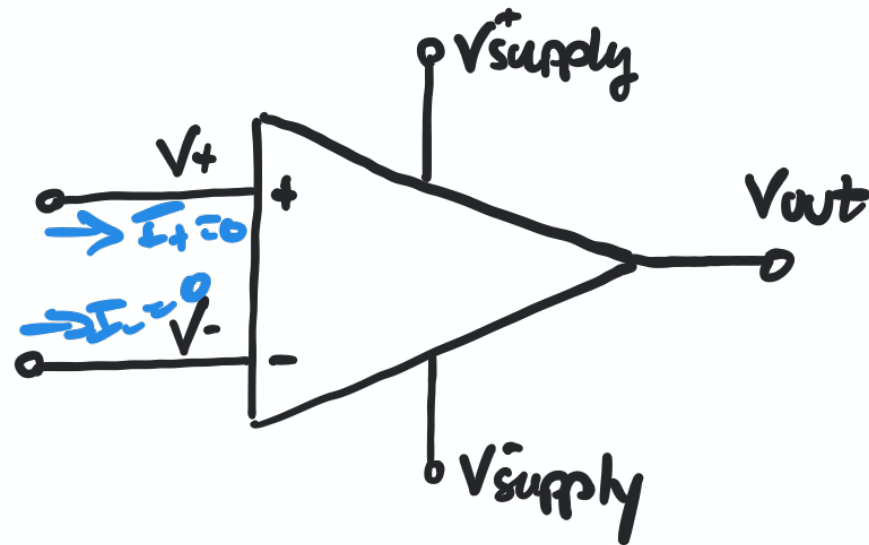


ideal op-amps

- an op-amp is a voltage amplifier, so $\begin{cases} \text{input} = \text{voltage} \\ \text{output} = \text{voltage} \end{cases}$

Golden Rule #1: no current ever flows into the
 V_+ or V_- terminals (due to $R_{in} = \infty$)
more important for 9CS9 1010

Golden Rule #2: when configured in negative feedback,
 $V_+ = V_-$ (due to assumption that $A_0 = \infty$)
9CS9 2010

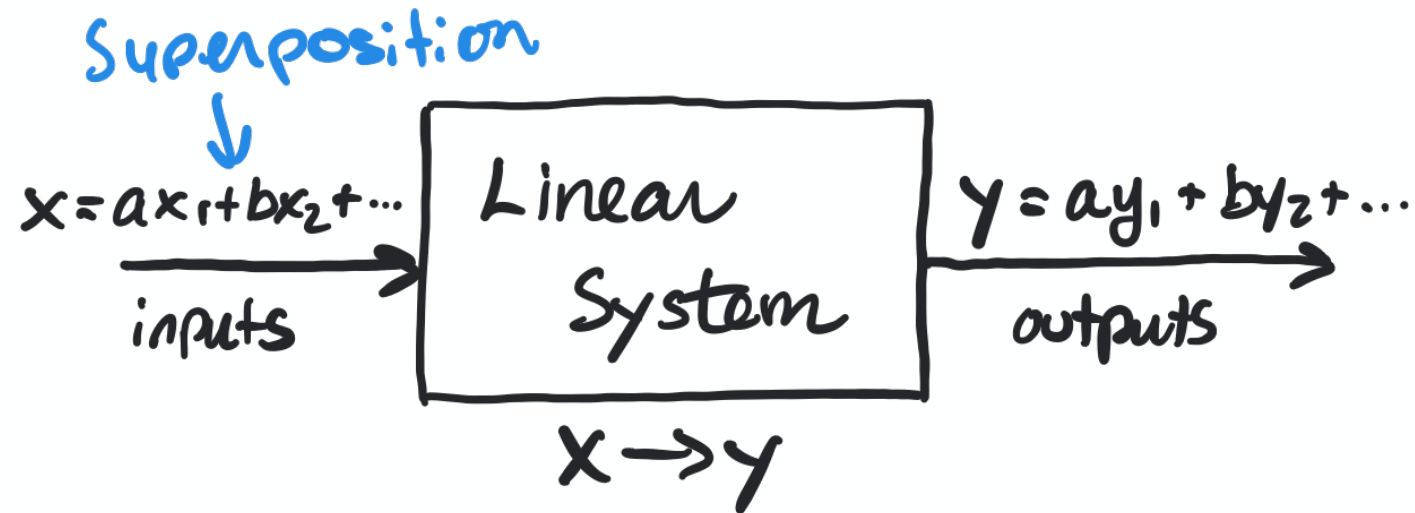iii) properties of linear devices and systems



Ex.

Inverting Op-amp

$H = -3 = \frac{V_{out}}{V_{in}}$

$V_{out} = -3V_{in}$

• What is $V_{out}(t)$? ↖ $V_{out, \text{ for } V_1(t)}$


$V_{out}(t) = V_{out,1}(t) + V_{out,2}(t)$

$V_{out,1} = -3V_1(t) = -0.3 \sin(2\pi ft)$

$V_{out,2} = -3V_2(t) = -0.10 \cos(2\pi ft)$

• $V_{out}(t) = -0.3 \sin(2\pi ft) - 0.10 \cos(2\pi ft)$

iv) Cascading op-amp circuits

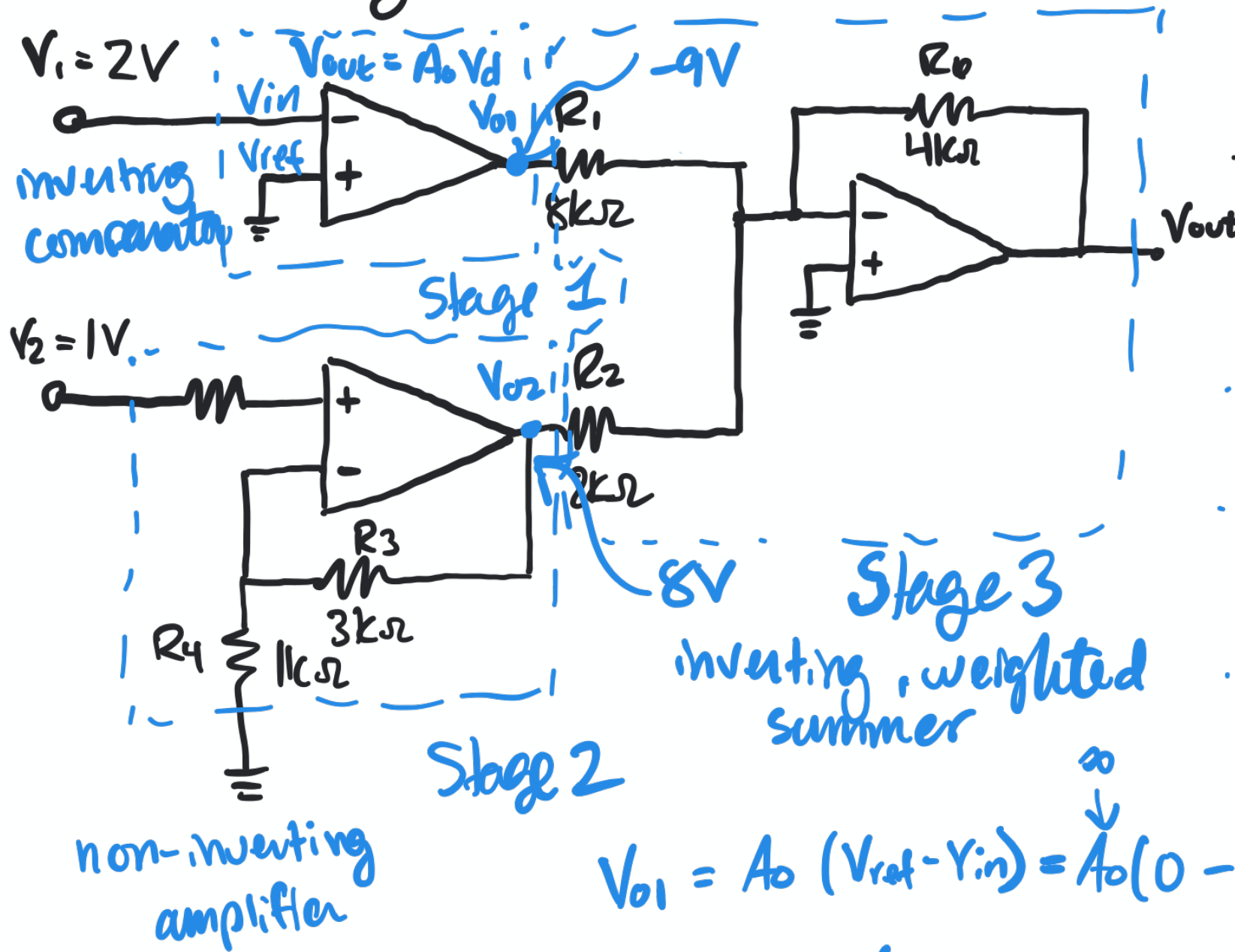

Supply voltages are $\pm 9V$, but are not shown

Find V_{out} : $V_{out} = A_o (V_+ - V_-)$

a) identify stages

b) function of stages

Stage 1: $V_{out} = \begin{cases} +9 V_{in} & V_{in} < V_{ref} \\ -9 V_{in} & V_{in} > V_{ref} \end{cases}$

Stage 2: $H_2 = (1 + \frac{R_3}{R_4}) = 4$

Stage 3: $V_{out} = (-\frac{R_0}{R_1} V_{o1} - \frac{R_0}{R_2} V_{o2}) - V_{supply}$

$V_{o1} = A_o (V_{ref} - V_{in}) = A_o (0 - 2V) = -9V = (-\frac{1}{2} V_{o1} - 2V_{o2})$

$V_{o2} = H_2 \cdot V_2 = 4 \cdot 1V = 4V$

$V_{out} = (-\frac{1}{2} (-9V) - 2(4V)) = 4.5V - 8V = -3.5V$