

ENGR-2300
Electronic Instrumentation
Quiz 1
Spring 2023

Print Name _____ **RIN** _____

Section _____

I have read, understood, and abided by the Collaboration and Academic Dishonesty statement in the course syllabus. The work presented here was solely performed by me.


Signature: _____

Date: _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also, it may be easier to answer parts of questions out of order.

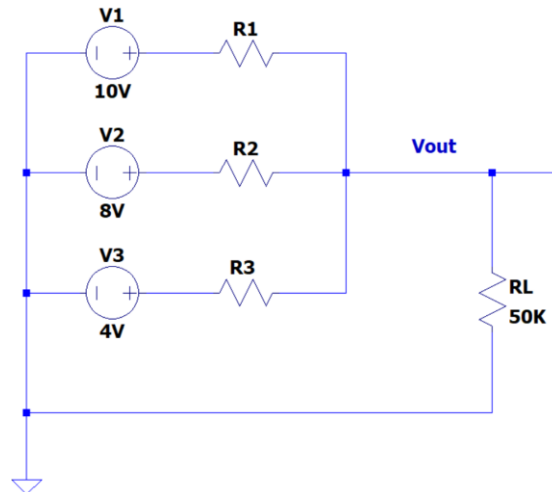I. Circuit Analysis (16 points)*DC Voltage Divider Questions*


The following circuit has three voltage sources:



1. (3 pts) Find V_{out} given the resistances $R1 = 10K$, $R2 = 5K$, and $R3 = 20K$ ohms.

2. (2 pts) Find the current through $R1$, $R2$, $R3$ and RL .

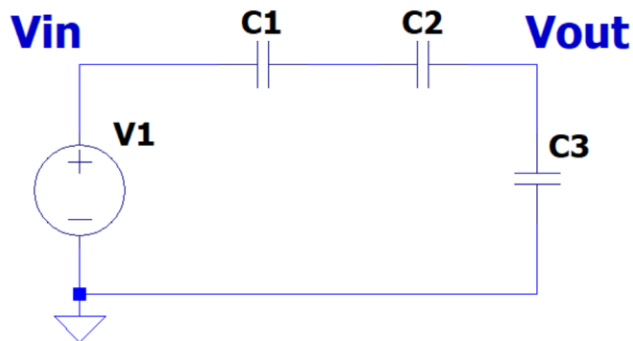3. (4 pts) The following circuit has a voltage dividing function. Derive the transfer function equation (V_{out}/V_{in}) in terms of V_1 , C_1 , C_2 and C_3 . (Hint: even though V_{in} is a DC source, still approach this question using the concept of the impedance of a capacitor.)



4. (1 pts) What is the value of V_{out} for the case of $V_1 = 12V$, $C_1 = 5\mu F$, $C_2 = 2\mu F$ and $C_3 = 7\mu F$?

3. (1 pt) Find the corner frequency of this RC circuit for the case: $R1 = 100 \text{ ohm}$, $C1 = 0.1\mu\text{F}$.


4. (1 pt) Is this a high pass or low pass filter?

3. (2 pts) Find the corner frequency of this RL circuit for the case: $R_1 = 100 \text{ ohm}$, $L_1 = 0.4\text{H}$.

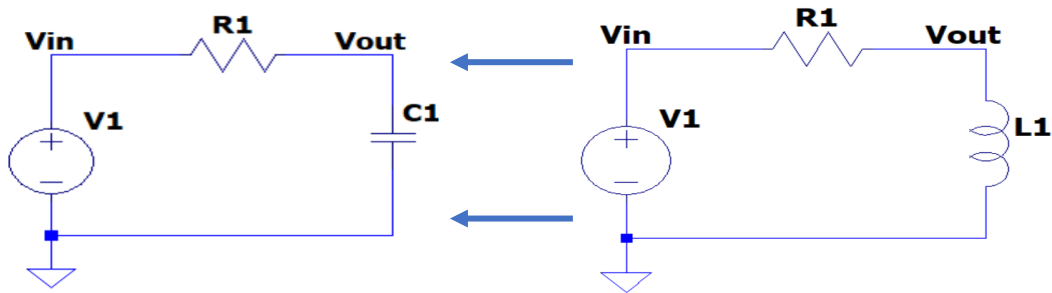
4. (1 pt) Is this a high pass or low pass filter?

RLC Circuit Questions

Now we want to build a new filter by cascading the filters above.




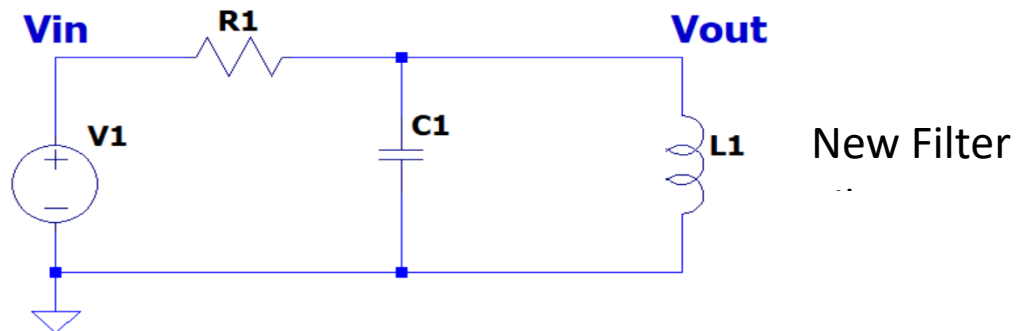Cascade two filters into one by sharing V_{in} source & $R1$



1. (4 pts) $V1$ input is the same: AC with varying frequency (ω). Find the transfer function (V_{out}/V_{in}) of the new filter in terms of ω , $R1$, $C1$, and $L1$.

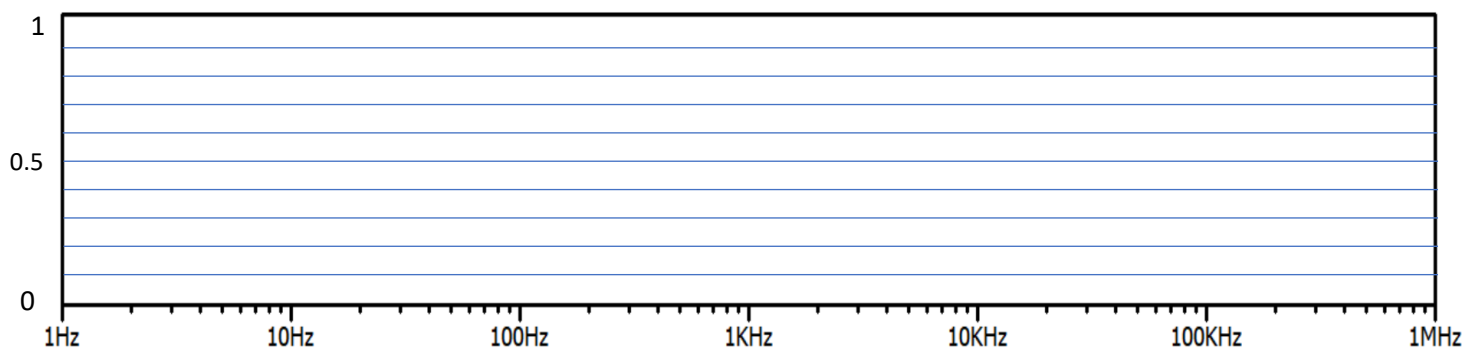
5. (2 pts) What is the phase angle of the transfer function at the resonant frequency? Show the calculation process.
6. (1 pt) Now we have two corner frequencies. If the values of R, C and L have the same values as in previous questions ($R=100\ \text{ohm}$, $L=0.4\ \text{H}$ and $C=0.1\ \mu\text{F}$), what kind of filter is this?
- Low pass filter
 - High pass filter
 - Band pass filter
 - Band reject filter
7. (2 pts) Draw the transfer function in a linear plot, specifying the two corner frequencies on the x-axis (frequency axis). A rough drawing is OK: $H(\omega)$ max is 1 on the y-axis. Labeling of the corner frequency and the relative amplitude on a linear scale on the y-axis is important.



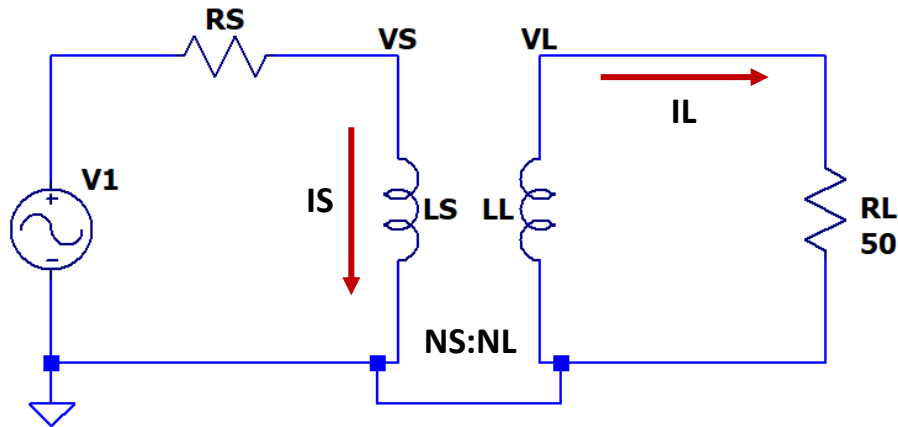III. Inductors, Transformers, and Phasors (20 points)

Inductors and Transformers

You are given a transformer connected to a source and load circuit, as shown below. You know nothing about the transformer except that the wire is wound around a ferrite core.





- (4 pts) With an AC voltage applied to the circuit, you measure $V_S = 4\text{V}$ and $I_S = 320\text{mA}$. If $Z_{in} = \frac{V_S}{I_S}$, what is the value of a ?

- (2 pts) If you remove R_L such that the load is now an open circuit, no current will flow through the load circuit and no voltage will form across the load side's inductor. In this case you can measure the impedance of L_S , the inductor on the source side.

At a frequency of $f = 10\text{kHz}$, you measure the impedance of the source side's inductor to be $Z_{L_S} = j188.5\Omega$. What is the inductance L_S ?



Phasors

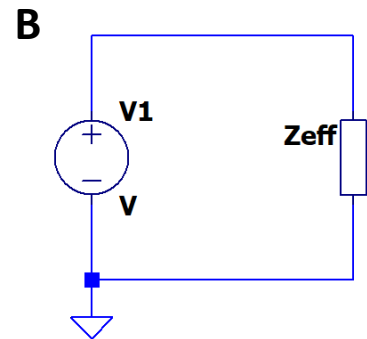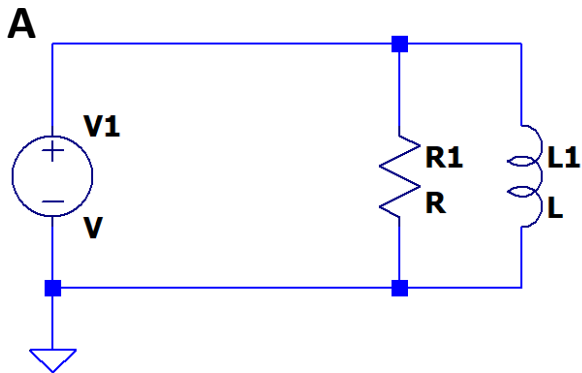7. (4 pts) If you combine the impedances in circuit A below into an effective impedance Z_{eff} , as shown in circuit B, what is the magnitude of Z_{eff} ?




IV. Instrumentation Fundamentals and Concepts (20 points)

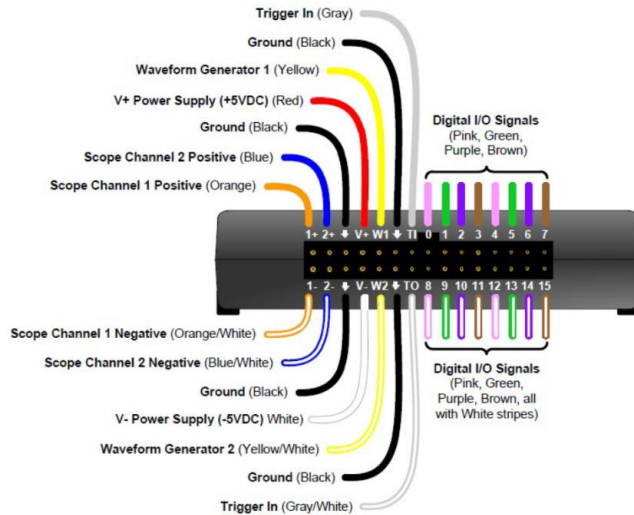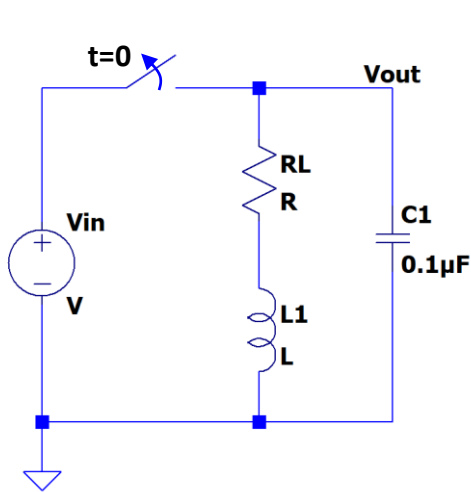1. (6 pts) In experiment 3, you estimated the inductance of your homemade inductor by measuring the resonant frequency of a circuit similar to the one below. By drawing lines from the channels to locations in the circuit, show how you would:
 - a. Source the voltage V_{in} from the instrumentation board
 - b. Measure the input voltage (V_{in})
 - c. Measure the output voltage (V_{out})



2. (2 pts) If you measured an oscillation frequency of $f_0 = 5 \text{ kHz}$, what would be your estimate for the inductance of inductor L1 (to the nearest 0.01 mH)?

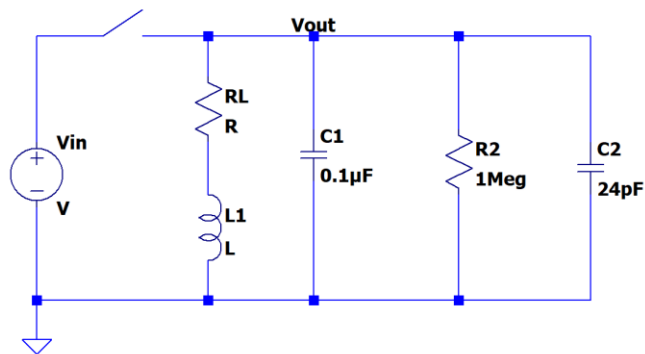3. (2 pts) If the non-idealities of the instrumentation board are considered, the input impedance of the board must also be modeled, resulting in the following circuit.




In this case, the value of the input resistance is $R_2 = 1\text{M}\Omega$ and the input capacitance is $C_2 = 24\text{pF}$. If you needed to find these values specifically for the M2K or the Analog Discovery 2 yourself, where would you find them?

4. (2 pts) To determine the effect of the input capacitance on your inductance estimate, combine C_1 and C_2 in the circuit in IV.3 into a single, effective capacitance and recalculate L_1 using the same resonant frequency as in IV.2 (to the nearest 0.01 mH).
5. (2 pts) Given that C_2 is fixed at 24pF for a given instrumentation board, under what circumstances for C_1 would you need to be concerned that the input capacitance of the board is significantly affecting your measurement?

Miscellaneous Concepts

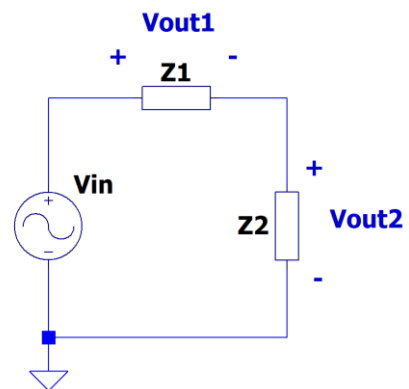6. (2 pts) Suppose that you calculate that the output voltage from a circuit should be $V_{out} = 500(1 + j)$ mV. What is the amplitude of the voltage that you expect to measure?
7. (1 pt) Why doesn't it matter where the two inductor coils of a transformer are located on a ferrite core, as opposed to an air core?
8. (1 pt) Circle one: you run an AC sweep of the circuit to the right and determine that the circuit acts as a high-pass filter when you measure the voltage across Z2 (V_{out2}). What kind of filter would you have if you instead measured across Z1 (V_{out1})?
- a) high-pass filter
 - b) low-pass filter
 - c) band-pass filter
 - d) band-reject filter
 - e) Not enough information to determine the type of filter



9. (1 pt) Describe how you would measure the current flowing through a resistor using the M2K or Analog Discovery 2.
10. (1 pt) Circle one: what effect would replacing the ferrite core of an inductor with an air core have on the inductance of that inductor?
- a) decrease the inductance
 - b) leave the inductance unchanged
 - c) increase the inductance
 - d) the inductance would be zero