
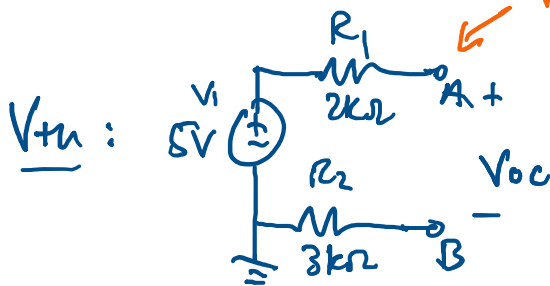



Question 1: Thevenin Equivalent Circuits [20 Points]

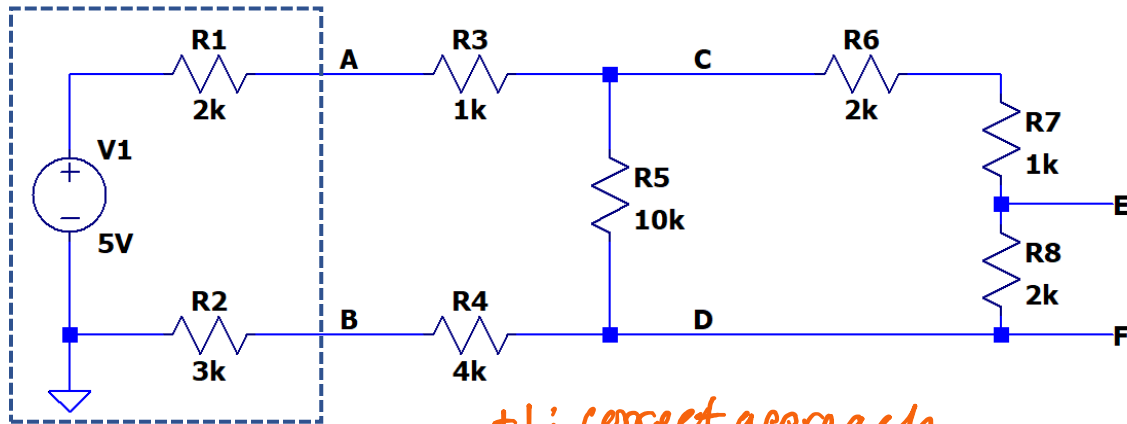Q1.1 [5 pts] Find the Thevenin Equivalent voltage and resistance between terminals A and B (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.



+1: correct approach

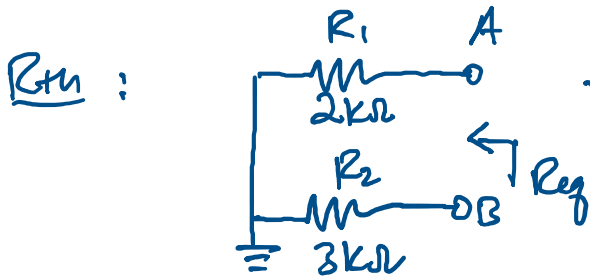
since no current flows due to it being an open circuit, $V_{oc} = 5V = V_{th}$ (+1)



$R_{eq} = R_1 + R_2 = 5k\Omega = R_{th}$ (+1)


+1: correct approach

Thevenin Equivalent Circuit:

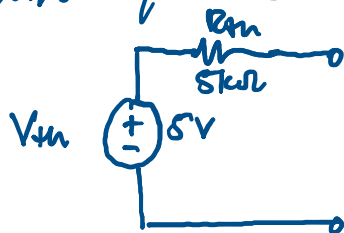


+1: correct circuit schematic for Thevenin equivalent

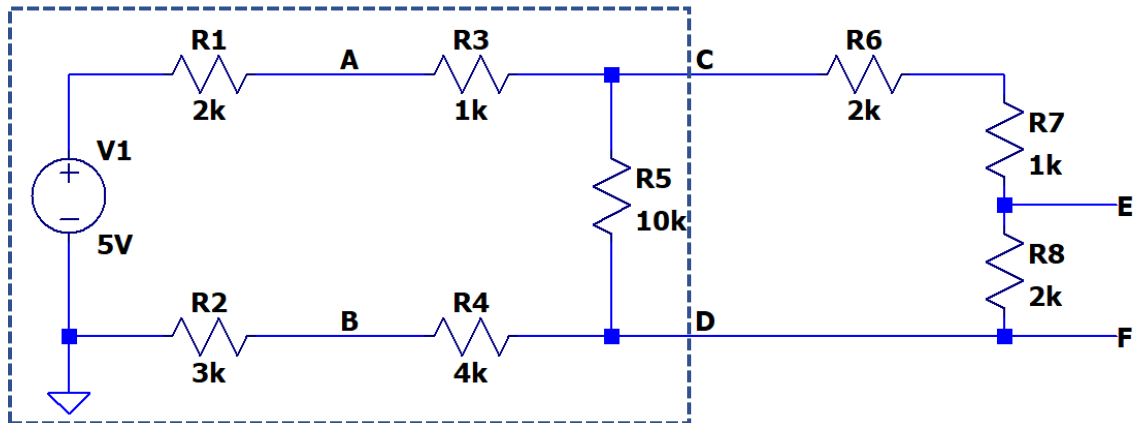Q1.2) [4 pts] Find the Thevenin Equivalent voltage and resistance between terminals C and D (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.



Using the Thevenin from above:

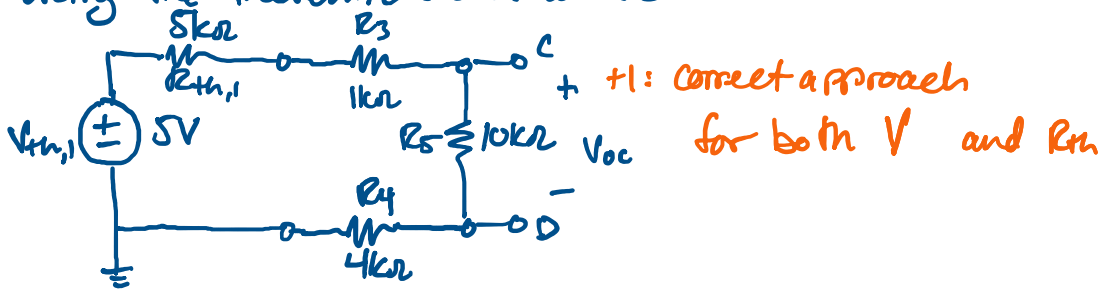


V_{th} : V_{oc} : voltage divider: $V_{oc} = 5V \frac{10k\Omega}{5k\Omega + 1k\Omega + 4k\Omega + 10k\Omega} = 2.5V$ (+1)

R_{th} : $R_{eq} = (R_{th1} + R_3 + R_4) \parallel R_5 = 10k\Omega \parallel 10k\Omega = 5k\Omega = R_{th2}$ (+1)


Thevenin Equivalent circuit:



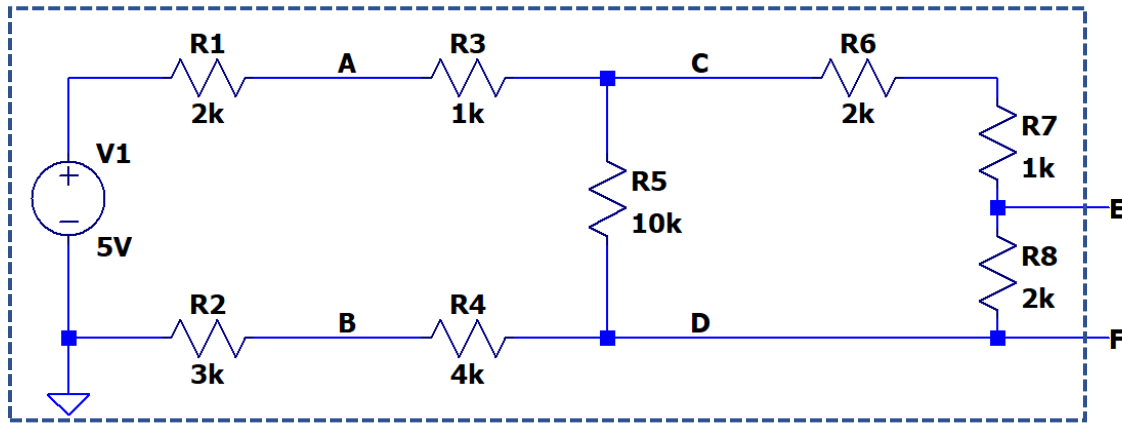Q1.3) [4 pts] Find the Thevenin Equivalent voltage and resistance between terminals E and F (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.




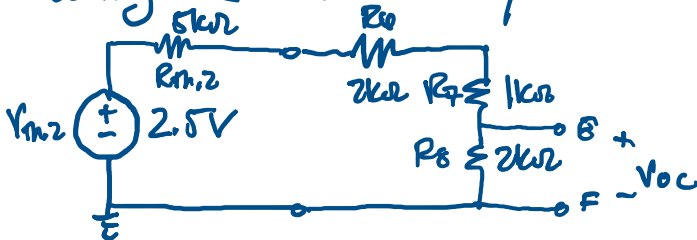Using The Thevenin Equivalent from above:




+1: correct approach for finding V_{th} and R_{th}

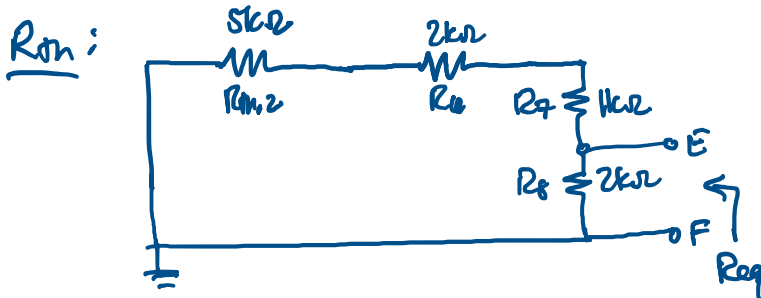V_{th} : Voltage divider: $V_{oc} = 2.5V \frac{2k\Omega}{5k\Omega + 2k\Omega + 1k\Omega + 2k\Omega} = 0.5V$ (+1)




$R_{th} = (R_{m,2} + R_6 + R_7) \parallel R_8$
 $= 8k\Omega \parallel 2k\Omega = \frac{16k\Omega}{10k\Omega} = 1.6k\Omega$ (+1)

Thevenin Equivalent:

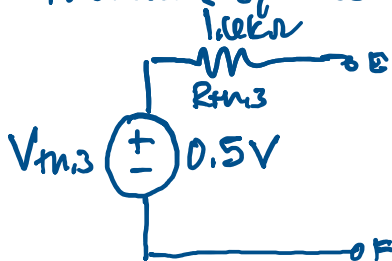


+1: correctly-drawn Thevenin equivalent

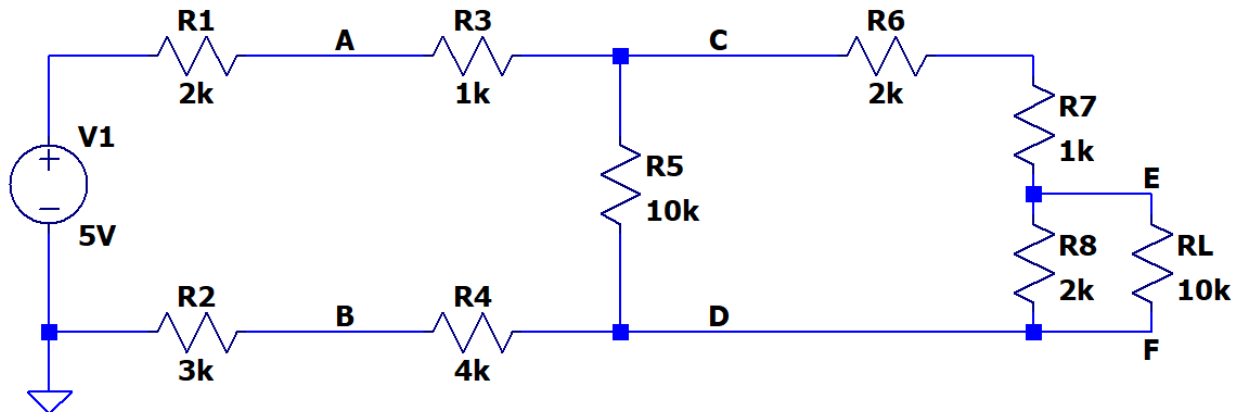Q1.4) [2 pts] If a load resistor with a value $R_L = 10k\Omega$ is connected across terminals E and F as shown below, how much power is delivered to the resistor?



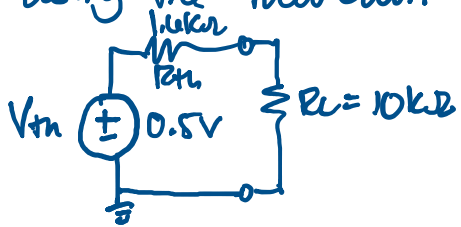Using the Thevenin Equivalent from above:



$P = I^2 R$ +1: correct approach

$$I = \frac{0.5V}{11.0k\Omega} = 43.1\mu A$$


$$P = (43.1 \times 10^{-6} A)^2 \cdot 10 \times 10^3 \Omega = \underline{18.6\mu W}$$

+1: correct calculation

Q1.5) [3 pts] Given an unknown resistive network, you connect a load resistor $R_L = 8k\Omega$ across the output terminals and apply a voltage $V_{in} = 3V$ across the input terminals. If you measure a voltage $V_{out} = 2V$, what is the equivalent resistance R_{eq} of the resistive network?



+1: correct approach

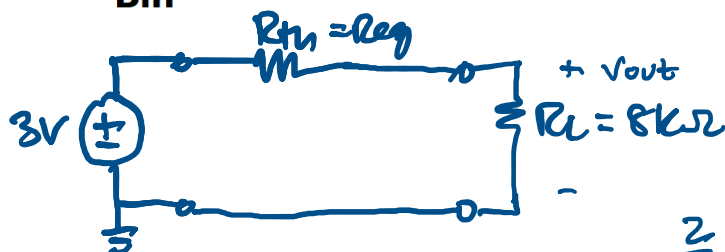

$$2V = 3V \frac{8k\Omega}{R_{th} + 8k\Omega}$$

$$\frac{2}{3} (R_{th} + 8k\Omega) = 8k\Omega$$

$$R_{th} = 8k\Omega \left(\frac{3}{2} - 1\right) = \underline{4k\Omega}$$

+1: correct calculation

Q1.6) [2 pts] True or False (circle one): only some linear circuits can be expressed as a voltage source in series with an impedance.

True


False

Thevenin's Theorem states that ALL linear circuits can be simplified to a voltage source in series with an equivalent resistance.

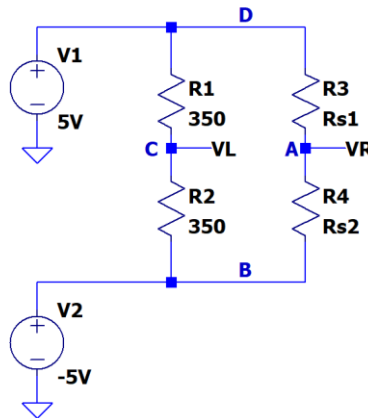
Question 2: Bridge Circuits, Strain Gauges, and Harmonic Oscillation

[20 Points]

In the circuit below, R_{s1} and R_{s2} represent the resistances of strain gauges which are attached to the top and bottom of a cantilever beam, as in Experiment 5 and Project 2.



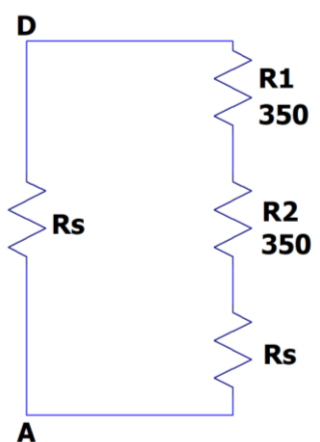Q2.1) [4 pts] When you measured the resistance of the strain gauges in Experiment 5 (for example between terminals D and A), you were measuring R_{s1} in parallel with the series combination of R_1 , R_2 , and R_{s2} , as shown below. If both strain gauges are assumed to have the same resistance R_s , what is the value of R_s if you measured a resistance of 263Ω between terminals A and D? Give your answer to the nearest ohm.



+2: correct approach

$$263\Omega = (350\Omega + 350\Omega + R_s) \parallel R_s$$

$$= \frac{(700\Omega + R_s)R_s}{2R_s + 700\Omega}$$

$$263\Omega (2R_s + 700\Omega) = (700\Omega + R_s)R_s$$

$$526\Omega \cdot R_s + 18410\Omega^2 = 700\Omega R_s + R_s^2$$

+1: got to equation

$$0 = R_s^2 + 174\Omega R_s - 18410\Omega^2$$

$$\underline{R_s \approx 350\Omega} \quad \text{i: correct calculation}$$

Q2.2) [3 pts] When the beam is deflected to its maximum extent, $V_{out} = V_L - V_R = 10\text{mV}$.

Assuming that the strain gauge resistances become $R_{s1} = R_s + \Delta R$ and $R_{s2} = R_s - \Delta R$, what is the value of ΔR ? Give your answer to the nearest 0.1Ω .

$$V_L = 0 \text{ because } R_1 = R_2 = 350\Omega \text{ (+1)}$$

$$V_R = -5V + 10V \cdot \frac{R_s - \Delta R}{(R_s + \Delta R) + (R_s - \Delta R)} = -5V + 10 \frac{R_s - \Delta R}{2R_s}$$

$$= -5V + 10V \left(\frac{1}{2} - \frac{\Delta R}{2R_s} \right) = -5V \cdot \frac{\Delta R}{350} = -\frac{\Delta R}{70} V \text{ (+1)}$$


$$V_{out} = V_L - V_R = +\frac{\Delta R}{70} V = 0.01V \rightarrow \underline{\Delta R = 0.7\Omega} \text{ (+1)}$$

Q2.3) [2 pts] The output voltage of the strain gauge and bridge circuit is fed into a differential amplifier. Given that $V_{out} = 10\text{mV}$ is the maximum output voltage of the bridge circuit and the op-amp voltage supplies are $+5V$ and $-5V$, what is the maximum gain of the differential amplifier, such that its output does not saturate?

If $V_{o,max} = +5V$ (+1) and $V_{in,max} = 10\text{mV}$,


$$\text{the maximum gain is } A = \frac{+5V}{0.01V} = \underline{500} \text{ (+1)}$$

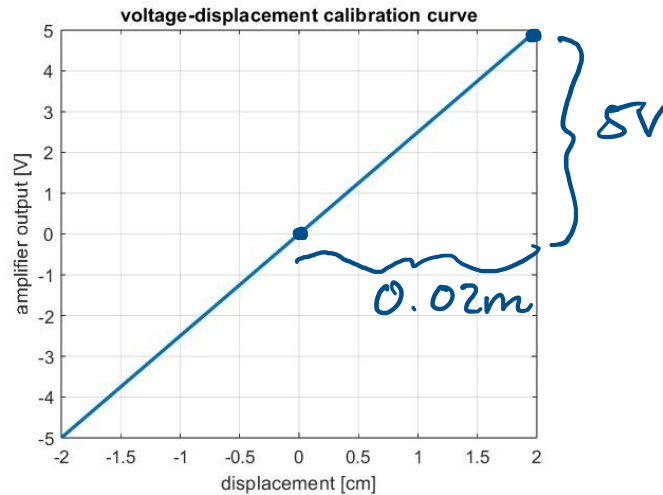Q2.4) [2 pts] Using the calibration curve below, calculate the proportionality constant that converts the voltage output of the differential amplifier in V to beam displacement in m to the nearest 0.01.



To convert voltage to displacement, we need to find $\frac{\Delta X}{\Delta V} = \frac{0.02m}{5V} = \frac{0.004m}{V}$ (+1)

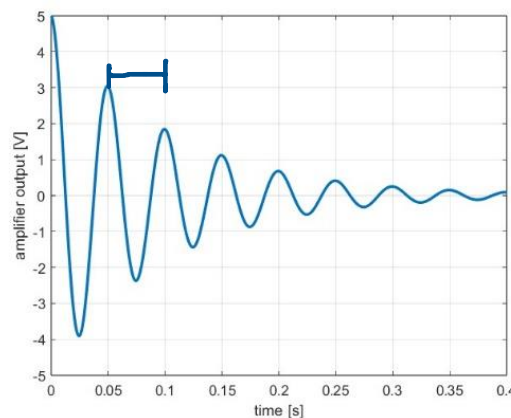Q2.5) [3 pts] Given the curve below, calculate the frequency (in Hz) of the beam oscillation and the decay constant to the nearest 0.1.



- $T = 0.05s$, so $f = 1/0.05s = \underline{20Hz}$ (+1)
- $V_i = V_0 e^{-a(t_i - t_0)}$ choose $V_i = 3V, V_0 = 5V$
 $t_i = 0.05s, t_0 = 0$

$$\alpha = -\ln\left(\frac{V_1}{V_0}\right) \frac{1}{(t_1 - t_0)} = -\ln\left(\frac{3}{5}\right) \frac{1}{0.055} = \frac{10.2}{(+1)}$$


Q2.6) [2 pts] Which type of op-amp circuit would you use to calculate velocity (up to a constant) from the data in Q2.5?

Since we've measured $x(t)$ \times a constant and we want $\frac{dx(t)}{dt}$, we need a differentiator.

Q2.7) [2 pts] If instead you were measuring the voltage signal from an accelerometer, which type of op-amp circuit would you need to calculate velocity (up to a constant)?

Since $v(t) = \int a(t) dt$, we would need an integrator.

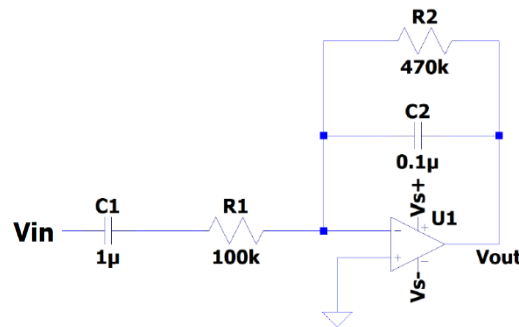
Q2.8) [2 pts] In the Miller Integrator circuit shown below, what is the function of the capacitor C1 at the input?



- The capacitor is a blocking capacitor since it prevents the DC component of a signal from reaching the integrator input. If a DC signal is integrated it may cause the integrator to saturate.

III. Op-Amp Applications and Analysis [26 points]

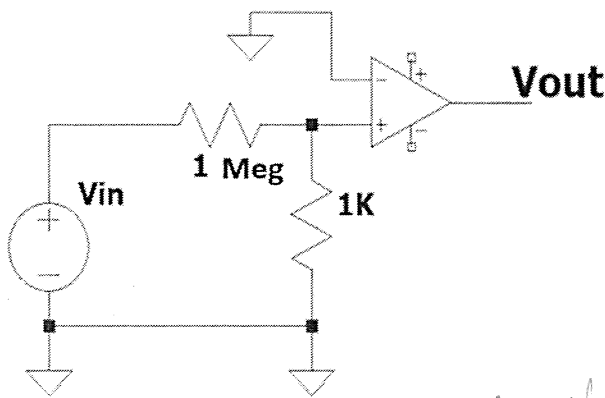- a) [4 pts] The op-amp circuit below uses an op-amp that is ideal except for having a **finite gain A**. If the measured V_{out} is 3.5V when V_{in} is 3.5V, what is the op-amp gain A?
 Hint: $V_{out} = A * (V_+ - V_-)$ when the op-amp is not configured in a feedback loop.



$$V_+ = V_{in} \cdot \frac{1K}{1M + 1K}$$

$$V_- = 0$$


$$V_{out} = A(V_+ - V_-)$$

$$= A \cdot V_{in} \cdot \left(\frac{10^3}{10^6 + 10^3} \right)$$

$$A = \frac{V_{out}}{V_{in}} \cdot \frac{10^6 + 10^3}{10^3} = \frac{3.5V}{3.5V} \cdot (10^3 + 1)$$

$$= \boxed{1001}$$

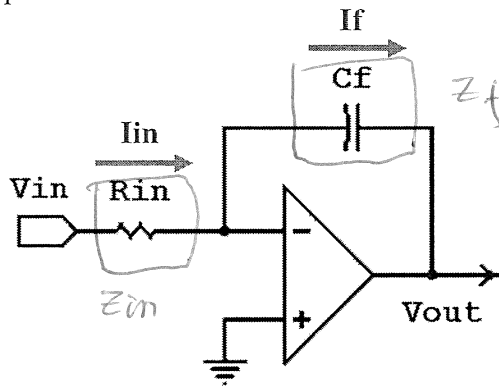- b) [12 pts] In the ideal integrator as shown below, $R_{in} = 100k$ ohm and the $C_f = 0.1\mu F$. A sine-wave signal is applied to the input V_{in} .



- i) [2 pts] Find I_{in} and I_f in terms of V_{in} , V_{out} , R_{in} , and the impedance of C_f . Indicate where you used the Golden Rules of op-amps.

rule 1 : $I_{in} = I_f$

rule 2 : $V_+ = V_- = 0$

$$I_{in} = \frac{V_{in} - V_-}{Z_{in}}$$

$$I_f = \frac{V_- - V_{out}}{Z_f}$$

Ans: ii) $I_{in} = I_f \Rightarrow \frac{V_{in}}{Z_{in}} = \frac{-V_{out}}{Z_f}$, (now $Z_{in} = R_{in}$
 $Z_f = \frac{1}{j\omega C_f}$)

~~Ans: ii)~~

- ii) [2 pts] Find the transfer function of this op-amp circuit: $H(j\omega) = V_{out}/V_{in}$.

$$H(j\omega) = \frac{V_{out}}{V_{in}} \quad \text{From } Z_{in} = Z_f$$

$$\frac{V_{in}}{Z_{in}} = \frac{-V_{out}}{Z_f} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_{in}} = -\frac{\frac{1}{j\omega C_f}}{R_{in}}$$

$$= -\frac{1}{j\omega R_{in} C_f}$$

- iii) [4 pts] At what frequency (in Hz) are the input and output signal equal in amplitude?

$$|H(j\omega)| = \left| \frac{1}{j\omega R_{in} C_f} \right| = 1$$

$$\omega R_{in} C_f = 1$$

$$f = \frac{1}{2\pi \cdot R_{in} C_f} = \frac{1}{2\pi \cdot 100 \cdot 10^3 \cdot (0.1 \cdot 10^{-6})}$$

$$= \underline{\underline{15.9 \text{ Hz}}}$$

[$R_{in} = 100 \text{ k}$
 $C_f = 0.1 \mu\text{F}$]

- iv) [2 pts] At that frequency, what is the phase of the output signal relative to the input signal?

$$H(j\omega) = -\frac{1}{j\omega R_{in} C_f} = -\frac{1}{j} \cdot \left(\frac{1}{\omega R_{in} C_f} \right)$$

$$\angle H(j\omega) = \angle -\frac{1}{j} = -90^\circ \text{ or } -\frac{\pi}{4}$$

90° lagging


- v) [2 pts] If the frequency is lowered by a factor of 10 from that found in iii), by what factor does the output voltage change? In what direction? Choose one: larger or smaller.

$$\angle H(j\omega) = -\frac{1}{j\omega R_{in} C_f}$$

$$\omega \downarrow = 10 \times \Rightarrow |H(j\omega)| \uparrow 10 \times$$

10 times, (Larger)

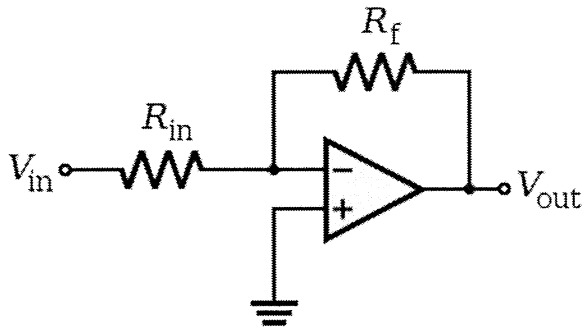c) [10 pts] In the following op-amp application circuit the power supply is $V_{cc} = \pm 5V$.




i) [2 pts] If $R_{in} = 10k \text{ ohm}$ and we want this amplifier to have a gain of *magnitude*: 10 V/V. What should be the value of the feedback resistor R_f ?

Wants gain mag. = 10 $\frac{V}{V}$


$$G \text{ of this inv. Amp} = \left| \frac{R_f}{R_{in}} \right| = 10$$

$$R_f = R_{in} \cdot 10 = \underline{\underline{100 \text{ k}\Omega}}$$

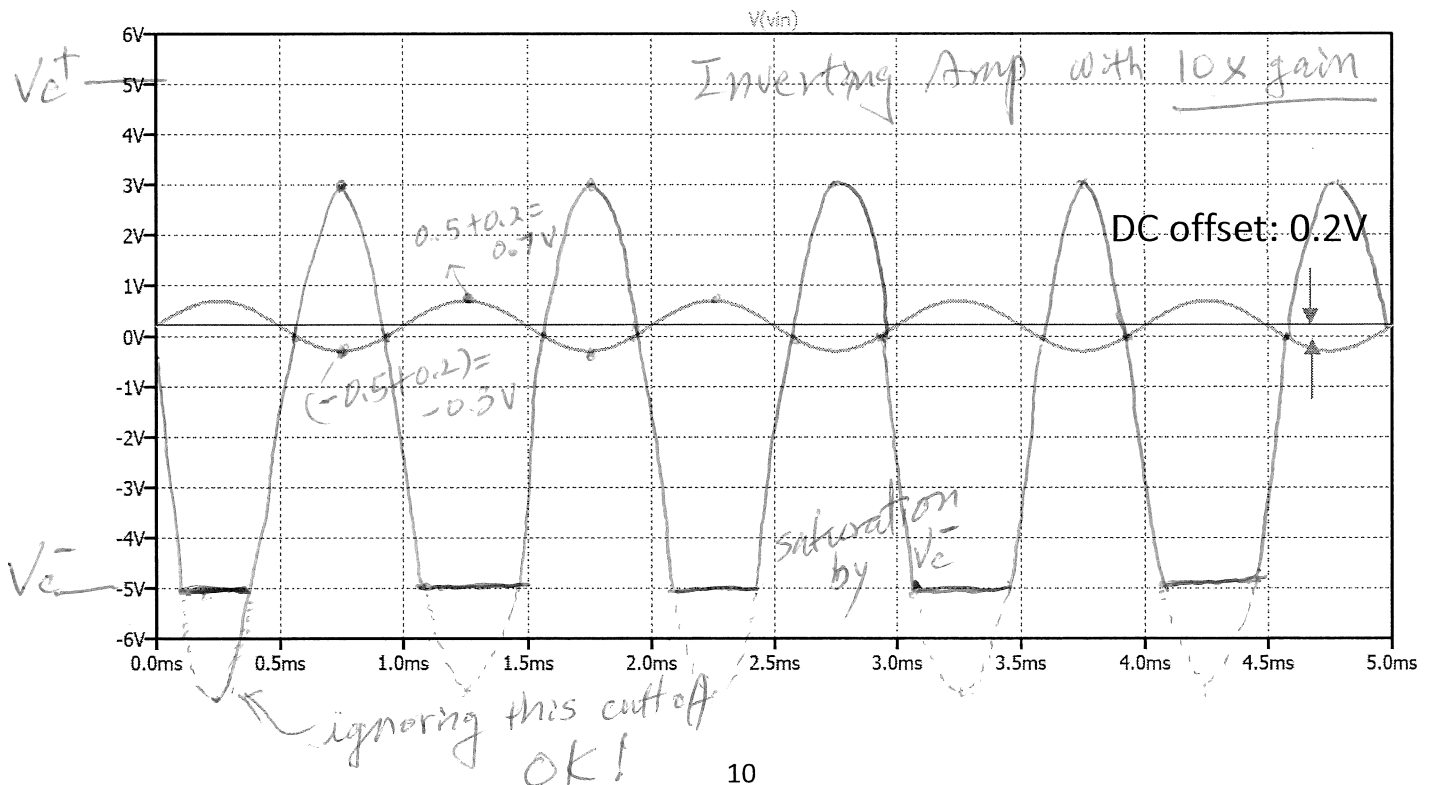ii) [5 pts] If V_{in} is a sinusoidal wave input of $0.5\sin(2\pi 1000t)V$ on top of DC offset of 0.2V, as drawn below on the V-time plot, draw the output wave form on the graph below. The DC offset is plotted on the graph below as well.



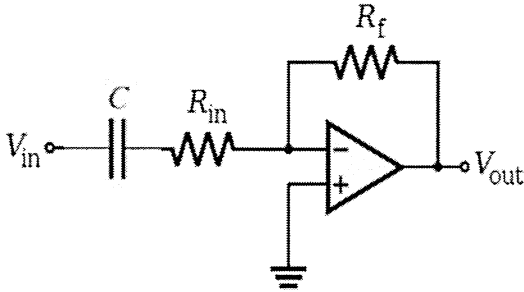- iii) [3 pts] Now we want to remove the effect of the DC offset from the V_{in} for proper amplification of the input signal. One way is to add a capacitor at the input. What is an appropriate value of the capacitor in the figure below, such that the circuit still operates as an **inverting amplifier**? Hint: what should the relative magnitude of the impedances of R_{in} and C ?



In order to perform as an inv. Amplifier
 $Z_c \ll Z_{in}$, just to block low freq.

$$\left| \frac{1}{j\omega C} \right| \ll R_{in}$$

$$C \gg \frac{1}{\omega R_{in}} = \frac{1}{2\pi \cdot (1000) \cdot 10k}$$


$$= \frac{1}{2\pi} \cdot 10^{-7}$$

$$= 15.9 \text{ nF}$$

$$\underline{\underline{C \gg 15.9 \text{ nF}}}$$

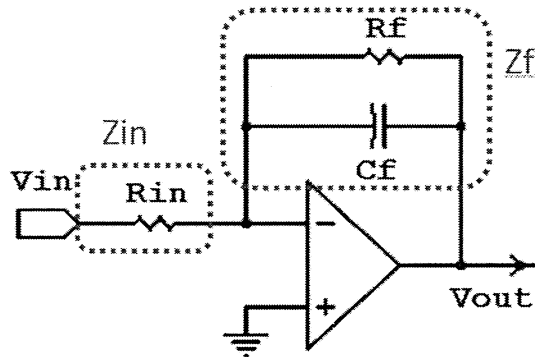IV. Op-Amp Integrators [14 points]

To improve the performance of the ideal integrator in QIII.b, a feedback resistor R_f is added on the feedback path of C_f .



- a) [4 pts] Using the same steps as in QIII.b.i and QIII.b.ii, find the transfer function of this op-amp circuit in terms of R_{in} , R_f and C_f .

$$H(j\omega) = -\frac{Z_f}{Z_{in}}$$

$$H(j\omega) = -\frac{Z_f}{Z_{in}} = -\frac{R_f \parallel C_f}{R_{in}}$$

$$= -\frac{R_f \cdot \frac{1}{j\omega C_f}}{R_f + \frac{1}{j\omega C_f}} \left(\begin{array}{l} \times j\omega C_f \\ \times j\omega C_f \end{array} \right)$$

$$= -\frac{R_f}{1 + j\omega R_f C_f}$$

$$= -\frac{R_f}{R_{in} (1 + j\omega R_f C_f)}$$

- b) [3 pts] Given that $R_{in} = 1\text{ k}\Omega$, assign values for R_f and C_f such that the DC gain is 100 and the corner frequency (3-dB frequency) is 40Hz.


for $R_{in} = 1\text{ k}\Omega$ want DC gain = 100 = $\frac{R_f}{R_{in}}$

$$R_f = 100\text{ k}\Omega$$

$$f_{\text{corner}} = \frac{1}{2\pi \cdot R_f \cdot C_f} = 40\text{ Hz}$$

$$C_f = \frac{1}{2\pi \cdot (100\text{ k}) \cdot (40)} = 0.04\text{ }\mu\text{F}$$

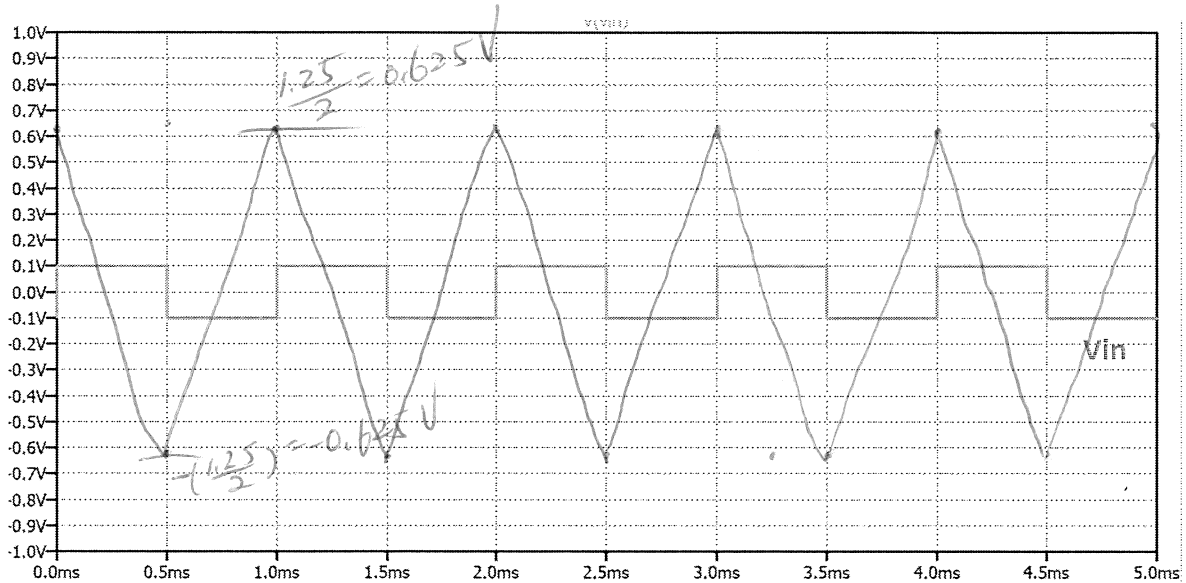- c) [5 pts] For a 0.1V peak-to-peak square wave input with a frequency of 1kHz, draw the output wave form on the voltage-time plot below. Indicate key values from your calculation (such as min and max) on the plot. Hint: since we are in steady-state the DC offset of the output voltage should be 0.



$$V_{out}(t) = \frac{1}{R_{in} C_f} \int_0^t V_{in}(t) dt$$

Constant part: $\frac{1}{R_{in} C_f} = \frac{1}{1k \cdot (0.04 \mu F)} = 2.5 \cdot 10^4$

integration of V_{in} : $(0.1 V)(0.5 ms) = 0.05 \cdot 10^{-3}$

$$V_{out}(t) = 2.5 \times 10^4 \cdot 0.05 \cdot 10^{-3} = 1.25 V \text{ (P-P)}$$

- d) [2 pts] At what frequency does the magnitude of the transfer function reduce to unity (=1)?

$$H(j\omega) = \left| -\frac{R_f}{R_{in}(1 + j\omega R_f C_f)} \right| = 1$$

$$R_f = R_{in}(1 + j\omega R_f C_f)$$

$$\frac{R_f}{R_{in}} - 1 = |j\omega R_f C_f| = 99$$

$$\omega = 2\pi f = \frac{99}{R_f C_f}$$

$$f = \frac{99}{2\pi \cdot R_f C_f} = \frac{99}{2\pi \cdot (100k)(0.04 \mu F)} \approx \underline{\underline{40kHz}}$$