


ENGR4300 Test 1

Spring 2010

Name _____

Section _____

1. Resistive circuits (20 points)

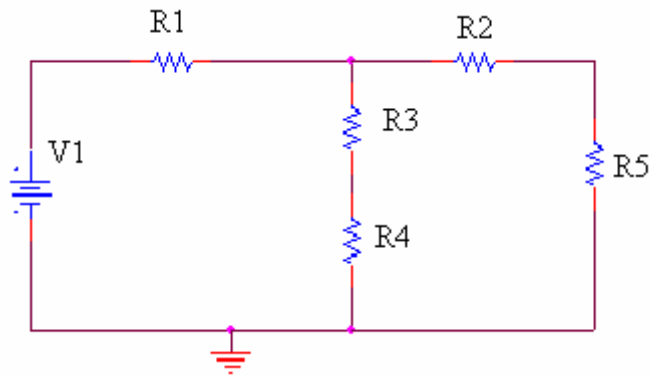

Given: $V_1=5$ volts. $R_1= 50\Omega$, $R_2= 1500\Omega$, $R_3= 2000\Omega$, $R_4= 680\Omega$, $R_5=430\Omega$

- a) (8 points) Find the combined resistance of the circuit including resistors R_1 to R_5 .
 R_3 and R_4 are in series.
 R_2 and R_5 are in series.
Branch containing R_3 and R_4 is in parallel with branch containing R_2 and R_5 .
 R_1 is in series with the equivalent resistance of the two branches.

$$R_{eq} = R_1 + \left(\frac{1}{R_3 + R_4} + \frac{1}{R_2 + R_5} \right)^{-1}$$

$$R_{eq} = 1172\Omega$$

- b) (4 points) Find the voltage across R_1 .

Use voltage division to determine voltage across R_1

$$V_{R1} = \frac{R_1}{R_{eq}} \cdot V_1$$

$$V_{R1} = 0.213V$$

Or find the current through R_1 and then find the voltage across R_1 using Ohm's Law

Let I_1 = current through R_1 .

$$I_1 = \frac{V_1}{R_{eq}}$$

$$V_{R1} = I_1 \cdot R_1 = \frac{V_1}{R_{eq}} \cdot R_1$$

- c) (8 points) Find the current through R_5 .

Let V_2 = Voltage of the node connecting R_2 and R_3 relative to the ground.

By Kirchoff's Voltage Law and then determining the current through R_5 , I_5 , using Ohm's Law.

$$V_2 = V_1 - V_{R1} = 4.787V$$


$$I_5 = \frac{V_2}{R_2 + R_5} = 0.00248A = 2.48mA$$

ENGR4300 Test 1

Spring 2010

Name _____
 Section _____

2. Thevenin circuits (20 points)

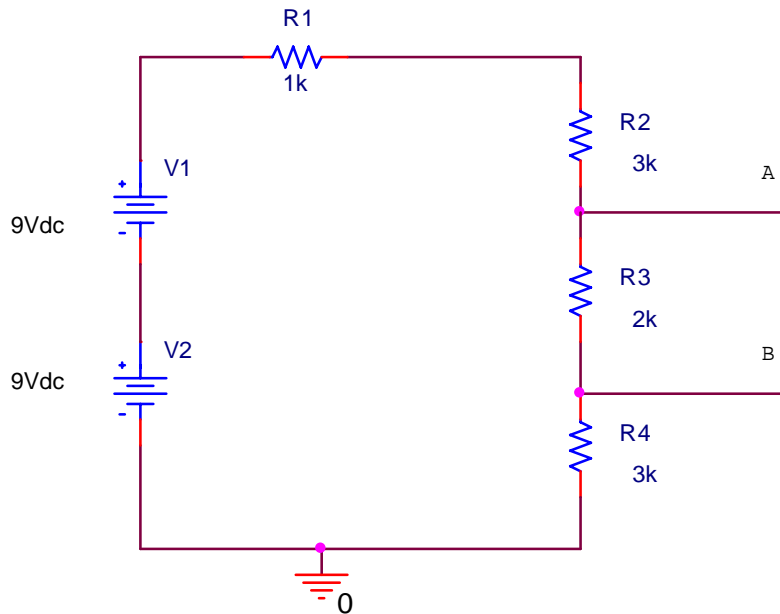

- a) (6 points) Find the Thevenin voltage (V_{oc}) of the circuit assuming the load will be connected between A and B.
- b) (6 points) Find the Thevenin resistance.
- c) (4 points) Draw the Thevenin equivalent circuit with a load of 2k ohms.
- d) (4 points) Find the voltage between A and B for this circuit with a load of 2k ohms.

V_{total}	V1	V2	R1	R2	R3	R4	R_{total}	I	R_{load}	
	18	9	9	1000	3000	2000	3000	9000	0.002	2000
V_{oc}			R_{th}	V_{load}						
			4	1555.556	2.25					

ENGR4300 Test 1

Spring 2010

Name _____

Section _____

3. Instrumentation and Sine Waves (20 points)

You follow this procedure using the Mobile Studio IOBoard and the Mobile Studio Desktop software:

- 1) Plug in the IOBoard and Open the Mobile Studio Desktop
- 2) Open the Oscilloscope and Function Generators on the Desktop
- 3) Connect a wire from AWG1 to A1+
- 4) Connect a wire from the AWG1 GND to the A1 GND and to A1-
- 5) Adjust Channel 1 of the Function Generator to 2kHz
- 6) Adjust the Pk-Pk Voltage of Channel 1 to 0.4V
- 7) Adjust the DC Offset of Channel 1 to 0.2V
- 8) In the Channel 1 Window of the Oscilloscope, adjust the Volts/Div to 200mV, Coupling to DC and Input to A1 SE.
- 9) In the Horizontal Window adjust the Time/Div to 200 μ s and the Mode to Y-T.
- 10) Adjust the vertical position for Channel 1 on the 'scope until it lines up with the horizontal axis on the display
- 11) Click the Start button and set the Trigger to Channel 1, Rising, and Trigger Level to 50%

a) (8 points) Find the following for the signal you have created (specify all units).

- i) the frequency (f)
- ii) the angular frequency (ω)
- iii) the period (T)
- iv) the peak-to-peak voltage (V_{p-p})
- v) the amplitude (A)
- vi) the DC offset voltage (V_{dc})
- vii) the rms voltage (V_{rms})
- viii) the phase (ϕ)

ENGR4300 Test 1

Spring 2010

Name _____

Section _____


1frequency	2000Hz		1 points
2 $\omega=2\pi*f$	12566.37061rad/sec		1 points
3period	1/f	0.0005sec	1 points
4Vp-p		0.4V	1 points
5amplitude	(Vp-p)/2	0.2V	1 points
6offset		0.2V	1 points
7Vrms	(Vamp)/(sqrt(2))	0.14V	1 points
8phase	$\omega*t_0$	0	1 points

mathematical expression $0.2+0.2\sin(12566t+0)$ **2 points**

b) (2 points) Write down the mathematical expression for the trace in the form:
 $v(t) = V_{dc} + A \sin(\omega t + \phi)$.

See table above.

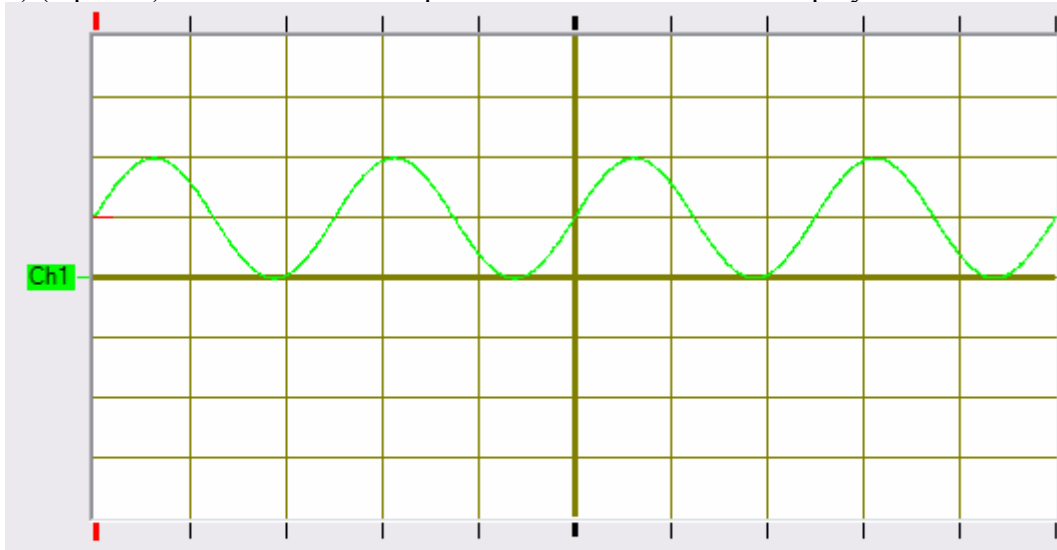c) (8 points) Sketch what the output should look like on the display below.



Horizontal: 200 μ s/Div Trigger: 0.197V
 Channel 1: Vertical: 200 mV/Div
 Coupling: DC
 Input: A1 SE


ENGR4300 Test 1

Spring 2010

Name _____

Section _____

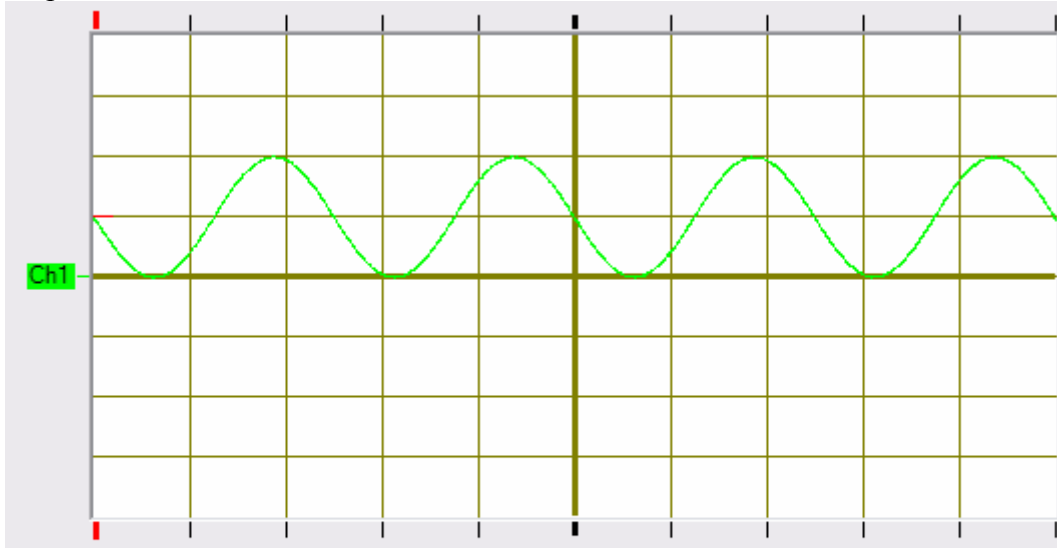d) (2 points) Assume that the Trigger setting was changed to Falling. Sketch the resulting output below.



Horizontal: 200 μ s/Div

Trigger: 0.197V

Channel 1: Vertical: 200 mV/Div
Coupling: DC
Input: A1 SE

Things checked on plots :

	points
amplitude	2 points
offset	2 points
frequency	2 points
start (raise/fall)	2 points


last plot

main thing looked is whether the plot changed its characteristic (raise-fall)

ENGR4300 Test 1
Spring 2010

Name _____
 Section _____

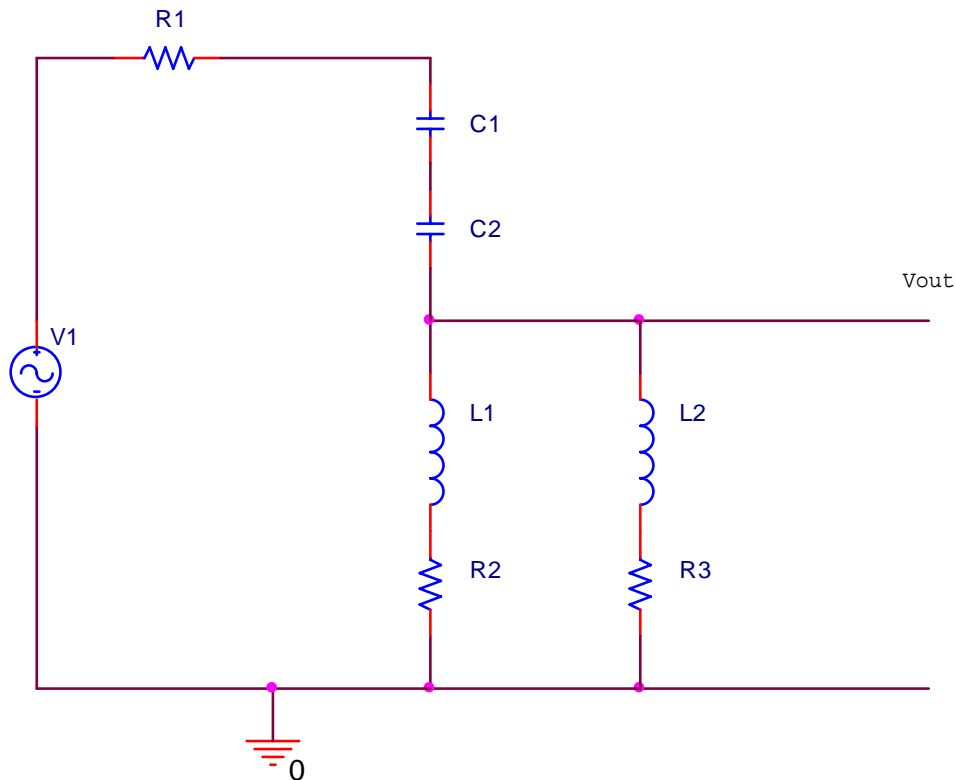4. Inductance and capacitance at very high and very low frequencies (20 points)



Consider the above circuit and apply your knowledge about the behavior of capacitors and inductors (i.e., open or short circuits at very high or very low frequencies).

- a) (6 points) Redraw this circuit when the source (V1) frequency is very low.
- b) (2 points) According to your redrawn circuit, what would be the value of the voltage at Vout with respect to ground at very low frequencies? (Circle the best answer.)

Vout=0 Vout = V1 $0 < V_{out} < V1/R1$ $V1/R1 < V_{out} < V1$

- c) (6 points) Redraw this circuit when the source (V1) frequency is very high.
- d) (2 points) According to your redrawn circuit, what would be the value of the voltage at Vout with respect to ground at very high frequency? (Circle the best answer.)

Vout=0 Vout = V1 $0 < V_{out} < V1/R1$ $V1/R1 < V_{out} < V1$


- e) (4 points) Using your knowledge of filters, what kind of filter would you say this is? (Circle the best answer).

high pass filter low pass filter band pass filter band reject filter

ENGR4300 Test 1
Spring 2010


Name _____
Section _____

(a) at low frequency

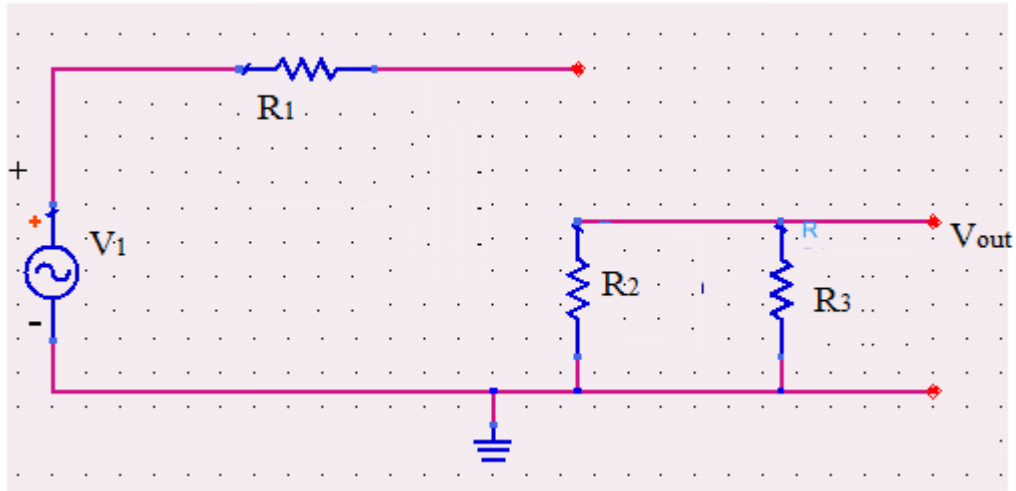

(b) $V_{out} = 0$

(c) at high frequency

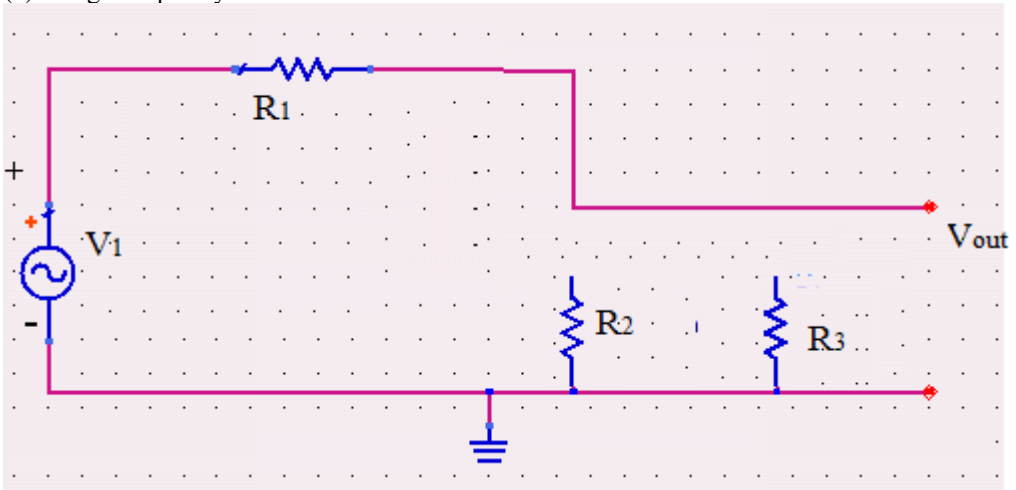

(d) $V_{out} = V_1$

(e) High pass


ENGR4300 Test 1 Spring 2010

Name _____

Section _____

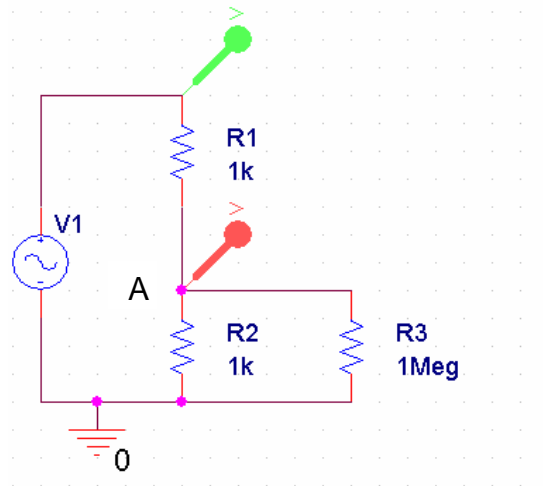
5. Capture/PSpice (20 points)

In experiment 1, you wired a circuit similar to the one below using real components and in PSpice:



a) (6 points) What does this circuit do? What do V1, R1, R2, and R3 represent?

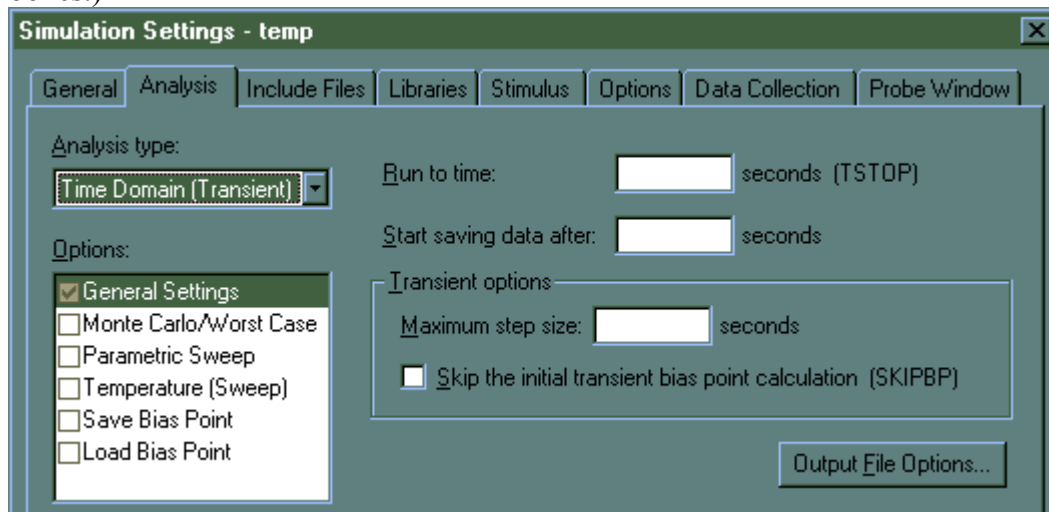b) (3 points) Suppose V1 has a frequency of 400 Hz, an amplitude of 3V, and a DC offset of 0. You want to run a transient analysis. How would you set up the simulation screen below to show exactly 3 smooth cycles of the output wave? (Fill in the three empty boxes.)



You can put your answers here for clarity:


c) (3 points) If you set up this transient simulation, what would be the frequency (in Hz) and the approximate amplitude (in V) of the signal at point A?

d) (5 points) If you replaced R2 with a resistor with color code green-black-brown-gold, what would be the frequency (in Hz) and the approximate amplitude (in V) of the signal at point A?

ENGR4300 Test 1
Spring 2010

Name _____
 Section _____

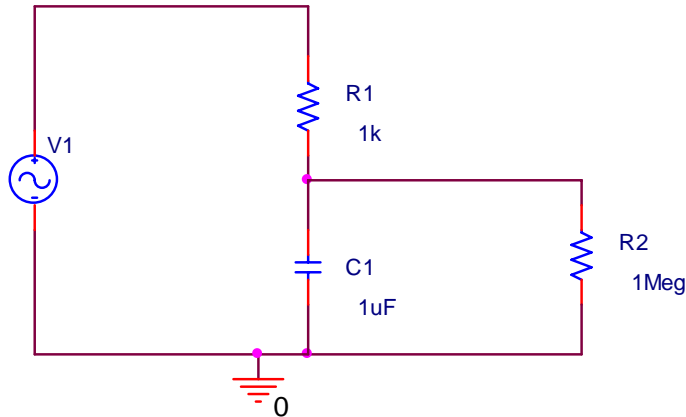e) (3 points) In experiment 2, you added a capacitor to a circuit in order to create a filter. We have added a capacitor to the circuit in this question.



What type of analysis (simulation) would you have to run to determine if this altered circuit is a high or low pass filter? (Circle the best answer.)

- Transient DC sweep AC sweep Bias Point

Extra credit (1 point): What type of filter is it and why?

Voltage divider
 V1 is source, R1 and R2 are divider resistors, 1Meg is scope or some other measuring device
 Freq 400
 Period 0.0025
 Four cycles 0.01 Three cycles 0.0075
 Start at t=0
 Use four cycles/1000 for time step Use three cycles/1000 for time step
 At pt A half the voltage, same frequency
 Figure out the color code and then do new divider
 AC Sweep would be good
 Low pass filter

Note that an answer is provided for both 4 and 3 cycles because one ends up looking neater than the other.