

ENGR-2300

Electronic Instrumentation

Quiz 2

Fall 2019

Name SOLUTIONS

RIN _____

Question I (20 points) _____

Question II (20 points) _____

Question III (20 points) _____

Question IV (20 points) _____


LMS Question is worth an additional 20pts

Total (80 points) _____

On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

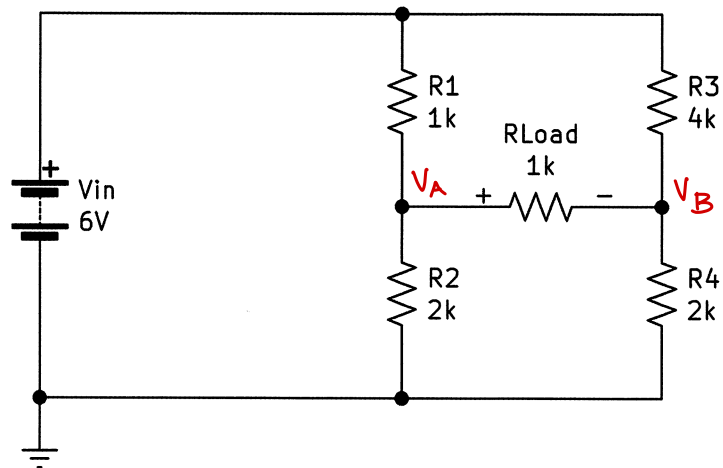1. Thévenin Equivalent And Voltage Follower (20 points)

The Thévenin Equivalent Circuit provides a very simple replacement for much more complex circuits. If we have this simple circuit, analyzing changing loads becomes quite easy. In this problem, you are to find the Thévenin voltage and resistance for a circuit.



- a) Find Thévenin Voltage for the circuit assuming RLoad as load resistor. {4pts}

$$V_{Th} = V_A - V_B \quad (\text{after removing load resistor})$$



$$V_A = V_{in} \left(\frac{R_2}{R_1 + R_2} \right) = 4V$$

$$V_B = V_{in} \left(\frac{R_4}{R_3 + R_4} \right) = 2V$$

$$V_{Th} = V_A - V_B = \boxed{2V}$$

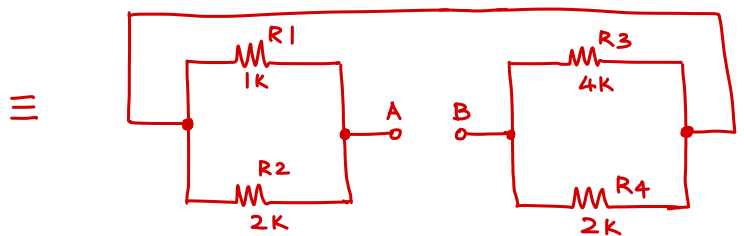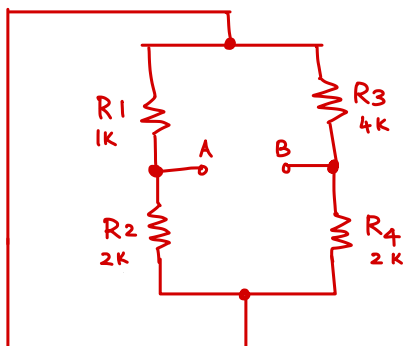- b) Find the Thévenin Resistance. {4 pts}


To find R_{Th} , switch V_{in} off $\Rightarrow V_{in} = 0$
(replace by short circuit)



$$R_{Th} = R_{AB} = (R_1 \parallel R_2) + (R_3 \parallel R_4)$$


$$= \boxed{2k\Omega}$$

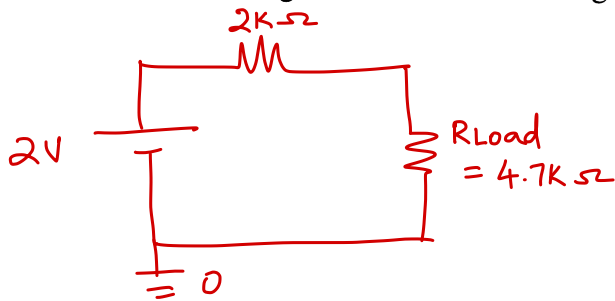- c) Find the current through R_{Load} after it is changed from $1k\Omega$ to $4.7k\Omega$ in the circuit. {2 pts}



$$I_{R_{Load}} = \frac{2V}{6.7k} = 0.298 \text{ mA} \text{ or } 298.5 \mu\text{A}$$

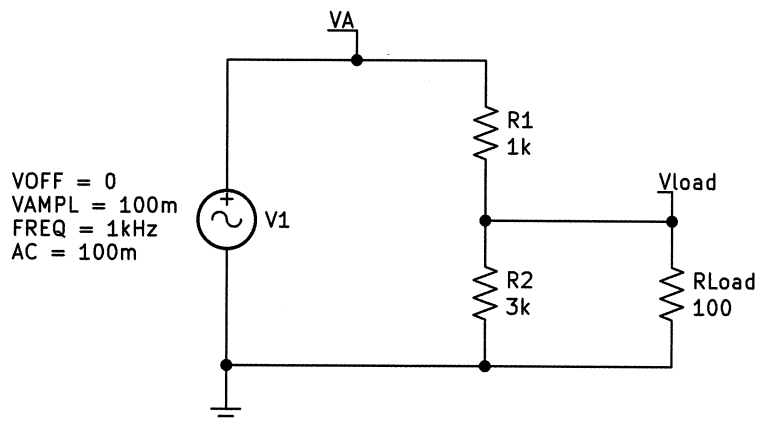
- d) **True** or **False**: A battery can be represented using a Thévenin equivalent circuit. {1 pt}
- e) **True** or **False**: Thévenin equivalent circuits are only useful for a specific load impedance {1 pt}
- f) Two students, students X and Y, are given the same task. They are both asked to design a circuit that is able to take in a sinusoidal voltage source V_1 with 100 mV amplitude, as shown in circuit diagrams below, and deliver the same sinusoid but with an amplitude of 75 mV to a load resistor of 100Ω .
- i. Student X designs a voltage divider as shown below. Will this student satisfy the design criterion? Provide reason for your answer by calculating V_{load} . {2 pts}



$$V_{load} = \frac{R_2 \cdot R_{Load}}{R_2 + R_{Load}} \cdot V_A \cdot \frac{1}{R_1 + \frac{R_2 \cdot R_{Load}}{R_2 + R_{Load}}} = 8.83 \text{ mV} \ll 75 \text{ mV}$$

No

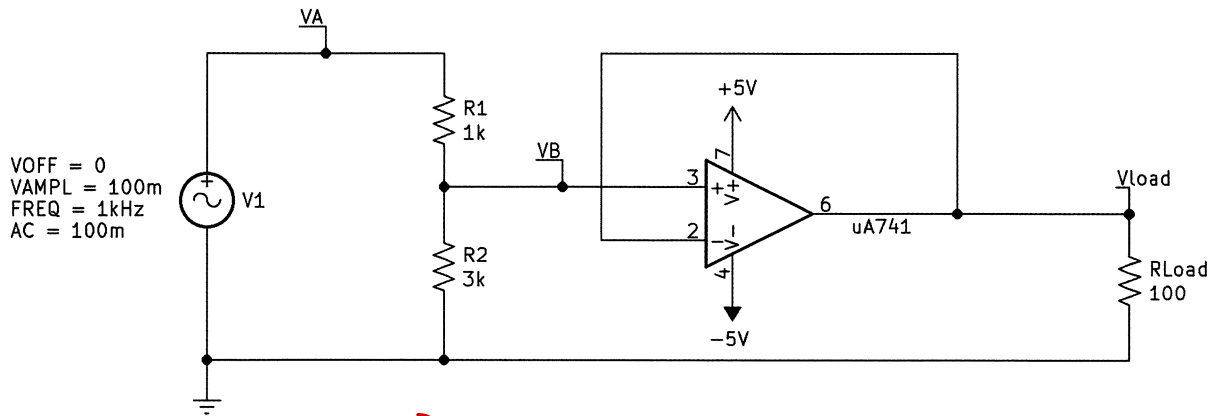- ii. Student Y designs a voltage follower as shown below. Will this student satisfy the design criterion? Provide reason for your answer by calculating V_{load} . {2 pts}




$$V_B = \frac{R_2}{R_1 + R_2} V_A = 75\text{mV}$$

$$V_B = V_{Load} \text{ (Voltage follower)}$$

YES!

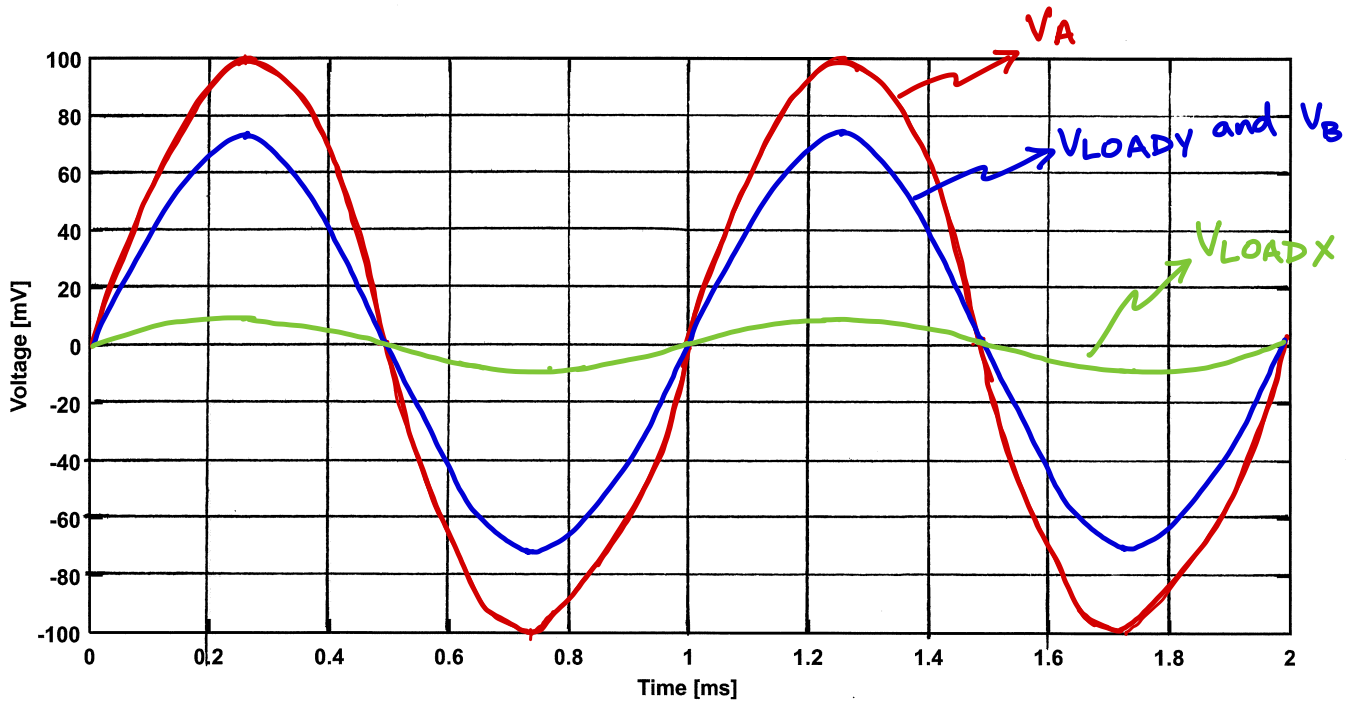- iii. Sketch the voltage waveform, V_{load} , measured by students X and Y across the load resistor. Also sketch voltage waveforms for V_A (same for both students) and pin 3 of op-amp, V_B (only for student Y), on the same plot. Label your line plots clearly. Use V_{loadX} , V_{loadY} , V_A , and V_B for labelling. {4 pts}




$$V_A \text{ amplitude} \rightarrow 100\text{mV}$$

$$V_{LOADX} \text{ amplitude} = 8.8\text{mV}$$

$$V_B \text{ and } V_{LOADY} \rightarrow 75\text{mV}$$

2. Strain Gauges and Bridges (20 points)

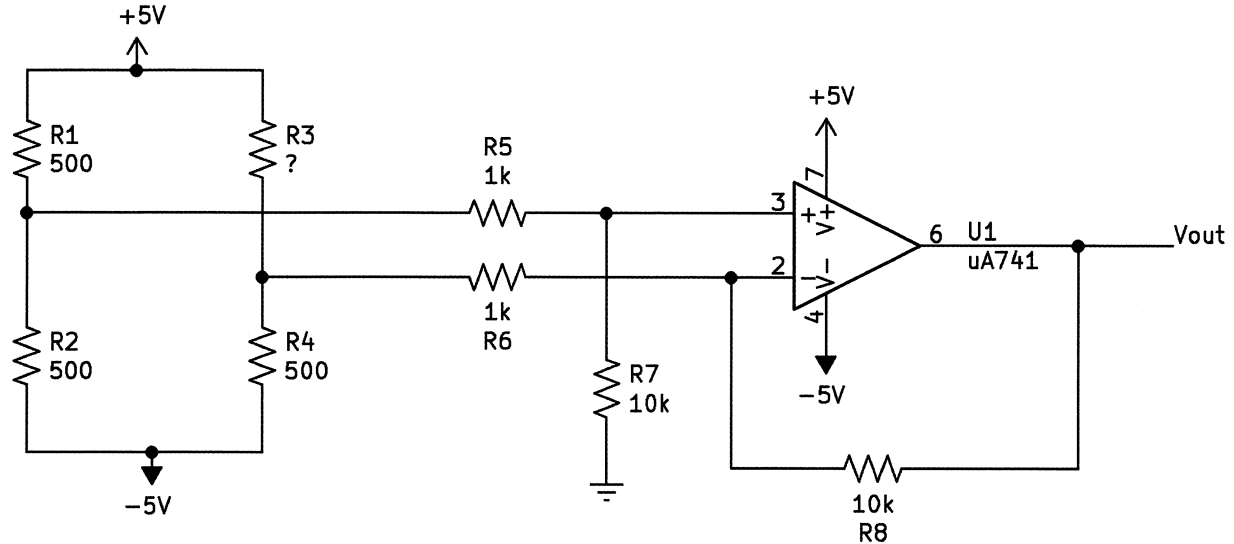

a) If V_{out} for the Bridge/Amp circuit output is 650 mV, find the value of R_3 . {8 pts}

Differential amplifier:

$$V_{out} = \frac{R_8}{R_6} (V_2 - V_1) = \frac{R_7}{R_5} (V_2 - V_1)$$

$$V_2 = \left[5 - (-5) \right] \frac{R_2}{R_1 + R_2} - 5 = 0V$$

$$650 \text{ mV} = \frac{10K}{1K} (0 - V_1)$$

$$V_1 = -65 \text{ mV} = \left[5 - (-5) \right] \frac{R_4}{R_3 + R_4} - 5$$

$$\Rightarrow V_1 = 10 \frac{R_4}{R_3 + R_4} - 5V = -65 \text{ mV}$$


$$\Rightarrow \frac{R_4}{R_3 + R_4} = 0.4935 \Rightarrow \boxed{R_3 = 513 \Omega}$$

- b) Now consider that R_4 is an atmospheric pressure sensor, located higher than sea level. At sea level, the sensor would balance the bridge ($V_{out} = 0$ V). Due to the increased elevation, there is a consistent offset away from 0 V due to the decreased average pressure. It is desired to re-balance the bridge to account for this (e.g., the offset is removed). To do this, a "trim" resistor is added. Assuming the solution from part a. is the offset value, what value would your trim resistor be and where would you place it? {4 pts}

Multiple options

- ① $13\ \Omega$ resistor in series with R_4 .
OR
② $13\ \Omega$ resistor in series with R_1 .
OR
③ $19.73\ k\Omega$ resistor in parallel with R_3 .

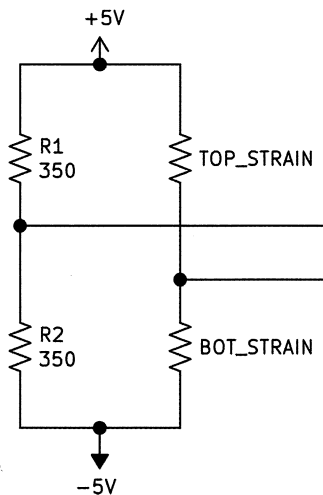
- c) In experiment 5 and project 2, the bridge had two strain gauges in it, as shown below. One was on the top of the beam and the other was on the bottom. What is the usefulness in having two strain gauges? {2pts}



As the beam bends, one of the strain gauges increases in resistance while the other decreases at the same rate.

This effectively doubles the sensitivity of the measurement.

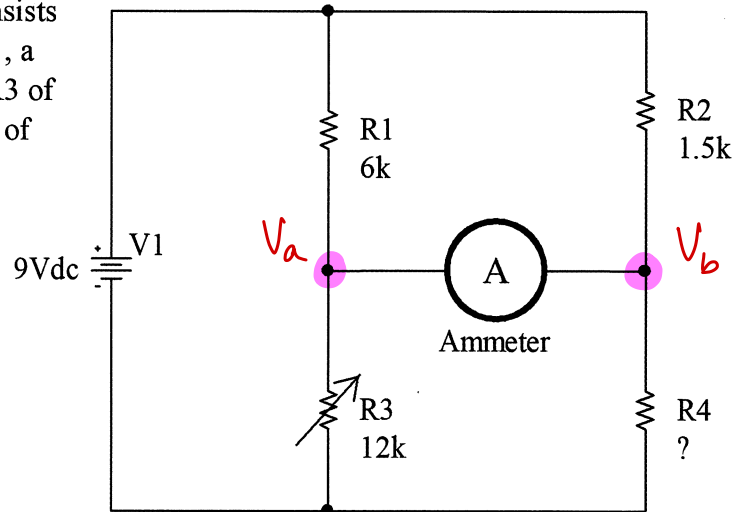- d) A circuit, shown to the right, consists of two fixed resistors R_1 and R_2 , a variable resistor, the resistance R_3 of which can be adjusted, a resistor of unknown value R_4 , and 9.0 volt battery. When R_3 is adjusted to 12k ohms, there is zero current through the ammeter. What is the unknown resistance R_4 ? {5 pts}



Zero current through ammeter $\Rightarrow V_a = V_b$

$$V_a = 9 \left(\frac{R_3}{R_1 + R_3} \right) = 9 \left(\frac{12K}{18K} \right) = 6V$$

$$V_b = 9 \left(\frac{R_4}{R_2 + R_4} \right) = \frac{9R_4}{1.5K + R_4} = 6V$$

$$\Rightarrow 9R_4 = 9K + 6R_4 \Rightarrow$$

$$R_4 = 3K\Omega$$


- e) **True or False:** Considering a bridge with only 1 active element (e.g., bridge from part a), the resistor in the same leg as the active element (R_4) must be the same value as the two resistors in the other leg (R_1, R_2). {1 pt}

3. Operational Amplifier Applications

a. For diagram shown V_p is the voltage on the non-inverting op amp terminal.

- i. (2pts) Determine V_p in terms of V_{in} . Assume an ideal op amp and use the Golden Rules, a.k.a. the op amp analysis rules.

$$i_p = 0 \quad V_{Ra} = 0 \quad \left| \quad V_p = V_{in} \right.$$

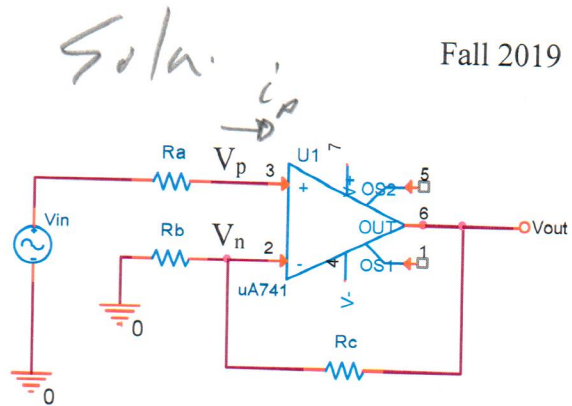

- ii. (2pts) Explain in 25 words or hopefully less how you determine the answer to part i.

Op Amp analysis rules: input current to + and - term is zero, Voltage on $R_a = 0$, $V_p = V_{in}$

OR: Since the input current is 0, V_p equals V_{in}


- iii. (2pts) For this circuit, if $V_{in}(t) = 0.2 \cos 2000t$ Volts, $R_a = 1k\Omega$, $R_b = 1k\Omega$, $R_c = 5k\Omega$ What is $V_{out}(t)$? Non-inverting conf.

$$\frac{V_{out}}{V_{in}} = \left(\frac{R_c}{R_b} + 1 \right) = 6 \quad \underline{V_{out} = 1.2 \cos 2000t}$$

b. The circuit shown is a Miller Integrator.

Given: $R_{in} = 2k\Omega$, $R_f = 20k\Omega$, $C_f = 0.5\mu F$

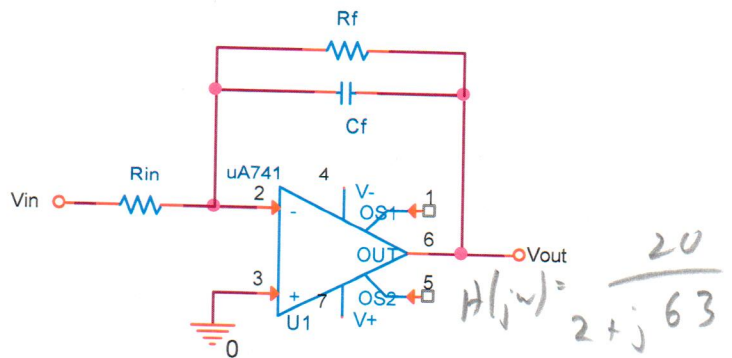- i. (3pts) AC Steady State: if V_{in} is a sinusoidal waveform with a frequency of 500Hz, determine ω and determine the complete transfer function $H(j\omega)$ plugging the component values. For the complete, don't simplify by assuming ω is either very large or small. Leave $H(j\omega)$ as a ratio.



$$H(j\omega) = \frac{20}{2 + j63}$$

$$\omega = 2\pi f = 3141 \text{ rad/sec}$$

From Crib sheet: $H(j\omega) = \frac{R_f}{R_{in}(1 + j\omega R_f C_f)} = \frac{20k}{2k(1 + j(3.14k)(20k)(5 \times 10^{-6}))}$

- ii. (2pts) If $V_{in} = 0.1V$ (dc) what is V_{out} ? And for this case is the circuit an integrator? (Yes or No)?


for dc, C_f is open $V_{out} = -\frac{R_f}{R_{in}} V_{in} = (-10)(0.1V) = -1V$

No - Not an integrator

Soln

c. For the circuit shown answer the following questions:

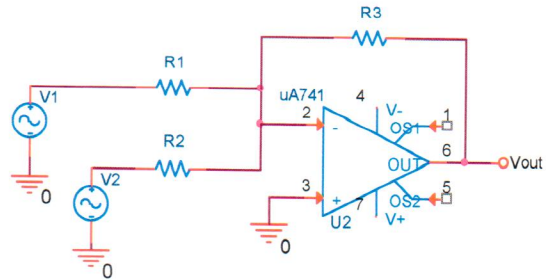- i. (4pts) Determine V_{out} if:
 $V_1 = 1V$ dc, $V_2 = 1\cos(5000t)V$
 $R_1 = 2k\Omega$, $R_2 = 1k\Omega$, $R_3 = 6k\Omega$



Answer $V_{out} = -\frac{R_3}{R_1} V_1 + -\frac{R_3}{R_2} V_2$

$$= \left(-\frac{6}{2}\right)(1) + -\frac{6}{1} \cdot 1\cos(5000t) = (-6\cos 5000t - 3)V$$

- ii. (2pts) Assume that the op amp is ideal except that it has finite voltage supplies. For this circuit to work as you have determine in part i. what are the restrictions on V_+ and V_- ?

also good

$$V_{out\ max} = 6 - 3 = 3V$$

Need $(V_-) \leq -9V$ $V_+ \geq 3V$

$$V_{out\ min} = -6 - 3 = -9V$$

Good answer is $V_- = -9V$
 $V_+ = +9V$

- d. (1pts) An integrator with an triangle wave input will have a sinewave at the output?

True or False

$$\int_a^b mt dt = \frac{1}{2} m t^2$$

Not sinewave

- e. (1pts) A differentiator circuit with a triangle wave input will have a square wave at the output?

True or False

$$\frac{d}{dt} (mt) = m$$

$m = \text{slope of triangle input}$

- f. (1pt) The reason that two strain gauges are mounted on the cantilever beam rather than just one is to improve reliability?


True or False

No if either fails the circuit fails

2 - one top one bottom to form $\frac{1}{2}$ of Bridge

No explanation needed

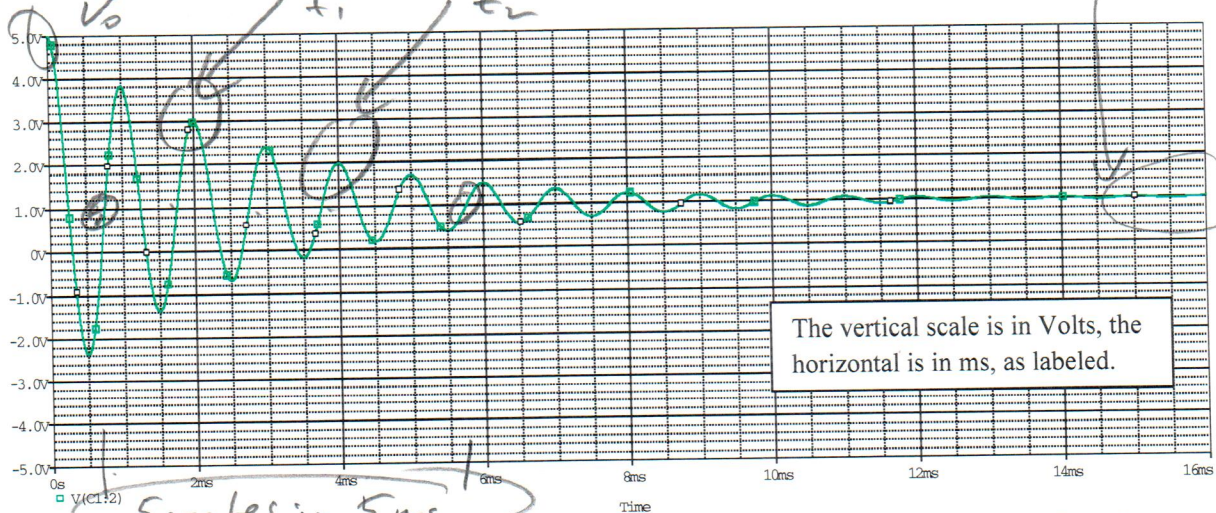4) Concepts, Troubleshooting and Data Analysis



a. (10pts) The trace shown is for a damped oscillation with an offset. Data collected from the cantilever beam often has an offset. The equation that represents this data is:

$$v(t) = V_0 e^{-\alpha t} \cos \omega t + V_{offset}$$

Use data from the plot and determine: V_0 , α , ω , and V_{offset} . **Include units. You must mark the points on the plot that you used.** Note that this must match the plot starting at time=0sec.

Handwritten work for part a:

- Annotations on the plot: V_0 , t_1 , t_2 , $V_{offset} = 1V$.
- Text box: "The vertical scale is in Volts, the horizontal is in ms, as labeled."
- Equation: $v(t) = V_0 e^{-\alpha t} \cos \omega t + V_{offset}$
- Text: "Use data from the plot and determine: V_0 , α , ω , and V_{offset} . Include units. You must mark the points on the plot that you used. Note that this must match the plot starting at time=0sec."
 - Handwritten: $5 \text{ cycles in } 5 \text{ ms} \Rightarrow 1 \text{ kHz}$
 - Handwritten: $\omega = 6.28 \times 10^3 \text{ rad/sec}$
 - Handwritten: $V_{offset} = 1V$ (Inspection)
 - Handwritten: V_0 can be by inspection, 5V at $t=0$
 - Handwritten: $V_0 = 5 - V_{offset} = 4V$
 - Text: "For α , pick 2 points where $\cos(\omega t) = 1$ "
 - Equation:
$$\frac{V(t_1) - V_{offset}}{V(t_2) - V_{offset}} = e^{-\alpha(t_1 - t_2)}$$
 - Handwritten: $\frac{3 - 1}{2 - 1} = e^{-\alpha(2 \text{ms} - 4 \text{ms})}$
 - Handwritten: $2 = e^{-\alpha(-2 \times 10^{-3})}$
 - Handwritten: $\ln(2) = -\alpha(-2 \times 10^{-3})$
 - Handwritten: $\alpha = 347 \text{ sec}^{-1}$

b. (2pts) Class room knowledge and tasks:

i. All of the resistors used for the experiments were supplied in the bag of parts.

True or False

ii. Before any signatures will be provided by the instructors or TAs, hand-drawn schematics must be prepared for all circuits in the experiment.

True or False

c. (6pts) Consider the strain gauge circuit on the cantilever beam. Which of the following can be used as a measurement of the beam tip velocity? Circle *Yes* or circle *No*

i. The strain gauge bridge signal with just a differential op amp circuit? *Yes* or *No*

ii. The accelerometer with just a differential amplifier? *Yes* or *No*

iii. The accelerometer with just a differentiator op amp circuit? *Yes* or *No*

iv. The strain gauge bridge signal with a differential op amp plus a differentiator op amp circuit? *Yes* or *No*

v. Is there another configuration of signal and circuit that can be used to measure the beam velocity? **And if yes, what is that circuit?** *Yes* or *No*

2pt

accelerometer with integrator circuit

Electrical Characteristics (Note 5) (Continued)											
Parameter	Conditions	LM741A			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Large Signal Voltage Gain	$T_A = 25^\circ\text{C}$, $R_L \geq 2\text{ k}\Omega$ $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$ $V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$	50			50	200		20	200		V/mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$, $R_L \geq 2\text{ k}\Omega$, $V_S = \pm 20\text{V}$, $V_O = \pm 15\text{V}$ $V_S = \pm 15\text{V}$, $V_O = \pm 10\text{V}$	32			25			15			V/mV
	$V_S = \pm 5\text{V}$, $V_O = \pm 2\text{V}$	10									V/mV
Output Voltage Swing	$V_S = \pm 20\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$		± 16								V
	$V_S = \pm 15\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$		± 15								V
	$V_S = \pm 15\text{V}$ $R_L \geq 10\text{ k}\Omega$ $R_L \geq 2\text{ k}\Omega$				± 12 ± 10	± 14 ± 13		± 12 ± 10	± 14 ± 13		V
Output Short Circuit Current	$T_A = 25^\circ\text{C}$	10	25	35		25			25		mA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$	10		40							mA

LM741

d. (2pts) Using the 741 op amp data sheet information above, answer the following questions:

i. If LM741A op-amp is powered with a +20V supply and a -20V supply, (V_S in data sheet), what is the range of output voltages that can be obtained if the load resistance is $2\text{ k}\Omega$?

$\pm 15\text{V}$ assumed

ii. If a 80Ω load resistor is connected between output of a LM741C op-amp and ground, for a circuit using +15V and -15V supplies, what is the expect range of obtainable output voltages?

$(25\text{mA}) \times 80\Omega = 2\text{V}$
 $\pm 2\text{V}$