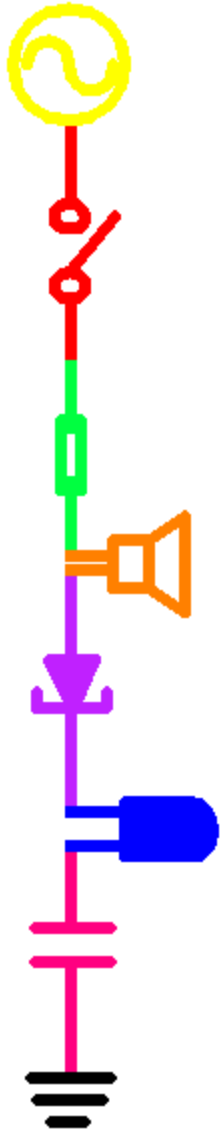


Electronic Instrumentation


Experiment 2

- * Part A: Intro to Transfer Functions and AC Sweeps
- * Part B: Phasors, Transfer Functions and Filters
- * Part C: Using Transfer Functions and RLC Circuits
- * Part D: Equivalent Impedance and DC Sweeps



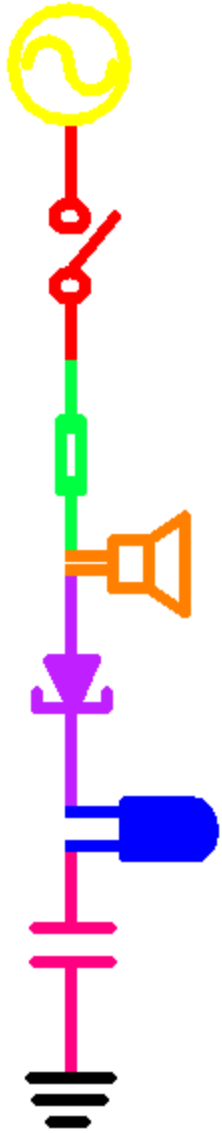Part A

- ◆ Introduction to Transfer Functions and Phasors
- ◆ Complex Polar Coordinates
- ◆ Complex Impedance (Z)
- ◆ AC Sweeps




Transfer Functions

$$H \equiv \frac{V_{out}}{V_{in}}$$

- ◆ The transfer function describes the behavior of a circuit at V_{out} for all possible V_{in} .



Simple Example

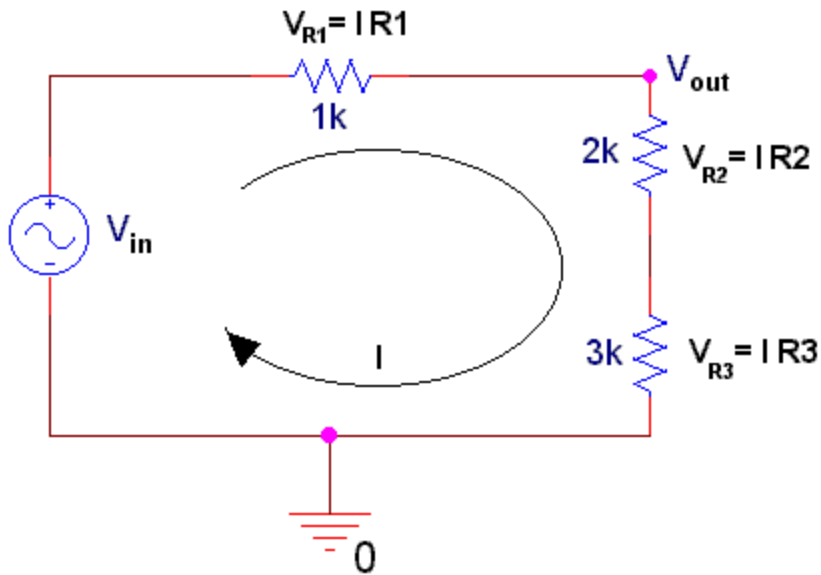


$$V_{out} = V_{in} * \frac{R2 + R3}{R1 + R2 + R3}$$

$$V_{out} = V_{in} * \frac{2k + 3k}{1k + 2k + 3k}$$


$$H \equiv \frac{V_{out}}{V_{in}} = \frac{5}{6}$$

$$\text{if } V_{in}(t) = 6V \sin\left(2kt + \frac{\pi}{2}\right) + 12V$$
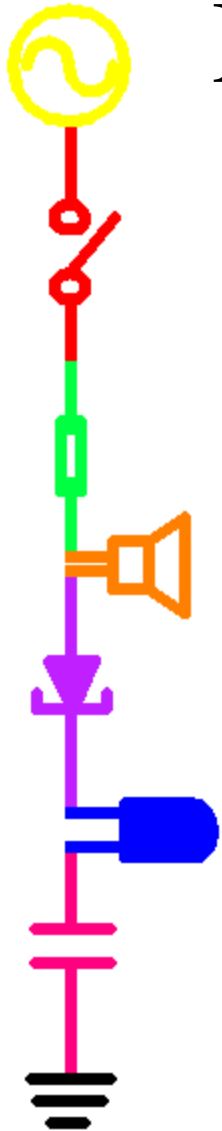
$$\text{then } V_{out}(t) = 5V \sin\left(2kt + \frac{\pi}{2}\right) + 10V$$




More Complicated Example

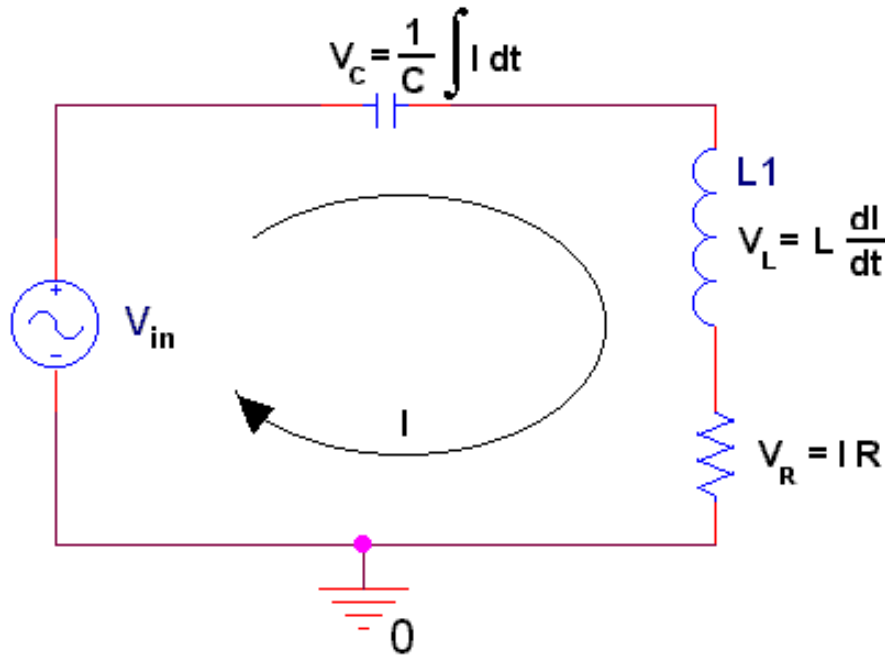

What is H now?

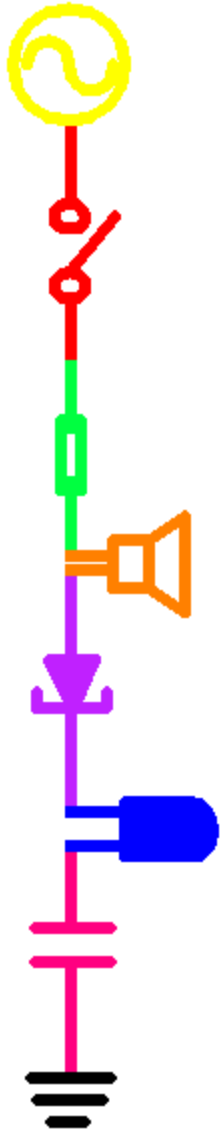- ◆ H now depends upon the input frequency ($\omega = 2\pi f$) because the capacitor and inductor make the voltages change with the change in current.



How do we model H?


- ◆ We want a way to combine the effect of the components in terms of their influence on the amplitude and the phase.
- ◆ We can only do this because the signals are sinusoids
 - cycle in time
 - derivatives and integrals are just phase shifts and amplitude changes



We will define Phasors


$$\vec{V} = f(A, \phi)$$

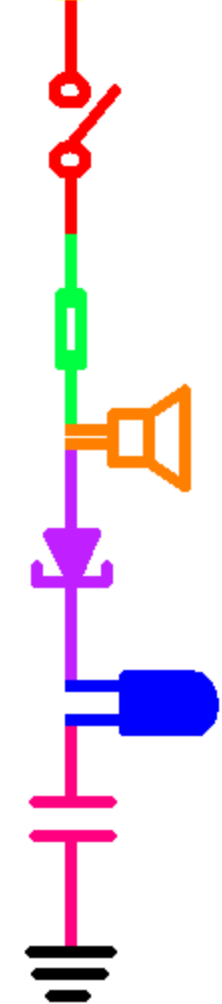- ◆ A phasor is a function of the amplitude and phase of a sinusoidal signal
- ◆ Phasors allow us to manipulate sinusoids in terms of amplitude and phase changes.
- ◆ Phasors are based on complex polar coordinates.
- ◆ Using phasors and complex numbers we will be able to find transfer functions for circuits.





Review of Polar Coordinates

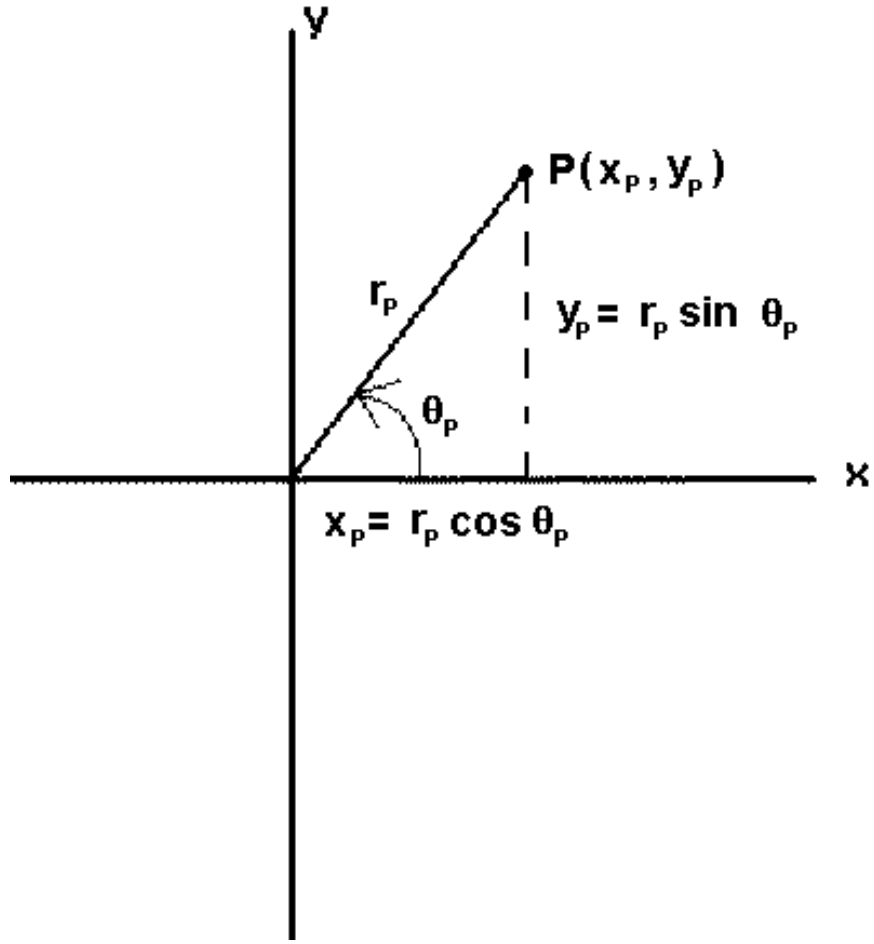


point P is at
 $(r_p \cos \theta_p , r_p \sin \theta_p)$

$$\theta_P = \tan^{-1} \left(\frac{y_P}{x_P} \right)$$
$$r_P = \sqrt{x_P^2 + y_P^2}$$




Review of Complex Numbers

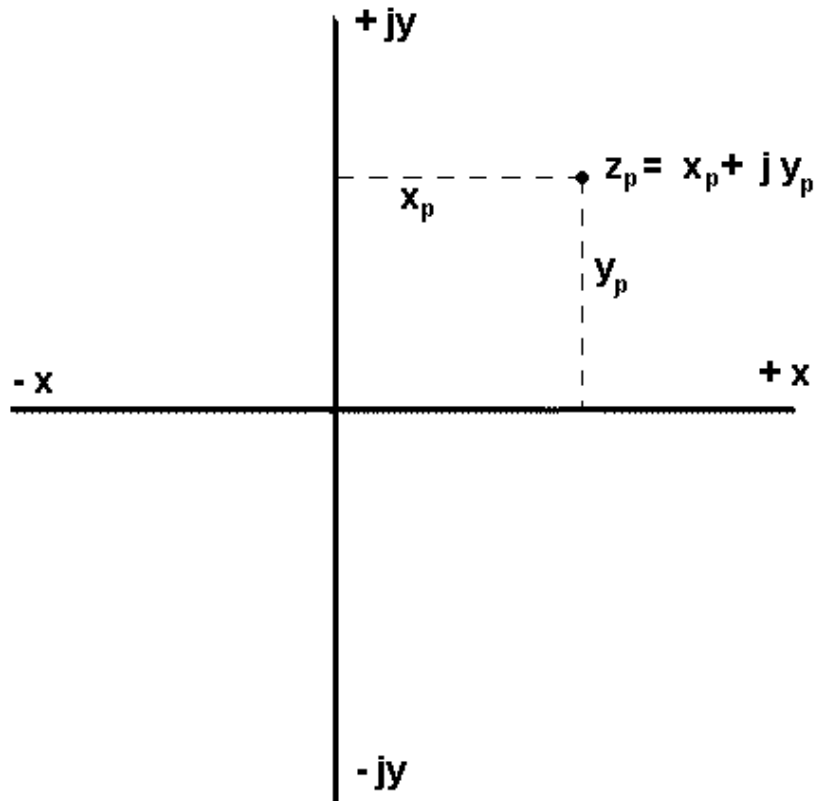


$$j \equiv \sqrt{-1}$$
$$j \cdot j = -1$$
$$\frac{1}{j} = -j$$

- ◆ z_p is a single number represented by two numbers
- ◆ z_p has a “real” part (x_p) and an “imaginary” part (y_p)

Complex Polar Coordinates

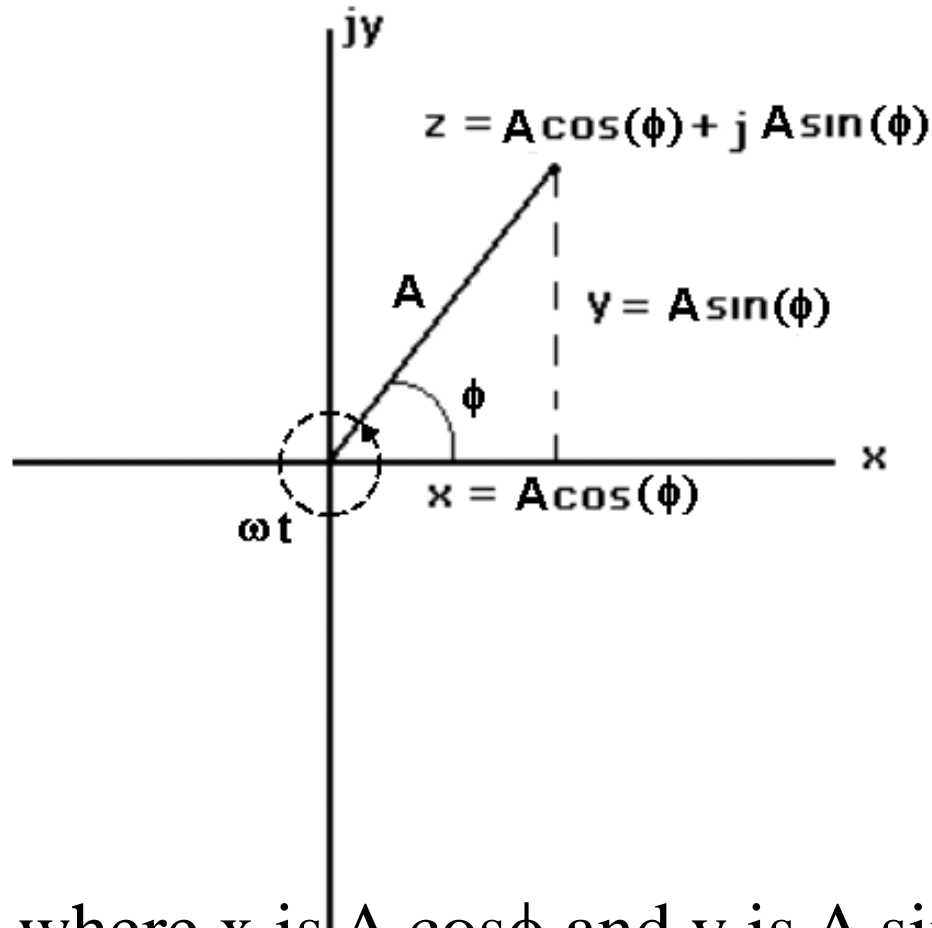

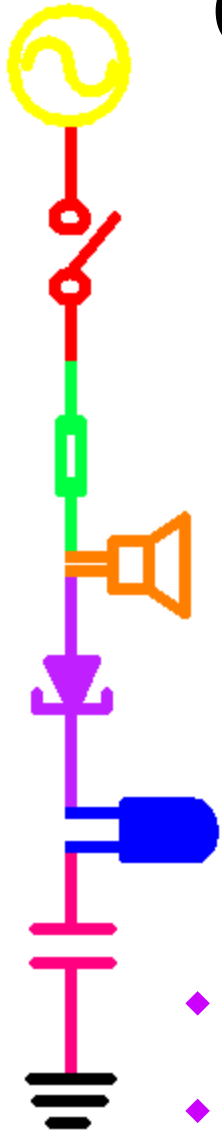- ◆ $z = x + jy$ where x is $A \cos \phi$ and y is $A \sin \phi$
- ◆ ωt cycles once around the origin once for each cycle of the sinusoidal wave ($\omega = 2\pi f$)



Now we can define Phasors


if $V(t) = A \cos(\omega t + \phi)$, then let


$$\vec{V} = A \cos(\omega t + \phi) + jA \sin(\omega t + \phi)$$

or simply, $\vec{V} = A \cos \phi + jA \sin \phi$

(ωt is common to each term, so it is dropped.)

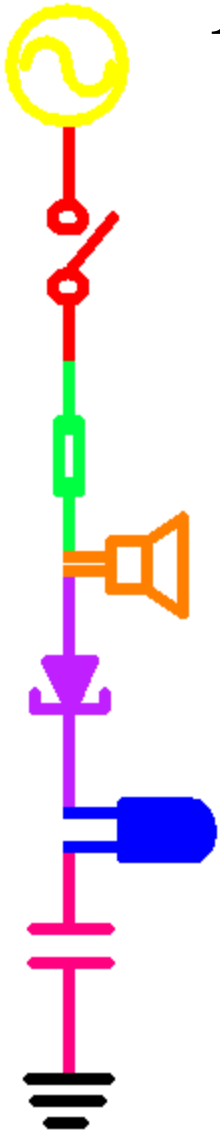- ◆ The real part is our signal.
- ◆ The two parts allow us to determine the influence of the phase and amplitude changes mathematically.
- ◆ After we manipulate the numbers, we discard the imaginary part.



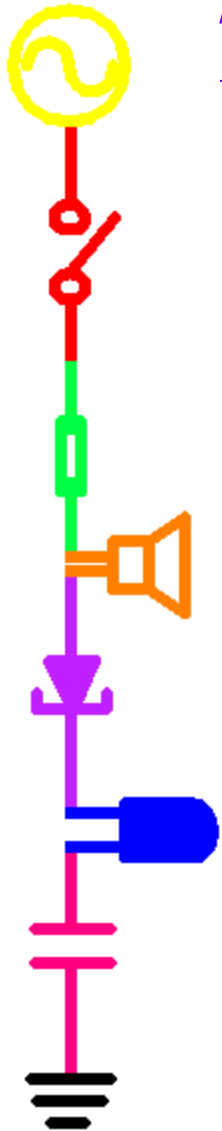

The “ $V=IR$ ” of Phasors

$$\vec{V} = \vec{I}Z$$

- ◆ The influence of each component is given by Z , its complex impedance
- ◆ Once we have Z , we can use phasors to analyze circuits in much the same way that we analyze resistive circuits – except we will be using the complex polar representation.




Magnitude and Phase

$$\vec{V} \equiv A \cos \phi + j A \sin \phi = x + jy$$

$$|\vec{V}| \equiv \sqrt{x^2 + y^2} = A \quad \text{magnitude of } \vec{V}$$

$$\angle \vec{V} = \tan^{-1} \left(\frac{y}{x} \right) = \phi \quad \text{phase of } \vec{V}$$

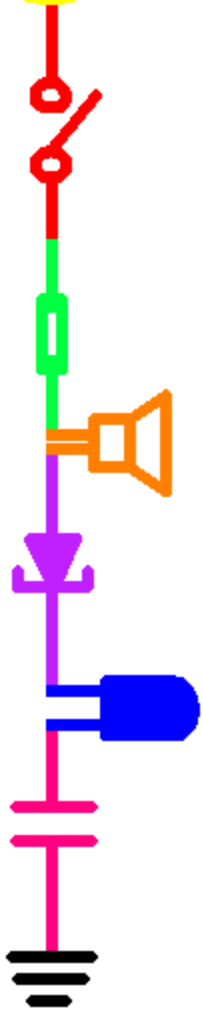- ◆ Phasors have a magnitude and a phase derived from polar coordinates rules.





Influence of Resistor on Circuit

$$V_R = I_R R$$

if $I_R(t) = A \sin(\omega t)$

then $V_R(t) = R * A \sin(\omega t)$

- ◆ Resistor modifies the amplitude of the signal by R
- ◆ Resistor has no effect on the phase



Influence of Inductor on Circuit

$$V_L = L \frac{dI_L}{dt}$$

Note:
 $\cos\theta = \sin(\theta + \pi/2)$

if $I_L(t) = A \sin(\omega t)$

then $V_L(t) = \omega L * A \cos(\omega t)$

or $V_L(t) = \omega L * A \sin(\omega t + \frac{\pi}{2})$

- ◆ Inductor modifies the amplitude of the signal by ωL
- ◆ Inductor shifts the phase by $+\pi/2$



Influence of Capacitor on Circuit

$$V_C = \frac{1}{C} \int I_C dt$$



if $I_C(t) = A \sin(\omega t)$

then $V_C(t) = \frac{-1}{\omega C} * A \cos(\omega t) = \frac{1}{\omega C} * A \cos(\omega t - \pi)$

or $V_C(t) = \frac{1}{\omega C} * A \sin(\omega t + \frac{\pi}{2} - \pi) = \frac{1}{\omega C} * A \sin(\omega t - \frac{\pi}{2})$

- ◆ Capacitor modifies the amplitude of the signal by $1/\omega C$
- ◆ Capacitor shifts the phase by $-\pi/2$

Understanding the influence of Phase

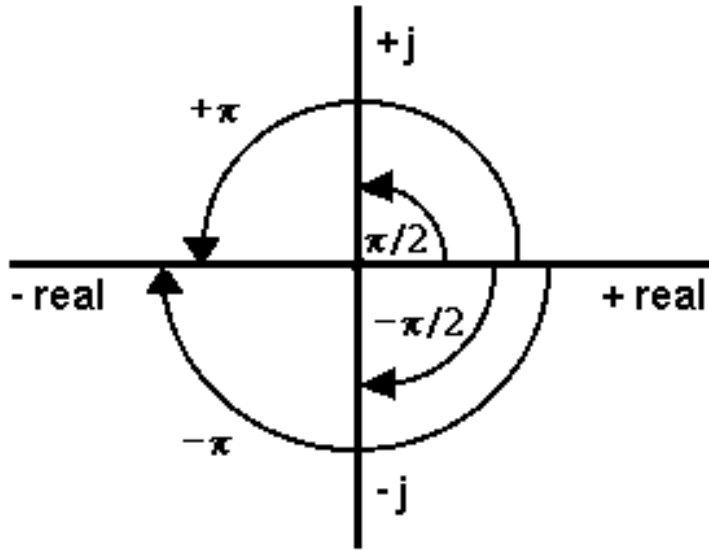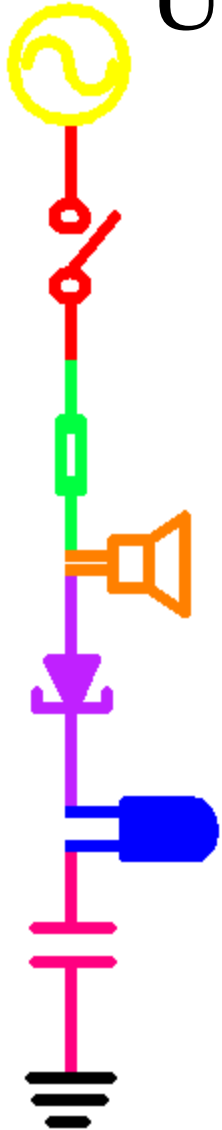

$$\angle \vec{V} = \tan^{-1} \left(\frac{y}{x} \right)$$

+ real: if $y = 0$ and $x > 0$

$$\text{then } \angle \vec{V} = \tan^{-1} \left(\frac{0}{x^+} \right) = 0$$

+ j: if $x = 0$ and $y > 0$


$$\text{then } \angle \vec{V} = \tan^{-1} \left(\frac{y^+}{0} \right) = \frac{\pi}{2} = 90^\circ$$

- j: if $x = 0$ and $y < 0$

$$\text{then } \angle \vec{V} = \tan^{-1} \left(\frac{y^-}{0} \right) = -\frac{\pi}{2} = -90^\circ$$

- real: if $y = 0$ and $x < 0$
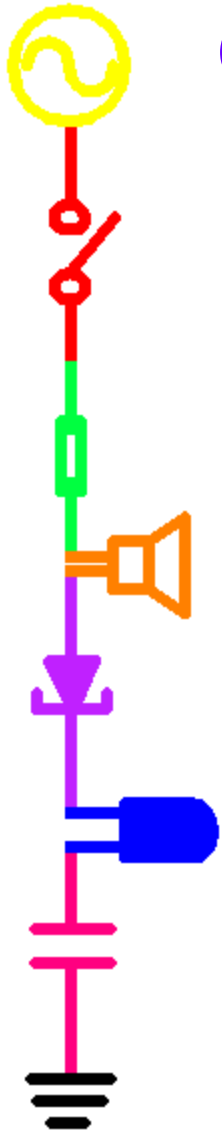
$$\text{then } \angle \vec{V} = \tan^{-1} \left(\frac{0}{x^-} \right) = \pi \text{ (or } -\pi) \\ = \pm 180^\circ$$






Complex Impedance $\vec{V} = \vec{I}Z$


- ◆ Z defines the influence of a component on the amplitude and phase of a circuit
 - Resistors: $Z_R = R$
 - change the amplitude by R
 - Capacitors: $Z_C = 1/j\omega C$
 - change the amplitude by $1/\omega C$
 - shift the phase -90 ($1/j = -j$)
 - Inductors: $Z_L = j\omega L$
 - change the amplitude by ωL
 - shift the phase $+90$ (j)

AC Sweeps


AC Source sweeps from 1Hz to 10K Hz

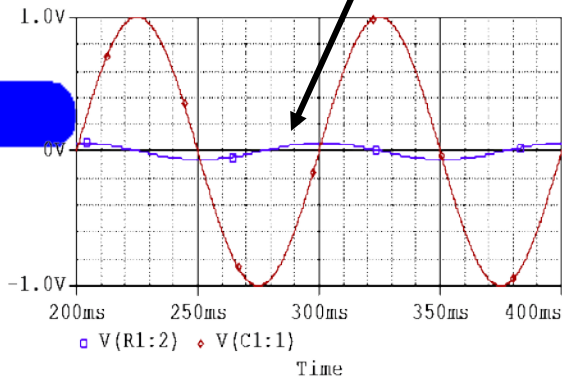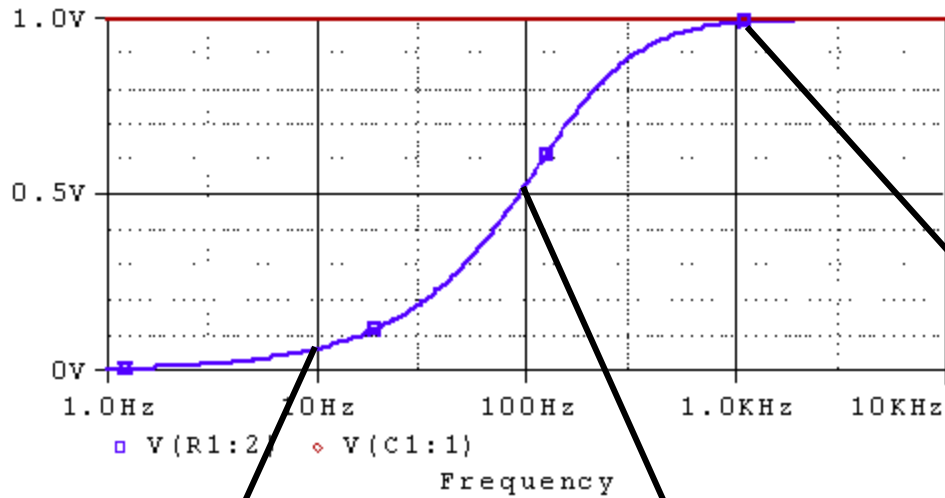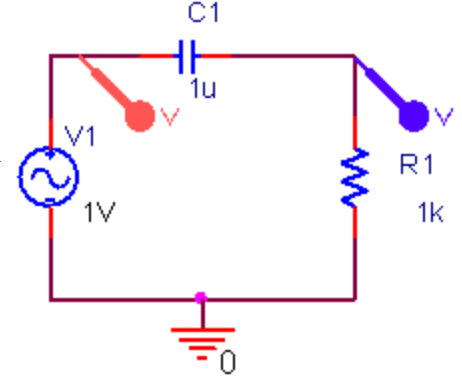


Transient at 10 Hz

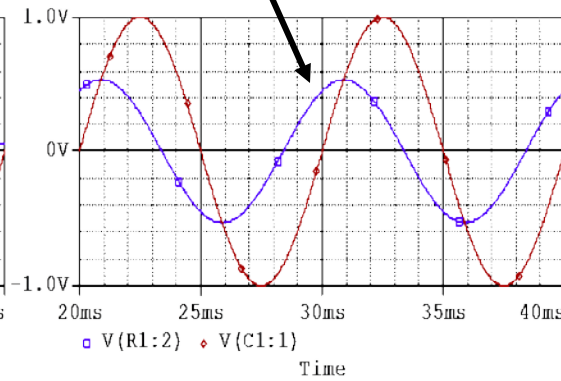

Transient at 100 Hz

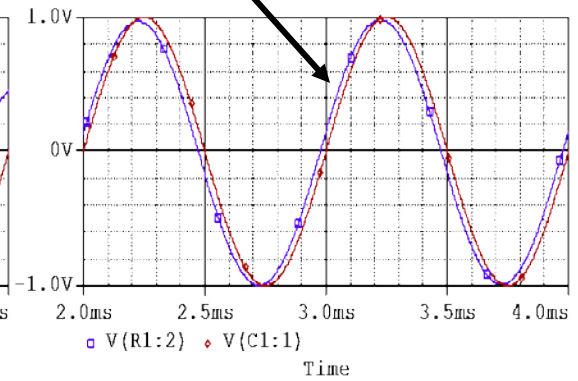


Transient at 1k Hz

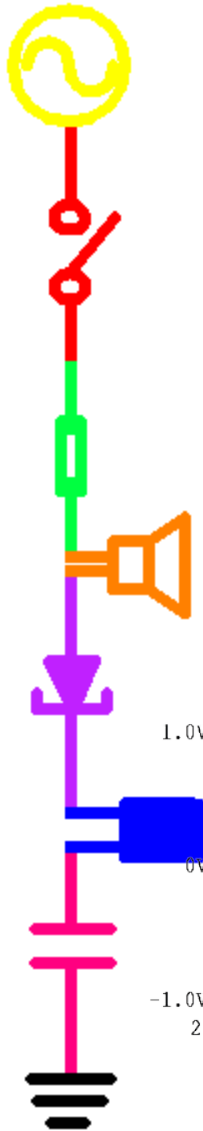



Notes on Logarithmic Scales

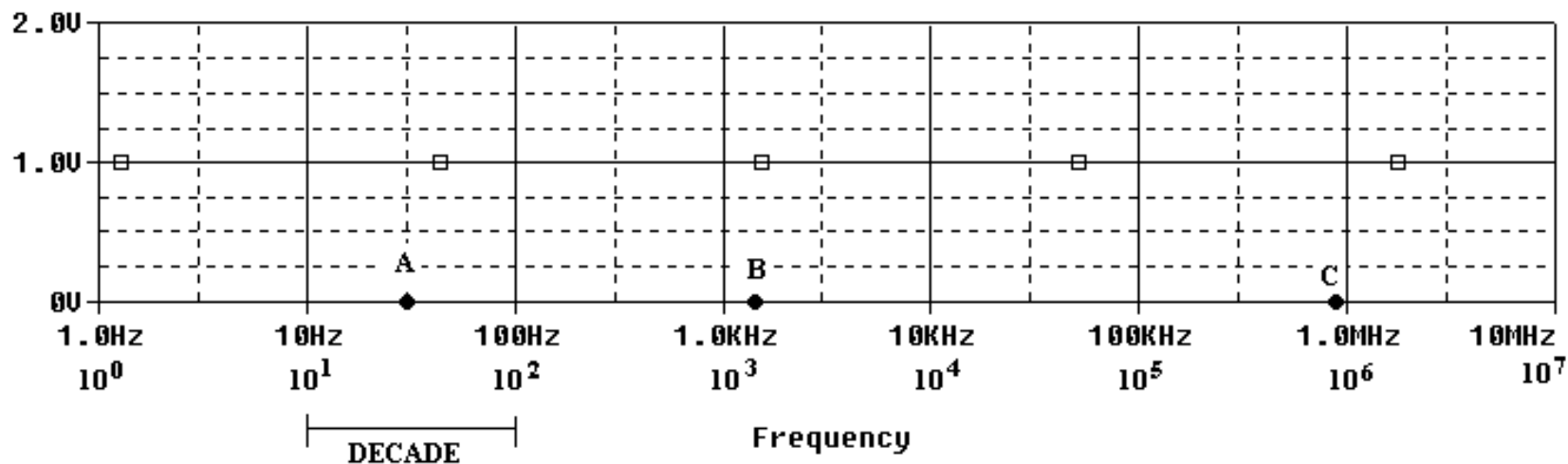

$$\text{Frequency} = 10^{[\text{decade}] \cdot [\% \text{ across decade}]}$$

$$\text{A: Frequency} = 10^{1.5} = 32 \text{ Hz}$$

$$\text{B: Frequency} = 10^{3.2} = 1600 \text{ Hz}$$

$$\text{C: Frequency} = 10^{5.9} = 790,000 \text{ Hz}$$

$$[\text{decade}] \cdot [\% \text{ across decade}] = \text{LOG} [\text{Frequency}]$$

$$\text{A: location} = \text{LOG}(32) = 1.5 \quad \text{decade 1 - 50\%}$$

$$\text{B: location} = \text{LOG}(1600) = 3.2 \quad \text{decade 3 - 20\%}$$

$$\text{C: location} = \text{LOG}(790000) = 5.9 \quad \text{decade 5 - 90\%}$$






Capture/PSpice Notes

- ◆ Showing the real and imaginary part of the signal
 - in Capture: PSpice->Markers->Advanced
 - ->Real Part of Voltage
 - ->Imaginary Part of Voltage
 - in PSpice: Add Trace
 - real part: R()
 - imaginary part: IMG()

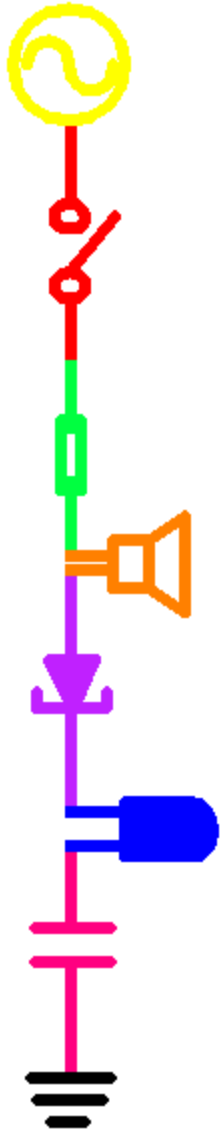- ◆ Showing the phase of the signal
 - in Capture:
 - PSpice->Markers->Advanced->Phase of Voltage
 - in PSpice: Add Trace
 - phase: P()



Part B


- ◆ Phasors
- ◆ Complex Transfer Functions
- ◆ Filters


Definition of a Phasor

if $V(t) = A \cos(\omega t + \phi)$, then let

$$\vec{V} = A \cos \phi + jA \sin \phi$$

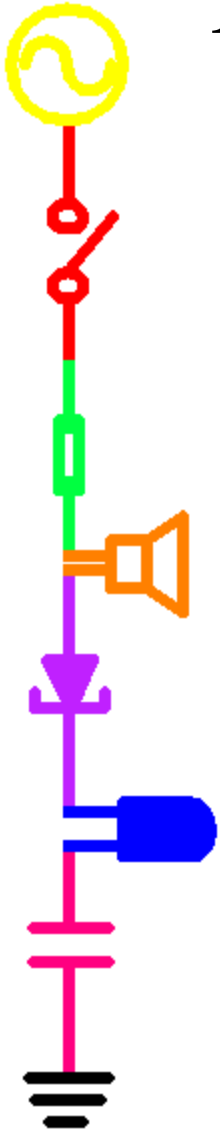
- ◆ The real part is our signal.
- ◆ The two parts allow us to determine the influence of the phase and amplitude changes mathematically.
- ◆ After we manipulate the numbers, we discard the imaginary part.



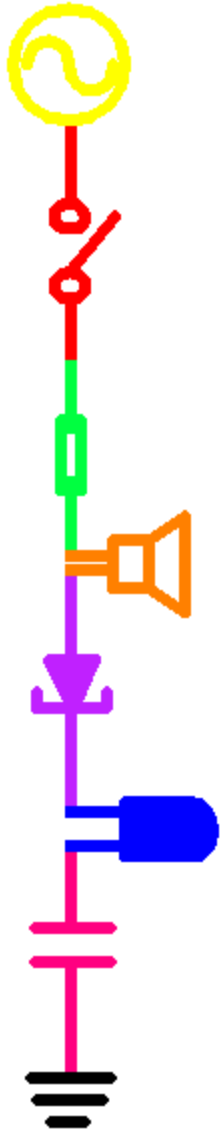

Phasor References

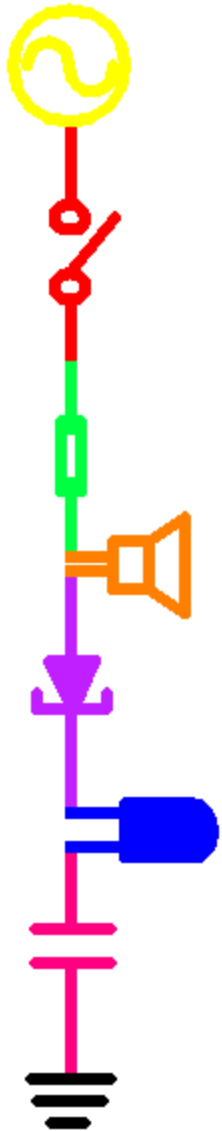- ◆ http://ccrma-www.stanford.edu/~jos/filters/Phasor_Notation.html
- ◆ <http://www.ligo.caltech.edu/~vsanni/ph3/ExpACCCircuits/ACCCircuits.pdf>
- ◆ <http://ptolemy.eecs.berkeley.edu/eecs20/berkeley/phasors/demo/phasors.html>




Phasor Applet



Rotating Phasors

The diagram shows a circular path of dots representing a phasor. A yellow vector rotates counter-clockwise from the positive x-axis. A red vector is shown at the positive x-axis. Below the circle is a graph of a yellow sine wave oscillating between approximately -1 and 1 on the vertical axis.

Clear	One	Pos / Neg	Two	Beats
Delta	Sawtooth	Square	Triangle	
On	Frequency	Amplitude	Phase	
	Hz	Raw	Deg	
<input checked="" type="checkbox"/>	0.25	1	0	
<input type="checkbox"/>				
<input type="checkbox"/>				
<input type="checkbox"/>				
<input type="checkbox"/>				
Apply Values				
Slower	TIME (x 0.00)		Faster	
<input type="button" value="◀"/> <input type="button" value="▶"/>				
Zoom In	GRAPH (7.00 sec)		Zoom Out	
<input type="button" value="◀"/> <input type="button" value="▶"/>				

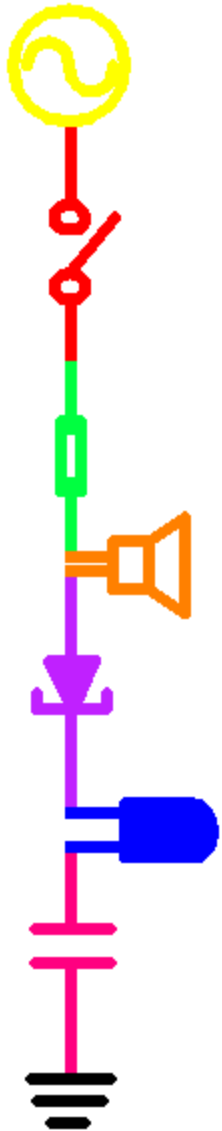

Adding Phasors & Other Applets

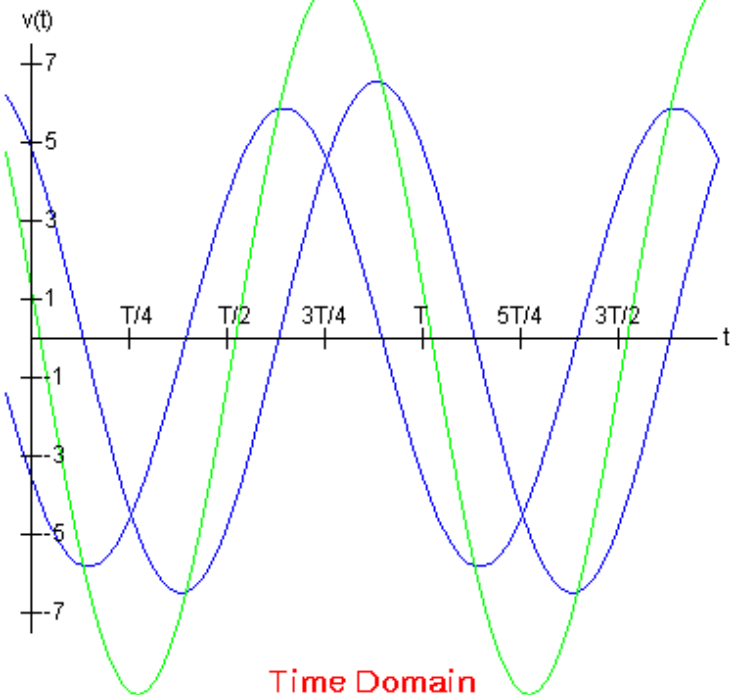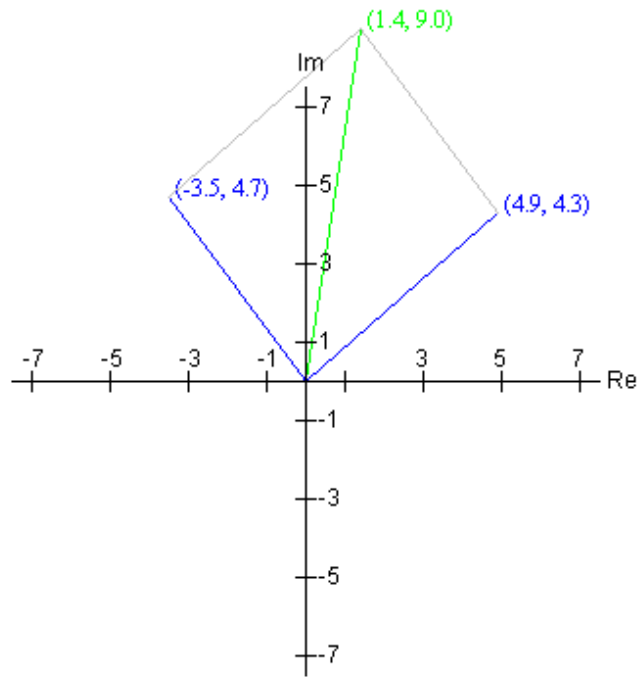




Magnitude and Phase

$$\vec{V} \equiv A \cos \phi + j A \sin \phi = x + jy$$

$$|\vec{V}| \equiv \sqrt{x^2 + y^2} = A \quad \text{magnitude of } \vec{V}$$

$$\angle \vec{V} = \tan^{-1} \left(\frac{y}{x} \right) = \phi \quad \text{phase of } \vec{V}$$

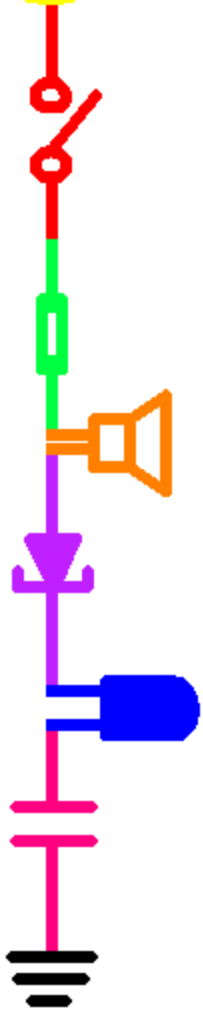- ◆ Phasors have a magnitude and a phase derived from polar coordinates rules.



Euler's Formula

$$e^{j\theta} = \cos \theta + j \sin \theta$$


if $z = x + jy = r \cos \theta + jr \sin \theta = re^{j\theta}$

then $z_3 = \frac{z_1}{z_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)}$

therefore, $r_3 = \frac{r_1}{r_2}$ and $\theta_3 = \theta_1 - \theta_2$

and $z_4 = z_1 \cdot z_2 = r_1 e^{j\theta_1} \cdot r_2 e^{j\theta_2} = r_1 \cdot r_2 e^{j(\theta_1 + \theta_2)}$

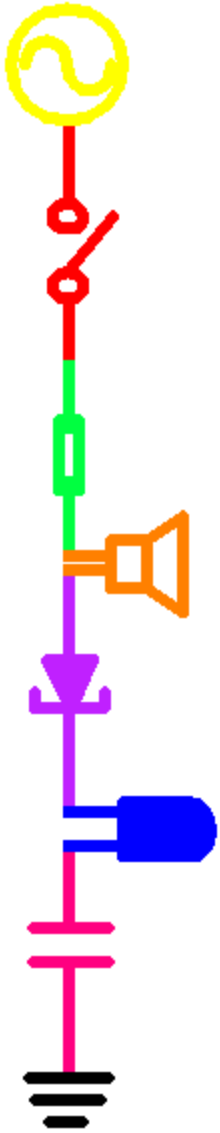therefore, $r_4 = r_1 \cdot r_2$ and $\theta_4 = \theta_1 + \theta_2$






Manipulating Phasors (1)

$$\vec{V} = A \cos(\omega t + \phi) + j \sin(\omega t + \phi) = A e^{j(\omega t + \phi)}$$

$$\vec{X}_3 = \frac{\vec{V}_1}{\vec{V}_2} = \frac{A_1 e^{j(\omega t + \phi_1)}}{A_2 e^{j(\omega t + \phi_2)}} = \frac{A_1}{A_2} \frac{e^{j\omega t} e^{j\phi_1}}{e^{j\omega t} e^{j\phi_2}} = \frac{A_1}{A_2} e^{j(\phi_1 - \phi_2)}$$

therefore, $\boxed{|\vec{X}_3| = \frac{A_1}{A_2}}$ and $\boxed{\angle \vec{X}_3 = \phi_1 - \phi_2}$

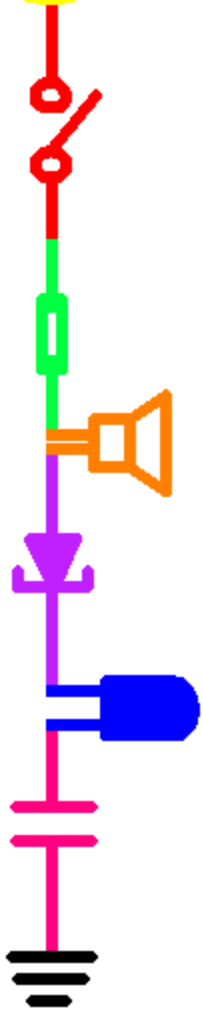- ◆ Note ωt is eliminated by the ratio
 - This gives the phase *change* between signal 1 and signal 2






Manipulating Phasors (2)

$$\vec{V}_1 = x_1 + jy_1 \quad \vec{V}_2 = x_2 + jy_2$$

$$\vec{V}_3 = x_3 + jy_3$$

$$\left| \vec{X}_3 \right| = \frac{\left| \vec{V}_1 \right|}{\left| \vec{V}_2 \right|} = \frac{\sqrt{x_1^2 + y_1^2}}{\sqrt{x_2^2 + y_2^2}}$$

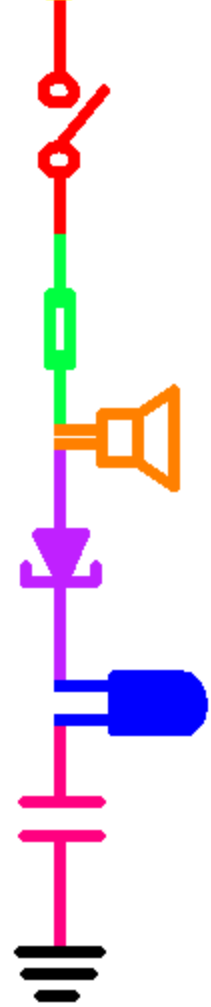
$$\angle \vec{X}_3 = \angle \vec{V}_1 - \angle \vec{V}_2 = \tan^{-1} \left(\frac{y_1}{x_1} \right) - \tan^{-1} \left(\frac{y_2}{x_2} \right)$$






Complex Transfer Functions
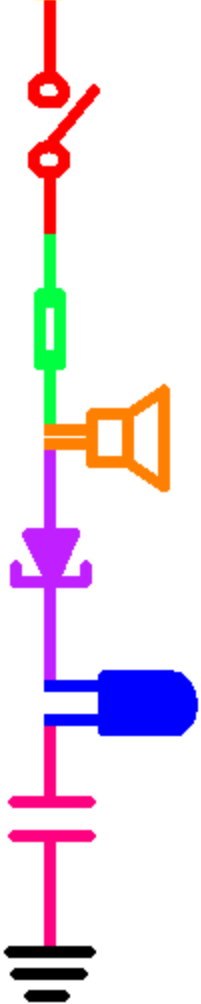
$$\vec{H}(j\omega) \equiv \frac{\vec{V}_{out}(j\omega)}{\vec{V}_{in}(j\omega)}$$




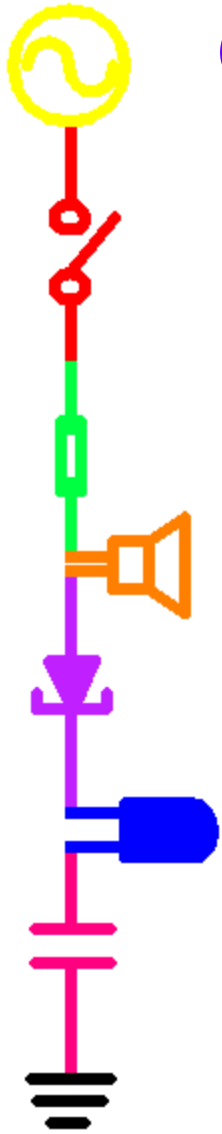- ◆ If we use phasors, we can define H for all circuits in this way.
- ◆ If we use complex impedances, we can combine all components the way we combine resistors.
- ◆ H and V are now functions of j and ω




Complex Impedance $\vec{V} = \vec{I}Z$

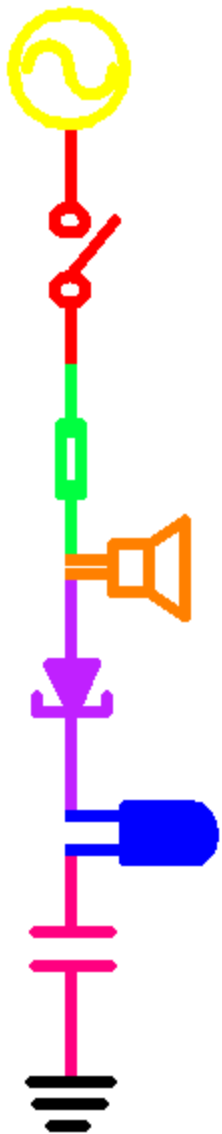- ◆ Z defines the influence of a component on the amplitude and phase of a circuit
 - Resistors: $Z_R = R$
 - Capacitors: $Z_C = 1/j\omega C$
 - Inductors: $Z_L = j\omega L$
- ◆ We can use the rules for resistors to analyze circuits with capacitors and inductors if we use phasors and complex impedance.



Simple Example

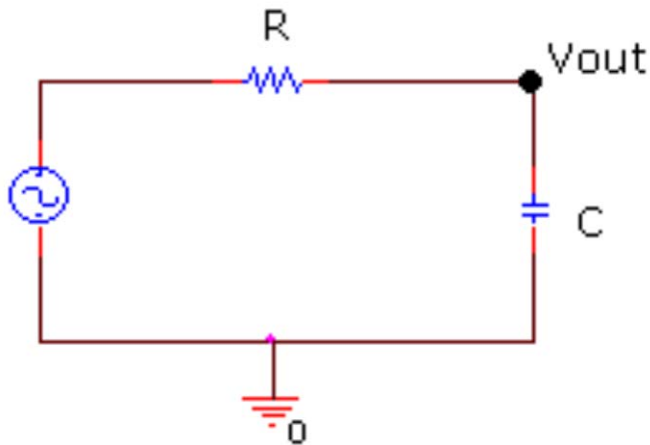

$$Z_R = R$$

$$Z_C = \frac{1}{j\omega C}$$

$$\vec{H}(j\omega) = \frac{\vec{V}_{out}(j\omega)}{\vec{V}_{in}(j\omega)} = \frac{Z_C \vec{I}}{(Z_R + Z_C) \vec{I}} = \frac{Z_C}{(Z_R + Z_C)}$$

$$\vec{H}(j\omega) = \frac{1}{R + \frac{1}{j\omega C}} \cdot \frac{j\omega C}{j\omega C}$$

$$\vec{H}(j\omega) = \frac{1}{j\omega RC + 1}$$



Simple Example (continued)

$$\bar{H}(j\omega) = \frac{1}{j\omega RC + 1}$$

$$|H(j\omega)| = \frac{|1 + j0|}{|1 + j\omega RC|} = \frac{\sqrt{1^2 + 0^2}}{\sqrt{1^2 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(j\omega) = \angle(1 + j0) - \angle(1 + j\omega RC)$$


$$\angle H(j\omega) = \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left(\frac{\omega RC}{1}\right) = -\tan^{-1}(\omega RC)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\angle H(j\omega) = -\tan^{-1}(\omega RC)$$



High and Low Pass Filters

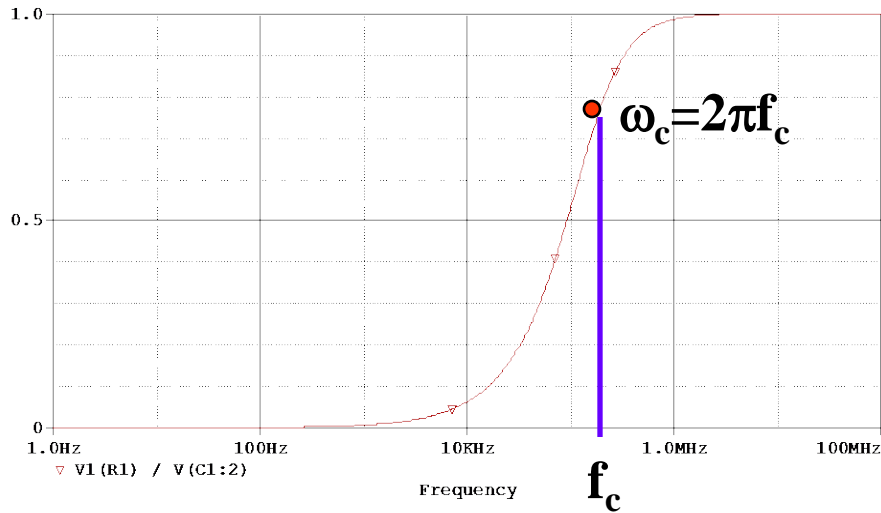


High Pass Filter

$$H = 0 \text{ at } \omega \rightarrow 0$$

$$H = 1 \text{ at } \omega \rightarrow \infty$$

$$H = 0.707 \text{ at } \omega_c$$

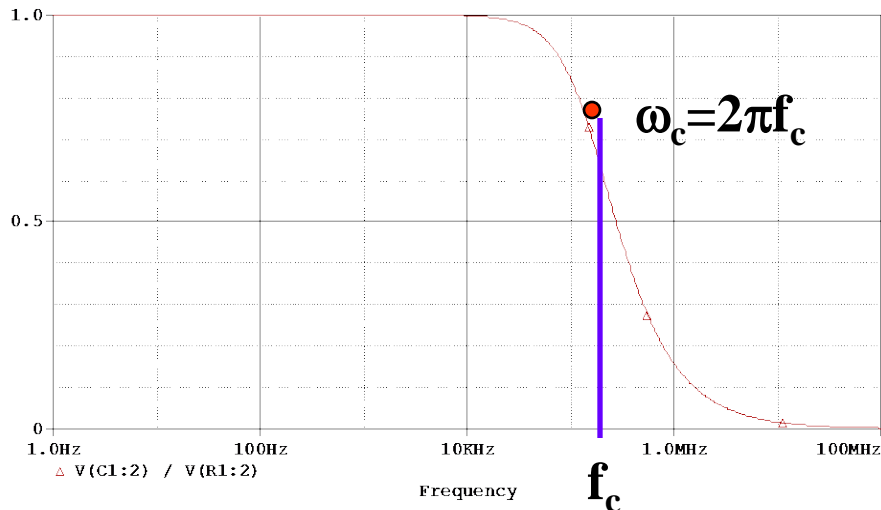

Low Pass Filter

$$H = 1 \text{ at } \omega \rightarrow 0$$

$$H = 0 \text{ at } \omega \rightarrow \infty$$



$$H = 0.707 \text{ at } \omega_c$$



Corner Frequency

- ◆ The corner frequency of an RC or RL circuit tells us where it transitions from low to high or visa versa.
- ◆ We define it as the place where $|H(j\omega_c)| = \frac{1}{\sqrt{2}}$
- ◆ For RC circuits: $\omega_c = \frac{1}{RC}$
- ◆ For RL circuits: $\omega_c = \frac{R}{L}$

Corner Frequency of our example

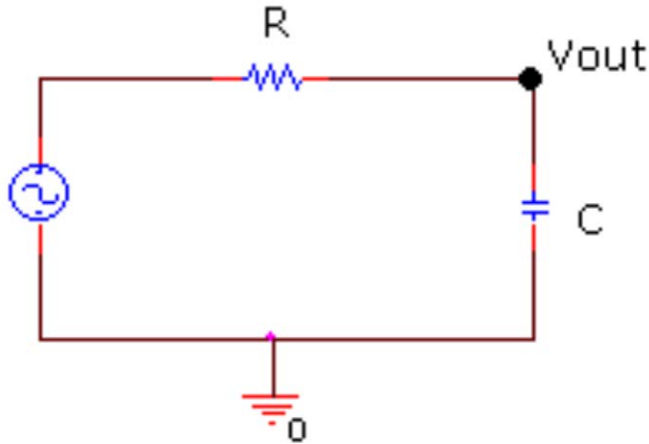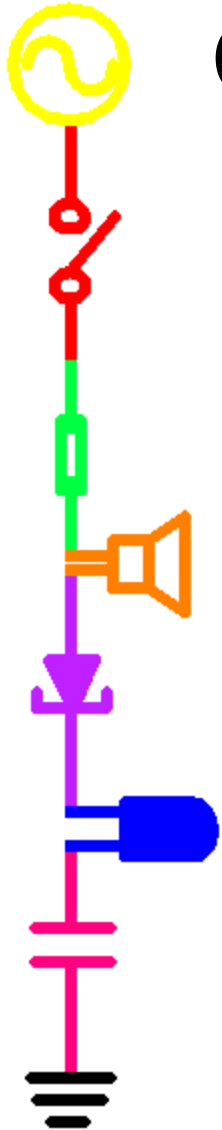

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{1 + (\omega RC)^2} = \frac{1}{2}$$

$$2 = 1 + (\omega RC)^2 \quad \frac{1}{(RC)^2} = \omega^2$$

$$\omega_c = \frac{1}{RC}$$



$H(j\omega)$, ω_c , and filters

- ◆ We can use the transfer function, $H(j\omega)$, and the corner frequency, ω_c , to easily determine the characteristics of a filter.
- ◆ If we consider the behavior of the transfer function as ω approaches 0 and infinity and look for when H nears 0 and 1, we can identify high and low pass filters.
- ◆ The corner frequency gives us the point where the filter changes:

$$f_c = \frac{\omega_c}{2\pi}$$



Taking limits


$$H(j\omega) = \frac{a_2\omega^2 + a_1\omega + a_0}{b_2\omega^2 + b_1\omega + b_0}$$

- ◆ At low frequencies, (ie. $\omega=10^{-3}$), lowest power of ω dominates

$$H(j\omega) = \frac{a_2 10^{-6} + a_1 10^{-3} + a_0 10^0}{b_2 10^{-6} + b_1 10^{-3} + b_0 10^0} \approx \frac{a_0}{b_0}$$

- ◆ At high frequencies (ie. $\omega = 10^{+3}$), highest power of ω dominates
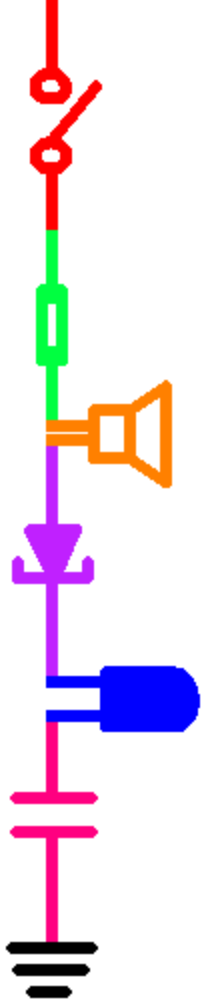
$$H(j\omega) = \frac{a_2 10^{+6} + a_1 10^{+3} + a_0 10^0}{b_2 10^{+6} + b_1 10^{+3} + b_0 10^0} \approx \frac{a_2}{b_2}$$





Taking limits -- Example


$$H(j\omega) = \frac{9\omega^2 + 15\omega}{3\omega^2 + 2\omega + 5}$$

- ◆ At low frequencies, (lowest power)



$$H_{LO}(j\omega) = \frac{15\omega}{5} = 3\omega$$

- ◆ At high frequencies, (highest power)
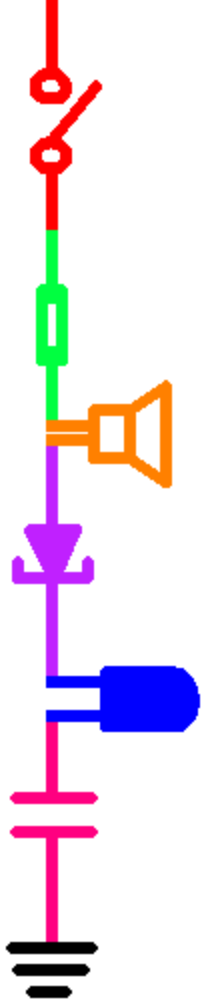
$$H_{HI}(j\omega) = \frac{9\omega^2}{3\omega^2} = 3$$



Our example at low frequencies

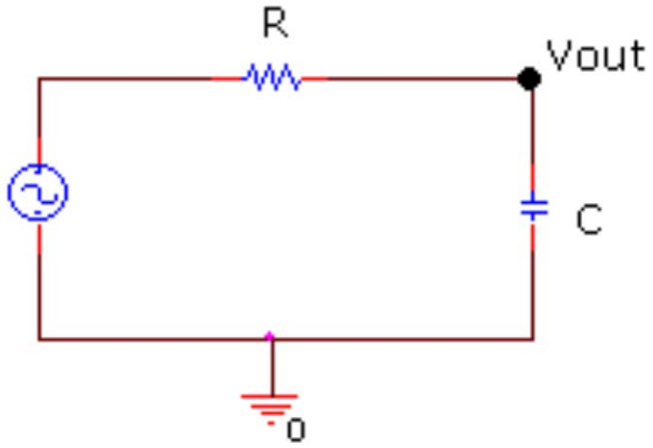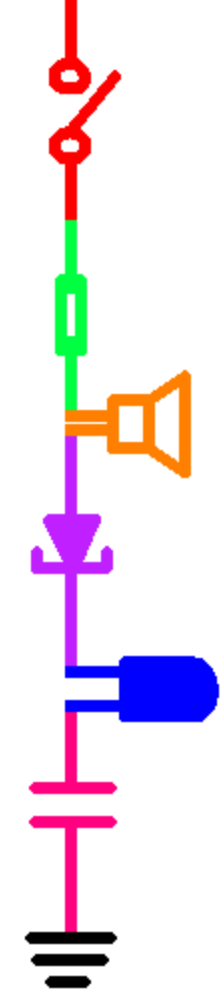



$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$H_{LOW}(j\omega) = \frac{1}{1 + 0} = 1$$

$$|H_{LOW}(j\omega)|_{as\ \omega \rightarrow 0} = |1| = 1$$

$$\angle H_{LOW}(j\omega) = \tan^{-1}\left(\frac{0}{1}\right) = 0 \text{ (on } +x \text{ axis)}$$

Our example at high frequencies

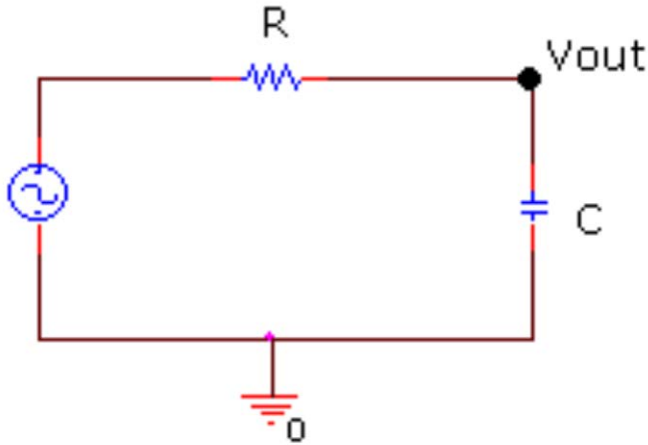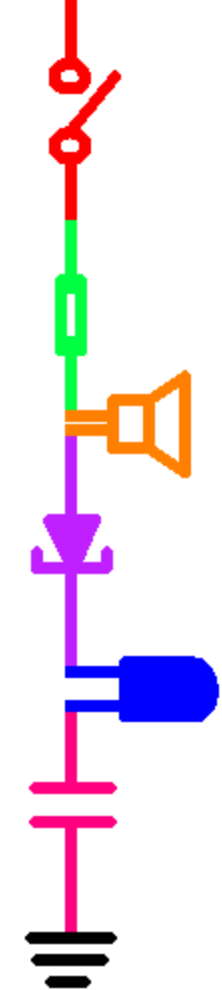



$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$H_{HIGH}(j\omega) = \frac{1}{j\omega RC}$$

$$|H_{HIGH}(j\omega)| \text{ as } \omega \rightarrow \infty = \left| \frac{1}{j\omega RC} \right| = \frac{1}{\infty} = 0$$


$$\angle H_{HIGH}(j\omega) = \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left(\frac{\omega RC}{0}\right) = 0 - \frac{\pi}{2} = -\frac{\pi}{2}$$

Our example is a low pass filter

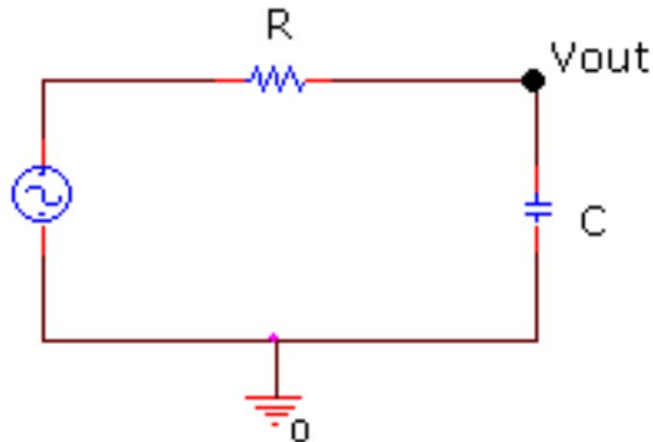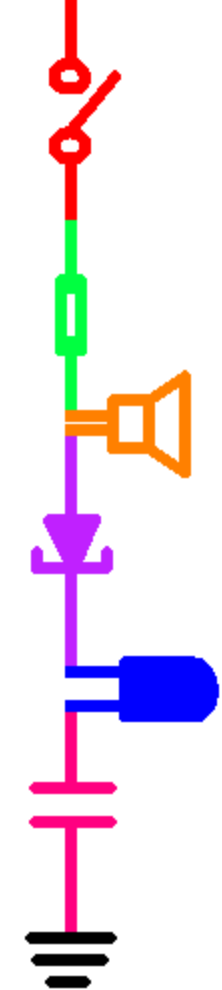

$$|H_{LOW}| = 1 \quad |H_{HIGH}| = 0$$


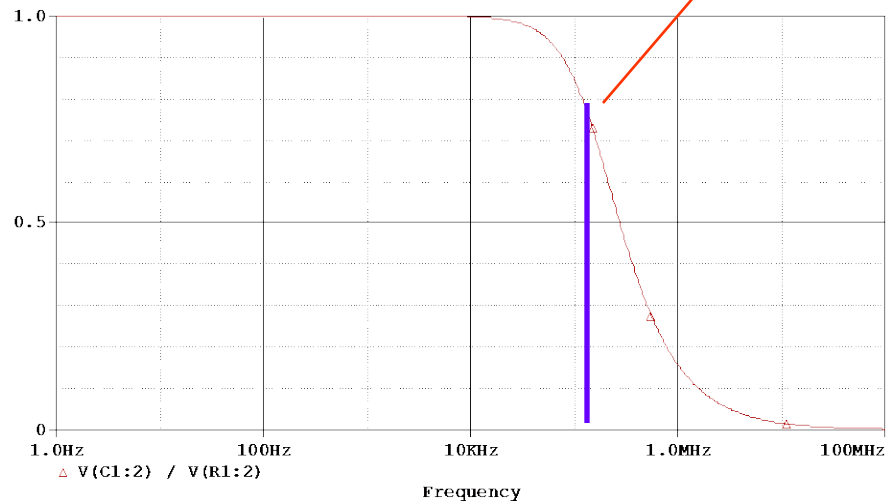
$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi RC}$$



What about the phase?



Our example has a phase shift

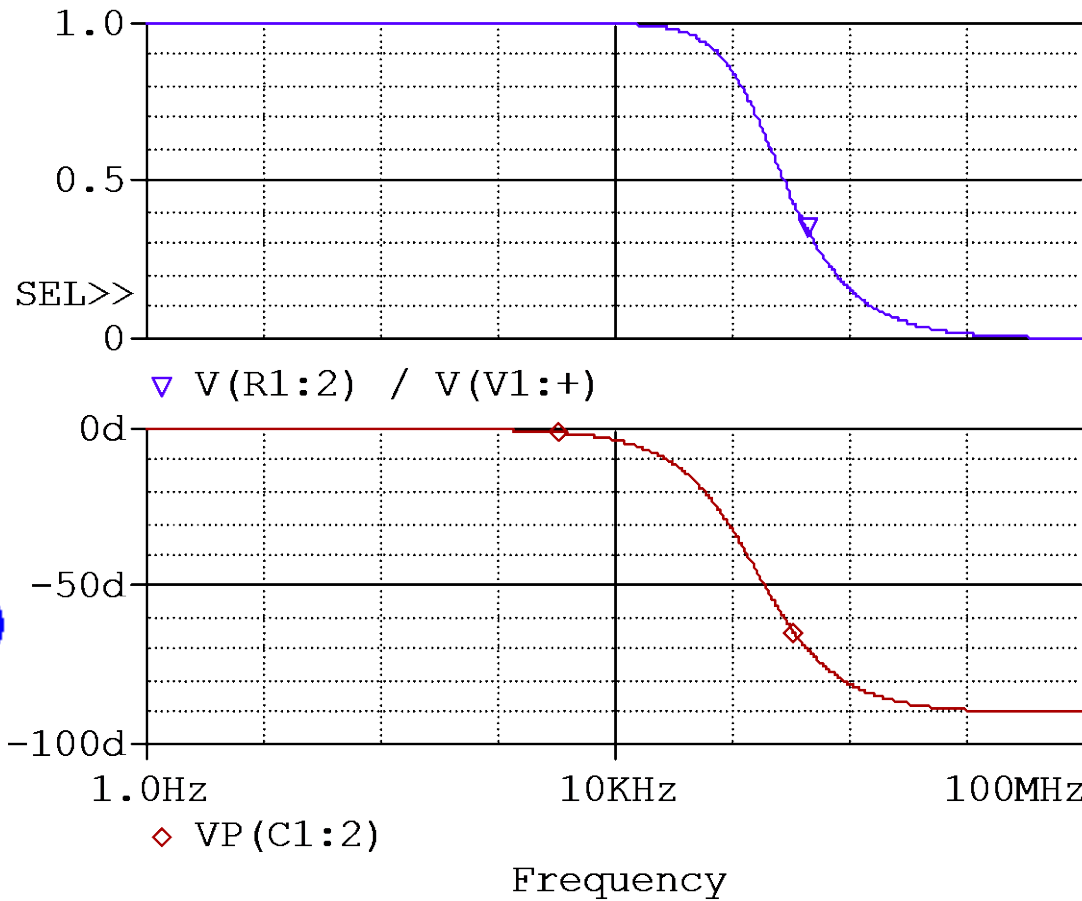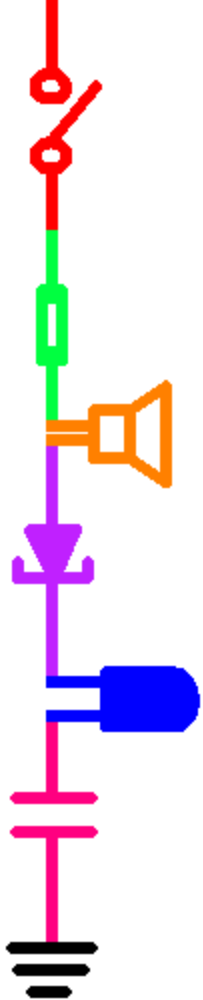


$$|H_{LOW}| = 1$$

$$|H_{HIGH}| = 0$$


$$\angle H_{LOW}(j\omega) = 0$$

$$\angle H_{HIGH}(j\omega) = -90^\circ$$

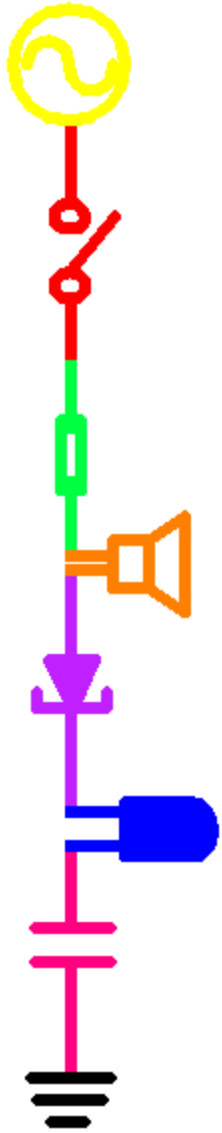

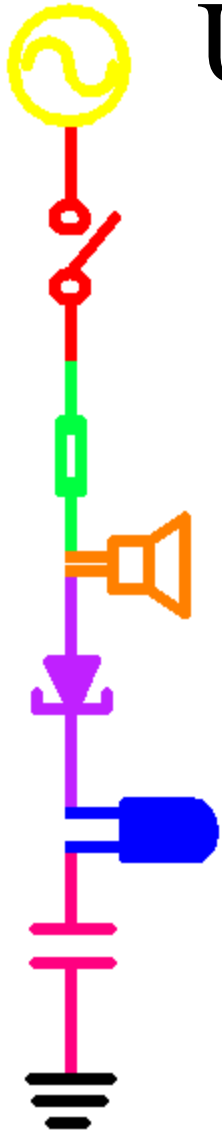Part C

- ◆ Using Transfer Functions
- ◆ Capacitor Impedance Proof
- ◆ More Filters
- ◆ Transfer Functions of RLC Circuits



Using H to find V_{out}

$$H(j\omega) = \frac{\vec{V}_{out}}{\vec{V}_{in}} = \frac{A_{out} e^{j\phi_{out}} e^{j\omega t}}{A_{in} e^{j\phi_{in}} e^{j\omega t}} = \frac{A_{out} e^{j\phi_{out}}}{A_{in} e^{j\phi_{in}}}$$



$$A_{out} e^{j\phi_{out}} = H(j\omega) A_{in} e^{j\phi_{in}}$$

$$A_{out} e^{j\phi_{out}} = |H(j\omega)| e^{j\angle H(j\omega)} A_{in} e^{j\phi_{in}}$$

$$A_{out} = |H(j\omega)| A_{in}$$

$$\phi_{out} = \angle H(j\omega) + \phi_{in}$$

Simple Example (with numbers)

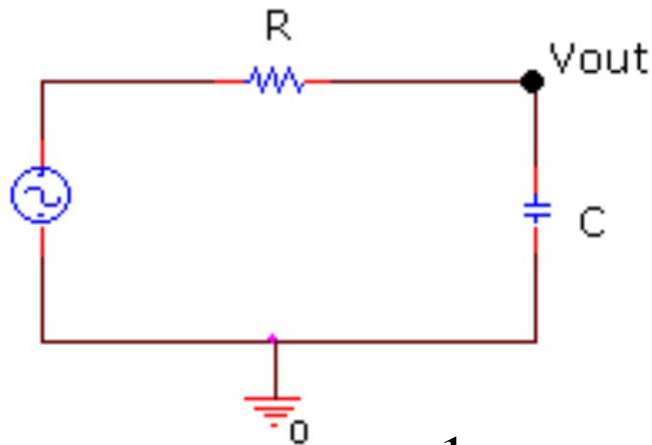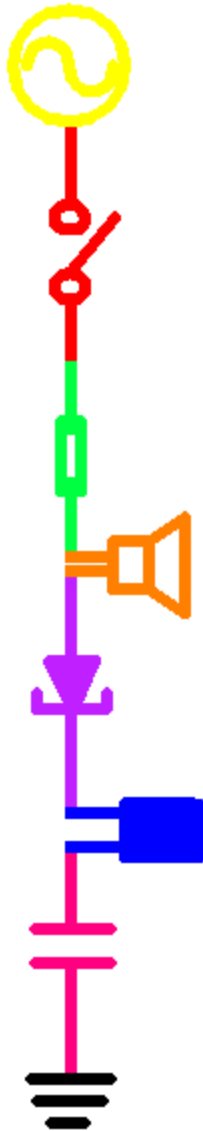

$$C = 1\mu F \quad R = 1k\Omega$$

$$V_{in}(t) = 2V \cos(2k\pi t + \frac{\pi}{4})$$

$$\bar{H}(j\omega) = \frac{1}{j\omega RC + 1} = \frac{1}{j2k\pi 1k1\mu + 1} = \frac{1}{2\pi j + 1}$$

$$|H(j\omega)| = \frac{1^2}{\sqrt{1 + (2\pi)^2}} = 0.157 \quad \angle H(j\omega) = 0 - \tan^{-1}\left(\frac{2\pi}{1}\right) = -1.41$$

$$V_{out}(t) = 0.157 * 2V \cos(2k\pi t + 0.785 - 1.41)$$

$$V_{out}(t) = 0.314V \cos(2k\pi t - 0.625)$$



Capacitor Impedance Proof

Prove: $Z_C = \frac{1}{j\omega C}$


$$I_C(t) = C \frac{dV_C(t)}{dt} \quad \text{and} \quad V_C(t) = A \cos(\omega t + \phi)$$

$$\vec{V}_C(j\omega) = A \cos(\omega t + \phi) + jA \sin(\omega t + \phi) = A e^{j(\omega t + \phi)}$$


$$\frac{d\vec{V}_C(j\omega)}{dt} = \frac{dA e^{j(\omega t + \phi)}}{dt} = Aj\omega e^{j(\omega t + \phi)} = j\omega \vec{V}_C(j\omega)$$

$$\frac{dV_C(t)}{dt} = \text{Re} \left\{ \frac{d\vec{V}_C(j\omega)}{dt} \right\} = j\omega A \cos(\omega t + \phi) = j\omega V_C(t)$$
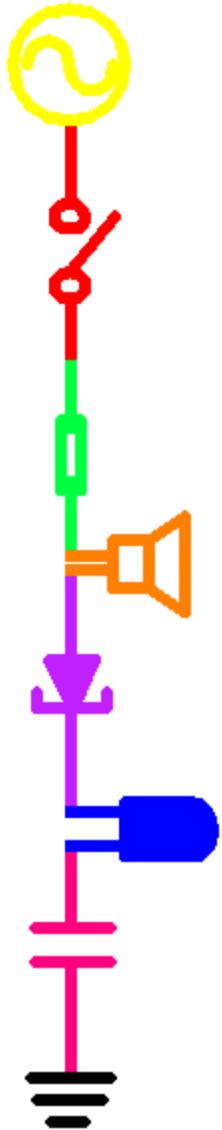
$$I_C(t) = C \frac{dV_C(t)}{dt} = Cj\omega V_C(t) \quad \boxed{V_C(t) = \frac{1}{j\omega C} I_C(t)}$$



Band Filters

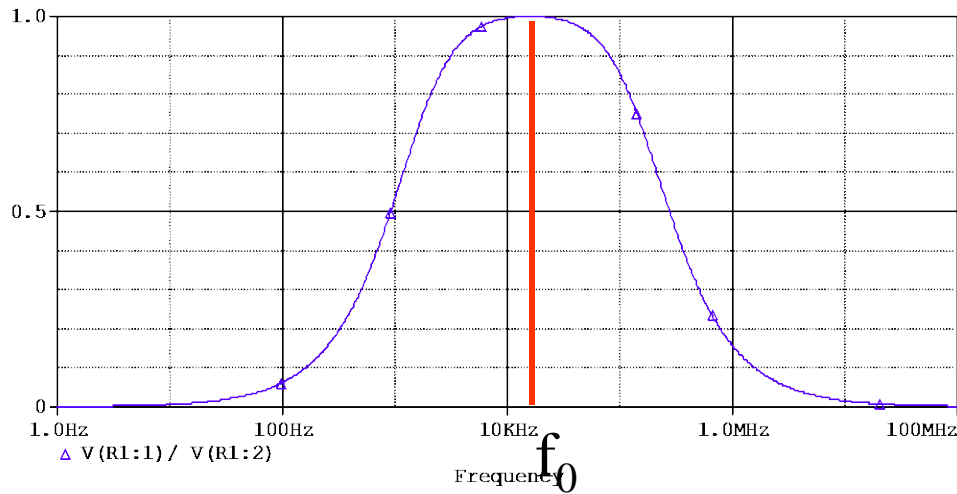


Band Pass Filter

$$H = 0 \text{ at } \omega \rightarrow 0$$

$$H = 0 \text{ at } \omega \rightarrow \infty$$
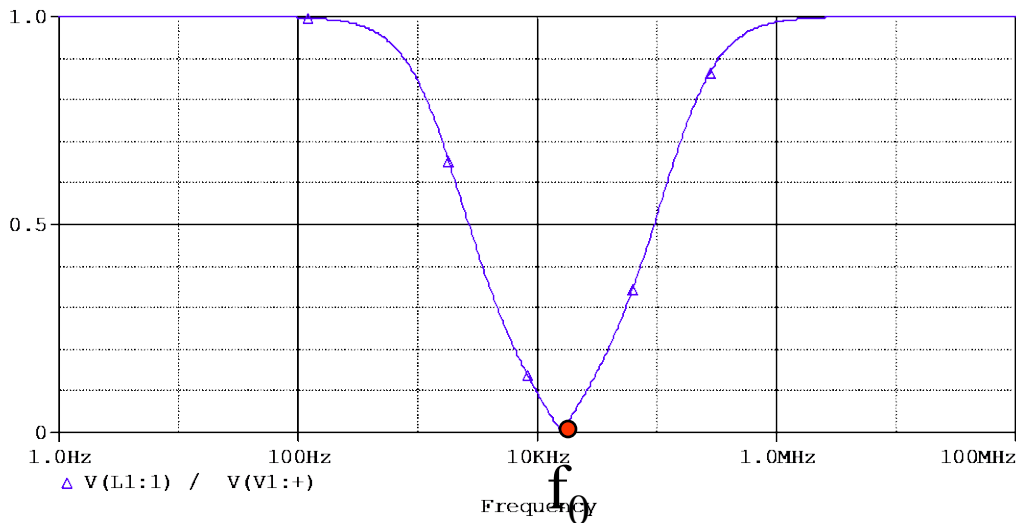
$$H = 1 \text{ at } \omega_0 = 2\pi f_0$$




Band Reject Filter

$$H = 1 \text{ at } \omega \rightarrow 0$$

$$H = 1 \text{ at } \omega \rightarrow \infty$$

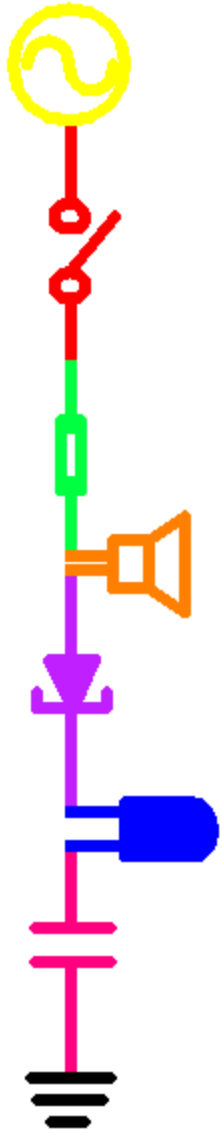
$$H = 0 \text{ at } \omega_0 = 2\pi f_0$$




Resonant Frequency

- ◆ The resonant frequency of an RLC circuit tells us where it reaches a maximum or minimum.
- ◆ This can define the center of the band (on a band filter) or the location of the transition (on a high or low pass filter).
- ◆ The equation for the resonant frequency of an RLC circuit is:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

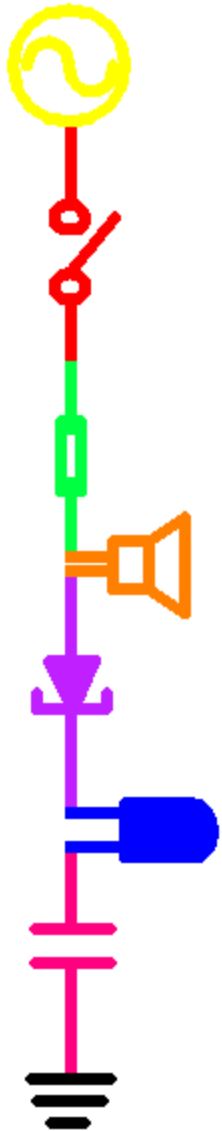

Another Example

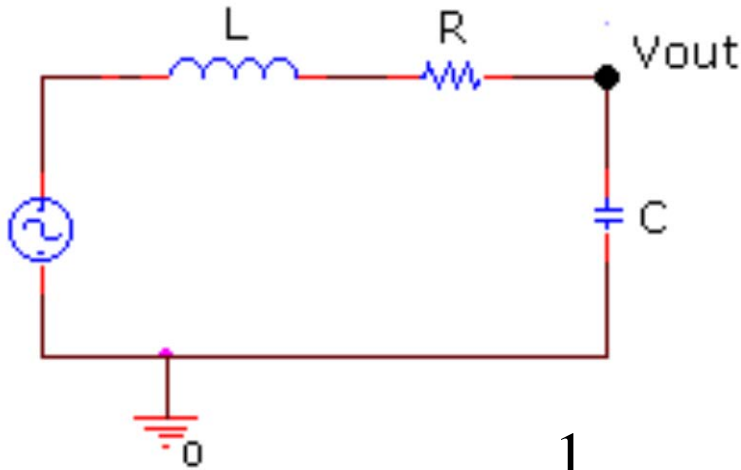


$$Z_R = R \quad Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C}$$

$$H(j\omega) = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + j^2\omega^2 LC + 1}$$
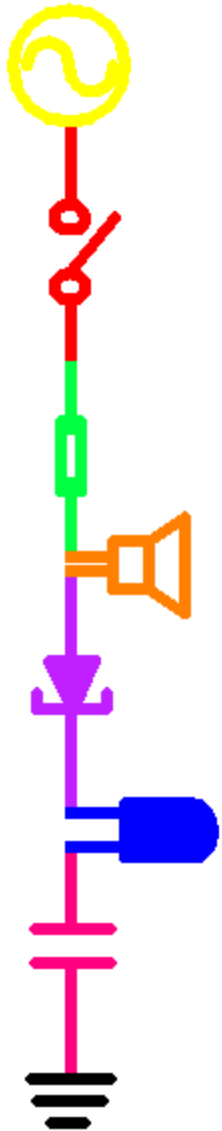
$$H(j\omega) = \frac{1}{(1 - \omega^2 LC) + j\omega RC}$$



At Very Low Frequencies

$$H_{LOW}(j\omega) = \frac{1}{1} = 1$$

$$|H_{LOW}(j\omega)|_{\omega \rightarrow 0} = 1$$

$$\angle H_{LOW}(j\omega) = 0$$


At Very High Frequencies

$$H_{HIGH}(j\omega) = \frac{1}{-\omega^2 LC}$$

$$|H_{HIGH}(j\omega)|_{\omega \rightarrow \infty} = \left| \frac{1}{\infty} \right| = 0$$

$$\angle H_{HIGH}(j\omega) = \pi \text{ or } -\pi$$

At the Resonant Frequency

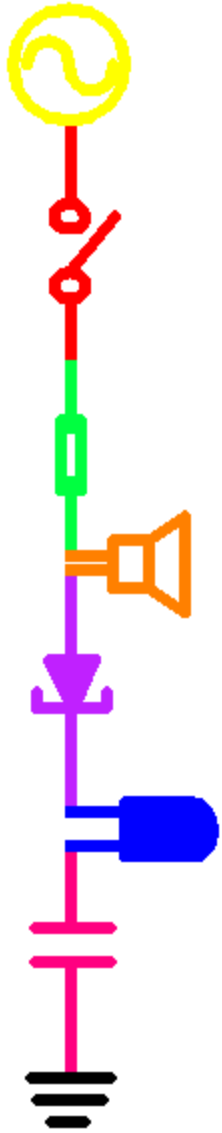

$$H(j\omega) = \frac{1}{(1 - \omega^2 LC) + j\omega RC} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$H(j\omega_0) = \frac{1}{(1 - \left(\frac{1}{\sqrt{LC}}\right)^2 LC) + j\left(\frac{1}{\sqrt{LC}}\right) RC} = \frac{1}{(1-1) + j\left(\frac{RC}{\sqrt{LC}}\right)}$$

$$H(j\omega_0) = -j \frac{\sqrt{LC}}{RC}$$

$$|H(j\omega_0)| = \frac{\sqrt{LC}}{RC}$$


$$\angle H(j\omega_0) = -\frac{\pi}{2}$$

if $L=1\text{mH}$, $C=0.1\mu\text{F}$ and $R=100\Omega$


$\omega_0=100\text{k rad/sec}$ $f_0=16\text{k Hz}$

$|H_0|=1$ $\angle H = -\frac{\pi}{2}$ radians

Our example is a low pass filter

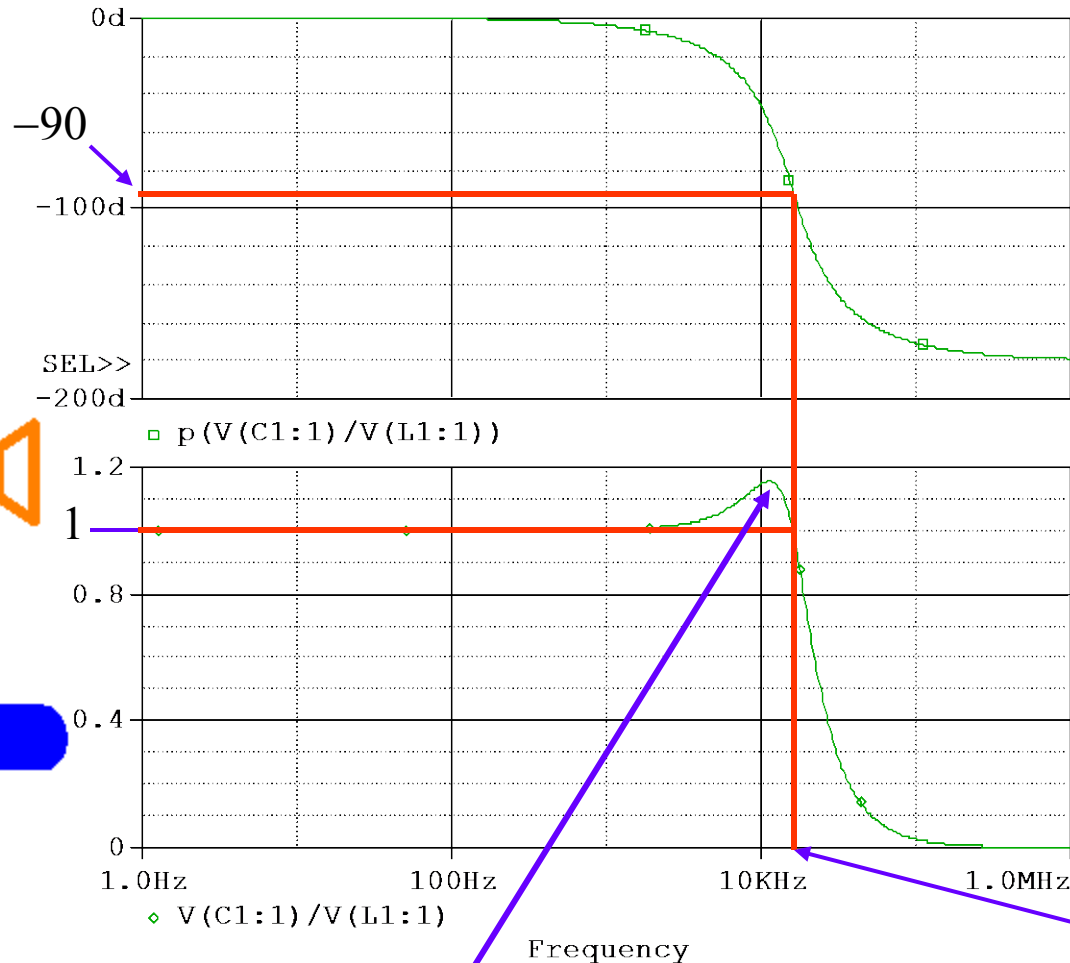


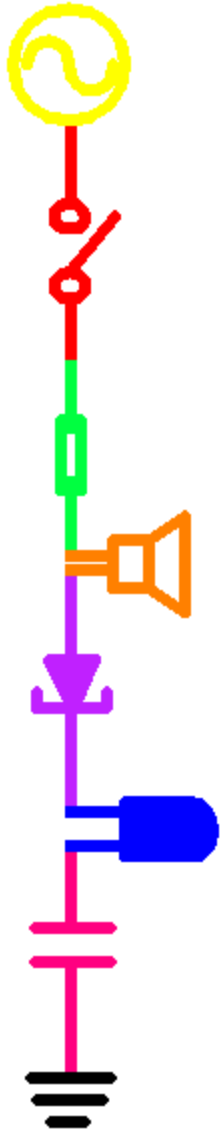Actual circuit resonance is only at the theoretical resonant frequency, f_0 , when there is no resistance.




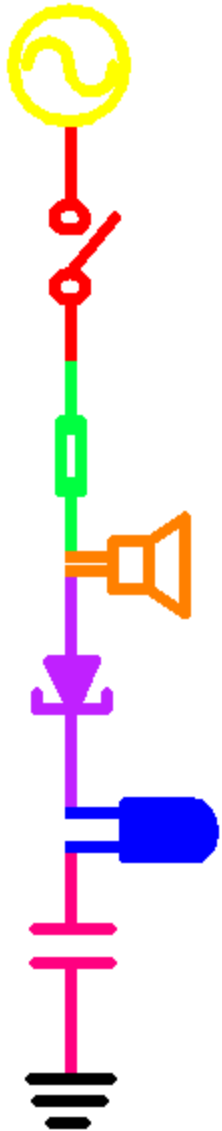Part D


- ◆ Equivalent Impedance
- ◆ Transfer Functions of More Complex Circuits




Equivalent Impedance

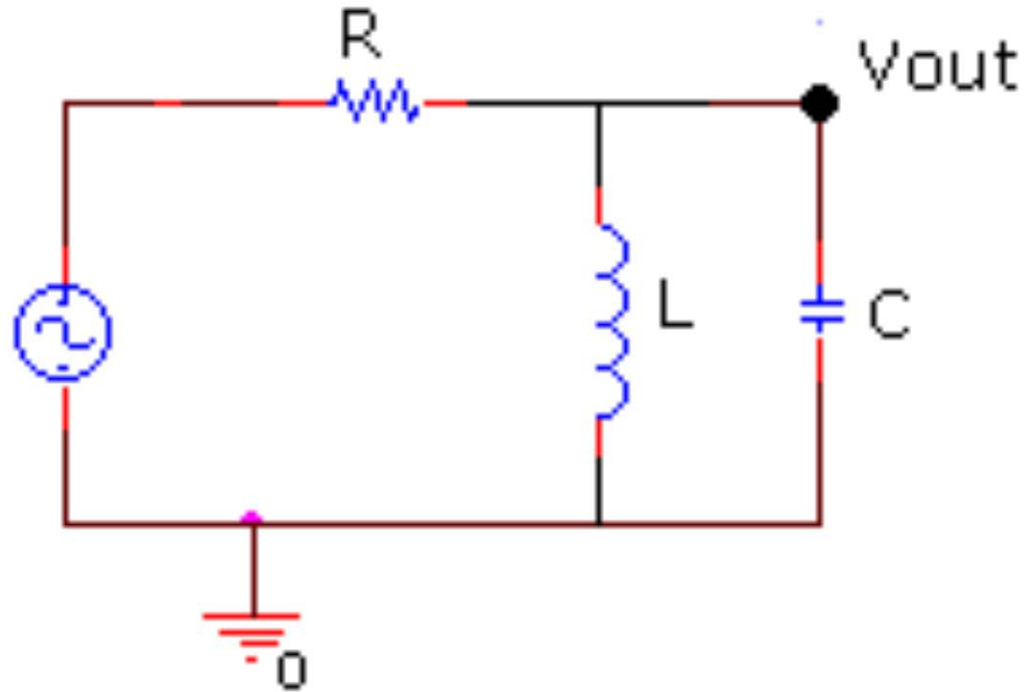

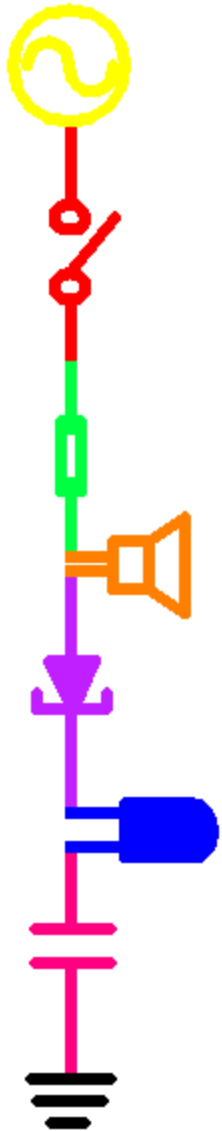
- ◆ Even though this filter has parallel components, we can still handle it.
- ◆ We can combine complex impedances like resistors to find the equivalent impedance of the components combined.



Equivalent Impedance

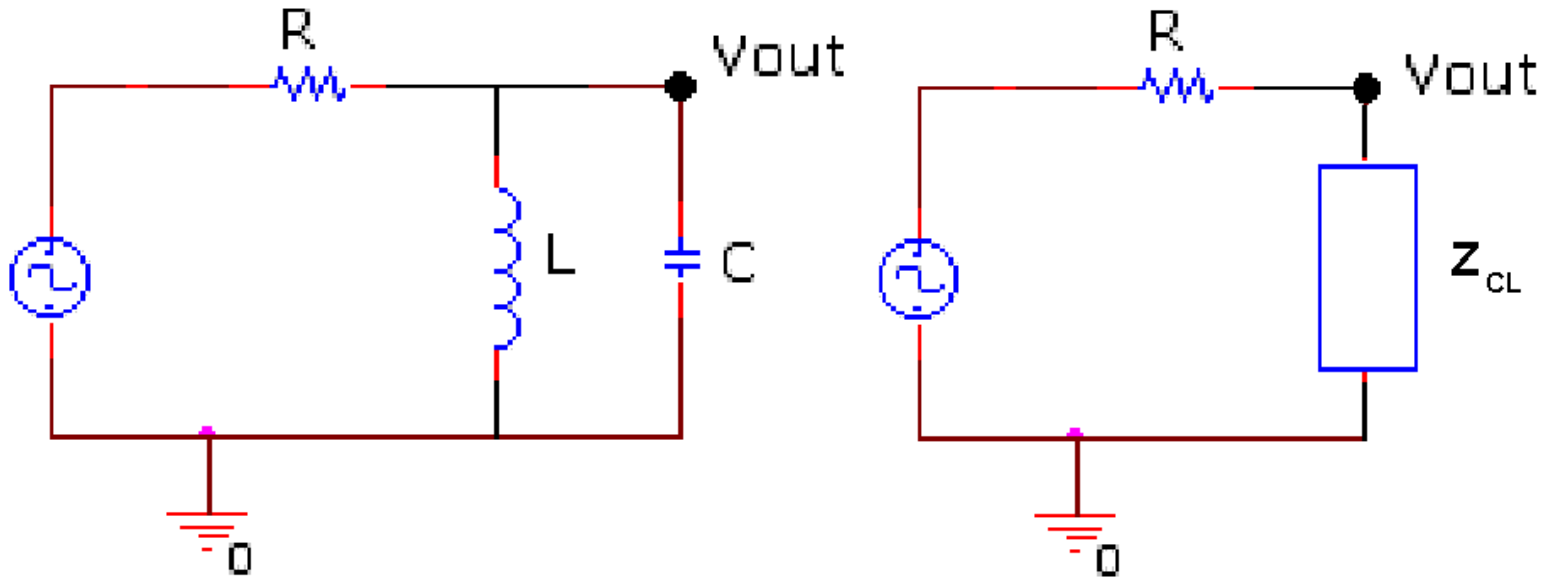
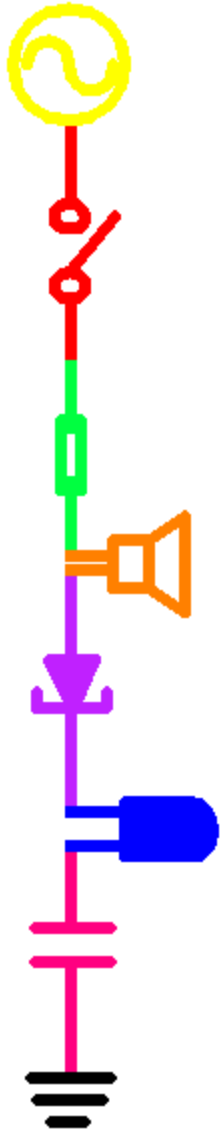
$$Z_{CL} = \frac{Z_L \cdot Z_C}{Z_L + Z_C} = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{j^2 \omega^2 LC + 1} = \frac{j\omega L}{1 - \omega^2 LC}$$




Determine H

$$Z_{CL} = \frac{j\omega L}{1 - \omega^2 LC}$$

$$H(j\omega) = \frac{Z_{CL}}{R + Z_{CL}}$$

$$H(j\omega) = \frac{\frac{j\omega L}{1 - \omega^2 LC}}{R + \frac{j\omega L}{1 - \omega^2 LC}} \quad \text{multiply by } \frac{1 - \omega^2 LC}{1 - \omega^2 LC}$$
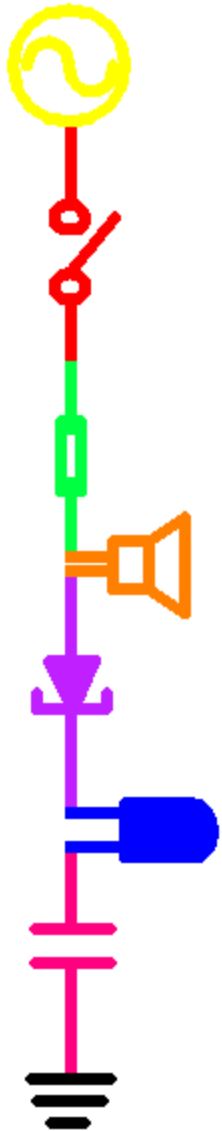
$$H(j\omega) = \frac{j\omega L}{R(1 - \omega^2 LC) + j\omega L}$$



At Very Low Frequencies

$$H_{LOW}(j\omega) = \frac{j\omega L}{R}$$

$$|H_{LOW}(j\omega)|_{\omega \rightarrow 0} = 0$$


$$\angle H_{LOW}(j\omega) = \frac{\pi}{2}$$

At Very High Frequencies

$$H_{HIGH}(j\omega) = \frac{j\omega L}{-\omega^2 LRC} = \frac{-j}{\omega RC}$$

$$|H_{HIGH}(j\omega)|_{\omega \rightarrow \infty} = \left| \frac{1}{\infty} \right| = 0$$
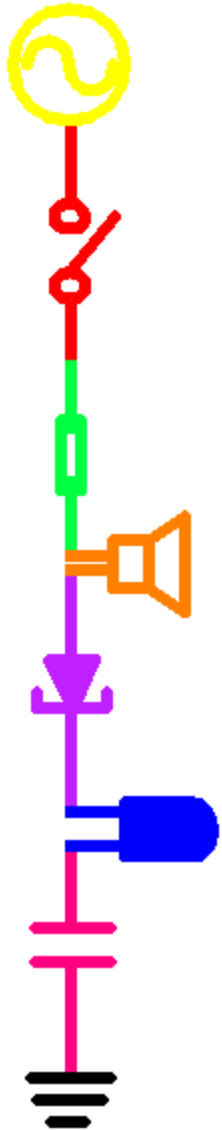
$$\angle H_{HIGH}(j\omega) = -\frac{\pi}{2}$$





At the Resonant Frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$H(j\omega_0) = \frac{j\left(\frac{1}{\sqrt{LC}}\right)L}{R\left(1 - \left(\frac{1}{\sqrt{LC}}\right)^2 LC\right) + j\left(\frac{1}{\sqrt{LC}}\right)L} = 1$$

$$|H(j\omega_0)| = 1 \quad \angle H(j\omega_0) = 0$$

Our example is a band pass filter

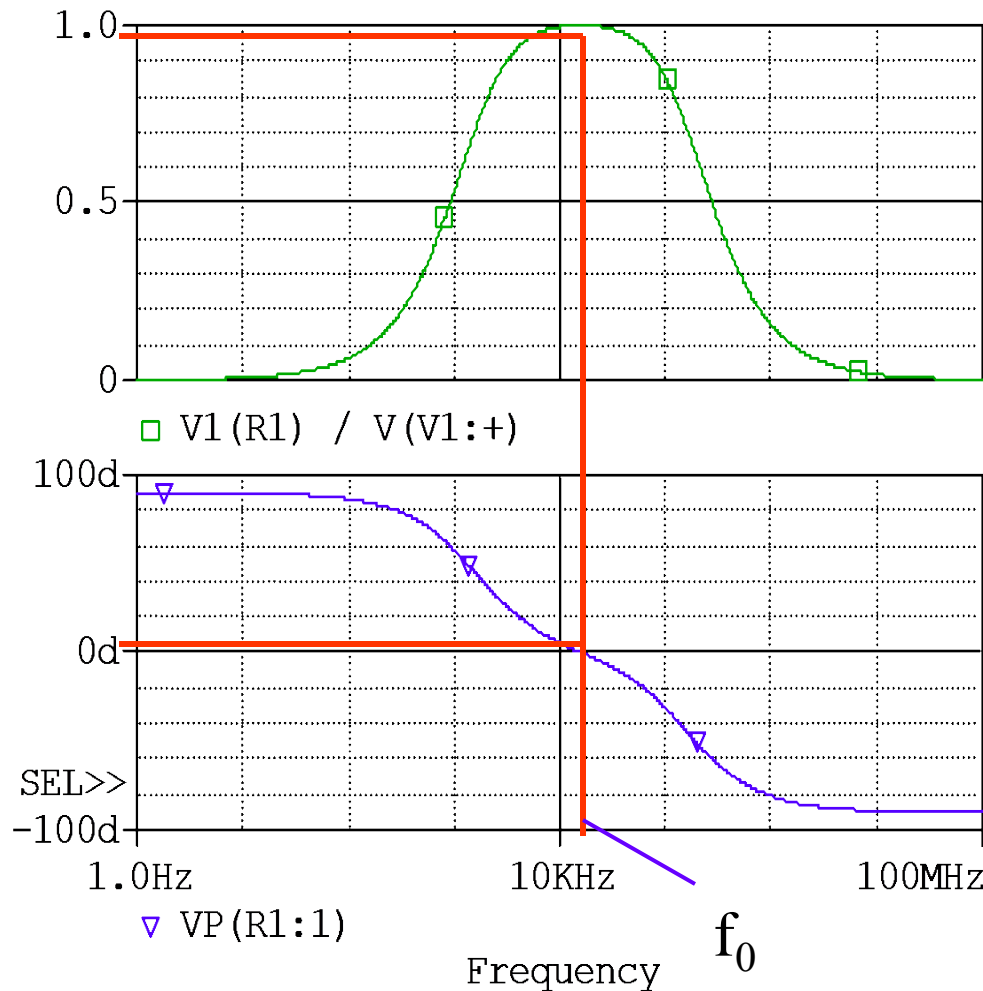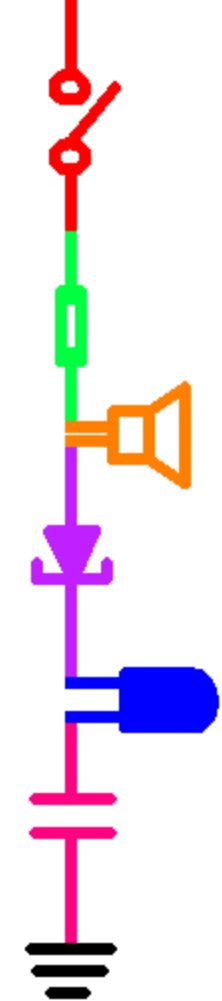

Magnitude

$$H = 0 \text{ at } \omega \rightarrow 0$$

$$H = 1 \text{ at } \omega_0$$

$$H = 0 \text{ at } \omega \rightarrow \infty$$

Phase

$$\phi = 90 \text{ at } \omega \rightarrow 0$$

$$\phi = 0 \text{ at } \omega_0$$

$$\phi = -90 \text{ at } \omega \rightarrow \infty$$