
 


Mushroom Timer Circuit

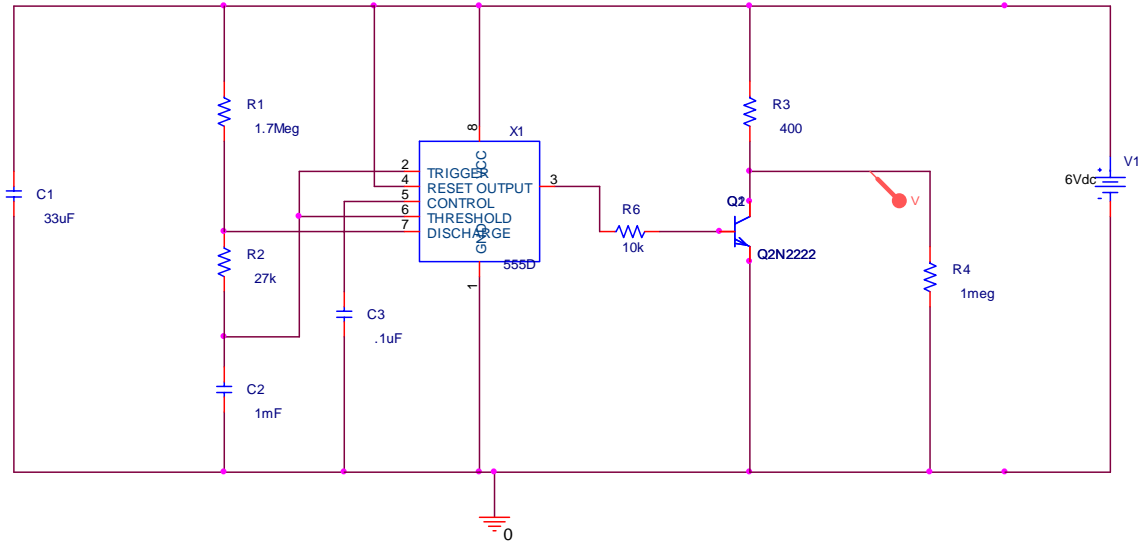The timer circuit described in the leda.lycaem.com link in Exp 7 was simulated using PSpice. Since the timing is very different from any other problem we have solved, it was necessary to modify one of the default simulation parameters. This is described on the last page of this report.



The top trace shows the output from pin 3 of the 555 chip, while the bottom trace shows the output from the transistor. The transistor output inverts the input voltage.

From the cursors placed on the figure, the total on plus off time is equal to 1218 seconds. The on time is about 20 seconds and the off time is about 20 minutes.

A 555 timer designer program was downloaded from a very useful website <http://www.electronicsaustralia.com.au/cgi-bin/downloads.pl?area=7>

555 Timer designer

Select run mode, R1, R2, and C1 then press OK

Choose run mode

- Monostable
- Astable
- Squarewave Astable

Choose C1 measure

- uF
- nF
- pF
- Farads

R1: 1700000

R2: 27000

C1: 1000

OK

Close

Time High: 1196.811 Seconds


Time Low: 18.711 Seconds

Frequency: 8.3381586566299! Hz


This does the simple calculations showing the high and low times for the choice of resistors and capacitor. This also confirms that the components chosen work as indicated.

Modifications to PSpice to simulate a circuit for over 20 minutes.

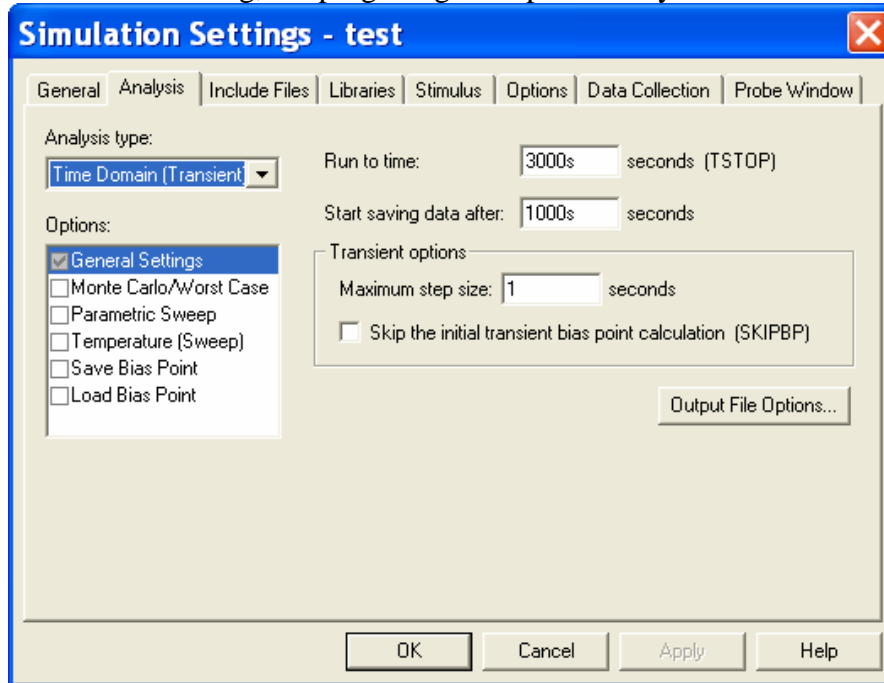First, the simulation settings must be specified. Note that the run to time (TSTOP parameter) is set to 3000 seconds. The first step in the simulation is very, very small. The simulation begins with a time step of about .03ns to keep the changes in voltages small. Since the total time is so long, the program gives up after only a few nano seconds.



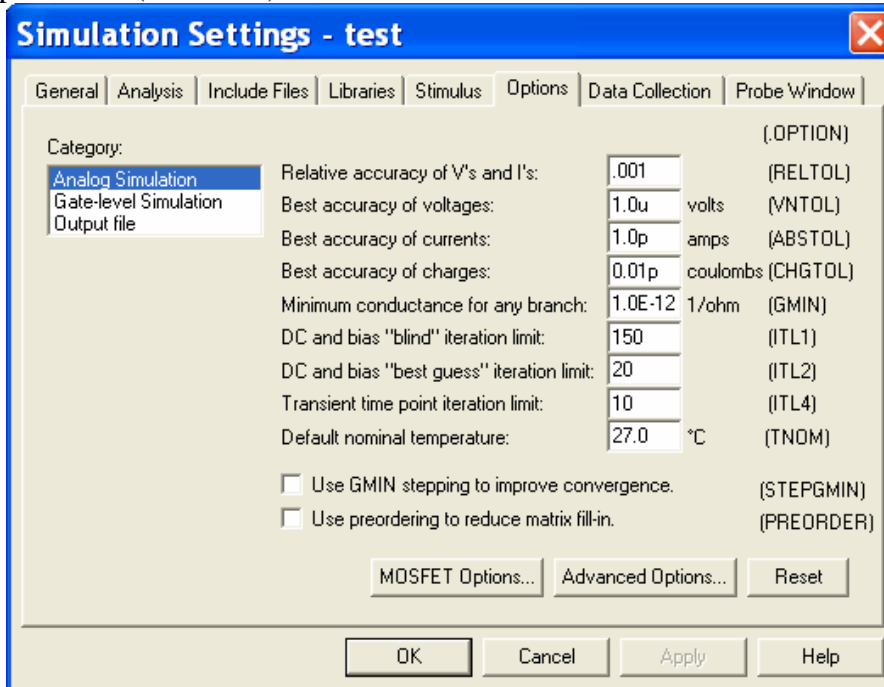To fix this problem, we need to go to the options tab above and change the relative accuracy parameter (RELTOL) from .001 to .1.



This changes the minimum time step according to the following:

$$\text{Minimum Time Step} = \text{TSTOP}/(\text{dynamic range of time})$$

where, dynamic range of time =

15 digits - the number of digits of accuracy required by RELTOL.

For example, if TSTOP = 1us and RELTOL = .001, then the minimum time step is: $1\text{E-}6/(1\text{E}15-1\text{E}3) = 1\text{E-}18$.

Thus, for our case, the minimum time step is: $3000/(1\text{e}15-1\text{e}1) = 3\text{e}3/1\text{e}14 = 3\text{e-}11$. Before we changed RELTOL, the minimum time step was $3\text{e-}13$. With such a small time step, the program gave up before it got past a few nanoseconds.