

ENGR-2300

Electronic Instrumentation

Quiz 2

Spring 2023

Print Name _____ **RIN** _____

Section _____

I have read, understood, and abided by the Collaboration and Academic Dishonesty statement in the course syllabus. The work presented here was solely performed by me.


Signature: _____

Date: _____


On all questions: SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS. No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also, it may be easier to answer parts of questions out of order.

I. Thevenin Equivalent Circuits [20 points]

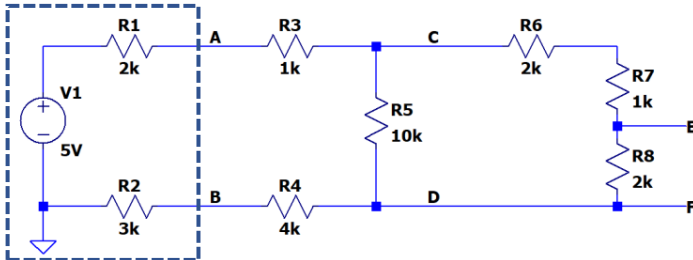
- a) [5 pts] Find the Thevenin Equivalent voltage and resistance between terminals A and B (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.



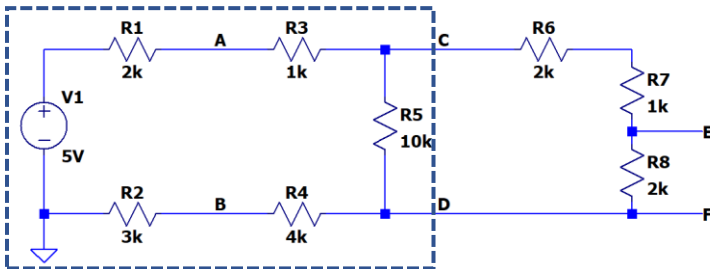
- b) [4 pts] Find the Thevenin Equivalent voltage and resistance between terminals C and D (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.



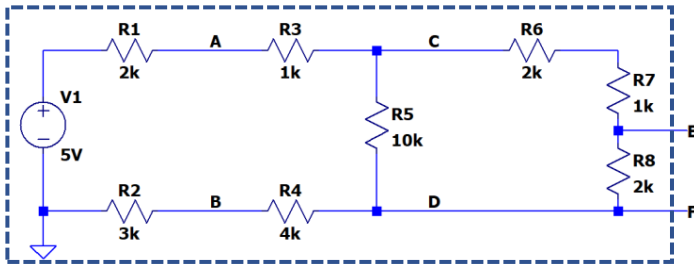
- c) [4 pts] Find the Thevenin Equivalent voltage and resistance between terminals E and F (for the portion of the circuit contained in the box). After finding V_{th} and R_{th} , draw the Thevenin Equivalent circuit.



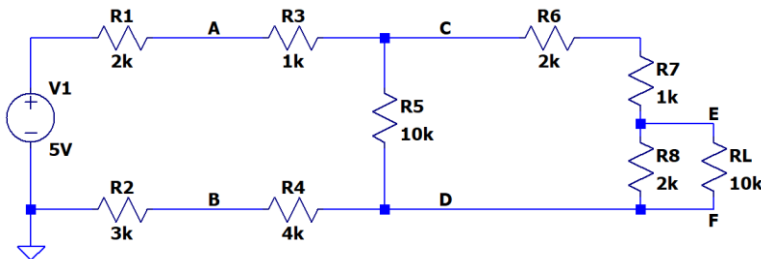- d) [2 pts] If a load resistor with a value $R_L = 10k\Omega$ is connected across terminals E and F as shown below, how much power is delivered to the resistor?



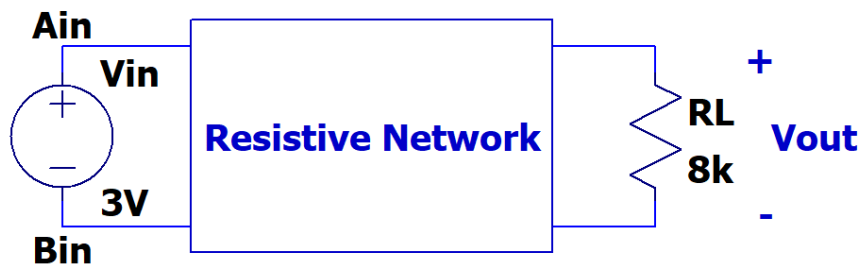- e) [3 pts] Given an unknown resistive network, you connect a load resistor $R_L = 8\text{k}\Omega$ across the output terminals and apply a voltage $V_{in} = 3\text{V}$ across the input terminals. If you measure a voltage $V_{out} = 2\text{V}$, what is the equivalent resistance R_{eq} of the resistive network?




- Q1.6)** [2 pts] True or False (circle one): only some linear circuits can be expressed as a voltage source in series with an impedance.

True


False

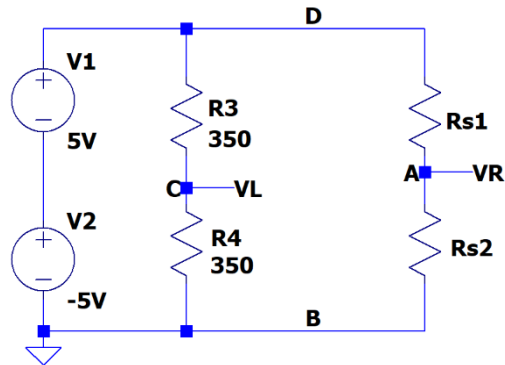II. Bridge Circuits, Strain gauges and Harmonic Oscillation [20 points]

In the circuit below, R_{s1} and R_{s2} represent the resistances of strain gauges which are attached to the top and bottom of a cantilever beam, as in Experiment 5 and Project 2.




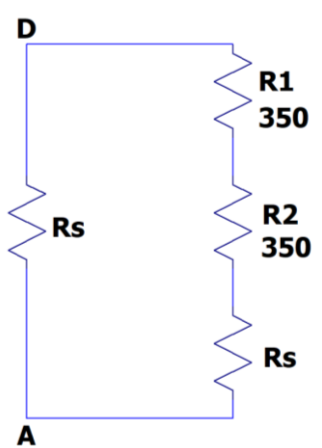- a) [4 pts] When you measured the resistance of the strain gauges in Experiment 5 (for example between terminals D and A), you were measuring R_{s1} in parallel with the series combination of R_1 , R_2 , and R_{s2} , as shown below. If both strain gauges are assumed to have the same resistance R_s , what is the value of R_s if you measured a resistance of 263Ω between terminals A and D? Give your answer to the nearest ohm.




- b) [3 pts] When the beam is deflected to its maximum extent, $V_{out} = V_L - V_R = 10\text{mV}$. Assuming that the strain gauge resistances become $R_{s1} = R_s + \Delta R$ and $R_{s2} = R_s - \Delta R$, what is the value of ΔR ? Give your answer to the nearest 0.1Ω .
- c) [2 pts] The output voltage of the strain gauge and bridge circuit is fed into a differential amplifier. Given that $V_{out} = 10\text{mV}$ is the maximum output voltage of the bridge circuit and the op-amp voltage supplies are $+5\text{V}$ and -5V , what is the maximum gain of the differential amplifier, such that its output does not saturate?

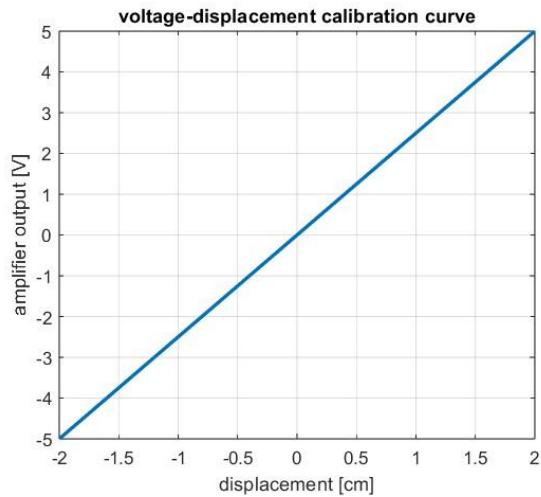- d) [2 pts] Using the calibration curve below, calculate the proportionality constant that converts the voltage output of the differential amplifier in V to beam displacement in m.



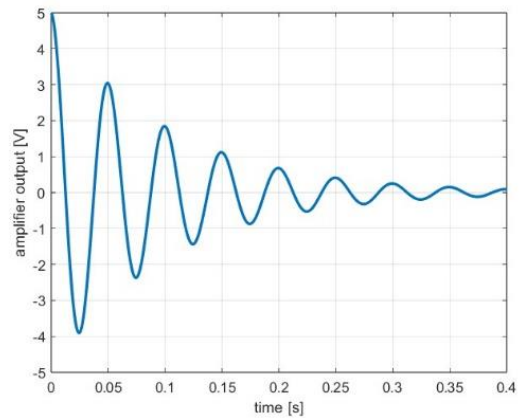
- e) [3 pts] Given the curve below, calculate the frequency (in Hz) of the beam oscillation and the decay constant to the nearest 0.1.



f) [2 pts] Which type of op-amp circuit would you use to calculate velocity (up to a constant) from the data in QII.e?


g) [2 pts] If instead you were measuring the voltage signal from an accelerometer, which type of op-amp circuit would you need to calculate velocity (up to a constant)?

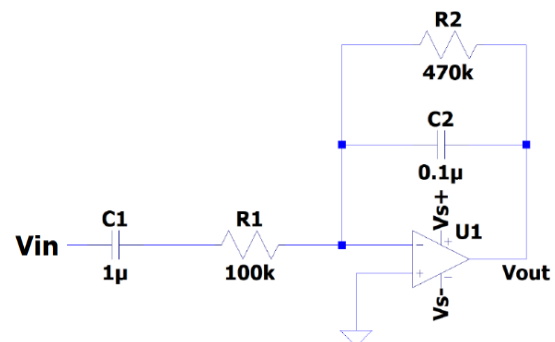h) [2 pts] In the Miller Integrator circuit shown below, what is the function of the capacitor C1 at the input?




III. Op-Amp Applications and Analysis [26 points]

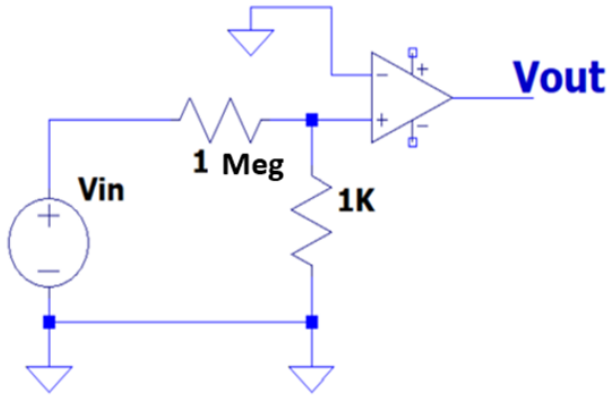- a) [4 pts] The op-amp circuit below uses an op-amp that is ideal except for having a **finite gain A**. If the measured V_{out} is 3.5V when V_{in} is 3.5V, what is the op-amp gain A ?
Hint: $V_{out} = A * (V_+ - V_-)$ when the op-amp is not configured in a feedback loop.



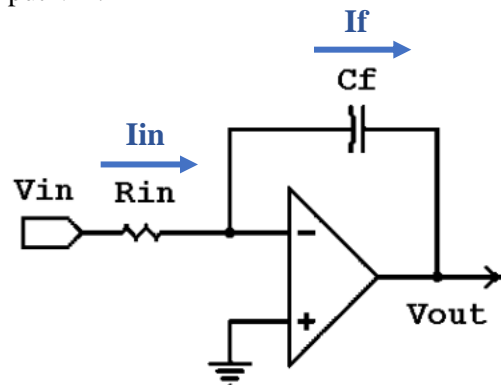
- b) [12 pts] In the ideal integrator as shown below, $R_{in} = 100 \text{ k ohm}$ and the $C_f = 0.1 \mu\text{F}$. A sine-wave signal is applied to the input V_{in} .




- i) [2 pts] Find I_{in} and I_f in terms of V_{in} , V_{out} , R_{in} , and the impedance of C_f . Indicate where you used the Golden Rules of op-amps.

- ii) [2 pts] Find the transfer function of this op-amp circuit: $H[j\omega] = V_{out}/V_{in}$.
- iii) [4 pts] At what frequency (in Hz) are the input and output signal equal in amplitude?
- iv) [2 pts] At that frequency, what is the phase of the output signal relative to the input signal?
- v) [2 pts] If the frequency is lowered by a factor of 10 from that found in iii), by what factor does the output voltage change? In what direction? Choose one: larger or smaller.

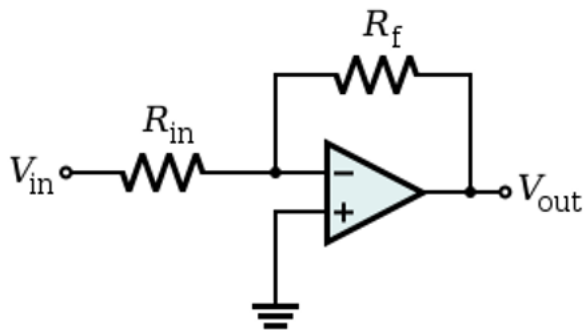
- c) [10 pts] In the following op-amp application circuit the power supply is $V_{cc} = \pm 5V$.



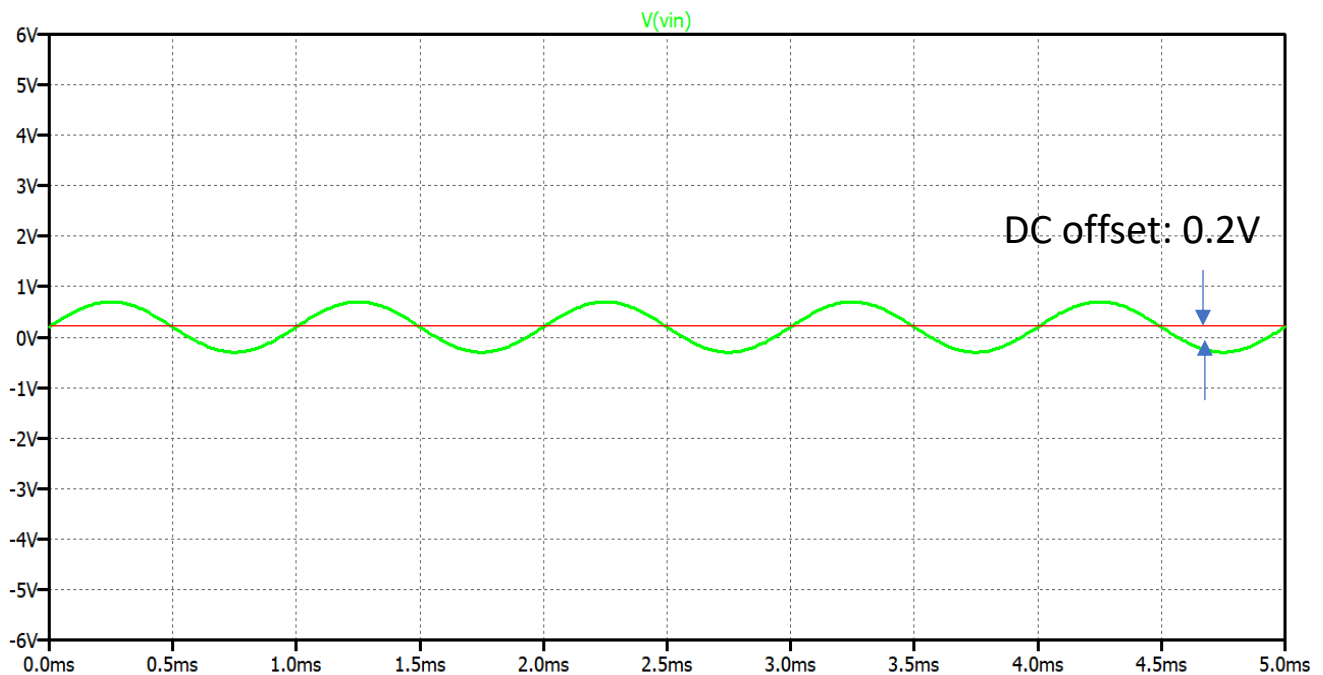- i) [2 pts] If $R_{in} = 10k \text{ ohm}$ and we want this amplifier to have a gain of *magnitude*: 10 V/V . What should be the value of the feedback resistor R_f ?
- ii) [5 pts] If V_{in} is a sinusoidal wave input of $0.5\sin(2\pi 1000t)V$ on top of DC offset of $0.2V$, as drawn below on the V-time plot, draw the output wave form on the graph below. The DC offset is plotted on the graph below as well.




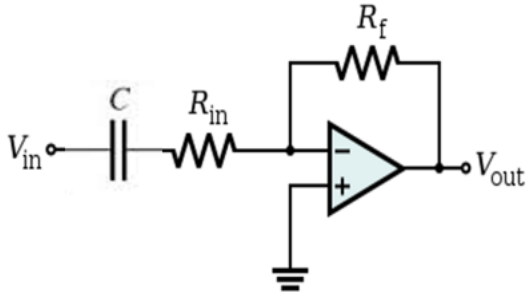- iii) [3 pts] Now we want to remove the effect of the DC offset from the V_{in} for proper amplification of the input signal. One way is to add a capacitor at the input. What is an appropriate value of the capacitor in the figure below, such that the circuit still operates as an **inverting amplifier**? Hint: what should the relative magnitude of the impedances of R_{in} and C ?



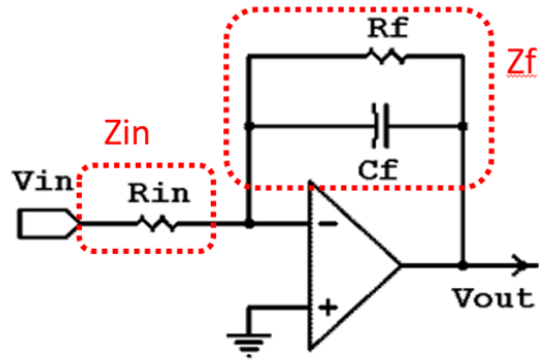IV. Op-Amp Integrators [14 points]


To improve the performance of the ideal integrator in QIII.b, a feedback resistor R_f is added on the feedback path of C_f .



- a) [4 pts] Using the same steps as in QIII.b.i and QIII.b.ii, find the transfer function of this op-amp circuit in terms of R_{in} , R_f and C_f .

- b) [3 pts] Given that $R_{in} = 1\text{ k}\Omega$, assign values for R_f and C_f such that the DC gain is 100 and the corner frequency (3-dB frequency) is 40Hz.

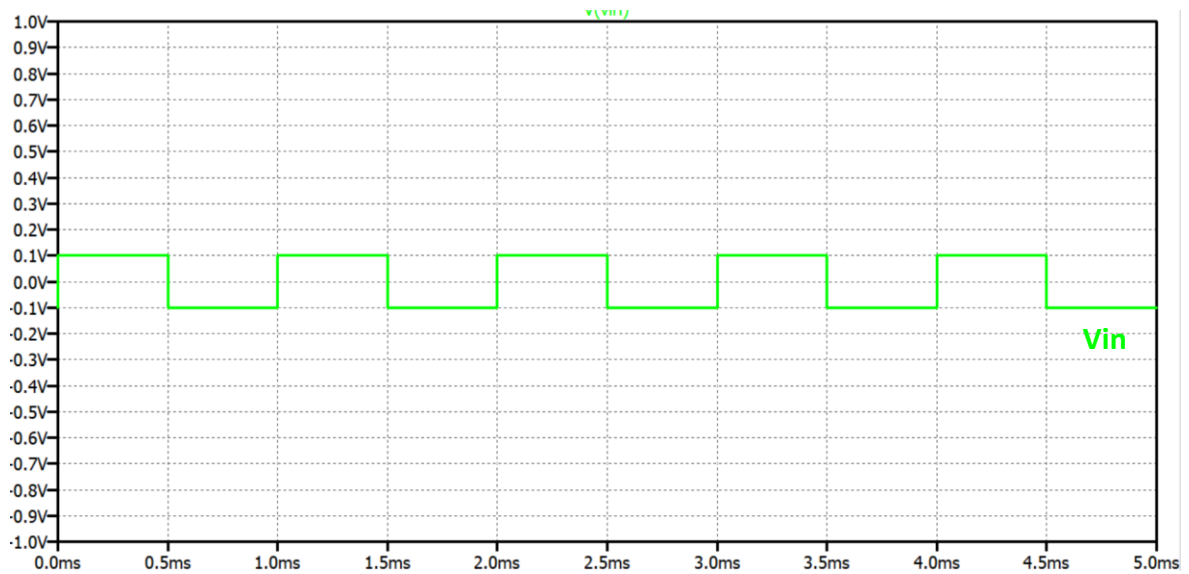- c) [5 pts] For a 0.1V peak-to-peak square wave input with a frequency of 1kHz, draw the output wave form on the voltage-time plot below. Indicate key values from your calculation (such as min and max) on the plot. Hint: since we are in steady-state the DC offset of the output voltage should be 0.



- d) [2 pts] At what frequency does the magnitude of the transfer function reduce to unity (=1)?