
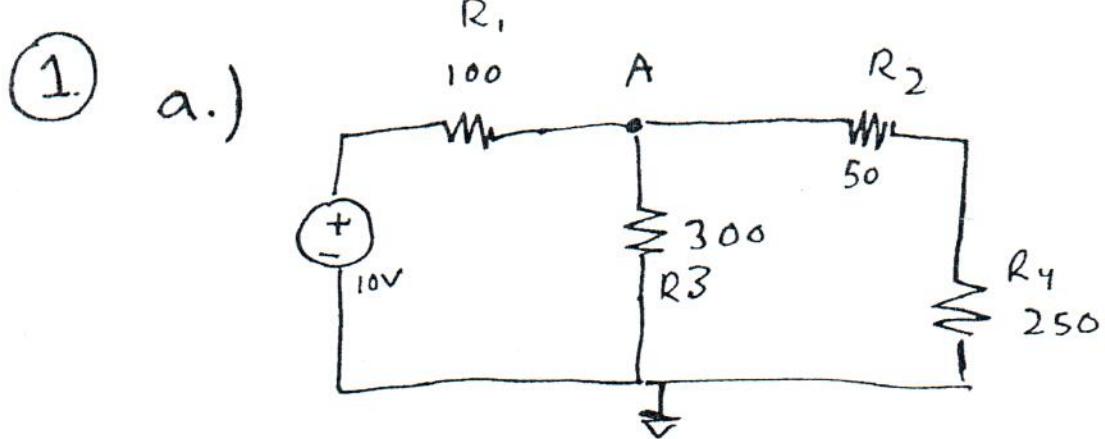


Quiz 1

soln.

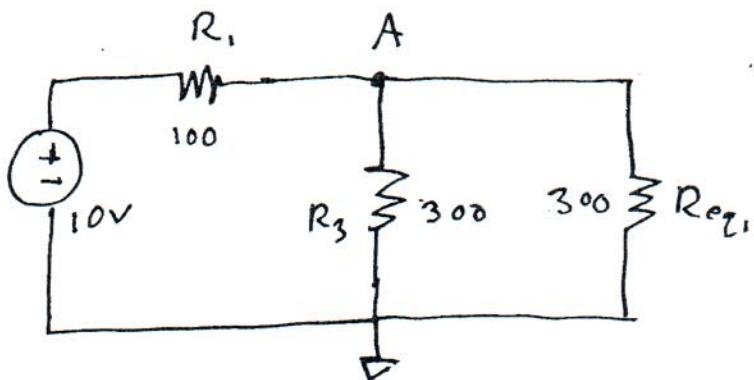


Resistors R_2 and R_4 are in series
and can be combined into a
single equivalent branch resistance:




R_3 and Req_1 are in parallel
and can be combined into Req_2 .
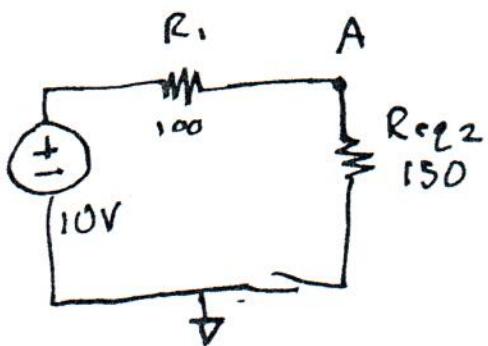
$$Req_2 = \frac{R_3 \times Req_1}{R_3 + Req_1} = \frac{(300)^2}{600} = 150\Omega$$



$$V_A = 10V \cdot \frac{(150\Omega)}{(100\Omega + 150\Omega)}$$


$$V_A = 6V$$

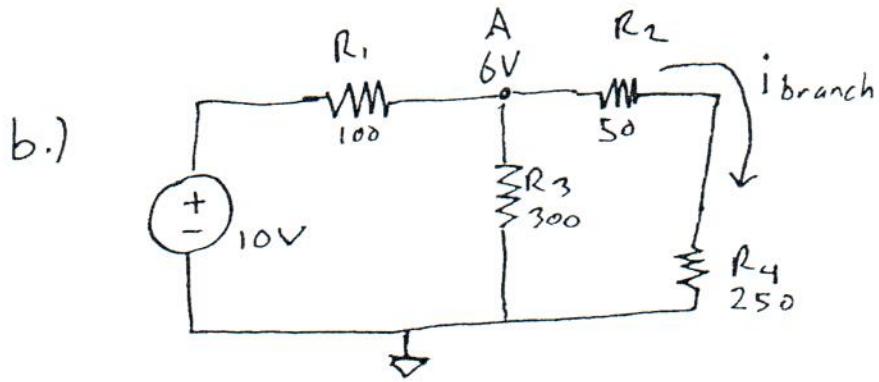

The circuit branch

between point A and ground
that has R_2 and R_4 on it has
 $R_{tot} = R_2 + R_4 = 300\Omega$.

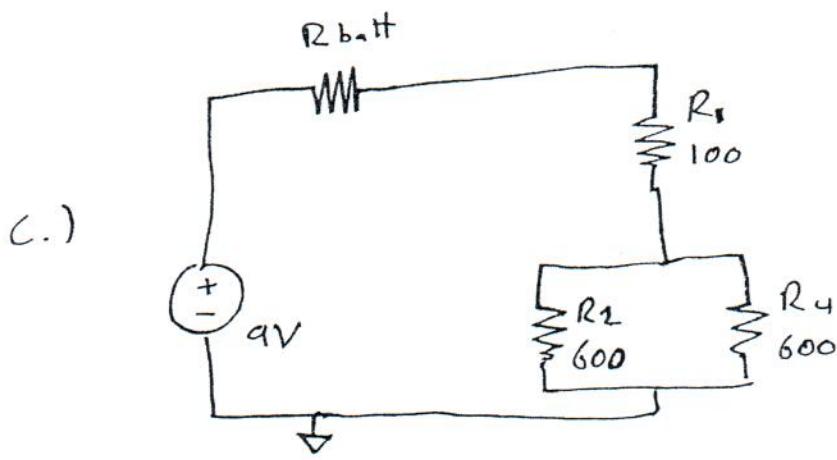
$$i_{branch} = \frac{V_A}{R_{tot}} = \frac{6V}{300\Omega} = 20mA$$



d.) The equivalent resistance of R_2 and R_4 together is

$$R_{\text{tot}} = \frac{R_2 R_4}{R_2 + R_4} = \frac{600^2}{1200} = 300$$

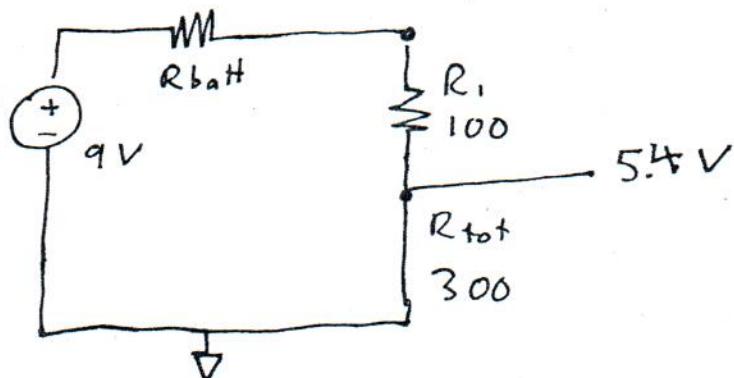there fore we draw the equivalent circuit:



$$V_{\text{out}} = 5.4V = 9V \cdot \frac{300\Omega}{300\Omega + (100\Omega + R_{\text{batt}})}$$

$$300\Omega + 100\Omega + R_{\text{batt}} = \frac{9V}{5.4V} \cdot 300\Omega$$


$$R_{\text{batt}} = \frac{9}{5.4} \cdot 300\Omega - 100\Omega - 300\Omega = 100\Omega$$

e.) This is more than usual; typical values are a few ohms or tenths of an ohm.

f.) A probe with lower input resistance would effectively place a third resistor in parallel with R_2 and R_4 , lowering R_{tot} and therefore lowering V_{out} .

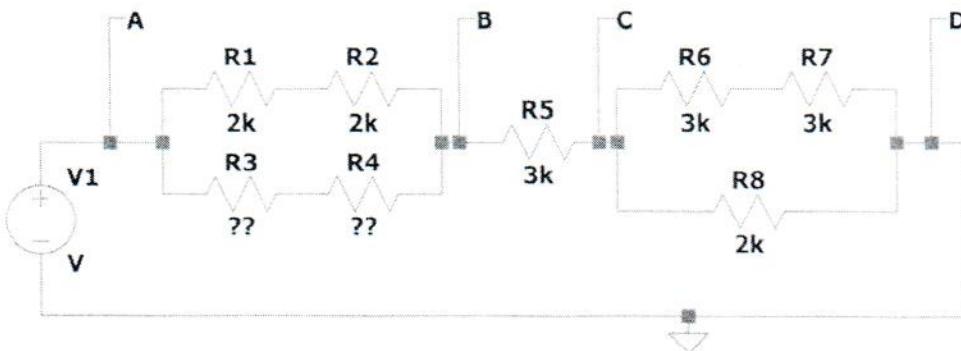II. Resistor Combinations, concepts and miscellaneous (20 points) Note: Page 2 of this quiz has background information. The crib sheet may also be useful.

The following circuit consists of 8 resistors and there are 4 voltage markers at points A, B, C, and D. V₁ is a dc voltage source which can be created using W1 of the instrumentation board. Note: several of the following questions are independent of each other, but not all.



- a. (4 pt) It is desired to have the effective resistance of R₃ combined with R₄ to be 8 kΩ. Using the table of standard 5% resistor values pick resistors for R₃ and R₄. State the resistance of each. These have 5% tolerance, what is the 4-band color code for each resistor? You should note that 8 k isn't a standard value.

Four solutions

- $R_3 = 6.2 \text{ k} \parallel 11.4 \text{ k}$ R₃ value: 6.2 Color bands: Blue, red, red, gold
- $6.2 \text{ k} \parallel 11.4 \text{ k}$ R₄ value: 1.8 Color bands: Brown, violet, red, gold
- $5.6 \text{ k} \parallel 2.4 \text{ k}$
- $4.7 \text{ k} \parallel 3.3 \text{ k}$ can switch which is R₃ or R₄

- b. (3 pts) If the voltage is measured to be 1V at point D, what is the current through R₇, R₈, and R₅? Be sure to include units on all answers.

$$I(R_7) = \frac{1\text{V}}{R_6 + R_7} = \frac{1}{6\text{k}} = 0.17\text{mA}, 167\mu\text{A} \quad I(R_7) \underline{0.17\text{mA}}$$

$$I(R_8) = \frac{1}{2\text{k}} = 0.5\text{mA} \quad I(R_5) = I(R_7) + I(R_8) = 0.67\text{mA} \quad I(R_5) \underline{0.67\text{mA}}$$

- c. (2 pts) What is the equivalent resistance between points A and B, Call this R_{AB}.

$$R_{AB} = \frac{(R_1 + R_2) \parallel (R_3 + R_4)}{(R_1 + R_2) \parallel (R_3 + R_4) + R_5} = \frac{4\text{k} \cdot 8\text{k}}{4\text{k} + 8\text{k}} = \frac{32\text{k}}{12} = 2.67\text{k}$$

$$R_{AB} \underline{2.67\text{k}\Omega}$$

- d. (2 pts) What is the equivalent resistance between points C and D, Call this R_{CD}.

$$R_{CD} = \frac{(R_6 + R_7) \parallel R_8}{(R_6 + R_7) \parallel R_8 + R_5} = \frac{6\text{k} \cdot 2\text{k}}{6\text{k} + 2\text{k}} = \frac{12}{8}\text{k} = 1.5\text{k} \quad R_{CD} \underline{1.5\text{k}\Omega}$$


EI

You must include units.

R total	8000			
R1	colors	R2	colors	Rtotal
6800	blue, gray, red, gold	1200	brown, red, red, gold	8000
6200	blue, red, red, gold	1800	brown, violet, red, gold	8000
5600	green, blue, red, gold	2400	red, yellow, red, gold	8000
4700	yellow, violet, red, gold	3300	orange, orange, red, gold	8000

Prop II a.

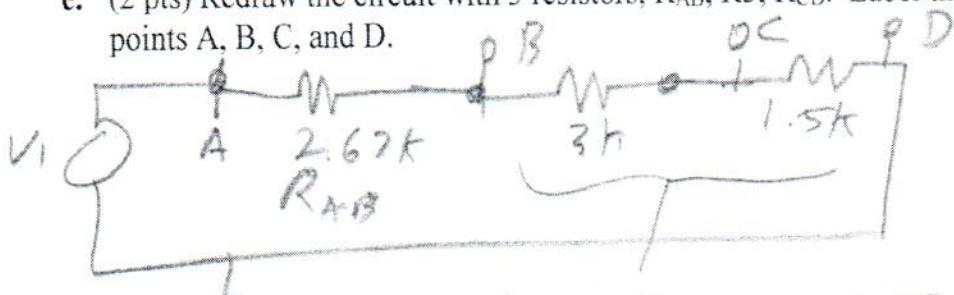- e. (2 pts) Redraw the circuit with 3 resistors, R_{AB} , R_5 , R_{CD} . Label the resistor values and mark points A, B, C, and D.




$$R_5 + R_{CD} = 4.5\Omega$$

- f. (2 pts) Using the figure you drew for part e., if $V_1=5V$ what is the voltage at point B?

$$V_B = V_1 \cdot \frac{R_5 + R_{CD}}{R_{AB} + R_5 + R_{CD}} = 5 \cdot \frac{4.5}{2.67 + 3 + 1.5} = 3.1V$$

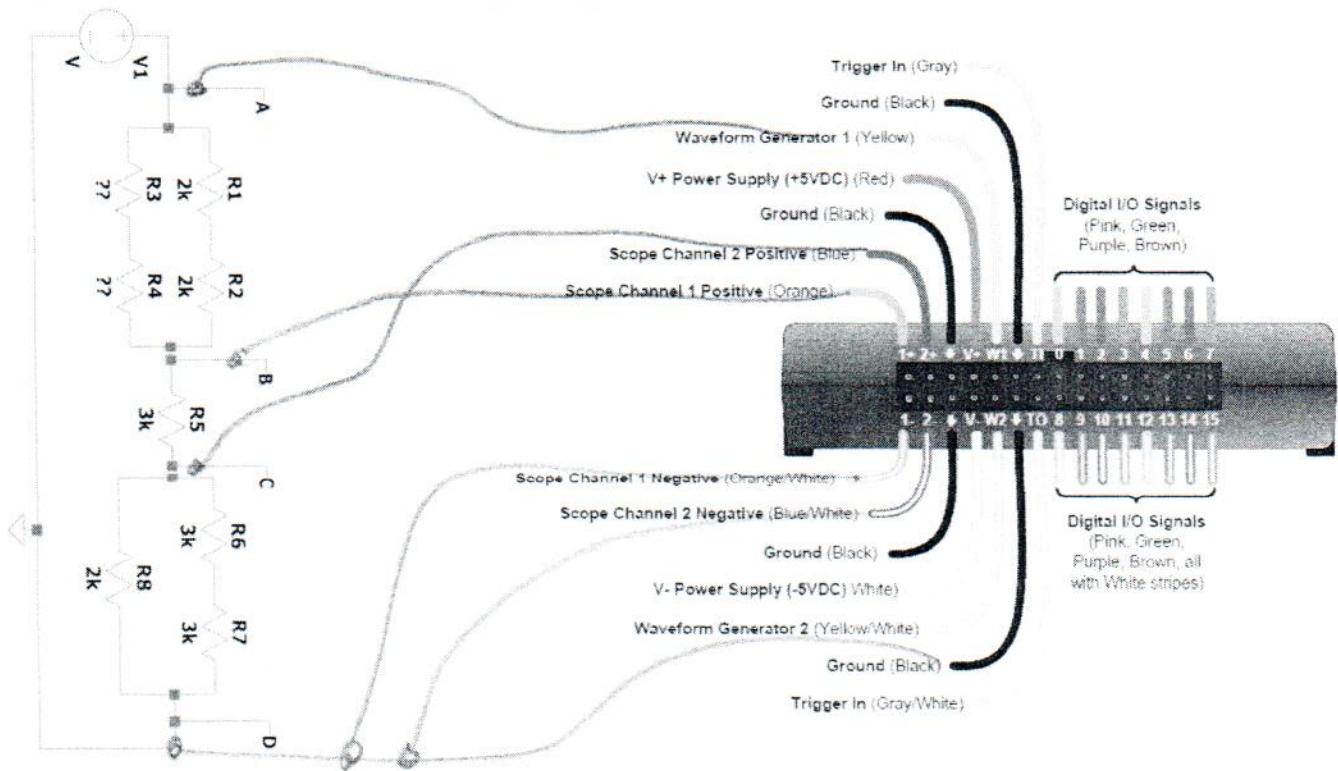- g. (5 pts) Wire this circuit by drawing lines on the figure below. Use the wave gen/signal gen to provide a signal for V_1 , which is point A. Use channel 1 to measure the signal at point B and use channel 2 to measure the signal at point C.



Draw lines between the 2 figures to indicate wires. Both the M2K and the AD2 have the same wiring and colors. W1 is called Signal Generator on the M2K and Waveform Generator on the AD2.

(3)

a.)

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_{eq}}{Z_{eq} + R}$$

$$\begin{aligned} Z_{eq} &= \frac{Z_C Z_L}{Z_C + Z_L} = \frac{\frac{1}{j\omega C} \cdot j\omega L}{j\omega L + \frac{1}{j\omega C}} \\ &= \frac{j\omega L}{1 - \omega^2 LC} \end{aligned}$$

$$H(j\omega) = \frac{\frac{j\omega L}{1-\omega^2 LC}}{\frac{j\omega L}{1-\omega^2 LC} + R} = \frac{j\omega L}{R(1-\omega^2 LC) + j\omega L}$$

b.) At low frequency,

$$H(j\omega) = \frac{j\omega L}{R - R\cancel{\omega^2 LC} + j\omega L} = \frac{j\omega L}{R}$$

$$|H(j\omega)| = \frac{\omega L}{R} \quad \angle H(j\omega) = 90^\circ$$

At high frequency,

$$H(j\omega) = \frac{j\omega L}{R - R\omega^2 LC + j\omega L} = \frac{-j}{\omega RC}$$

$$|H(j\omega)| = \frac{1}{\omega RC}$$

$$\angle H(j\omega) = -90^\circ$$


c.)

The magnitude of the transfer function is low at low frequencies due to the low impedance of the inductor and also low at high frequencies due to the low impedance of the capacitor. It will reach its maximum amplitude at an intermediate frequency. Therefore it is a band pass filter.

d.)

Z_1	Z_2	Low-pass	High-pass
R	C	Y	N
C	R	N	Y
R	R	Y	Y
R	L	N	Y
L	R	Y	N


e.)

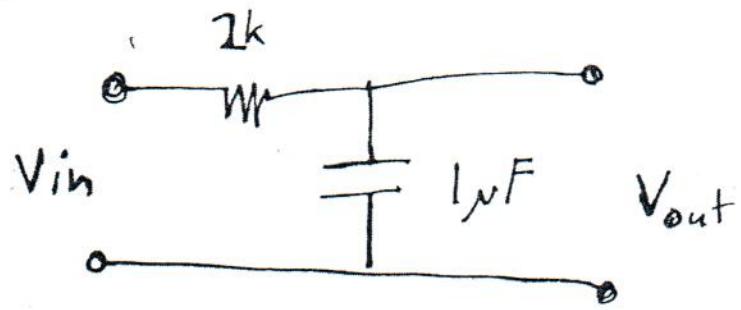

$$\omega_c = \frac{1}{R C} = \frac{1}{(2 \times 10^3)(1 \times 10^{-6})} = 500 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \frac{500}{2\pi} = 79.6 \text{ Hz}$$

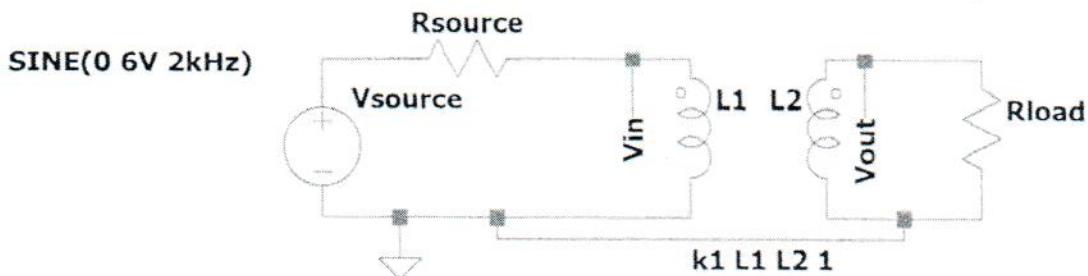IV – Phasors and Transformers (20 points)



- 1) Assume L1 and L2 form an ideal transformer with full coupling. The transformer has these specifications:

$$a=1/3, L_1 = 300\text{mH}$$

- a. Determine the value of L2 that will match the allow the result in the transformer matching these specs: (2pts)

$$a = \sqrt{\frac{L_2}{L_1}} \quad L_2 = a^2 L_1 = \left(\frac{1}{3}\right)(300\text{mH}) = 33.3\text{mH} \quad L_2 = 33\text{mH}$$

- b. Determine the ratios V_{out}/V_{in} , and I_{out}/I_{in} (4 pts)

$$\frac{V_{out}}{V_{in}} = a = \frac{1}{3}$$

$$\frac{I_{out}}{I_{in}} = \frac{1}{a} = 3$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{3} \approx 0.33$$

$$\frac{I_{out}}{I_{in}} = 3$$

- c. Find the value of R_{load} that results in $R_{in} = 3\text{k}\Omega$ (R_{in} is V_{in}/I_{in}) (3 pts)

$$R_{in} = \frac{R_{load}}{a^2} \quad R_{load} = a^2 R_{in} = \left(\frac{1}{3}\right)^2 (3\text{k}) \\ = 333\text{ }\Omega \quad R_{load} = 333\text{ }\Omega$$

- d. Given $R_{source} = 500\Omega$ and $V_{source} = 6\sin(2\pi \cdot 2000t)$ What is the time domain value of V_{in} ? Give the answer in the form of: $v(t)=V_1\sin(\omega t+\theta_1)$ (2 pts)

$$V_{in} = \frac{R_{in}}{R_{in} + R_{source}} \cdot V_{source}$$

$$\frac{R_{in}}{R_{in} + R_{source}} = \frac{3\text{k}}{3\text{k} + 500} = 0.56$$

Any Form

$$V_{in} = \frac{5.14 \sin(2\pi \cdot 2000t)}{0.56} \text{ V}$$

$$V_{in} = (0.96) \times 6 \sin(2\pi \cdot 2000t) \text{ V}$$

$$= 5.14 \sin(2\pi \cdot 2000t) \text{ V} \\ = 5.14 \sin(2\pi \cdot 2000t + 0^\circ) \text{ V}$$

$$= 5.14 \sin(1.26 \times 10^4 t) \text{ V}$$

- e. The ideal transformer model assumes that self-inductance L1 and L2 are infinite, $|j\omega L_1|$ and $|j\omega L_2|$ approach infinity. On the practical side the transformer is close to ideal if $|j\omega L_1| > 10 \cdot R_{\text{source}}$ and $|j\omega L_2| > 10 \cdot R_{\text{load}}$. Just looking at L1, will this transformer be close to the ideal? If not, how could the transformer be changed to approach ideal but yet have the same value for a? (3pts) $|j\omega L_1| = (2\pi)(20\text{m})(0.3) = 3.77 \text{ mH}$

~~(No)~~ $|j\omega L_1| = 50 \text{ mH} \quad 3.77 \text{ mH}$ ~~Is it near ideal? Yes or No~~
If not say in words how the transformer could be changed to approach ideal but without changing the value of a.

Increase L1 by ~~at least~~ a factor-


of $\frac{50}{3.77} \approx 13$, then change L2 by same factor to keep from changing a

Sufficient to say to increase L1 to meet the criteria + then increase L2 by same percentage.

2. Phasors: This circuit shown has 2 complex impedances, Z1 and Z2, connected as shown.

Given: $V_{\text{in}} = 6V \angle 0^\circ$ and the voltage across Z2 is measured to be $V_{z2} = 4V \angle -45^\circ$ (This format is a magnitude and a phase angle.)

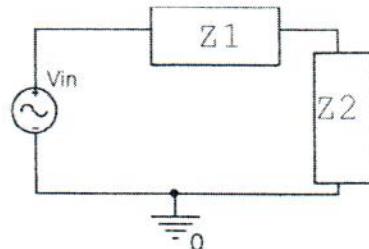- a. Write V_{in} and V_{z2} in Cartesian form. (2pts)



$$V_{\text{in}} = 6 + 0j = 6V$$

$$V_{z2} = 4 \cos(-45^\circ) + j 4 \sin(-45^\circ) = 2.8 - j 2.8V$$

- b. Determine V_{z1} , the voltage across Z1 in Cartesian and polar form (2pts)

$$\text{KVL} \quad V_{\text{in}} = V_{z1} + V_{z2} \quad 6V = (a + jb + 2.8 - j 2.8)V$$

$$a = 6 - 2.8 = 3.2$$

$$b = 0 - (-2.8) = 2.8$$

$$V_{z1} = \frac{3.2 + j 2.8}{2.8} = 1.14 + j 1.0V$$

3. Give the names of 2 of the people teaching this course. This can be first names or last names and can be the professors, teaching assistants, or undergraduate student assistants. Spelling doesn't count. Using their Discord name is also valid. (1pt)

Many correct answers.