

ENGR-2300
Electronic Instrumentation
Quiz 2
Spring 2022

Print Name _____ **RIN** _____

Section ____


I have read, understood, and abided by the Collaboration and Academic Dishonesty statement in the course syllabus. The work presented here was solely performed by me.

Signature: _____

Date: _____


On all questions: **SHOW ALL WORK. BEGIN WITH FORMULAS, THEN SUBSTITUTE VALUES AND UNITS.** No credit will be given for numbers that appear without justification. Unless otherwise stated in a problem, provide 3 significant digits in answers. Read the entire quiz before answering any questions. Also it may be easier to answer parts of questions out of order.

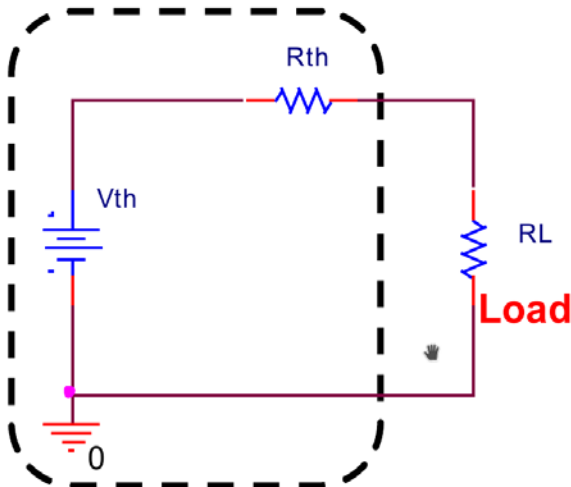- I. Thevenin Equivalent And Voltage Follower (20 points) As stated on the cover page: Round answers to 3 significant digits. Show formulas first and show your work. No credit will be given for numbers that appear without justification.




The Thevenin Equivalent Circuit consists of a voltage source in series with a resistor, which provides a very simple replacement for much more complex circuits. If we have this simple source, analyzing complex loads becomes quite easy.

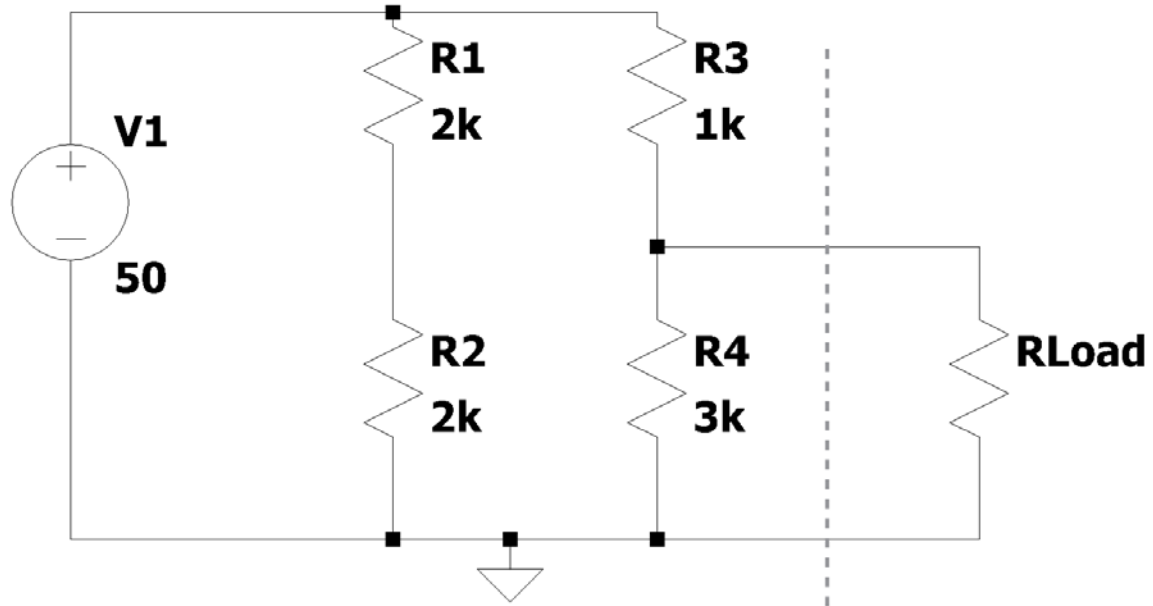
- a) (7 pts) Find the Thévenin equivalent voltage and resistance for the circuit below. The load is to the right of the dashed line.




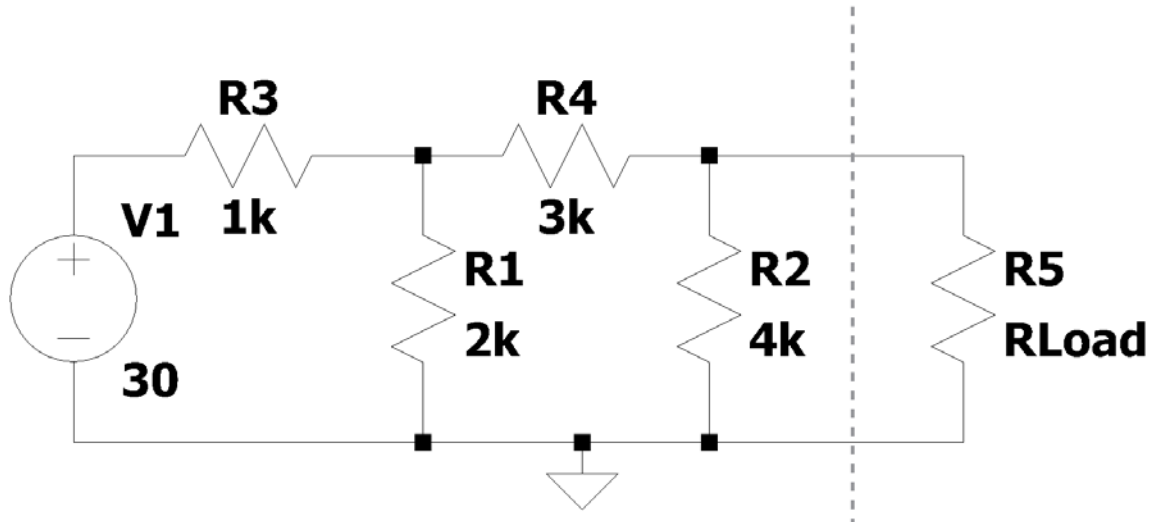- b) (7 pts) Now find the Thévenin equivalent voltage and resistance for the circuit below. The load is to the right of the dashed line. (*Hint. It may be useful to do this in stages. Calculate the Thévenin voltage and resistance of the voltage source and first two resistors, then add in R_4 and R_2 .*)




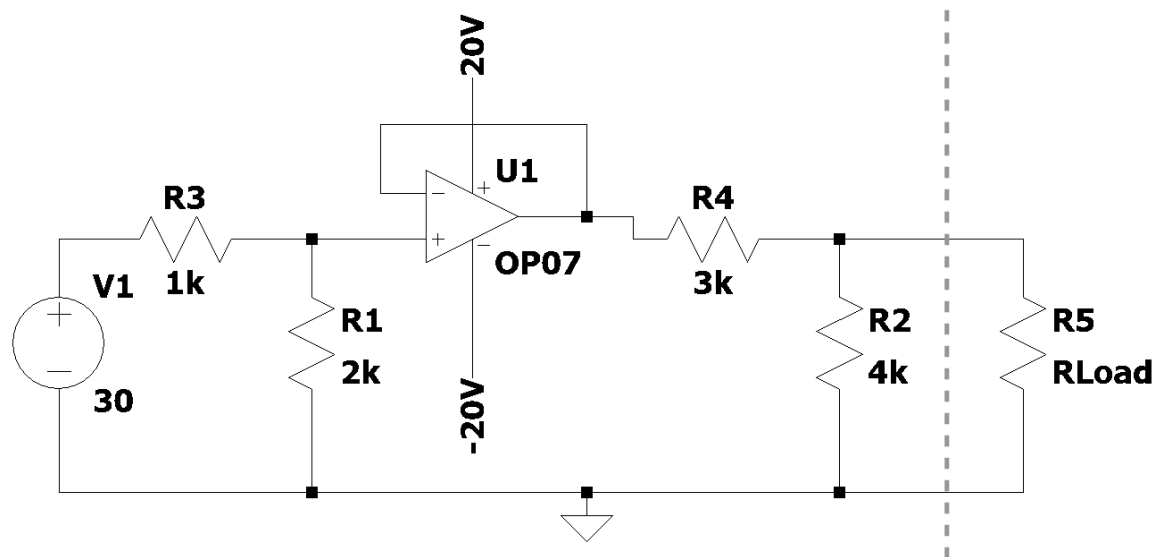- c) (4 pts) An ideal voltage follower is now placed between R1 and R4 as shown below. If we do not connect an RLoad resistor to the circuit, what is the voltage at the load resistor?



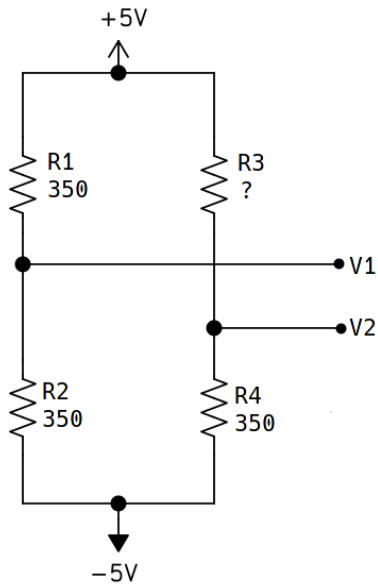II. Strain Gauges and Bridges (20 points)

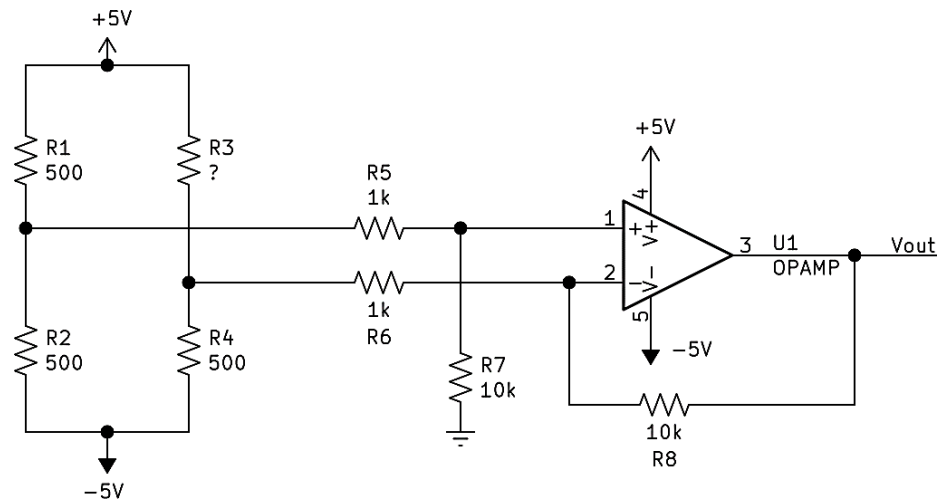- a. (3 pts) In the strain gauge above, suppose that R3 has a value of 370Ω . What is the differential voltage output ($V1 - V2$)?




- b. (6 pts) Now we look at a new strain gauge connected to a differential amplifier as shown above. If the voltage V_{out} is 1.2V, find the value of R_3 . (Assume that the op amp is a rail-to-rail chip, meaning that the output can reach the voltage of the power supplies; otherwise assume it is ideal.)


- c. (6 pts) Suppose that the value of R3 in part b varies during normal operation. Assuming that you keep the values of R7 and R8 equal, what is the maximum resistance that R3 can have without saturating the op-amp? What is the minimum resistance it can have without saturating the op-amp?
- d. (3 pts) Name one change you could make to the differential amplifier circuit to increase its sensitivity (in other words, the amount of change in the output voltage for every ohm of change in R3. Your answer should not be dependent on the current value of R3.)
- e. (2 pts) In Experiment 5 and Project 2, you were asked to consistently use the same cantilever beam and strain gauge each time you came to class or open shop. Why was this the case?

III. Operational Amplifier Applications (20 points)

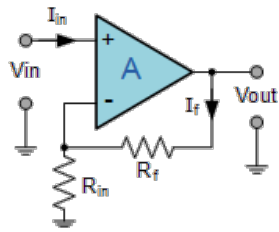
a. For the circuits below, assume the op amps are ideal:



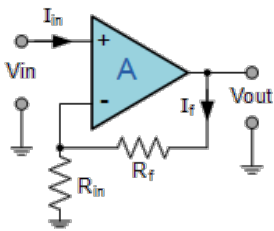
- i. (2 pts) For the circuit on the left, given $R_f = 4k\Omega$ and $R_{in} = 1k\Omega$
 1. Write an equation for V_{out}/V_{in}



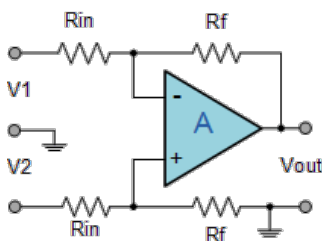
- ii. (2pts) For the circuit on the left, given $R_f = 4k\Omega$ and $R_{in} = 1k\Omega$
 1. Write an equation for V_{out}/V_{in}



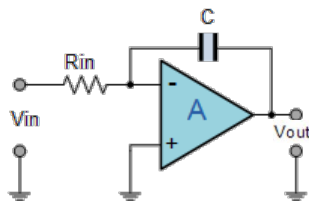- iii. (2pts) For the circuit on the left, given $R_f = 3k\Omega$ and $R_{in} = 1k\Omega$
 1. Write an equation for V_{out} as a function of V_1 and V_2 .




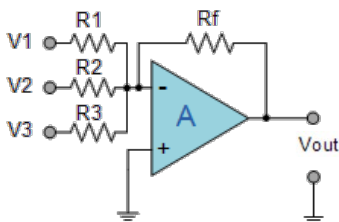- iv. For the circuit on the left, given $R_{in} = 10k\Omega$ and $C = 1\mu F$
 1. (1pt) Write an equation for $V_{out}(t)$ as a function of $V_{in}(t)$
 2. (2pt) What is $V_{out}(t)$ for $t > 0$ if $V_{in} = 0.2V$ (dc) and if $V_{out} = 0V$ when $t = 0$.
 3. (2pts) For AC steady state, what is the magnitude and phase angle of V_{out} if V_{in} has a magnitude of $2V$, a phase angle of 0° and a frequency of 10 Hz .



- v. (2pts) For the circuit on the left, given $R_1 = 1k\Omega$, $R_2 = 500\Omega$, $R_3 = 1k\Omega$, and $R_f = 1k\Omega$:
 1. Write an equation for V_{out}/V_{in}
 2. What is V_{out} if $V_1 = -2V$, $V_2 = 2V$ and $V_3 = 0.5V$

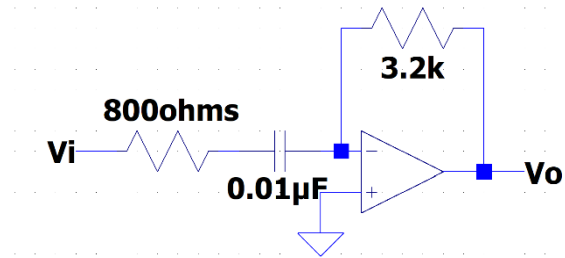- b. Answer the following questions based on the differentiator circuit show. For parts i. and ii. assume the op amp is ideal.



- i. (2pts) For what range of frequencies will this circuit behave as a differentiator?
Give your answer in Hz.


- ii. (2pts) For AC steady state, if V_i is a 5kHz sine wave with an amplitude of 2V and a phase angle of 0° , what is the amplitude and phase of V_o ?

- iii. (3pts) Now assume the op amp is ideal except that V_o is limited to be $-4 < V_o < 4V$, this limit is due to saturation of the op amp.

If V_i is a 4kHz sine wave, what is the maximum amplitude for V_i that won't result in saturation of the output stage of the op amp?


IV – Concepts, Troubleshooting and Data Analysis (20 points)

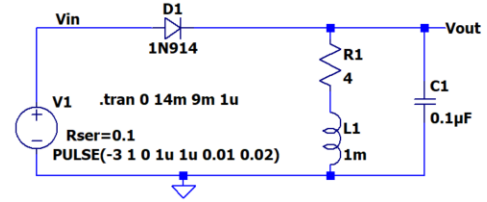a. (4 pts) Real components compared to ideal: In Experiment 5 you built and modeled the circuit on the right.




i. For the LTspice model you included R1. But you didn't put a resistor there when you built the circuit. Why not? {1pt}

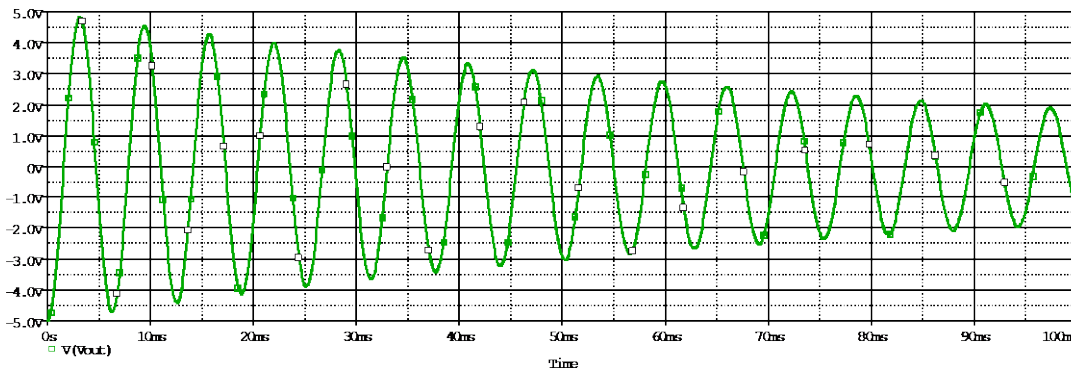ii. Your partner wired the circuit with a 0.01µF capacitor rather than the 0.1µF capacitor called for in the experiment. Would the oscillation frequency go up or down and by what percentage (to the nearest 1%)? {3pt}




b. (4pts) The plot above shows a damped oscillation. The horizontal scale is time (5ms per small division) and the vertical scale is voltage (0.5V per small division). The horizontal scale is from 0s to 100ms. The vertical scale is from -5V to 5V. Find the decay constant α and the angular frequency ω for this data. **You must mark the data points on the plot that you use for your answer.**


OP37

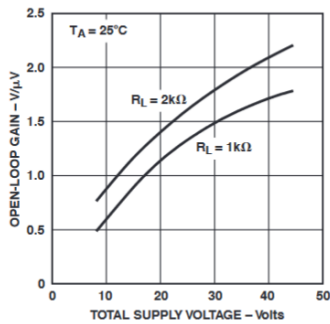


TPC 19. Open-Loop Voltage Gain vs. Supply Voltage

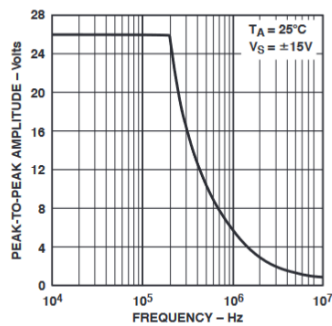


TPC 20. Maximum Output Swing vs. Frequency

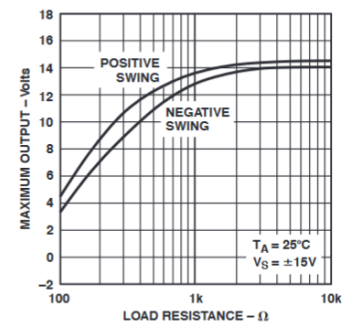


TPC 21. Maximum Output Voltage vs. Load Resistance

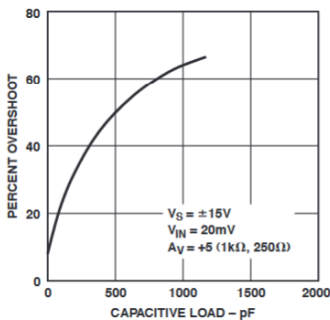

TPC 22. Small-Signal Overshoot vs. Capacitive Load

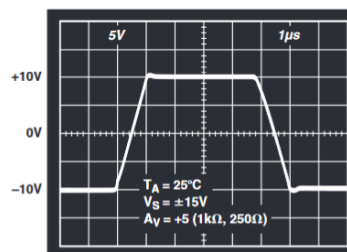

TPC 23. Large-Signal Transient Response

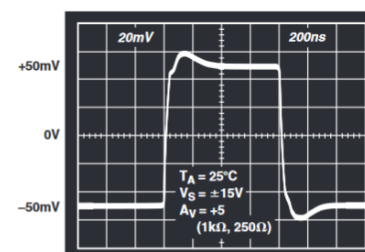

TPC 24. Small-Signal Transient Response

- c. (6 pts) The OP37 is included in the ADALP2000 kit of parts and a page of the data sheet is shown above. Use this to answer the following questions.
- (2pt) If the OP37 is powered by $\pm 15\text{V}$ supplies and has a $10\text{k}\Omega$ load, what are the expected max and min output voltages that the OP37 can achieve?
 - (2pt) If the load is changed to 600Ω , what is the expected max and min output voltages?
 - (2pt) Staying with the OP37 and $\pm 15\text{V}$ supplies, and using a high resistance load (greater than or equal to $10\text{k}\Omega$): if a 1MHz signal is applied, what is the maximum output voltage that the OP37 is expect to be able to provide?

d. (2pts) Which of the following op-amp configurations works best to amplify the signal from a strain gauge bridge circuit? Circle one.

Voltage Follower

Inverting

Non-Inverting

Differential

Adder

Integrator

Differentiator

e. (2pts) Explain in 25 words or less: Why does the Miller Integrator (practical integrator) have a resistor across the capacitor while the ideal integrator doesn't have one?

f. (2pts) What is the likely capacitance of a capacitor with a label of 104 on the side?