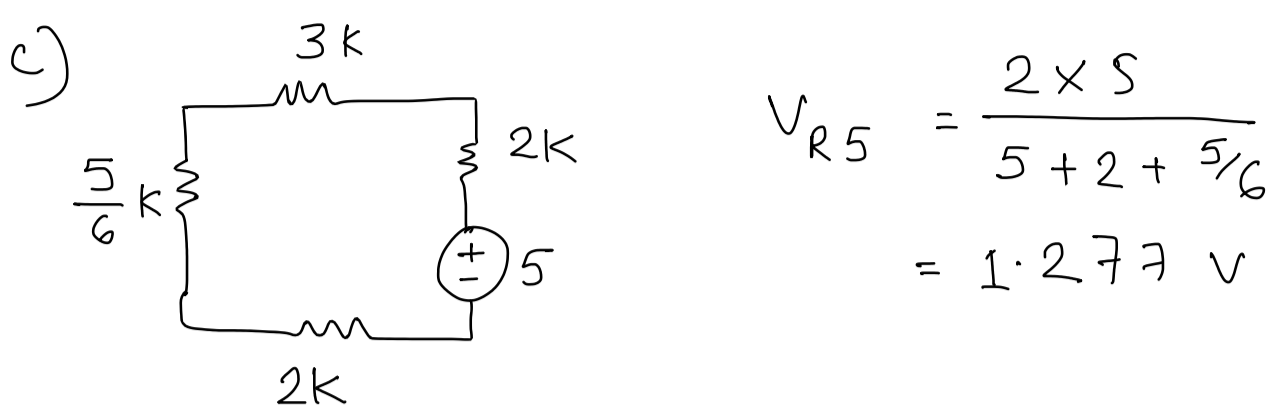


Problem 1:

a) R_3 & R_4 in series


b) R_1 & R_2 in parallel




d) current in total = $\frac{5}{7.833} = 0.6383$

current through R_1 ($5k$) = 0.1063

e) $R_{eq} = 7.833$

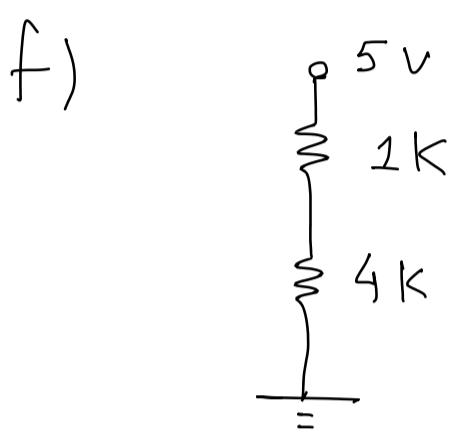

Problem 2

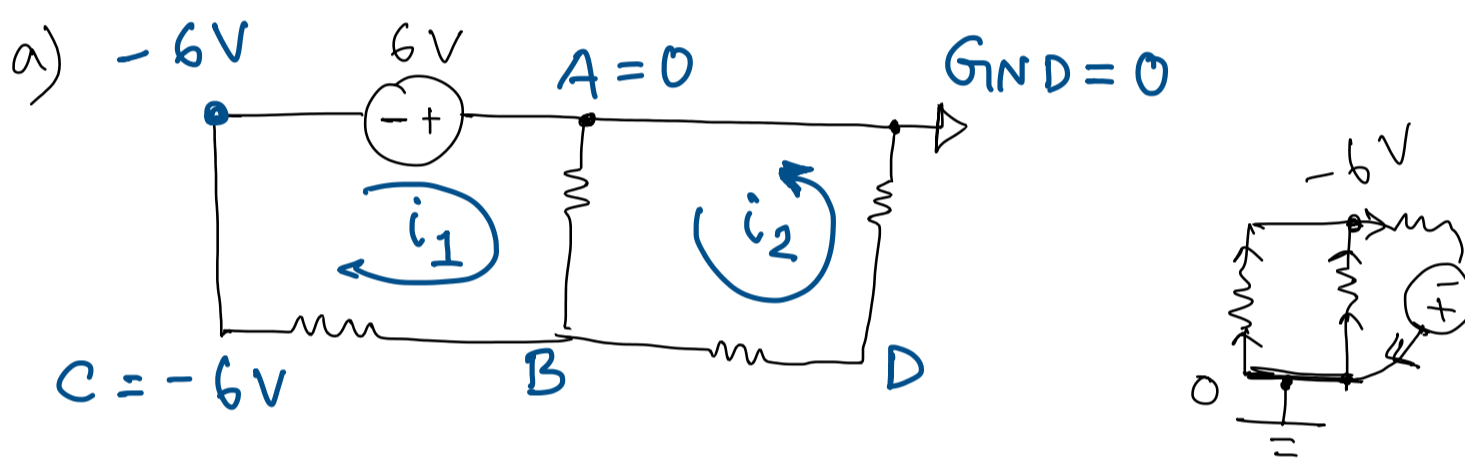

b) unknown voltages: 2
 unknown currents: 2

c) ?

d) $i_1 R_1 + (i_1 + i_2) R_3 = 6$
 $(i_2 + i_1) R_3 + i_2 R_4 + i_2 R_2 = 0$

e) $6i_1 + 5i_2 = 6$
 $5i_1 + 12i_2 = 0$

$$\begin{bmatrix} 6 & 5 \\ 5 & 12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \end{bmatrix}$$

$\Rightarrow i_1 = 1.532 \text{ A}; \quad \begin{cases} V_B = -4.4685 \\ V_D = -1.9149 \end{cases}$
 $i_2 = -0.6383 \text{ A}.$

Problem 3

a) False

