

Intro to ECSE Class 07: Electric Circuit 1

Fundamentals

I) Terminology + Basic Quantities

1. Charge: what flows through a circuit.
electrons have "+" charge.

→ units: Coulombs (C)

→ variable: Q or q

→ most fundamental quantity in a circuit

2. Current: flow of charge

→ definition: Charge passing a point / time

→ units: Amperes (A) = $\frac{\text{Coulombs (C)}}{\text{second (s)}} = \text{C/s}$

→ variable: I

→ Terminology: current **flows**

• through an element (i.e. resistor)

• into or out of a location (i.e. node)

• mathematical def.: $I = \frac{\Delta \text{Charge}}{\Delta \text{time}} = \frac{dQ}{dt}$

3. Voltage : an electrical potential difference²

→ units : Volts (V)

→ variable : V

→ Terminology : Voltage

· across a component (i.e. resistor)

· at a location (i.e. node)

· mathematical definition : $V = \frac{\Delta \text{Potential } E \text{ } dQ}{\Delta \text{Charge } dQ}$


→ Note : Voltage is always measured between 2 points : differential measurement

4. Ground : our standard reference pt. for

→ Symbol: \equiv ∇

all voltages : $V_{\text{end}} = 0$

→ Examples:

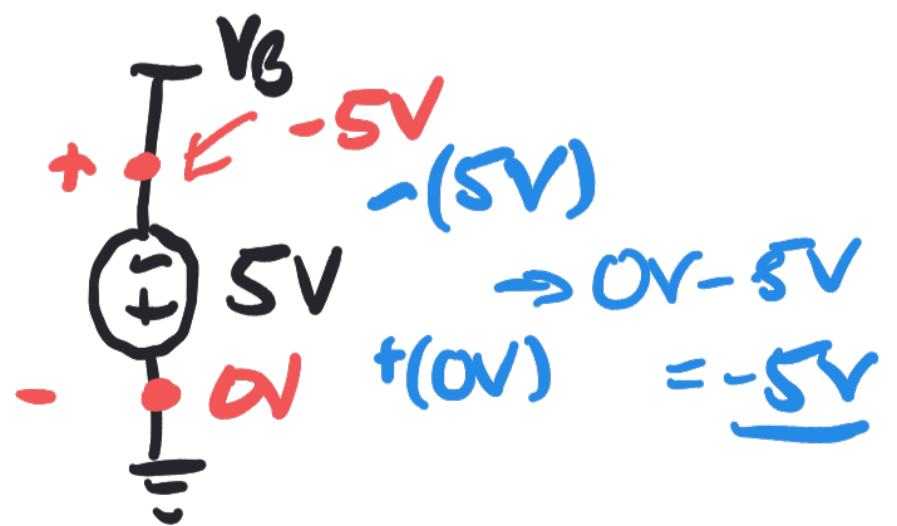

$$V_A = \underline{5V} - \underline{0V} = 5V$$

$$V_B = \underline{-5V}$$

5. Power: work done by a circuit

→ Units: Watts (W) = $\frac{\text{energy}}{\text{time}}$ = J/s

→ Variable: P

→ Terminology: power is

- dissipated by a component (i.e. resistor)
- delivered to an element (i.e. resistor)


· mathematical definition: $P = \frac{\Delta \text{energy}}{\Delta \text{time}} = \frac{dE}{dt}$

→ Note: power is always in reference to a circuit element. Something must be using it.

II | Metric Prefixes

4

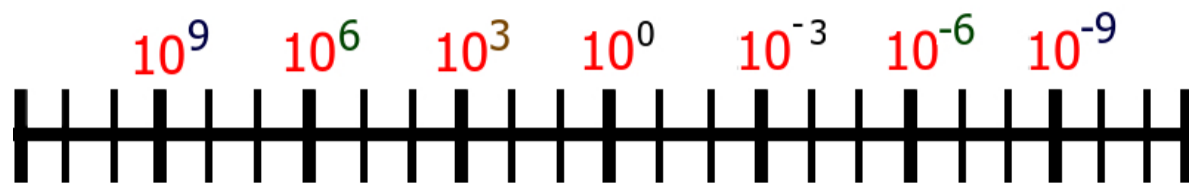- Appear before units and correspond to a power of 10.



<u>Power</u>	<u>Prefix</u>	<u>Example ECSE Unit</u>	<u>Example ECSE Use</u>
10^{-9}	nano-	meters	IC dimensions (transistors)
10^{-6}	micro-	henries	inductors (standard)
10^{-3}	milli-	amperes	typical circuit current
10^{-2}	centi-	meter	scale (semiconductor physics)
10^0	—	volts	typical voltage
10^3	kilo-	ohms	(Standard) resistors
10^6	mega-	watts	power (power plant)
10^9	giga-	bytes	computer storage (standard)
10^{12}	tera-	flops	processing power
10^{-12}	pico-	farads	capacitors (standard)
10^{-15}	femto-	seconds	timescale for radiation (lasers)
10^{18}	exa-	bytes	big storage
10^{15}	peta-	bytes	"


III) Basic Circuit Elements

5

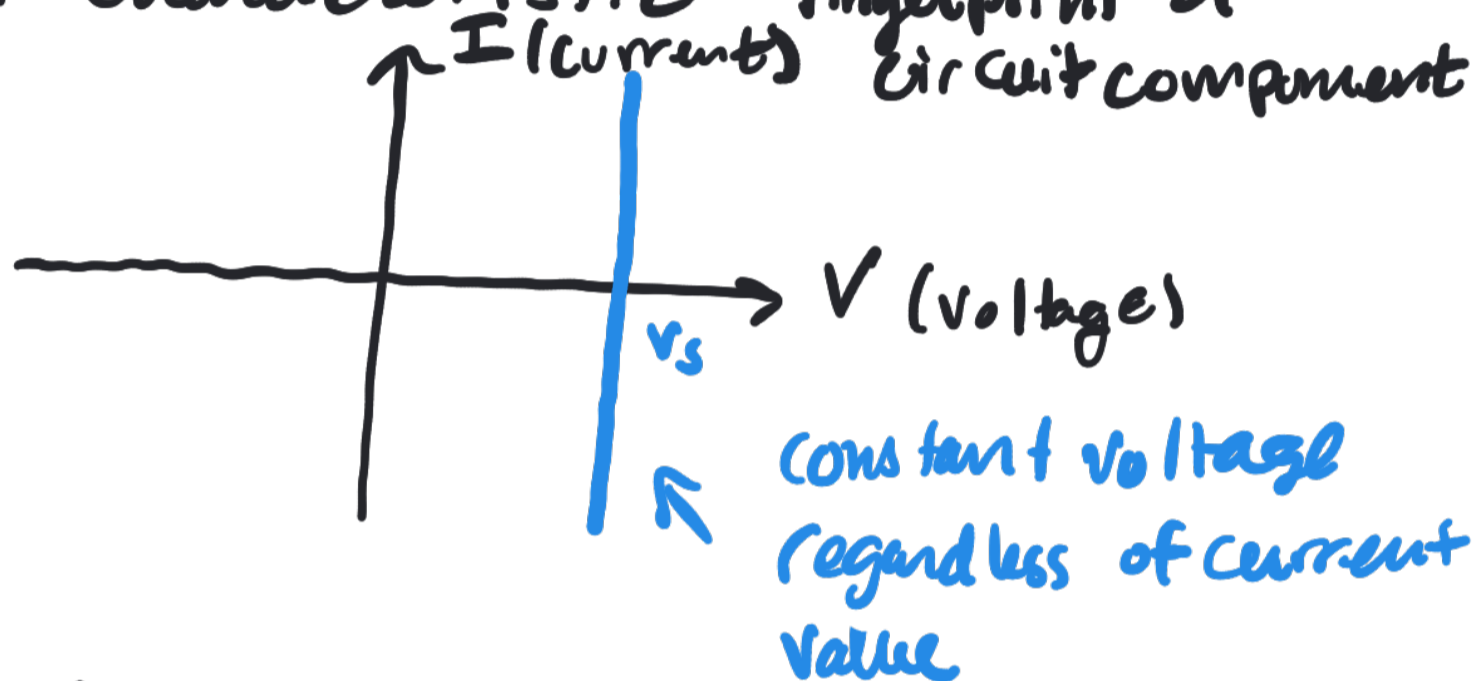1. Voltage Source: provides a voltage to circuit


→ Symbol: 

→ I-V characteristic: fingerprint of circuit component




→ Examples: DC power supply, battery, function generator

2. Current Source: provides a constant current

→ Symbol: 

→ I-V characteristic

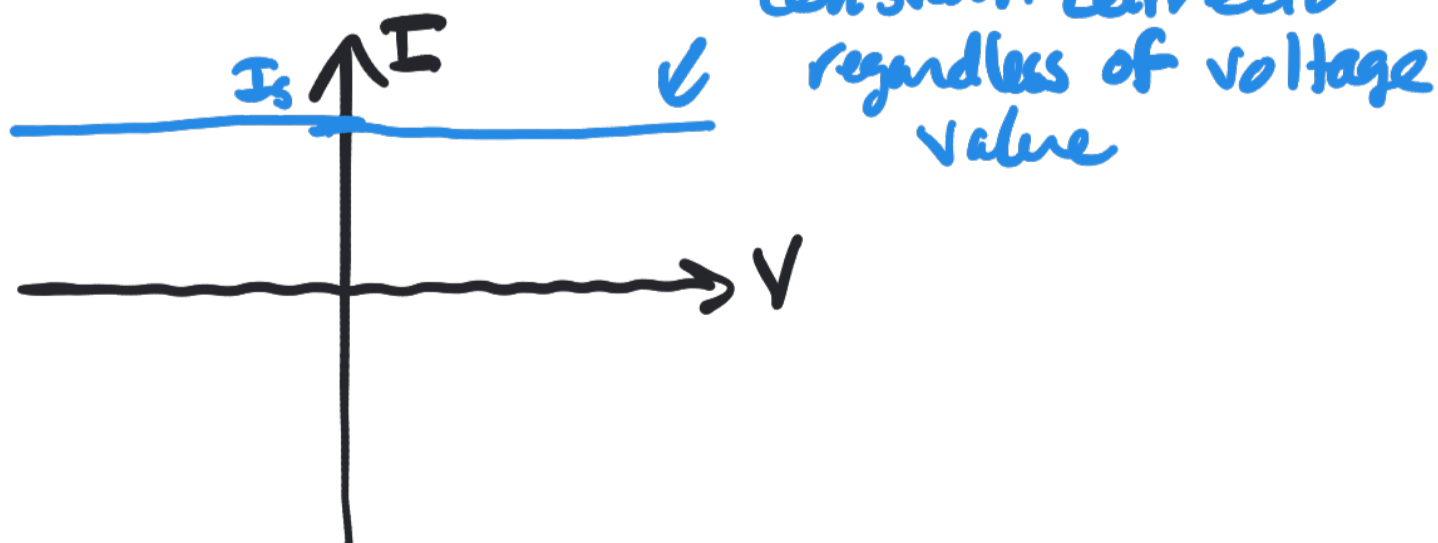

→ Examples: photodiode, transistors


3. Resistor

→ Symbol: $\overset{R}{\text{---} \text{m} \text{---}}$ (us) $\text{---} \text{---} \text{---}$ (Europe)

→ Variable: R

→ Units: Ohms (resistance) = $\frac{\text{Volts}}{\text{Amperes}} = \frac{V}{A}$

→ I-V Characteristic

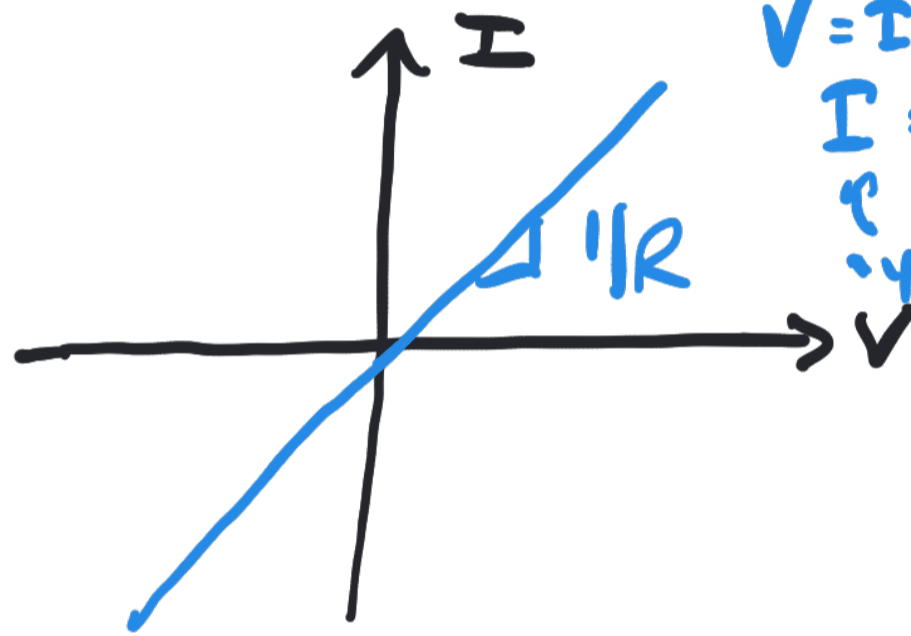

4. Capacitor

→ Symbol: $\text{---} \text{---} \text{---} \text{---} \text{---}$ C

→ Variable: C

→ Units: Capacitance: farads (F)

5. Inductor

7

→ Symbols: $\overset{L}{\text{---}\text{m}\text{---}}$

→ Variable: L

→ Units: Inductance = Henries (H)

IV) Fundamental Circuit Laws

8

1. Passive Sign Convention: In EE, current (conventional current) flows from "+" to "-"



2. Ohm's Law: relates voltage difference, current, and resistance

$$\Delta V = IR$$




$$V_R = V_A - V_B = IR$$

3. Kirchhoff's Voltage Law (KVL)

→ the sum of all voltages in a loop is zero

$$-V_S + V_{R1} + V_{R2} = 0$$

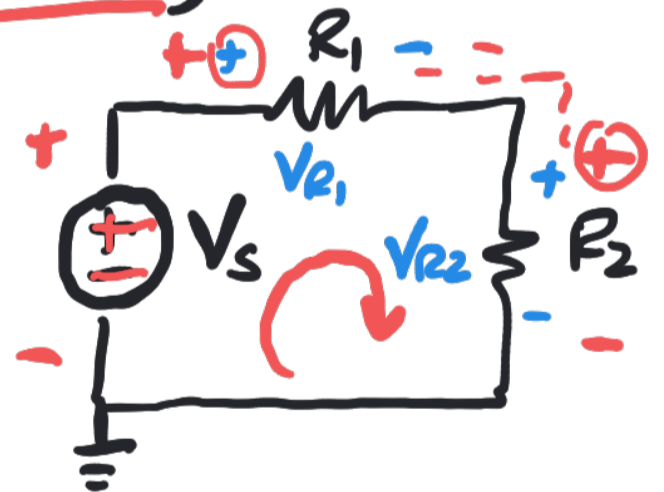

4. Kirchhoff's Current Law (KCL)

→ the sum of all currents at a node is zero

$$I_1 + I_2 + I_3 = 0$$

