

Intro to ECSE Class 08:

1

Circuit Reduction & KCL/KVL/Ohm's Law I

I) KCL & KVL: Nodes and Loops

- KCL: all currents flowing into or out of a node sum to zero
- KVL: all voltages around a loop sum to zero
- Ohm's Law: $V = IR$

1. What is a node?


how many nodes? 3

- any connection between any number of circuit components

- in circuits we assume

0V across a wire is 0

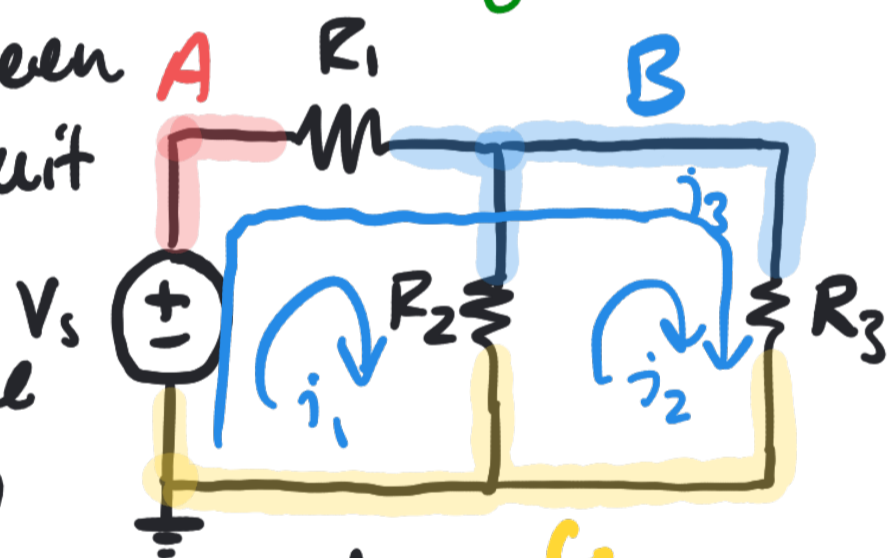- All parts of a circuit connected to a node only by a wire have the same voltage as the node.




2. What is a loop?

how many loops? 3

- Any enclosed circle in a circuit

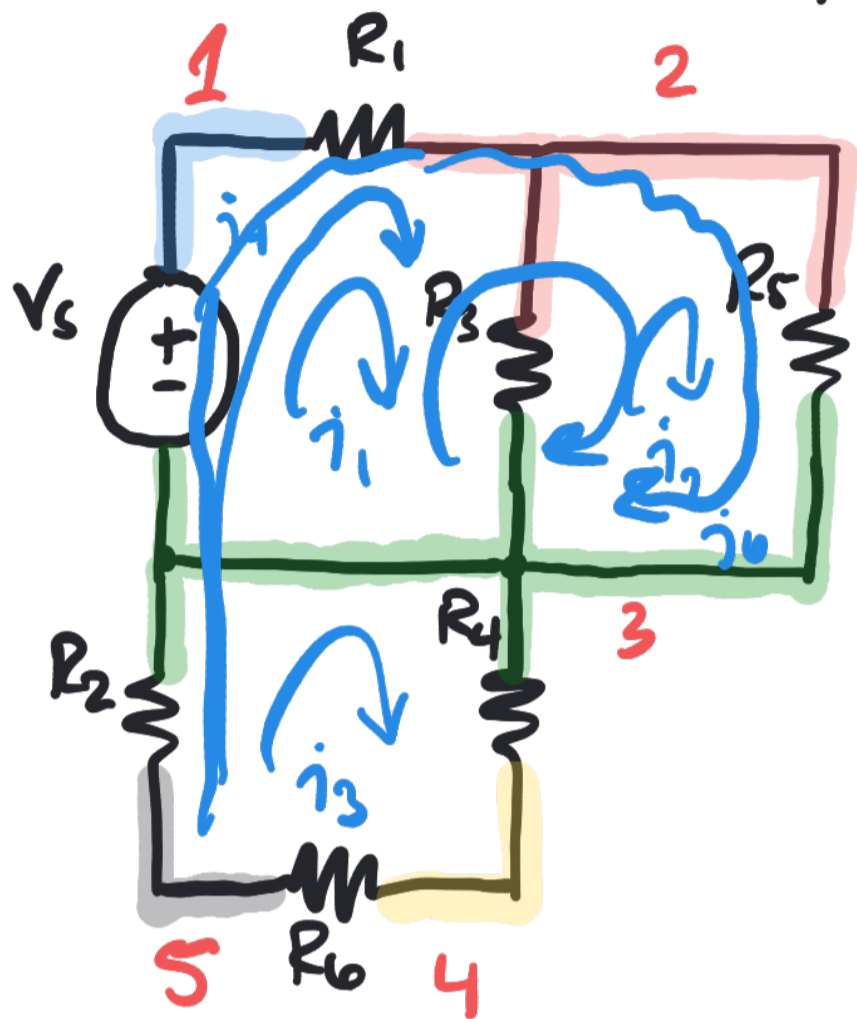Example: How many **nodes** are in the circuit below? How many **loops**? 2




nodes: 5
loops: 6

II] Circuit Analysis Method #1: Circuit Reduction³

We can solve some circuits just by combining resistances

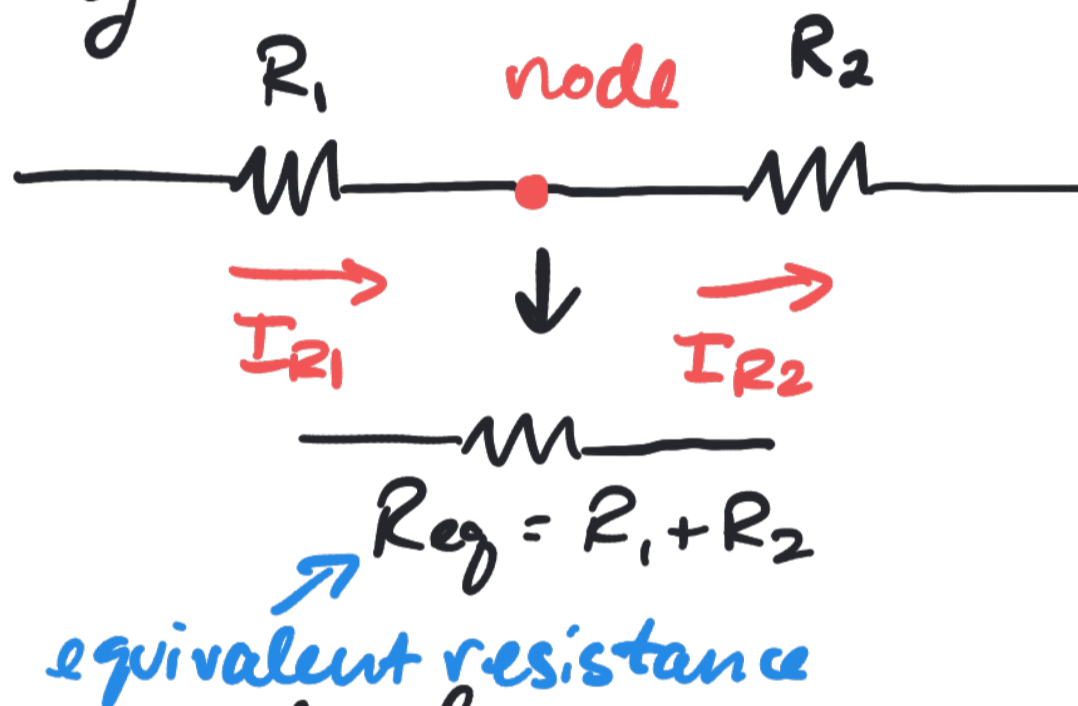1. Combining resistors in *series*

- resistors in series have one common node with no other components sharing it




- in general, for N resistors $R_1, \dots, R_i, \dots, R_N$

$$R_{eq} = \sum_{i=1}^N R_i$$

- if we apply KCL at the node between two resistors in series:


$$-I_{R1} + I_{R2} = 0 \rightarrow I_{R1} = I_{R2}$$

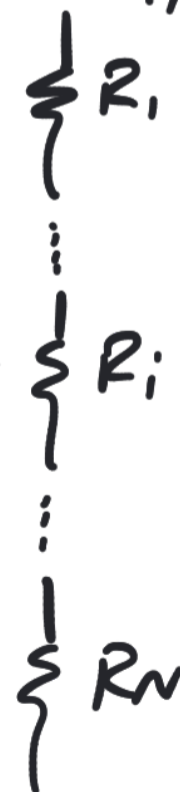- resistors in series have the same current



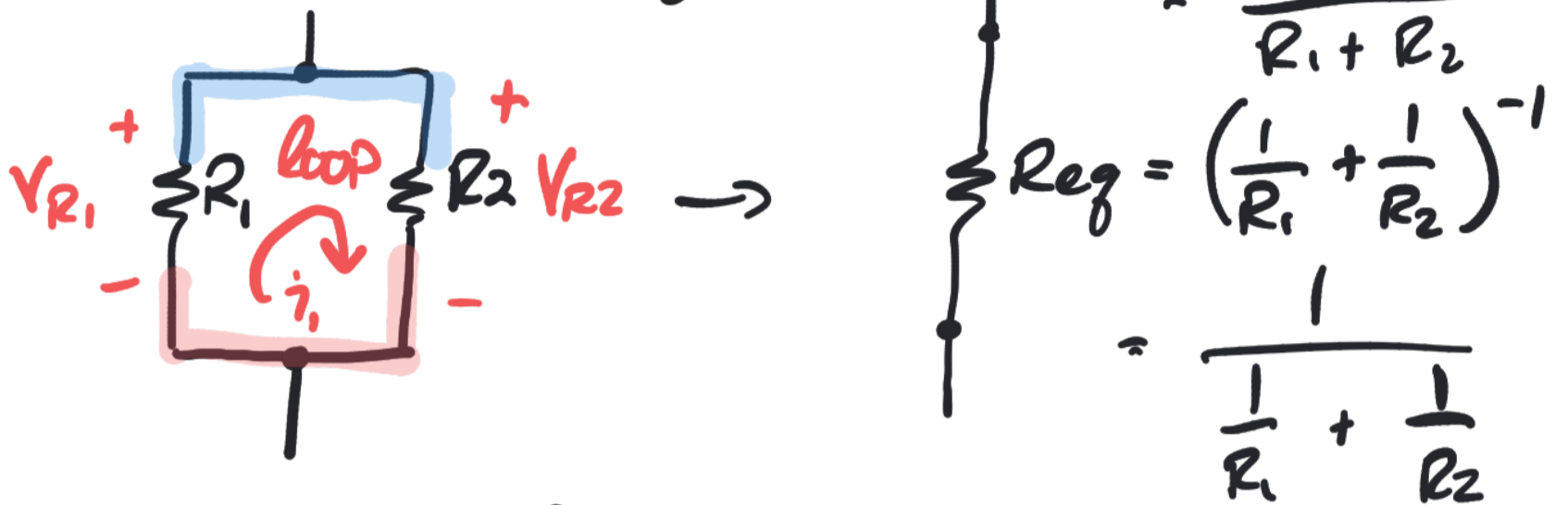2. Combining resistors in parallel 4

- resistors in parallel form a loop containing only two resistors for 2 R only



- in general, for N resistors in parallel

$$R_1, \dots, R_i, \dots, R_N: \quad R_{eq} = \left(\sum_{i=1}^N \frac{1}{R_i} \right)^{-1}$$


- if we apply KVL around the loop containing two resistors in parallel:

$$-V_{R1} + V_{R2} = 0 \rightarrow V_{R1} = V_{R2}$$

- resistors in parallel have the same voltage drop across them

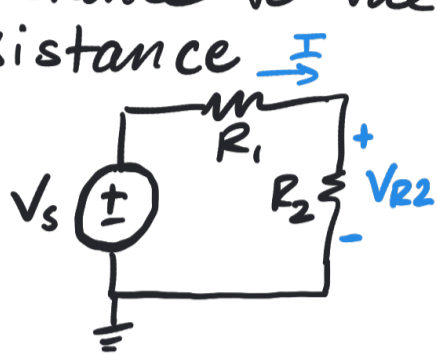3. The Voltage Divider

In a series circuit with a voltage source V_s , the voltage gets divided up among the resistors proportional to the ratio of the individual resistance to the total series resistance



$$V_{R2} = V_s \frac{R_2}{R_1 + R_2}$$

↑ source
↑ total series resistance
↓ Resistor we want the voltage across

where does this come from? Let's find an expression for the voltage across V_{R2} :

$$V_{R2} = I \cdot R_2 \quad \text{Ohm's Law}$$

↑ unknown

What is I ?

$$I = \frac{V_s}{R_{eq}} = \frac{V_s}{R_1 + R_2} \quad \text{Ohm's Law}$$

Calculate V_{R2} :

$$V_{R2} = I \cdot R_2 = \frac{V_s}{R_1 + R_2} \cdot R_2 \rightarrow V_{R2} = V_s \frac{R_2}{R_1 + R_2}$$


we've derived the voltage divider eqn.

General form:

$$V_{out} = V_s \frac{R_{out}}{\sum_{i=1}^N R_i}$$

↑ total series resistance

we have N resistors in series

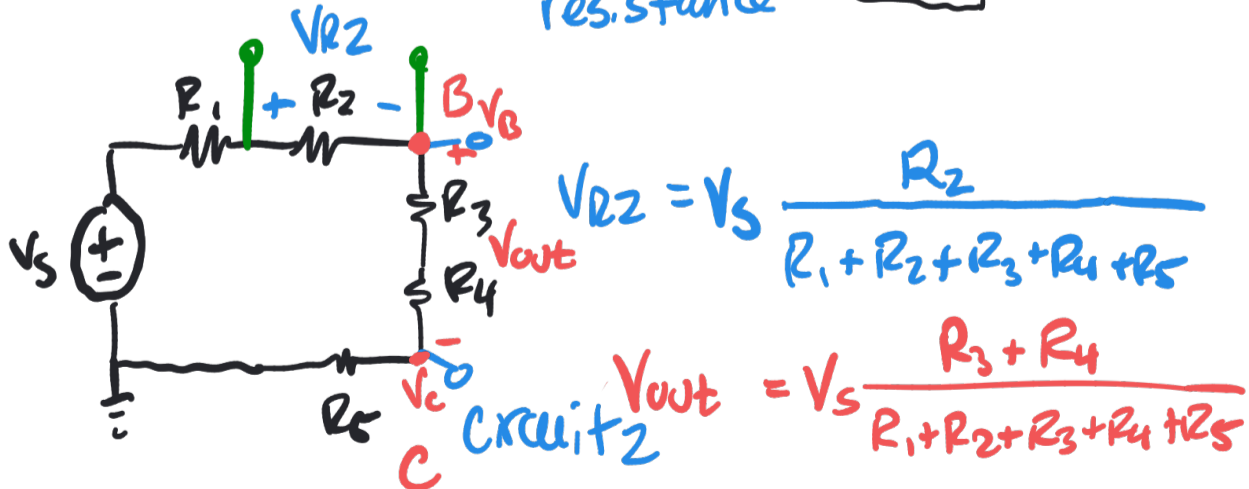


$$V_{out} = V_B - V_C = V_{R3} + V_{R4}$$

↑ nodal voltages

4. Circuit Reduction Technique 6

• Strategy: given a circuit with resistors + sources, combine the resistors to simplify the circuit, then use Ohm's Law and the voltage divider equation to solve for the desired quantity


• Example: Find $V_{out} = V_{R4}$

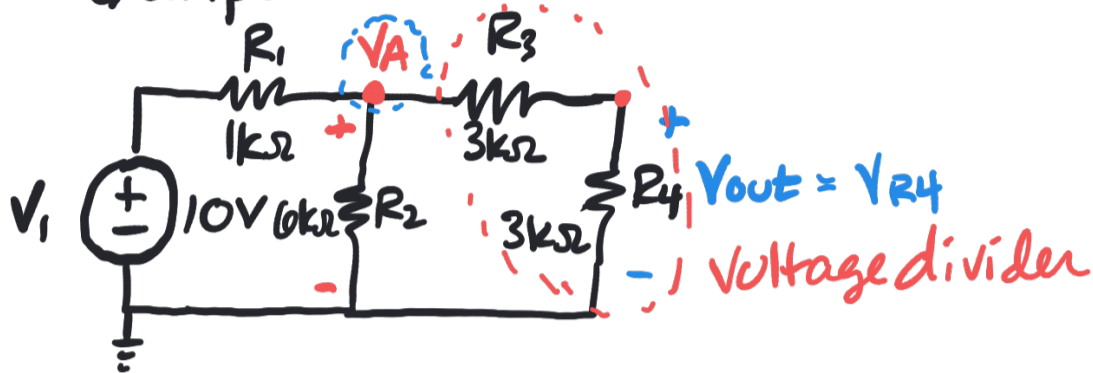

• We want to find V_A because

$$V_{out} = V_{R4} = V_A \frac{R_4}{R_3 + R_4} \quad (1)$$

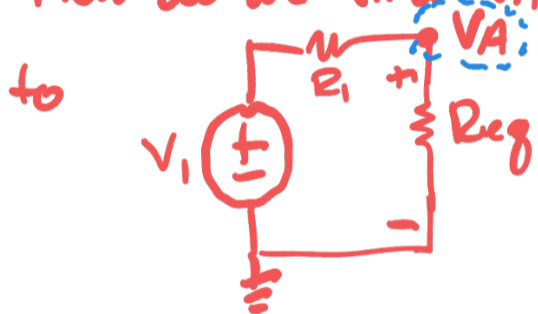
• How do we find V_A ? Reduce the circuit




$$V_A = V_1 \frac{R_{eq}}{R_1 + R_{eq}} \quad (2)$$

• R_3 + R_4 are in series: $R_{34} = R_3 + R_4$

$$= 3k\Omega + 3k\Omega = 6k\Omega$$

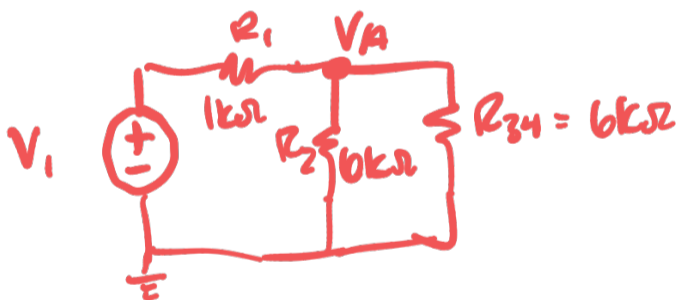

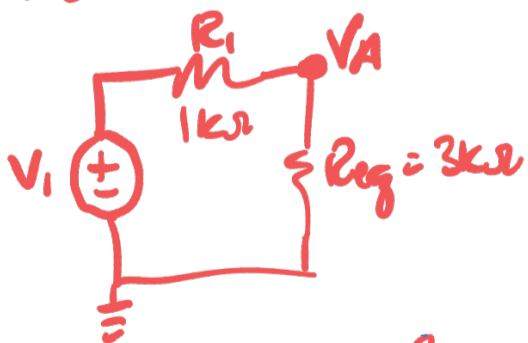• R_2 and R_{34} are in parallel \downarrow in parallel




$$R_{eq} = R_2 \parallel R_{34} = \frac{R_2 R_{34}}{R_2 + R_{34}} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_{34}}} \quad \text{formal definition}$$

$$= \frac{6k \cdot 6k}{6k + 6k} = 3k\Omega$$


$$(2) V_A = V_1 \cdot \frac{R_{eq}}{R_1 + R_{eq}} = 10V \cdot \frac{3k\Omega}{1k\Omega + 3k\Omega} = 10V \cdot \frac{3}{4} = \underline{7.5V}$$

$$(1) V_{out} = V_A \cdot \frac{R_4}{R_3 + R_4} = 7.5V \cdot \frac{3k\Omega}{3k\Omega + 3k\Omega} = 7.5V \cdot \frac{1}{2} = \underline{3.75V}$$

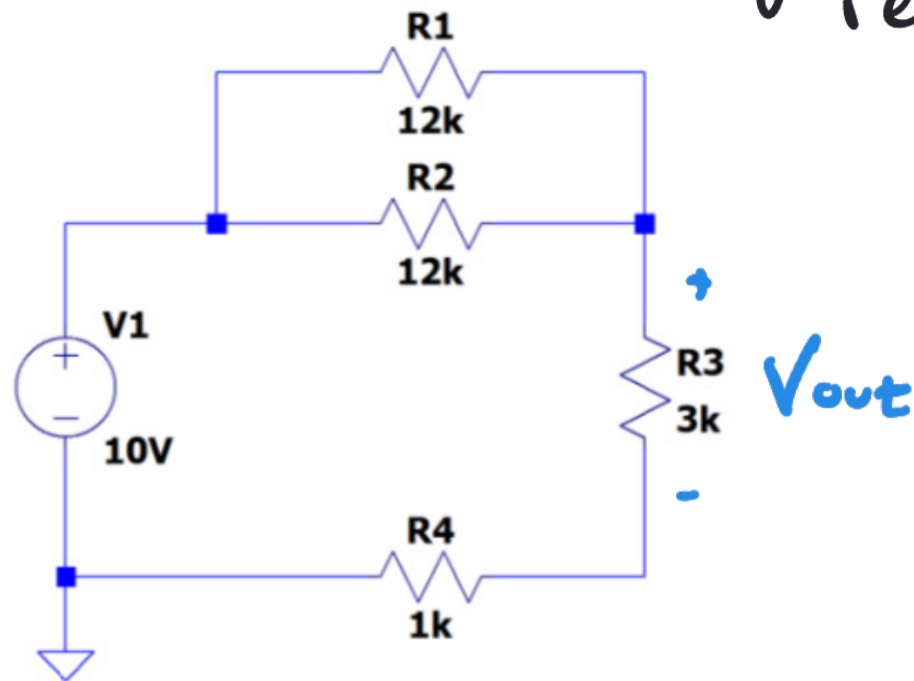Example #2: Find V_{out} using circuit reduction



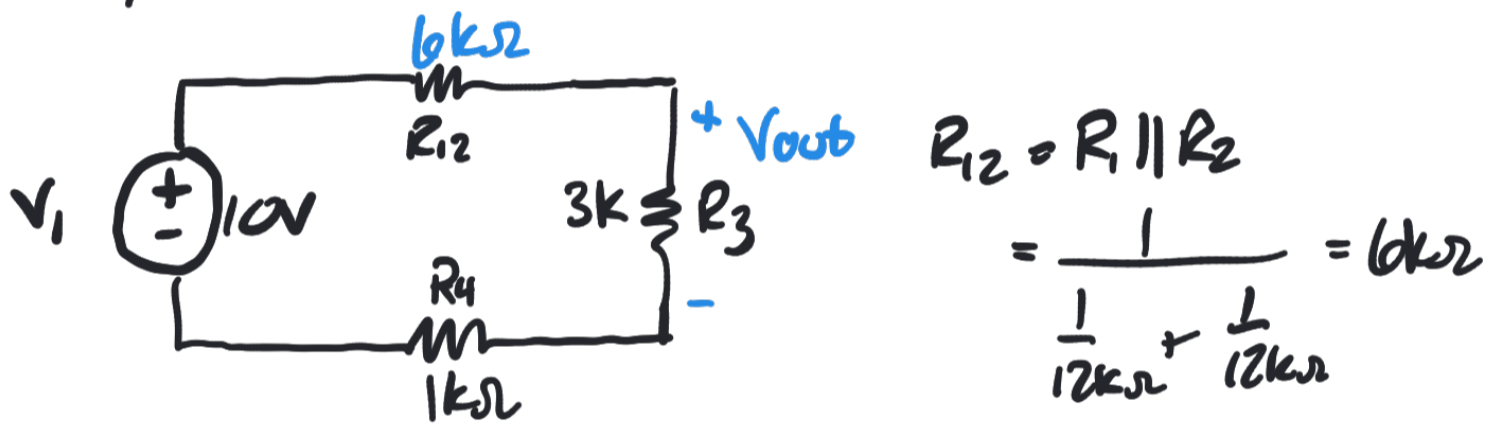- If we put the circuit in the following form, we can use a voltage divider



- Using the voltage divider eqn.:

$$V_{out} = V_{R3} = V_1 \frac{R_3}{R_{12} + R_3 + R_4} = 10V \cdot \frac{3k\Omega}{6k\Omega + 3k\Omega + 1k\Omega}$$

$$= 10V \cdot \frac{3}{10} = \underline{\underline{3V}}$$