


Intro to ECSE Class 12 :

1

Circuit Analysis Method #3: Nodal Analysis


I] How is it different from KCL/KVL/Ohm's Law?

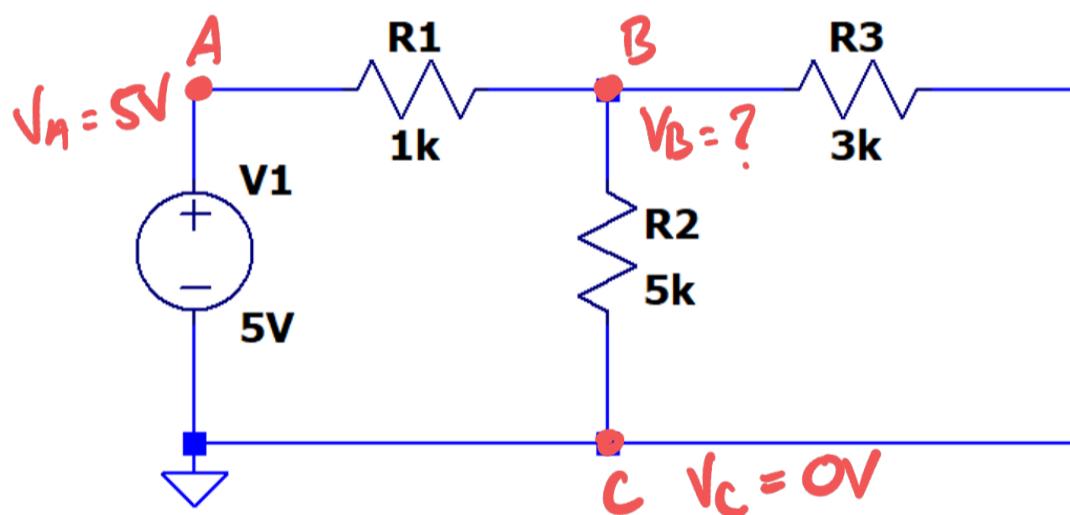1. It's more "efficient". No more "guessing" what the right equations are and usually fewer equations.
2. Covers more of the circuit: handles voltage and current sources more easily.
3. Unknowns are now nodal voltages, not resistor voltages/ currents



- How many unknowns?
 - KCL/KVL/Ohm's Law method: 3 resistors = 3 unknowns
 - Nodal Analysis method: 1 unknown nodal voltage V_B
↳ there is an equation for this:
 $\# \text{unknowns} = \# \text{nodes} - \# \text{Voltage sources} - 1$
Known nodal voltages ground
- We only use KCL in nodal analysis:
How many equations do we need?
1 equation

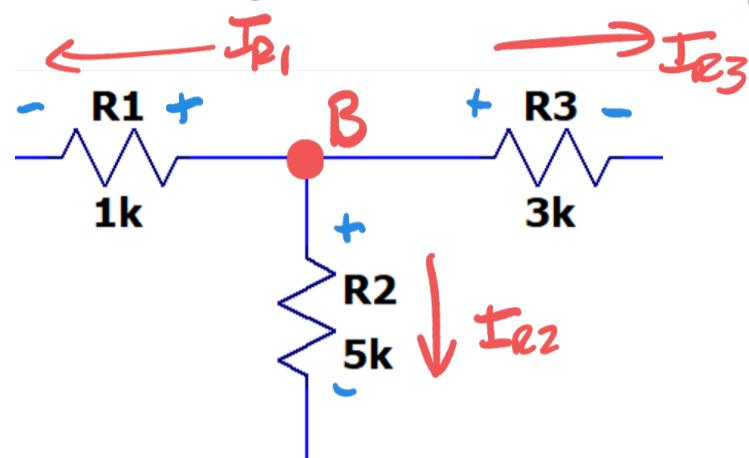4. Passive sign convention : we set the direction of current flow first, as opposed to how we measure voltage differences (the "+" and "-" signs)



. We must choose whether current entering or leaving a node positive or negative
 \rightarrow Doesn't matter \rightarrow just be consistent

II| Nodal Analysis Method Steps


- Determine the number of unknowns / how many equations we need

$$\# \text{unknowns} = \# \text{nodes} - \# \text{voltage sources} - 1$$

- Label all nodes and the known nodal voltages (sources and ground)
- Write a KCL equation for each node with an unknown voltage
 - Write equations in terms of nodal voltages (V_A, V_B, V_C , etc.) \rightarrow new
 - Put equations in standard form (optional)
- Put into matrix form and solve

III | Nodal Analysis Example Problem


3

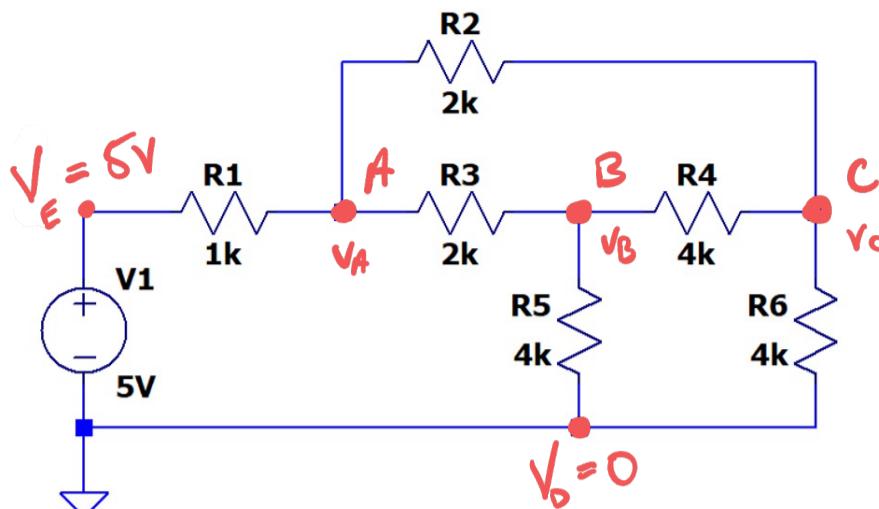


- Determine the number of unknowns / equations required
 $\# \text{unknowns} = 5 - 1 - 1 = 3$
 need 3 equations

2. Label all nodes and known nodal voltages

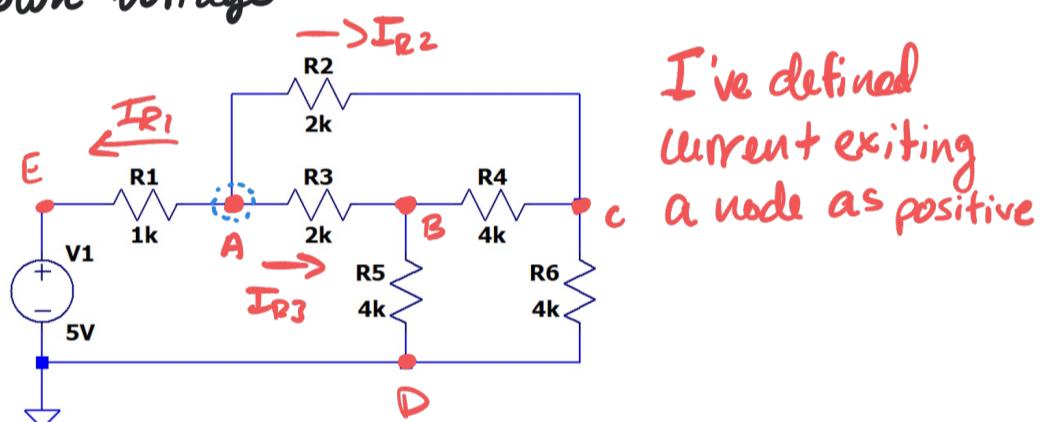
3. Write a KCL equation for each node with an unknown voltage



$$A: I_{R1} + I_{R2} + I_{R3} = 0$$

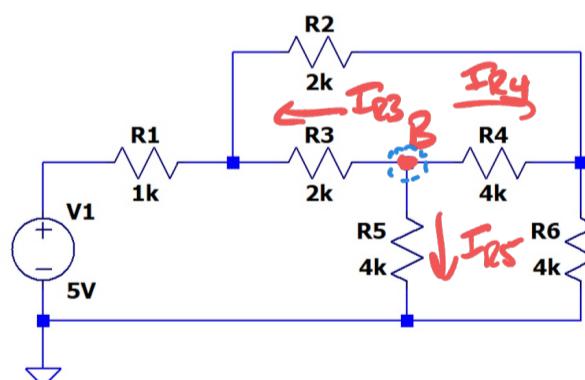


$$B: I_{R3} + I_{R4} + I_{R5} = 0$$

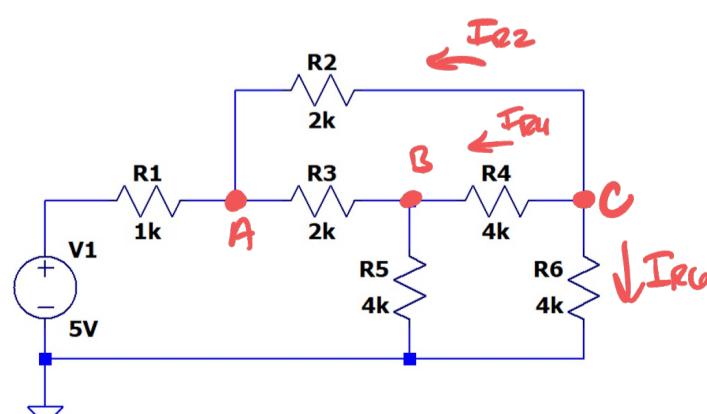

$$C: I_{R2} + I_{R4} + I_{R6} = 0$$

a) Write each equation in terms of nodal voltages. How? 4

$$A: I_{R1} + I_{R2} + I_{R3} = 0$$

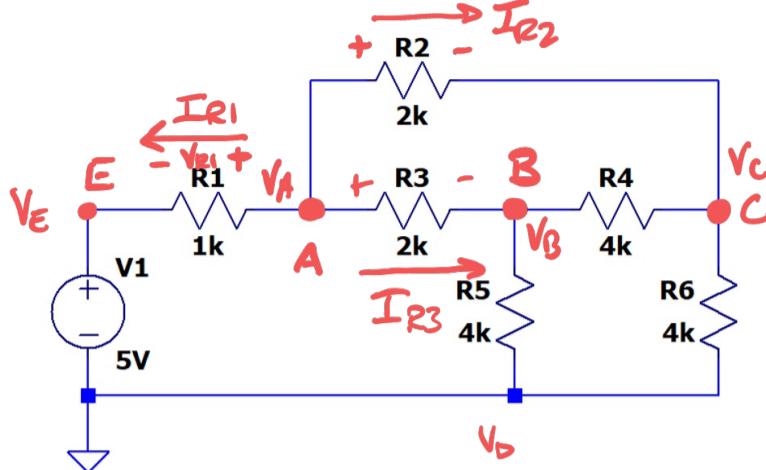


$$\text{node } A: I_{R1} = \frac{V_A - V_E}{R_1} = \frac{V_A - 0}{R_1}$$

$$I_{R2} = \frac{V_A - V_C}{R_2} = \frac{V_A - V_C}{R_2}$$

$$I_{R3} = \frac{V_A - V_B}{R_3} = \frac{V_A - V_B}{R_3}$$


$$A: \frac{V_A - V_E}{R_1} + \frac{V_A - V_C}{R_2} + \frac{V_A - V_B}{R_3} = 0$$

$$B: I_{R3} + I_{R4} + I_{R5} = 0$$

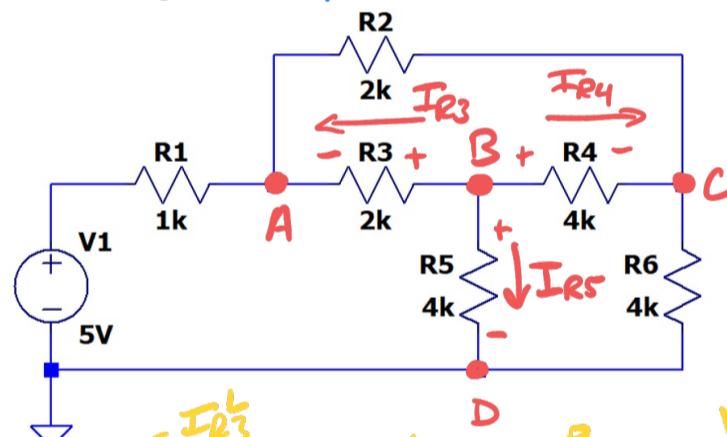

$$B: \frac{V_B - V_A}{R_3} + \frac{V_B - V_C}{R_4} + \frac{V_B - V_D}{R_5} = 0$$

$$C: I_{R2} + I_{R4} + I_{R6} = 0$$

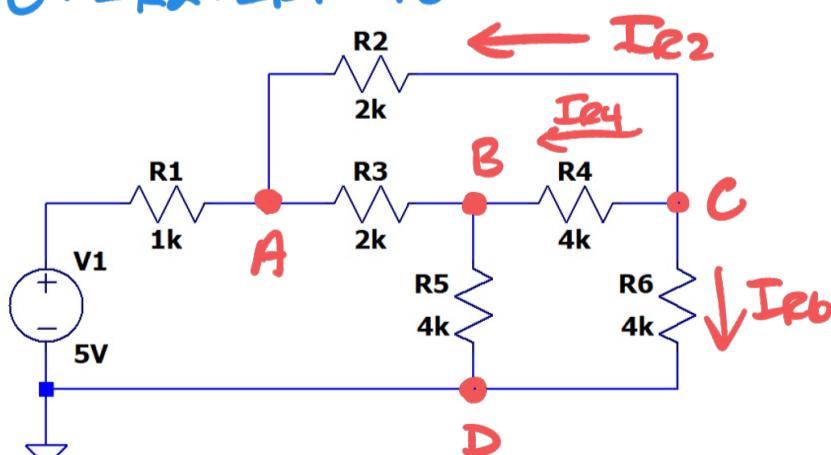

$$C: \frac{V_C - V_A}{R_2} + \frac{V_C - V_B}{R_4} + \frac{V_C - V_D}{R_6} = 0$$

b. Put equations in standard form (optional)

Standard form:

$$(\dots)V_A + (\dots)V_B + (\dots)V_C = \text{constants}$$

$$A: \frac{\cancel{V_A} - V_E}{R_1} \stackrel{V_E=5V}{\cancel{=}} \text{const.} \frac{\cancel{V_A} - V_C}{R_2} + \frac{\cancel{V_A} - V_B}{R_3} = 0 \quad V_E = 5V$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_A + \left(-\frac{1}{R_3} \right) V_B + \left(-\frac{1}{R_2} \right) V_C = \frac{V_E}{R_1} \quad \text{constant}$$

$$B: \frac{V_B - V_A}{R_3} + \frac{V_B - V_C}{R_4} + \frac{V_B - V_D}{R_5} = 0$$

$$\left(-\frac{1}{R_3} \right) V_A + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) V_B + \left(-\frac{1}{R_4} \right) V_C = \frac{V_D}{R_5} \quad V_D = 0 \quad \text{constant}$$

$$C: \frac{V_C - V_A}{R_2} + \frac{V_C - V_B}{R_4} + \frac{V_C - V_D}{R_6} = 0$$

$$\left(-\frac{1}{R_2} \right) V_A + \left(-\frac{1}{R_4} \right) V_B + \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_6} \right) V_C = \frac{V_D}{R_6} \quad V_D = 0 \quad \text{constant}$$

4. Put into matrix form & solve

6

$$A: \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_A + \left(-\frac{1}{R_3} \right) V_B + \left(-\frac{1}{R_2} \right) V_C = \frac{V_E}{R_1}$$

$$B: \left(-\frac{1}{R_3} \right) V_A + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) V_B + \left(-\frac{1}{R_4} \right) V_C = \frac{V_D}{R_5}$$

$$C: \left(-\frac{1}{R_2} \right) V_A + \left(-\frac{1}{R_4} \right) V_B + \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_6} \right) V_C = \frac{V_D}{R_6}$$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) & \left(-\frac{1}{R_3} \right) & \left(-\frac{1}{R_2} \right) \\ \left(-\frac{1}{R_3} \right) & \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) & \left(-\frac{1}{R_4} \right) \\ \left(-\frac{1}{R_2} \right) & \left(-\frac{1}{R_4} \right) & \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_6} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{V_E}{R_1} \\ \frac{V_D}{R_5} \\ \frac{V_D}{R_6} \end{bmatrix}$$

↓ numerical values

$$\begin{bmatrix} \left(\frac{1}{1000} + \frac{1}{2000} + \frac{1}{4000} \right) & \left(-\frac{1}{2000} \right) & \left(-\frac{1}{4000} \right) \\ \left(-\frac{1}{2000} \right) & \left(\frac{1}{2000} + \frac{1}{4000} + \frac{1}{6000} \right) & \left(-\frac{1}{4000} \right) \\ \left(-\frac{1}{4000} \right) & \left(-\frac{1}{4000} \right) & \left(\frac{1}{2000} + \frac{1}{4000} + \frac{1}{6000} \right) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{5}{1000} \\ 0 \\ 0 \end{bmatrix}$$

$$V_A = 3.75V$$


$$V_B = 2.50V$$

$$V_C = 2.50V$$

IV | Extra Practice Problem

Using nodal analysis, solve for V_{R1}

7

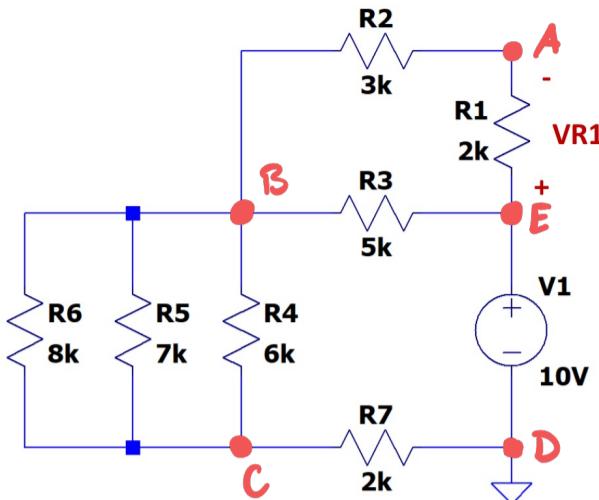

1) # equations: 5 nodes - 1 voltage source - 1
= 3 equations

2) Known nodal voltages: $V_D = 0V$; $V_E = 10V$

3) KCL equations:

$$\text{node A: } \frac{V_A - V_B}{R_2} + \frac{V_A - V_E}{R_1} = 0$$

$$(\frac{1}{R_1} + \frac{1}{R_2})V_A + (-\frac{1}{R_2})V_B = \frac{V_E}{R_1}$$

$$\rightarrow (\frac{1}{2000} + \frac{1}{3000})V_A + (-\frac{1}{3000})V_B = \frac{10}{2000}$$

$$\text{node B: } \frac{V_B - V_A}{R_2} + \frac{V_B - V_E}{R_3} + \frac{V_B - V_C}{R_4} + \frac{V_B - V_C}{R_5} + \frac{V_B - V_C}{R_6} = 0$$

$$(-\frac{1}{R_2})V_A + (\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6})V_B + (-\frac{1}{R_1} - \frac{1}{R_5} - \frac{1}{R_6})V_C = \frac{V_E}{R_3}$$

$$\rightarrow (-\frac{1}{3000})V_A + (\frac{1}{3000} + \frac{1}{5000} + \frac{1}{6000} + \frac{1}{7000} + \frac{1}{8000})V_B + (-\frac{1}{6000} - \frac{1}{7000} - \frac{1}{8000})V_C = \frac{10}{5000}$$

$$\text{node C: } \frac{V_C - V_B}{R_4} + \frac{V_C - V_B}{R_5} + \frac{V_C - V_B}{R_6} + \frac{V_C - V_D}{R_7} = 0$$

$$(-\frac{1}{R_4} - \frac{1}{R_5} - \frac{1}{R_6})V_B + (\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_7})V_C = \frac{V_D}{R_7}$$

$$\rightarrow (-\frac{1}{6000} - \frac{1}{7000} - \frac{1}{8000})V_B + (\frac{1}{6000} + \frac{1}{7000} + \frac{1}{8000} + \frac{1}{2000})V_C = 0$$

$$\begin{bmatrix} (\frac{1}{2000} + \frac{1}{3000}) & (-\frac{1}{3000}) & 0 \\ (-\frac{1}{3000}) & (\frac{1}{3000} + \frac{1}{5000} + \frac{1}{6000} + \frac{1}{7000} + \frac{1}{8000}) & (-\frac{1}{6000} - \frac{1}{7000} - \frac{1}{8000}) \\ 0 & (-\frac{1}{6000} - \frac{1}{7000} - \frac{1}{8000}) & (\frac{1}{6000} + \frac{1}{7000} + \frac{1}{8000} + \frac{1}{2000}) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{10}{2000} \\ \frac{10}{5000} \\ 0 \end{bmatrix}$$

$$V_A = 8.530V$$

$$V_B = 6.324V$$

$$V_C = 2.941V$$

$$V_{R1} = V_E - V_A = 10V - 8.530 \\ = \underline{1.470V}$$

Upcoming Assignments + Due Dates

1) Project Plan update (before Lab 02)

- Incorporate feedback from 1st project plan Due 10/10
- Make any changes you want to
- Add detail for lab 02 and lab 03

2) Metacognition journal entry on EE vs. CSE vs. CS Due 10/10

3) Problem Set #4 : Nodal Analysis
Due 10/10

4) Proof of Skills Optimization #1
(See instructions on course website under Course Resources/Proof of Skills) Due 10/12

5) Problem Set #5 : Nodal Analysis Practice

Due 10/12

* Next Thursday 10/12 : Plan of Study review!
· Complete your plan of study and bring a copy with you!